



# CS 598: Spectral Graph Theory. Lecture 17

## Effective Resistance

Alexandra Kolla

# Today

- Resistance in networks and motivation from Physics.
- Ohm, Kirchoff and Laplacian.
- Effective Resistance.
- Linear Equations in Laplacians.

# Resistor Networks

- One of our main motivations for studying the Laplacian matrix is its role in the analysis of physical systems.
- Given graph, we treat each edge as resistor.
- If graph unweighted, resistance is 1.
- Generally, resistance is  $\frac{1}{w(e)}$ .
- The smaller the weight, the larger resistance (if no edge, the infinite resistance).

# Resistor Networks

- **Ohm's Law:** Potential drop across a resistor is equal to the current flowing over the resistor times the resistance

$$V=IR$$

- For graph, define for each edge  $(a,b)$  the current flowing from  $a$  to  $b$  as

$$i(a, b) = -i(b, a)$$

- If  $v \in R^n$  is the vector of potentials, then  $i(a, b) = w(a, b) \cdot (v(a) - v(b))$  (flowing from high to low potential)

# Resistor Networks

- We want to write the equation in matrix form.
- Treat  $i$  as a vector with entries for every edge  $(a,b)$  where  $a < b$ .
- Recall the edge-vertex adjacency matrix

$$U((a, b), c) \begin{cases} 1 & \text{if } a = c \\ -1 & \text{if } b = c \\ 0 & \text{o.w} \end{cases}$$

- If  $W$  is the matrix with weights of edges in diagonal, then  $i = WUv$ .

# Resistor Networks

- **Kirchoff's Law:** Resistor networks cannot hold current. All flow entering from vertex  $a$  from edges in the graph must exit  $a$  to an external source.
- Let  $i_{ext} \in R^n$  denote the external currents, where  $i_{ext}(a)$  is the amount of current entering the graph through node  $a$ .
- $$i_{ext}(a) = \sum_{b:(a,b) \in E} i(a, b)$$

# Resistor Networks

- In matrix form

$$i_{ext} = U^T i = U^T W U v = L v$$

- External nodes when  $i_{ext} \neq 0$ , internal nodes when its zero.
- For internal nodes and unweighted graph, this equation implies:

$$0 = L(a, \cdot) v = \sum_{(a,b) \in E} (v(a) - v(b)) = d(a)v(a) - \sum v(b)$$

- So voltages are weighted average of neighbors.

# Resistor Networks

- We would like to apply the equation in reverse, and find the potentials from the currents.

$$i_{ext} = Lv = L^{-1}i_{ext} \Rightarrow v$$

- Laplacian has no inverse!!
- Define Pseudoinverse, since we are only interested in currents that sum to zero.



# Resistor Networks

- **Definition** (Pseudoinverse).

$$LL^+ = \Pi$$

Where  $\Pi$  is symmetric projection onto span of  $L$ .

- **Claim.**  $L^+ = \sum_{i>1} \frac{1}{\lambda_i} v_i v_i^T$
- In general, for every rational function of the laplacian...

# The Path Graph

- Example: the path with unit flow.

# Effective Resistance

- Effective resistance between vertices  $a$  and  $b$  is the resistance between  $a$  and  $b$  given by the whole network, if we treat it as a resistor.
- Recall serial and parallel composition.
- $i(a, b) = \frac{v(a) - v(b)}{r_{a,b}}$ . Define  $R_{eff}(a, b)$  to be the potential different between  $a$  and  $b$  if we send one unit of current through  $a$  and remove it from  $b$ .

# Effective Resistance

- Define

$$i_{ext}(c) = \begin{cases} 1 & \text{if } c = a \\ -1 & \text{if } c = b \\ 0 & \text{o.w} \end{cases}$$

- This corresponds to a flow of 1 from a to b.
- Solve for voltage as before:  $Lv = i_{ext} \Rightarrow v = L^+ i_{ext} \Rightarrow v(a) - v(b) = i_{ext}^T v = i_{ext}^T L^+ i_{ext}$ , the effective resistance.
- We can shift by multiple of all-1's vector.

# Effective Resistance

- **Claim.**  $R_{\text{eff}}(a, b) = i_{\text{ext}}^T L^+ i_{\text{ext}} = v^T L v$
- **Claim.** If  $a, b$  the external nodes and every other node  $c$  is internal, then  $v(a) \geq v(c) \geq v(b)$ .
- Using this claim, show triangle inequalities. Effective Resistance is a distance.

# Fixing Potentials

- We can see effective resistance by fixing potentials.
- Solve linear equations in Laplacians to find the potentials.
- Rest of class: properties of submatrices of Laplacian (see board).

# Positive Inverse

- We will show the following claims:
- **Claim.** Let  $A$  be a symmetric matrix with evals  $-1 < \mu_1 \leq \dots \leq \mu_n < 1$ .  
Then

$$(I - A)^{-1} = \sum_j A^j$$

# Positive Inverse

- We will show the following claims:
- **Claim.** Let  $L=D-A$  the Laplacian of a connected graph. Let  $X$  be a diagonal, non-negative, non-zero matrix. Then
  - $D - A + X$  is positive definite
  - $D + A + X$  is positive definite
  - $(L + X)_{ij}^{-1} > 0$  for all  $i,j$ .