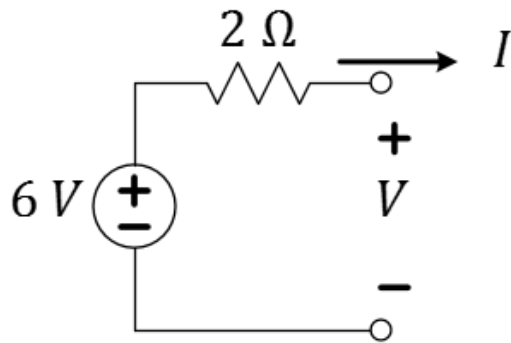
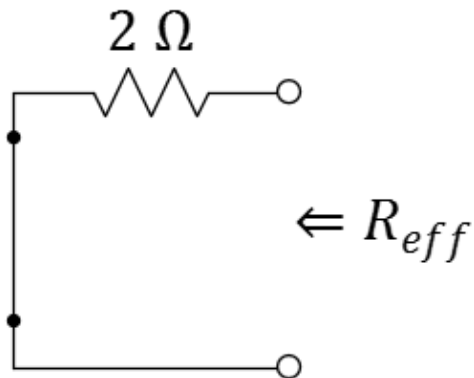


Find the effective resistance,  $R_{eff}$ , for the Circuit.



**Step 1.** Replace the voltage sources with short circuits and the current sources with open circuits.

There is only one voltage source. Replace it with a short circuit (i.e. a wire).



**Step 2.** Use series and parallel relationships between the remaining resistances to find  $R_{eff}$ .

This leaves only the  $2\ \Omega$  resistor. This value is  $R_{eff}$ .

Answer:  $R_{eff} = 2\ \Omega$