

L10Q1	Is one of the resistors in parallel with the voltage source?	Yes, the 3Ω resistor at the top of the schematic.			
L10Q2	What is the value of the labeled current?	3	A		
L10Q3	How many nodes are in the circuit?	4			
L10Q4	What is the value of the labeled current?	1	A		
L10Q5	How many nodes are in the circuit?	4			
L10Q6	What is the value of the labeled current?	-0.6	A		
L10Q7	What is the power supplied or consumed by each element?	9V source: -1.5 W; source: -7 W; resistor: +1/2 W; resistor: $8 \frac{1}{6}$ W	1A 12 Ω 6 Ω W	supplied by voltage & current source; consumed by resistors	
L10Q8	What is the value of the labeled current?	0	mA		