

L15Q1	Given these constraints, can the "dependent" current source deliver power?	No. $P = I_c \cdot V_{out}$ always $> 0$			
L15Q2	Right-side KVL: Find equation relating $I_{max}$ to $I_{min}$	$I_{max} = (V_{cc} - V_{min}) / R_c$			
L15Q3	Left-side KVL: Find the smallest $V_{in}$ such that $I_b > 0$ (if $V_{on} = 0.7V$ )	$V_{in} > 0.7V$			
L15Q4	What is $I_b$ if $V_{in} = 3V$ and $R_b = 4.6k\Omega$ ?	0.5 mA		0.0005	A
L15Q5	Let $V_{cc} = 6V$ , $R_c = 580\Omega$ , $V_{min} = 0.2V$ , $\beta = 100$ . What is $I_c$ under the same input settings as the previous question?	transistor in SATURATION			
	$I_c = I_{max}$	10 mA		0.01	A
L15Q6	Approximate values of $\beta$ (hfe), $V_{beon}$ , $V_{cesat}$ from the datasheet.	If used under conditions similar to those used in the lab $\beta \sim 50$ , $V_{beon} \sim 0.9V$ , and $V_{cesat} \sim 0.6V$			
L15Q7	Find $I_b$	$I_b = 100\mu A$			
L15Q8	Find $I_c$	$I_c = 10mA$			
L15Q9	Find $I_b$	$I_b = 0$			
L15Q10	Find $I_c$	$I_c = 0$			
L15Q11	Find $I_b$	$I_b = 0.4mA$			
L15Q12	Find $I_c$	$I_c = 19.33333mA$			
L15Q13	Find $I_c$ and identify which regime the transistor is operating	operating at the transition between the CUTOFF and ACTIVE regions			
	$I_b$	0 mA			
	$I_c$	0 mA			
L15Q14	Find $I_c$ and identify in which regime the transistor is operating.	operating in the ACTIVE region			
	$I_c$	10 mA		0.01	A
L15Q15	Determine the power consumed by the transistor.	$P = I_b \cdot V_{be} + I_c \cdot V_{ce}$			
		62.1 mW		0.062	W