

L19Q1	What happens to drain current when $V_{GS} - V_{TH}$ doubles?	$I_D$ quadruples	
L19Q2	What is the current into the gate of the MOSFET model?	0	A
L19Q3	What are the units of $k$ ?	$\frac{A}{V^2}$ or $\frac{mA}{V^2}$ or $\frac{\mu A}{V^2}$	
L19Q4	If $I_1=100mA$ , what is the value of $k$ ?	100	$\frac{mA}{V^2}$
L19Q5	At which operating point above would the MOSFET be in "cutoff"?	E	
L19Q6	At which operating point above would the MOSFET be "active"?	D	
L19Q7	At which operating point above would the MOSFET be "ohmic"?	B	
L19Q8	Use the IV plot to find the FET regime and operating point.		
	find graphically the operating point at	$\sim(1.3 V, 75 mA)$	
L19Q9	Find the Gate-to-Source voltage, $V_{GS}$ .	4	V