L9Q1	What is the Thevenin equivalent of the circuit above?				
	4/52				
	- m				
	5v +	-0			
L9Q2	How is Reff related to the slope of the I-V line?	 Reff= 1/slope			
L9Q3	What is Reff for the circuit above?	Reff=0.8Ω			
L9Q4	Decides Deff is it engine to find less on Voc	A matter of opinion, but finding Isc involves less			
L9Q5	Besides Reff, is it easier to find Isc or Voc? What is Reff for the circuit with the given i-V line?	algebra for THIS circuit. Reff= 1/slope =2.5kΩ			
L9Q6	What are the Thevenin and Norton equilvalents for the circuit above?		6 V	VT	
			3 mA	Reff=RT=RN	