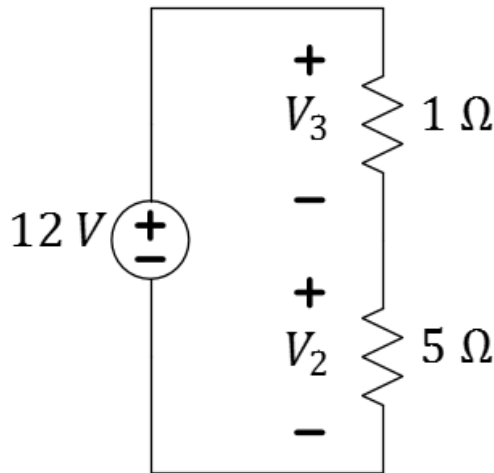
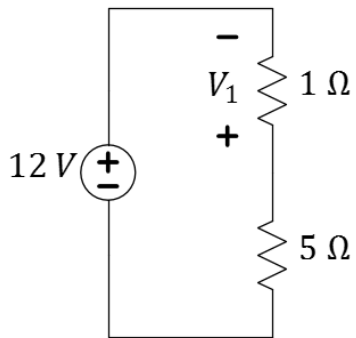
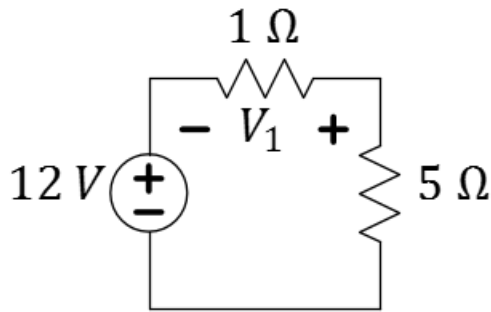


Use Voltage Divider Rule to find  $V_1$ .



**Step 1.** Identify the series resistances responsible for voltage drops.

The  $1\ \Omega$  resistor is in series with the  $5\ \Omega$  resistor. This is easier to see after rearranging the sketch as shown in the second schematic.

**Step 2.** Apply KVL to equate the sum of the voltage drops to the voltage being divided.

Voltage  $V_1$  is in the “reverse” polarity that we typically see it. While this is not inherently a problem, it can lead to confusion in the sign of the final voltage. We will define  $V_3 = -V_1$  for the comfort of the aspiring engineering student. Around the loop we get:

$$12 - V_3 - V_2 = 0$$

$$\Rightarrow V_3 + V_2 = 12$$

Which tells us that  $12\ V$  is being divided by the two resistor voltages,  $V_3$  and  $V_2$ .

**Step 3.** Apply VDR.

$$V_k = \frac{R_k}{R_{eq}} V$$

$$V_3 = \frac{1}{1+5} 12 = \frac{1}{6} 12 = 2\ V$$

$$V_1 = -V_3 = -2\ V$$

Answer:  $V_1 = -2\ V$