

1.2 Physical Structures

The major components of a power system can be represented in a block-diagram format, as shown in Figure 1.1.

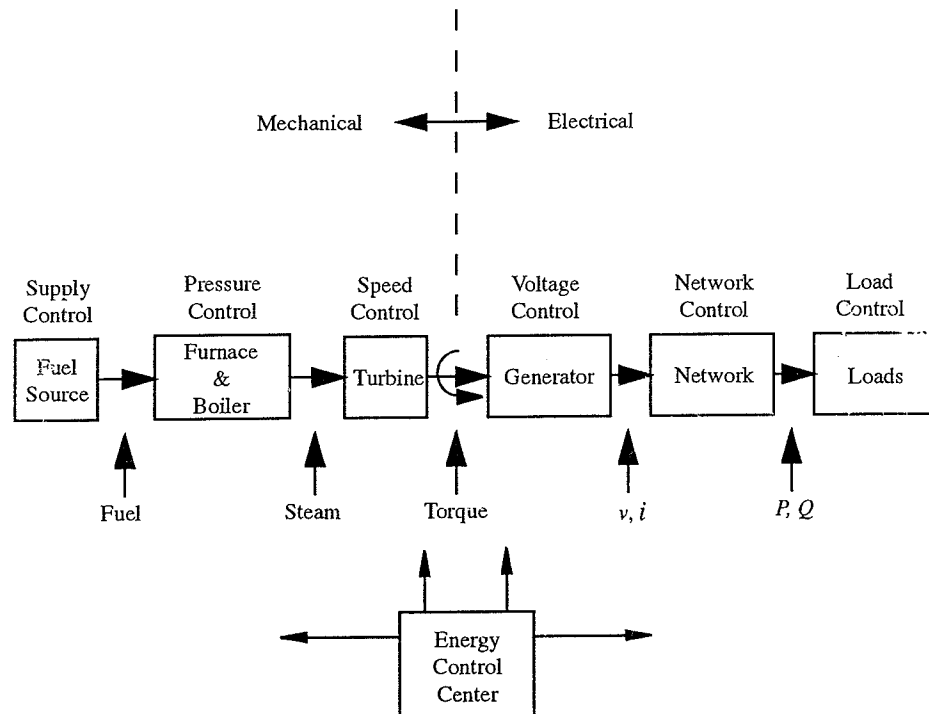


Figure 1.1: *System dynamic structure*

While this block diagram representation does not show all of the complex dynamic interaction between components and their controls, it serves to broadly describe the dynamic structures involved. Historically, there has been a major division into the mechanical and electrical subsystems as shown. This division is not absolute, however, since the electrical side clearly contains components with mechanical dynamics (tap-changing-under-load (TCUL) transformers, motor loads, etc.) and the mechanical side clearly contains components with electrical dynamics (auxiliary motor drives, process controls, etc.). Furthermore, both sides are coupled through the monitoring and control functions of the energy control center.

Power & 3φReview Phasors

Consider $v(t) = V_m \cos(\omega t + \theta_v)$


Euler's expansion $e^{j\theta} = \cos\theta + j\sin\theta$

$$\begin{aligned} \text{SO: } v(t) &= \text{Re}\{V_m e^{j(\omega t + \theta_v)}\} = \text{Re}\{V_m e^{j\theta_v} e^{j\omega t}\} \\ &= \text{Re}\{\sqrt{2} \bar{V} e^{j\omega t}\} \end{aligned}$$

$$\bar{V} \triangleq \frac{V_m}{\sqrt{2}} e^{j\theta_v} \quad (\text{RMS PHASOR - COSINE REF})$$

$$\left(\text{Recall } F_{\text{RMS}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} |f(t)|^2 dt} \right) \quad (\text{ROOT OF MEAN OF SQUARE})$$

STOP #1

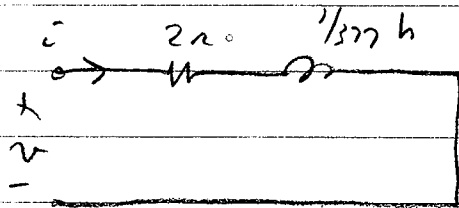
Example

For $i = 10 \sin 377t$ A, find v

$$v = iR + L \frac{di}{dt} = 20 \sin 377t + \frac{1}{377} (377 \times 10 \cos 377t)$$


$$= 20 \sin 377t + 10 \cos 377t = \sqrt{20^2 + 10^2} \cos(377t - \tan^{-1} \frac{20}{10})$$
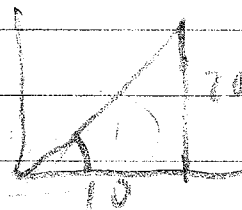
$$= \underline{22.36 \cos(377t - 63.4^\circ)} \text{ V}$$



#2

OR, use frequency (phasor) domain

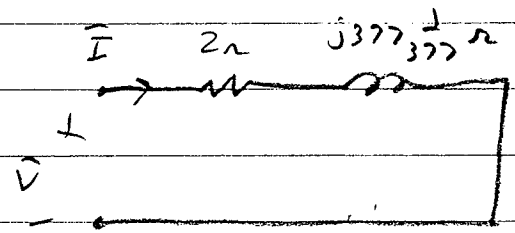

$\bar{I} = 7.07 \angle -90^\circ$ A. RMS

$\bar{V} = (2 + j1) 7.07 \angle -90^\circ = \sqrt{5} \angle 26.6^\circ 7.07 \angle -90^\circ = 15.8 \angle -63.4^\circ$ V. RMS

$v(t) = 22.36 \cos(377t - 63.4^\circ)$ V.

Recall

$v(t) \rightarrow \bar{V}$

$R \rightarrow R$

$i(t) \rightarrow \bar{I}$

$L \rightarrow j\omega L = jX_L$ ($X_L = \omega L$)

$C \rightarrow \frac{1}{j\omega C} = jX_C$ ($X_C = -\frac{1}{\omega C}$)

Series R, L $\bar{Z} = R + j\omega L$


Series R, C $\bar{Z} = R - j\frac{1}{\omega C}$

Series R, L, C $\bar{Z} = R + j(\omega L - \frac{1}{\omega C})$

$\bar{V} = \bar{Z} \bar{I}$ (\bar{Z} is not a phasor)

~~NOTE: The phasor should have been...~~

~~...~~

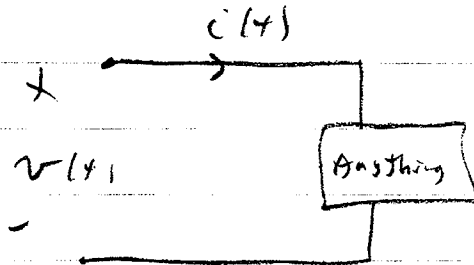

1. $P_{in}(t) = v(t)i(t)$ watts instantaneous power

2. If $v(t) = V_m \cos(\omega t + \theta_v)$

$i(t) = I_m \cos(\omega t + \theta_i)$

Then $p_{in}(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$

$$= V_m I_m \left\{ \frac{1}{2} \cos[(\omega t + \theta_v) - (\omega t + \theta_i)] \right.$$

$$\left. + \frac{1}{2} \cos[(\omega t + \theta_v) + (\omega t + \theta_i)] \right\}$$

$$= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i)$$

2009
2004
3. $P_{in} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$ (Avg or real power) watts

2005
4. $PF = \cos(\theta_v - \theta_i)$ power factor at P_{in}
lagging if $0 < \theta_v - \theta_i < 180$
leading if $-180 < \theta_v - \theta_i < 0$

5. $P_{app} = \frac{V_m I_m}{2}$ (Apparent power) voltamps

$$p(t) = P(1 + \cos(2\omega t + 2\theta_i)) - Q \sin(2\omega t + 2\theta_i)$$


(4)

STOP 2006

6. $Q_{in} = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$ (reactive power) vars

7. $\bar{S}_{in} = P_{in} + jQ_{in}$ (complex power) voltamps

$$= P_{app} \angle \theta_v - \theta_i$$

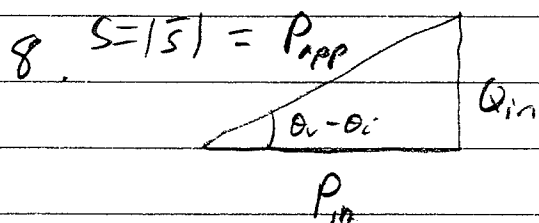

$$S = |\bar{S}| = \sqrt{P_{in}^2 + Q_{in}^2}$$

9. Note, for \bar{V} \bar{I} rms phasors,

$$\bar{S} = \bar{V} \bar{I}^* = \frac{V_m}{\sqrt{2}} \angle \theta_v \frac{I_m}{\sqrt{2}} \angle -\theta_i = \frac{V_m I_m}{2} \angle \theta_v - \theta_i$$


10. Note also, $\bar{V} = \bar{Z} \bar{I}$

$$\bar{Z} = \frac{\bar{V}}{\bar{I}} \quad \angle \bar{Z} = \angle \bar{V} - \angle \bar{I} = \theta_v - \theta_i$$

So: angle on \bar{Z} equals angle on \bar{S}

For \bar{Z} , $PF = \cos(\text{angle on } \bar{Z})$

Example

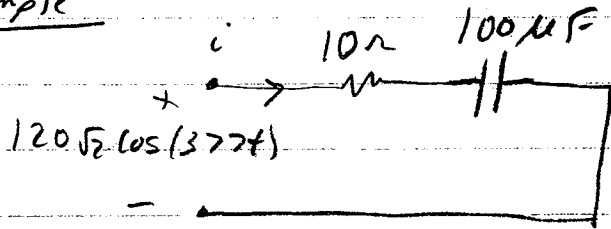

Find: i_{ss} \bar{S}_{in} P_{in} Q_{in} PF

Sdn: $\bar{V} = 120\angle 0$ $\bar{Z} = 10 - j26.5 = 28.3\angle -69^\circ$

$\bar{I} = \frac{120\angle 0}{28.3\angle -69^\circ} = 4.24\angle +69^\circ$

$i_{ss} = 4.24\sqrt{2} \cos(377t + 69^\circ)$

$\bar{S}_{in} = \bar{V} \bar{I}^* = 120\angle 0 \cdot 4.24\angle -69^\circ = 509\angle -69^\circ$ voltamperes

$P_{in} = 509 \cos -69^\circ = 182$ W

$Q_{in} = 509 \sin -69^\circ = -475$ vars

note $P^2 + Q^2 = 151^2$

PF = $\cos -69^\circ = 0.34$ lead ($\theta_v - \theta_i = -69^\circ$)


Work Series parallel examples

Summary

Add this to text
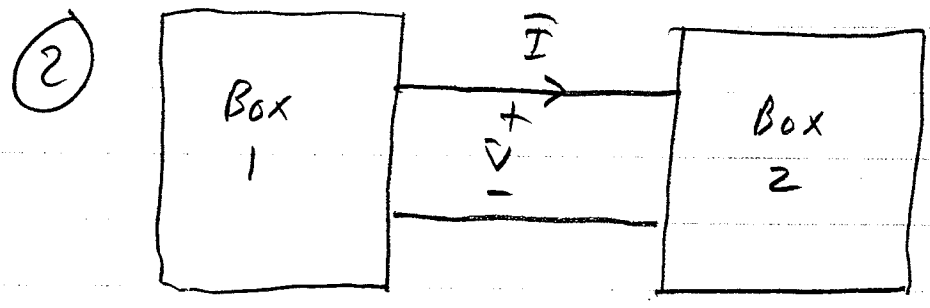
#3


- ① \bar{V} & \bar{I} are phasors
- \bar{S} & \bar{Z} are not phasors



We have "assumed" box 2 is the "load"

Suppose
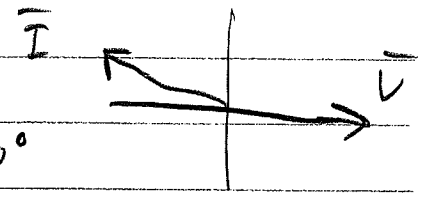
$$\bar{V} = 120 \angle 0 \quad \bar{I} = 4 \angle 150^\circ$$



$$\bar{S}_{IN, \text{Box 2}} = 480 \angle -150^\circ \quad \text{PF is not defined (Box 2 is source)}$$

$$= \bar{S}_{OUT, \text{Box 1}}$$


$$\bar{S}_{OUT, \text{Box 2}} = -480 \angle -150^\circ = 480 \angle 30^\circ \quad \text{PF} = .866 \text{ lag}$$

$$\bar{S}_{IN, \text{Box 1}} = \bar{S}_{OUT, \text{Box 2}}$$

So source must supply complex conjugate

Start 7/1

Sketch phasors

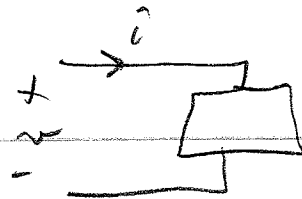


$$v(t) = 10\sqrt{2} \cos(\omega t + 30^\circ)$$

$$\bar{V} = 10 \angle 30^\circ$$

$$i(t) = 5\sqrt{2} \sin(\omega t + 70^\circ)$$

$$\bar{I} = 5 \angle -20^\circ$$

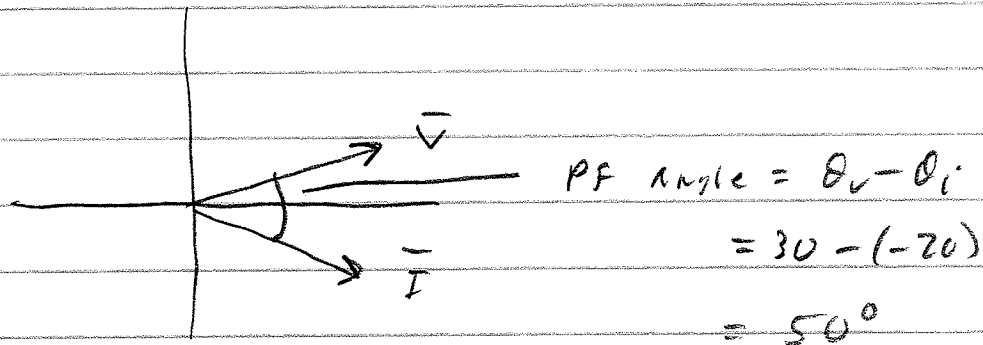

$$\bar{S}_{IN} = \bar{V} \bar{I}^* = 10 \angle 30^\circ 5 \angle 20^\circ = 50 \angle 50^\circ$$

$$= (50 \cos 50^\circ + j 50 \sin 50^\circ)$$

$$= 32.14 + j 38.3 = P_{IN} + j Q_{IN}$$

How many VARs do you need to "add" to make it unity power factor?

2003 Ans: 38.3

How many VARs do you need to "add" to make PF = .9 lag?

$$S = \frac{32.14}{.9} = 35.71$$

$$\theta = \cos^{-1} .9 = 25.84$$

$$35.71 \sin 25.84 = 15.56$$

Ans
22.7

Series

Parallel

Power triangle

Specifying Power of Load

S (kVA) + power factor

S (kVA) + P (watts)

S (kVA) + Q (VARs)


P (watts) + Q (VARs)

\bar{V} , \bar{I} (note can assume angle on I)

\bar{V} , \bar{Z}

\bar{I} , \bar{Z}

Problem 2.11

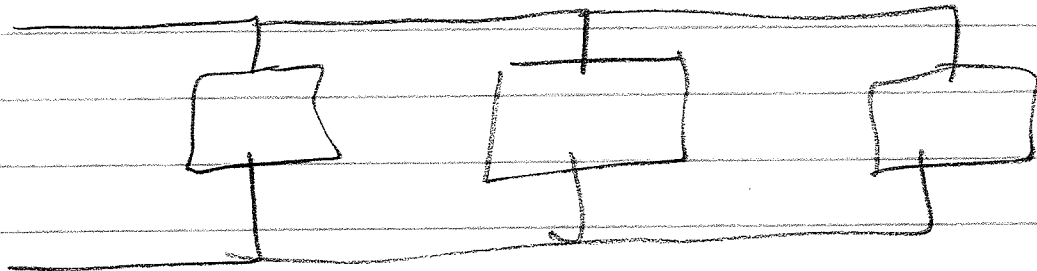

250 kVA
.5 PF lag

180 kW
.8 lead

$283 + j100$ kVA

$$\bar{S}_{TOT} = 250k \left[\cos^{-1}.5 \right] + \frac{180k}{.8} \left[-\cos^{-1}.8 \right] + (283 + j100)k$$

$$= 125k + j216.5k + 180k - j135k + 283k + j100k$$

$$= 588k + j181.5k$$

$$= 615k \left| 17.15^\circ \right. \quad \underline{PF = .9555 \text{ lag}}$$

Find Q to make PF = 0.8 lead (not sure why)

$$\bar{S} = 588k + j181.5k + jQ_{add}$$

$$\text{Want } \bar{S} = \frac{588k}{.8} \left[-\cos^{-1}.8 \right] = 735k \left[-37^\circ \right] = 588 - j442 \text{ k}$$


$$181.5k + Q_{add} = -442 \quad Q_{add} = -182 - 442$$

STOP #3


Do 1-phase residential first

#4


Three phase

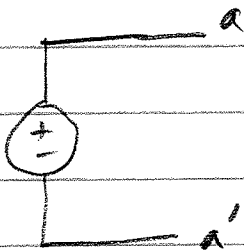
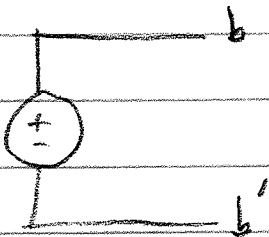
$$v_{aa'} = V_m \cos(\omega t + \theta_v)$$


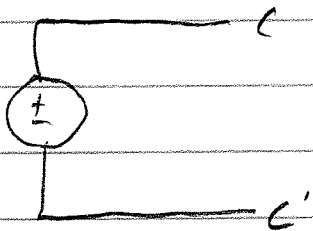
$$v_{bb'} = V_m \cos(\omega t + \theta_v - 120^\circ)$$



$$v_{cc'} = V_m \cos(\omega t + \theta_v + 120^\circ)$$

This is called positive (abc) sequence

An alternative would be negative (acb) sequence

- change (-120°) to $(+120^\circ)$ on b

- change $(+120^\circ)$ to (-120°) on c


abc

$$\bar{V}_{aa'} = \frac{V_m}{\sqrt{2}} \angle \theta_v$$

$$\bar{V}_{bb'} = \frac{V_m}{\sqrt{2}} \angle \theta_v - 120^\circ$$

$$\bar{V}_{cc'} = \frac{V_m}{\sqrt{2}} \angle \theta_v + 120^\circ$$

Let $\theta_v = 0$

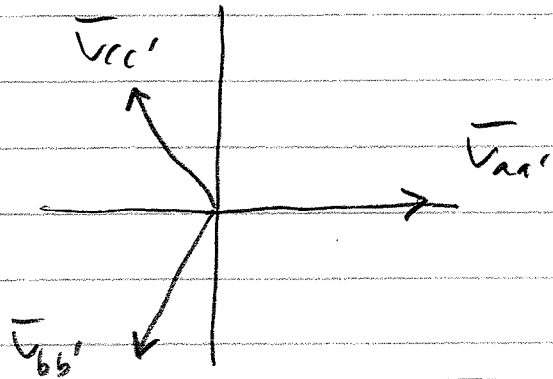

Note: $\bar{V}_{aa'} + \bar{V}_{bb'} + \bar{V}_{cc'} = 0$


acb

$$\bar{V}_{aa'} = \frac{V_m}{\sqrt{2}} \angle \theta_v$$

$$\bar{V}_{bb'} = \frac{V_m}{\sqrt{2}} \angle \theta_v + 120^\circ$$


$$\bar{V}_{cc'} = \frac{V_m}{\sqrt{2}} \angle \theta_v - 120^\circ$$

Let $\theta_v = 0$

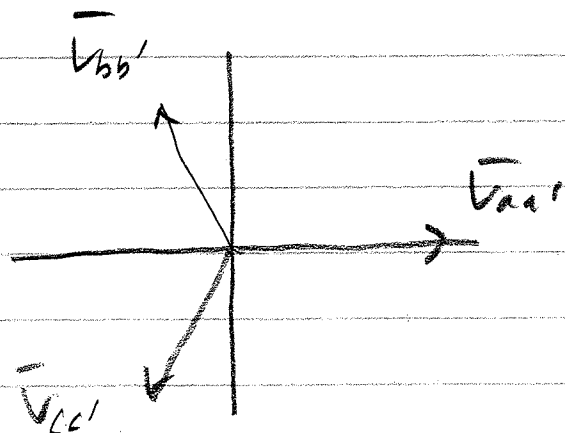

3-phase connections

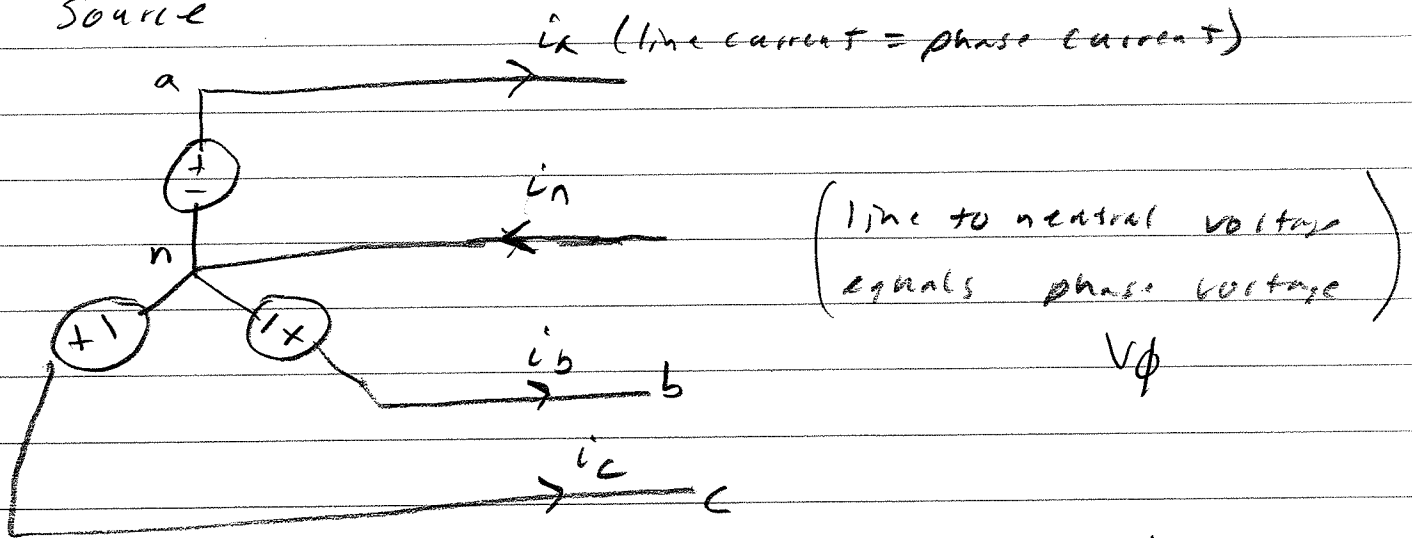
4-wire WYE ($\frac{Y}{n}$) (connect primes together)
 Source



("line" voltage = voltage between 2 lines)
 i.e. $V_{AB} = V_{an} + V_{nB} = V_{an} - V_{bn}$


For ABC sequence ($\theta_v = 0$)
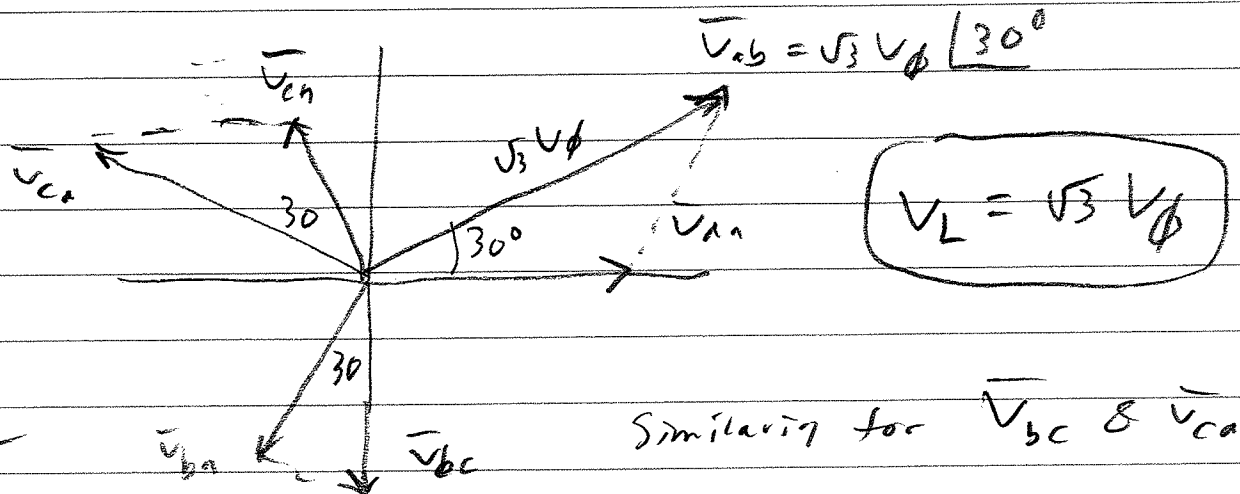
$$\vec{V}_{AB} = V_\phi \angle 0 - V_\phi \angle -120^\circ$$



Similarity for \vec{V}_{bc} & \vec{V}_{ca}

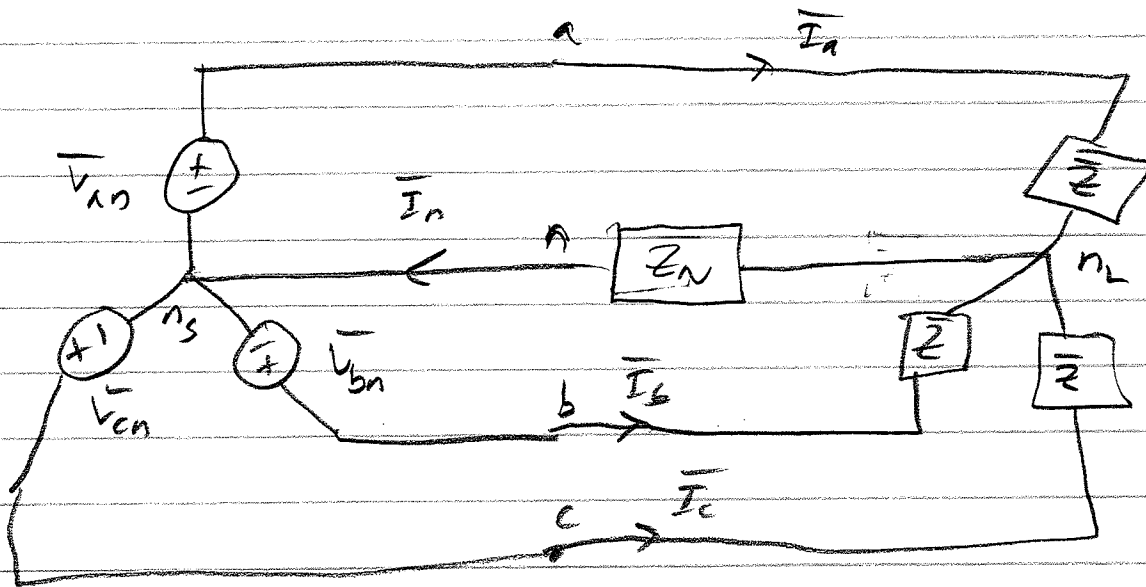4-wire Wye Source + 4-wire Wye Load (balanced)



note: $I_{Line} = I_{phase}$

$$-V_{ans} + I_a \bar{Z} + I_n \bar{Z}_n = 0 \quad (I_\phi)$$

$$-V_{bns} + I_b \bar{Z} + I_n \bar{Z}_n = 0$$

$$-V_{cns} + I_c \bar{Z} + I_n \bar{Z}_n = 0$$

add

$$0 + \bar{Z} (I_a + I_b + I_c) + 3 I_n \bar{Z}_n = 0$$

but by KCL $I_a + I_b + I_c = I_n$

$$\text{so: } I_n (\bar{Z} + 3 \bar{Z}_n) = 0$$


$$\text{so: } I_n = 0 \quad \text{so } V_{anL} = V_{ans} \text{ etc.}$$

$$I_a = \frac{V_{ans}}{\bar{Z}} \text{ etc.}$$
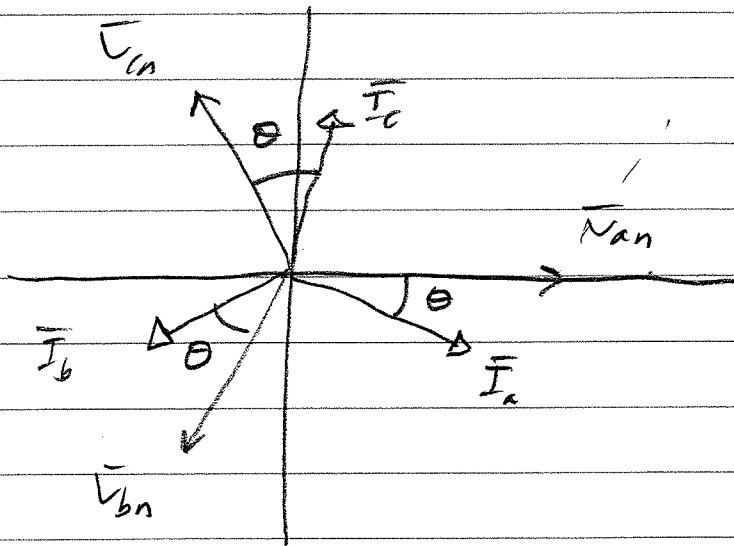
#5

$$\text{Let } \bar{z} = z \angle \theta \quad \text{and } \theta_v = 0$$

$$\bar{I}_a = \frac{V_\phi \angle 0}{z \angle \theta} = \frac{I_L \angle -\theta}{\phi} = I_L \angle -\theta$$



$$\bar{S}_{3\phi} = \bar{S}_a + \bar{S}_b + \bar{S}_c + \bar{S}_n$$

$$= \bar{V}_{anL} \bar{I}_a^* + \bar{V}_{bnL} \bar{I}_b^* + \bar{V}_{cnL} \bar{I}_c^* + \bar{V}_{nLnS} \bar{I}_n^*$$

$$= \bar{V}_{aNS} \bar{I}_a^* + \bar{V}_{bNS} \bar{I}_b^* + \bar{V}_{cNS} (-\bar{I}_a - \bar{I}_b)$$

$$= \bar{V}_{ac} \bar{I}_a^* + \bar{V}_{bc} \bar{I}_b^* = \bar{V}_{bc} \bar{I}_b^* - \bar{V}_{ca} \bar{I}_a^*$$

$$= \sqrt{3} V_\phi \angle -90^\circ I_L \angle +170^\circ + \theta - \sqrt{3} V_\phi \angle 150^\circ I_L \angle +\theta$$

$$= \sqrt{3} V_\phi I_L \left(1 \angle 30^\circ + \theta - 1 \angle 150^\circ + \theta \right)$$

$$\vec{S}_{3\phi} = \sqrt{3} V_{\phi} I_L \begin{pmatrix} \cos(30+\theta) + j \sin(30+\theta) \\ -\cos(150+\theta) - j \sin(150+\theta) \end{pmatrix}$$

$$= \sqrt{3} V_{\phi} I_L \begin{pmatrix} \frac{\sqrt{3}}{2} \cos \theta - \frac{1}{2} \sin \theta + j \frac{1}{2} \cos \theta + j \frac{\sqrt{3}}{2} \sin \theta \\ + \frac{\sqrt{3}}{2} \cos \theta + \frac{1}{2} \sin \theta - j \frac{1}{2} \cos \theta + j \frac{\sqrt{3}}{2} \sin \theta \end{pmatrix}$$

$$= \sqrt{3} V_{\phi} I_L (\sqrt{3} \cos \theta + j \sqrt{3} \sin \theta)$$


$$= 3 V_{\phi} I_L \angle \theta$$

$$= \sqrt{3} V_L I_L \angle \theta$$

$$P_{3\phi} = \sqrt{3} V_L I_L \cos \theta$$

$$Q_{3\phi} = \sqrt{3} V_L I_L \sin \theta$$

#6

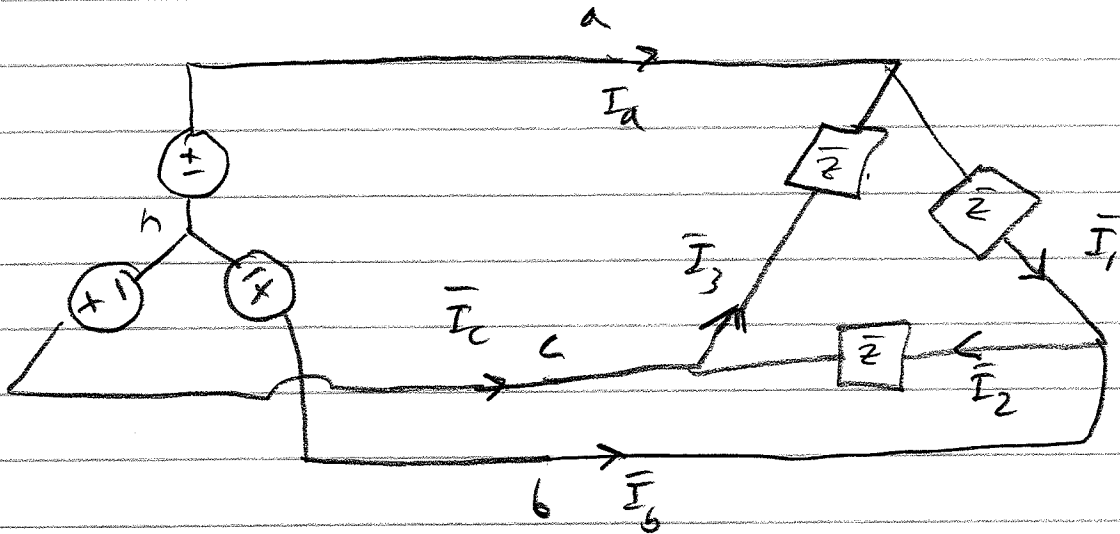3-wire X_{source} supplying Δ load

$$\bar{I}_1 = \frac{\bar{V}_{ab}}{Z} \quad \bar{I}_2 = \frac{\bar{V}_{bc}}{Z} \quad \bar{I}_3 = \frac{\bar{V}_{ca}}{Z}$$

Assume $\bar{V}_{ab} = V_L \angle 0^\circ$ (same as assume $\theta_V = -30^\circ$)
ABC sequence


Assume $Z = Z \angle \theta$ $\theta = 45^\circ$

2003

$$\bar{I}_a = \bar{I}_1 - \bar{I}_3$$

$$\bar{I}_b = \bar{I}_2 - \bar{I}_1$$

$$\bar{I}_c = \bar{I}_3 - \bar{I}_2$$

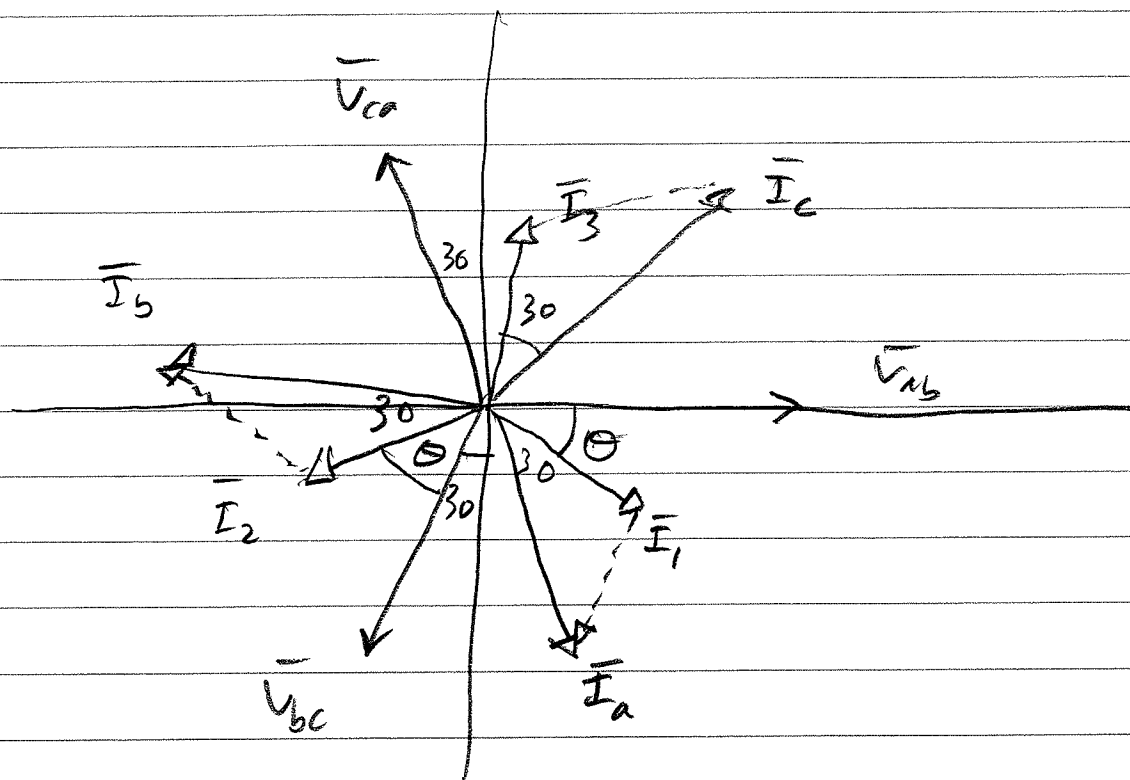

For $\bar{I}_1 = I_\phi \angle -\theta$

$$\bar{I}_a = \sqrt{3} I_\phi \angle -\theta - 30^\circ = I_L \angle -\theta - 30^\circ$$

etc.

Point is

$$I_L = \sqrt{3} I_\phi$$

$$\overline{S}_{3\phi} = \overline{S}_{ab} + \overline{S}_{bc} + \overline{S}_{ca}$$

$$= \overline{V}_{ab} \overline{I}_1^* + \overline{V}_{bc} \overline{I}_2^* + \overline{V}_{ca} \overline{I}_3^*$$

$$= V_L \angle 0^\circ I_0 \angle +\theta + V_L \angle -120^\circ I_0 \angle +120^\circ + \theta + V_L \angle +120^\circ I_0 \angle -120^\circ + \theta$$

$$= 3 V_L I_0 \cos \theta$$

$$= \sqrt{3} V_L I_L \cos \theta$$

$$P_{3\phi} = \sqrt{3} V_L I_L \cos \theta$$

Same as Y-Y

$$Q_{3\phi} = \sqrt{3} V_L I_L \sin \theta$$

Example (Text problem 2.16)

$$V_L = 345 \text{ kV} \quad S_{3\phi} = 750 \text{ MVA} \quad \text{PF} = 0.8 \text{ lag}$$

Delta connected load

Find: a) $\bar{Z}_{\text{per phase}}$ b) I_L & I_{ϕ} c) P & Q per phase

d) $S_{3\phi}$

Soln: Delta connected load, so $I_{\phi} = \frac{750 \text{ MVA} / 3}{345 \text{ kV}}$

$$(a) I_{\phi} = \frac{250 \times 10^6}{345 \times 10^3} = 725 \text{ A}$$

$$\bar{Z} = \frac{345 \text{ kV}}{725 \text{ A}} = 476 \Omega$$

$$\theta = +\cos^{-1} 0.8 = 37^\circ$$

$$\bar{Z} = 476 \angle 37^\circ$$

per phase

$$(b) I_{\phi} = 725 \quad I_L = \sqrt{3} I_{\phi} = 1256 \text{ A}$$

$$(c) P_{\text{per phase}} = 345 \text{ kV} \times 725 \text{ A} \times 0.8 = 200 \text{ MW}$$

$$Q_{\text{per phase}} = 345 \text{ kV} \times 725 \text{ A} \times \sin(37^\circ) = 150 \text{ MVAR}$$

$$\begin{aligned}
 (d) \quad \bar{S}_{3\phi} &= (3 \times 200 + j3 \times 150) \text{ mVA} \\
 &= 600 + j450 \text{ mVA} \\
 &= 750 \angle 37^\circ
 \end{aligned}$$

check: $\theta = 37^\circ \checkmark$

check: $P_{3\phi} = \sqrt{3} \times 345 \text{ k} \times 1256 \times \cos(37^\circ) \approx 600 \text{ MW} \checkmark$

$Q_{3\phi} = \sqrt{3} \times 345 \text{ k} \times 1256 \times \sin(37^\circ) \approx 450 \text{ MVAR} \checkmark$

$$\bar{S}_{3\phi} = \sqrt{3} \times 345 \text{ k} \times 1256 \angle 37^\circ$$

$$= 750 \angle 37^\circ \text{ mVA} \checkmark$$

Example (HEAT 2.22)

$$\bar{S}_3 = 15k \angle -\cos^{-1} 0.8 + \frac{72k}{0.8} \angle +\cos^{-1} 0.8$$

$$= 15k \angle -37^\circ + 90k \angle 37^\circ$$

$$= 12,000 - j9,600 + 71,900 + j54,200$$

$$= 83,900 + j44,600 = 95,300 \angle 28^\circ$$

$$a) \quad 95,300 = \sqrt{3} \times 2000 \times I_L \quad I_L = 27.5 \text{ A}$$

$$\text{PF} = \cos 28^\circ = 0.88 \text{ lag}$$



b) need 45.2 kVAR to bring PF to unity

#7

Per-phase equivalents

For Y-Y


Just use phase a quantities

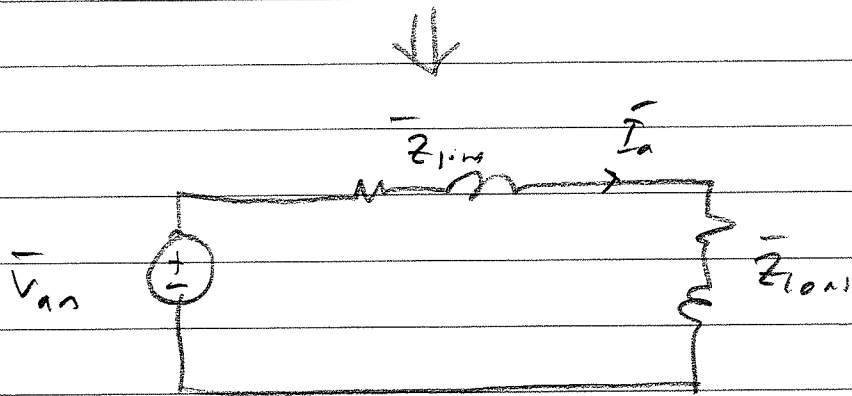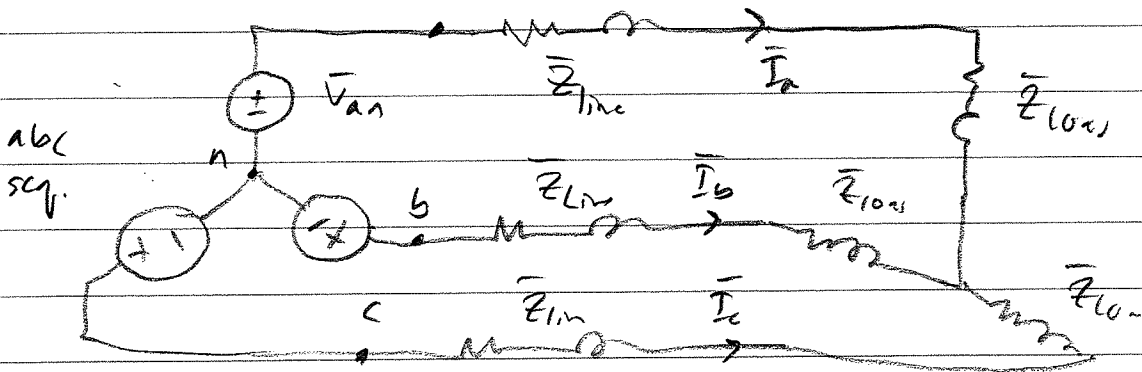

$$\bar{I}_a = \frac{\bar{V}_{an}}{\bar{Z}_{line} + \bar{Z}_{load}}$$

Then rotate 120° for \bar{I}_b \bar{I}_c

For Y Δ

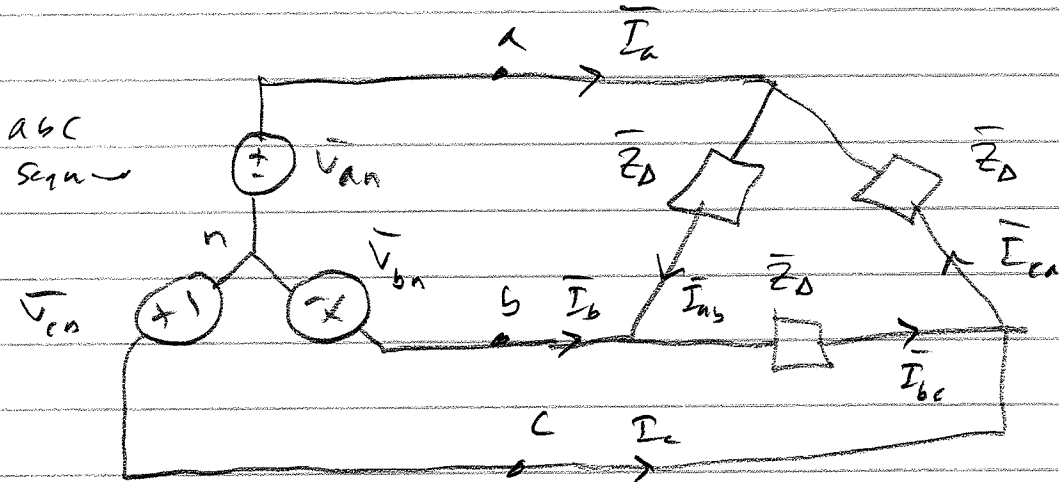


$$\begin{aligned} \bar{V}_{an} = V \angle 0 &\rightarrow \bar{V}_{ab} = \sqrt{3} V \angle 30^\circ \\ \bar{V}_{bc} &= \sqrt{3} V \angle -90^\circ \\ \bar{V}_{ca} &= \sqrt{3} V \angle 150^\circ \end{aligned}$$

$$\bar{I}_{ab} = \frac{\sqrt{3} V \angle 30^\circ}{\bar{Z}_D} \quad \bar{I}_{bc} = \frac{\sqrt{3} V \angle -90^\circ}{\bar{Z}_D} \quad \bar{I}_{ca} = \frac{\sqrt{3} V \angle 150^\circ}{\bar{Z}_D}$$

$$\bar{I}_a = \bar{I}_{ab} - \bar{I}_{ca} = \sqrt{3} \angle -30^\circ \bar{I}_{ab} = \frac{3V}{\bar{Z}_D} \angle 0 = \frac{V_{an}}{\bar{Z}_D/3} = \frac{\bar{V}_{an}}{\bar{Z}_Y}$$


$$\bar{Z}_Y = \frac{\bar{Z}_\Delta}{3}$$

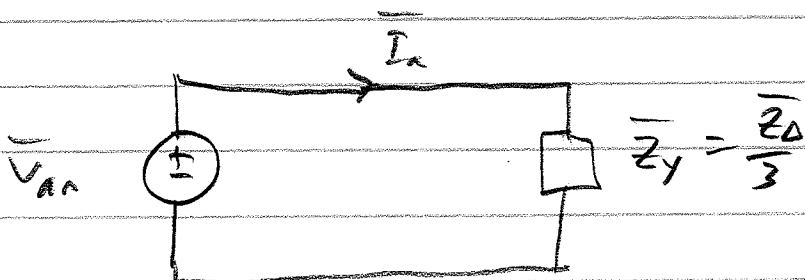

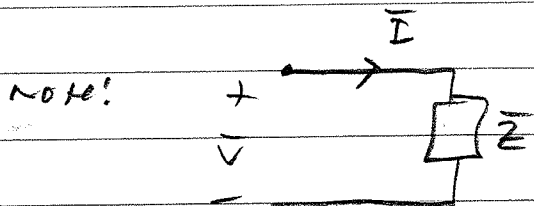Example (text 2.23)

$$\bar{S}_{3\phi} = 1000k \angle 37^\circ = 800k + j600k \quad V_L = 4160v$$

$$\begin{aligned} \bar{S}_{\Delta} &= (800k + j600k) - (200k + j0) \\ &= 600k + j600k = 848k \angle 45^\circ \end{aligned}$$



$$\bar{S} = V \bar{I}^* = V \cdot \left(\frac{V}{Z} \right)^* = \frac{|V|^2}{Z^*}$$

$$\frac{600k + j600k}{3} = \frac{4160^2}{Z^*} \quad (1\phi \text{ connected})$$

$$\bar{Z} = \frac{4160^2 \times 3}{600k - j600k} = \frac{51.9 \times 10^6}{600\sqrt{2}k \angle -45^\circ}$$

$$= 61.2 \angle 45^\circ \Omega = 43.3 + j43.3 \Omega$$

NOTE: $1000k = \sqrt{3} \times 4160 \times I_{L \text{ TOTAL}}$

$$I_{L \text{ TOTAL}} = 139A$$

$$I_L = I_\phi = \frac{200k}{\sqrt{3} \times 4160} = 28A$$


$$I_{L \Delta} = \frac{848k}{\sqrt{3} \times 4160} = 118A$$

$$I_\phi = \frac{118}{\sqrt{3}} = 68A$$

(Checks with $\frac{4160v}{61.52}$)

Suppose the "Line" has an impedance

Per phase circuit

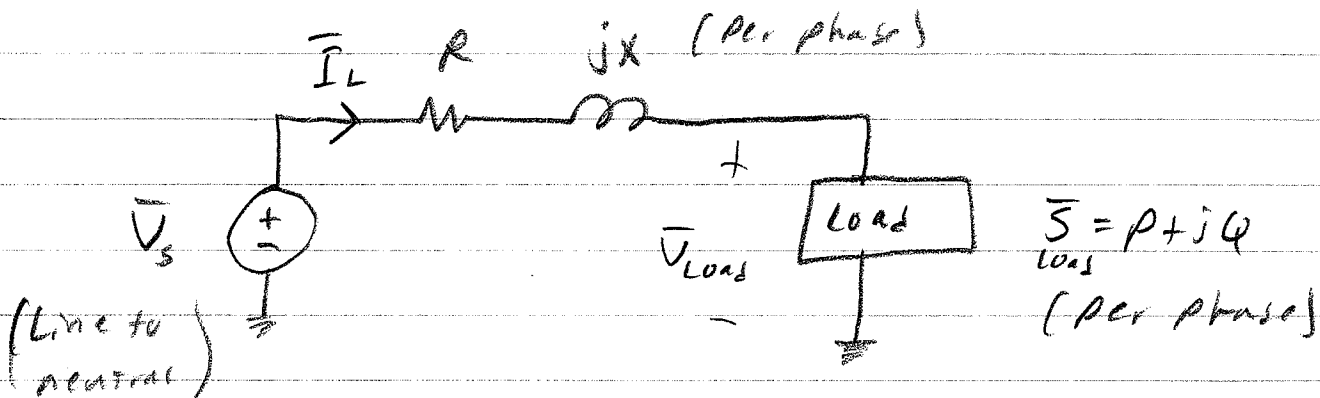

Given: P, Q, R, X, V_{Load} (magnitude)

Find: V_s (magnitude)

assume this

Soln: $\bar{S}_{Load} = P + jQ = V_{Load} \angle 0 \bar{I}_L^*$

$$\bar{I}_L = \left(\frac{\bar{S}_{Load}}{V_{Load} \angle 0} \right)^*$$


Then: $\bar{V}_s = (R + jX) \bar{I}_L + \bar{V}_{Load}$

— work other text problems

Chapter 3

Magnetic Circuits

Review of EM

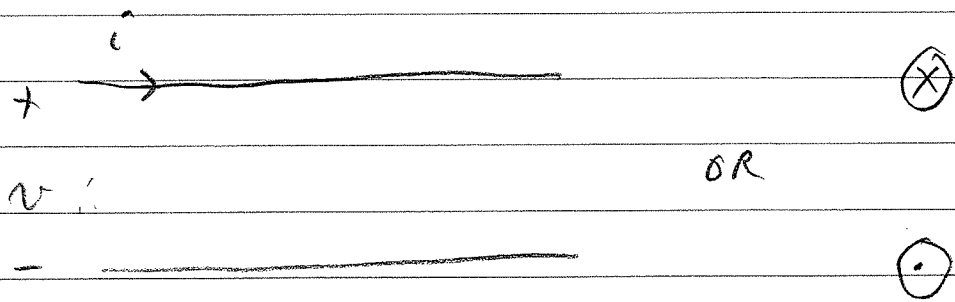

Normally taught that i produces H, B (Ampere)

v produces E, D (Faraday)

Example


Ampere's Law

$$\oint_C \underline{H} \cdot d\underline{l} = \int_S \underline{J}_f \cdot d\underline{a}$$

could be 3 dimensional

"C" encloses "S" $\underline{n} \perp \underline{S}$ IAW RHR dir of C

Assume uniform H, B around conductor.

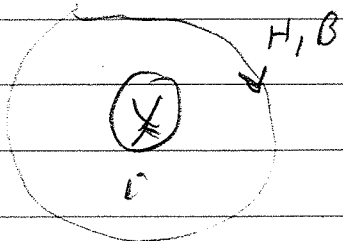

$$Hl = i$$

$$H = \frac{i}{l}$$

The B and H go in air to get around the conductor

Ampere's Law


$$\oint_C \underline{H} \cdot d\underline{l} = \int_S \underline{J} \cdot d\underline{a}$$

"C"
encloses
"S"

$\underline{n} \perp$ to S IAW RHR of dir of C

Assume i

& H

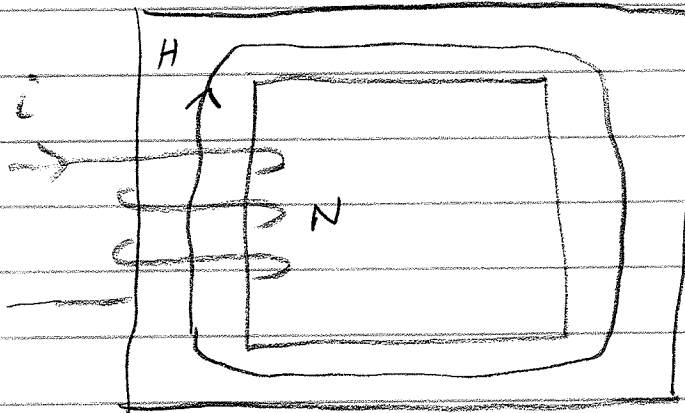

Assume most H
is in iron
because
 μ is large

Take contour around H path

$$Hl = Ni \quad (\text{MMF} - \mathcal{F})$$

$$H = \frac{Ni}{l} \quad \text{Amp turns/m}$$

STOP 2005
+ 2012

Assume linear $B = \mu H = \frac{\mu Ni}{l}$ weber/m² (Tesla)


$$\phi = BA = \left(\frac{\mu A}{l} \right) Ni \quad \text{wb} \quad (\text{Reluctance}) \quad R = \frac{l}{\mu}$$

Faraday's Law

$$\oint_C \underline{E} \cdot d\underline{l} = - \frac{d}{dt} \int_S \underline{B} \cdot \underline{n} da$$

$\underline{n} \perp$ to S IAW RHR DIR of C

Assum ν
& H

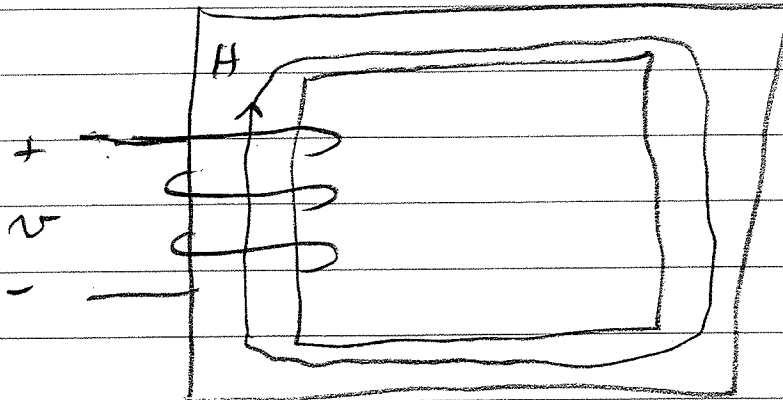

Assum

$$\sigma \rightarrow \infty$$

(no R)

$$J = \sigma E$$

$$J \text{ finite} \quad E_{\text{wire}} \rightarrow 0$$

$$-\nu + 0 = - \frac{d}{dt} (NBA) \quad \lambda$$

$$\nu = N \frac{d\phi}{dt} = \frac{d\lambda}{dt} \quad (\lambda = N\phi)$$

Put these two together:

$$\nu = N^2 \frac{\mu A}{l} \frac{di}{dt} = L \frac{di}{dt}$$

#9

Example

$$v = 120\sqrt{2} \cos 2\pi 60t$$

$$N = 100 \text{ turns}$$

$$A = .0049 \text{ m}^2$$

$$l = 40 \text{ cm}$$

$$\mu = 1000\mu_0 = 1000 \times 4\pi \times 10^{-7} \text{ H/m}$$

Find: L (steady state)

$$120\sqrt{2} \cos(2\pi 60t) = 100 \frac{d\phi}{dt}$$

$$\phi = \frac{120\sqrt{2} \sin 2\pi 60t}{100 \times 2\pi 60} = .0045 \sin 2\pi 60t \text{ wb}$$

(steady state)

$$B = \frac{\phi}{A} = \frac{.0045 \sin 2\pi 60t}{.0049} = 0.92 \sin 2\pi 60t \text{ T}$$

$$H = \frac{B}{\mu} = \frac{0.92 \sin 2\pi 60t}{1000 \times 4\pi \times 10^{-7}} = 731 \sin 2\pi 60t \frac{\text{Amp} \cdot \text{turns}}{\text{m}}$$

$$P = \frac{\mu A}{l} = \frac{1000 \times 4\pi \times 10^{-7} \times (.07)^2}{.4} = 1.54 \times 10^{-5} \text{ H}$$

$$R = \frac{1}{P} = 64,961 \text{ H}^{-1}$$

$$L = N^2 P = 100^2 \times 1.54 \times 10^{-5} = 0.154 \text{ H}$$

$$v = L \frac{di}{dt}$$

$$170 \sqrt{2} \cos 2\pi 60 t = 0.154 \frac{di}{dt}$$

$$i = \frac{120 \sqrt{2} \sin 2\pi 60 t}{0.154 \times 2\pi 60} = 2.9 \sin 2\pi 60 t$$


(Steady state)

$$\lambda = Li = 0.154 \times 2.9 \sin 2\pi 60 t$$

$$= 0.45 \sin 2\pi 60 t \text{ Wb turns} //$$

check $v = \frac{d\lambda}{dt} = 170 \cos 2\pi 60 t \quad \checkmark$

#10

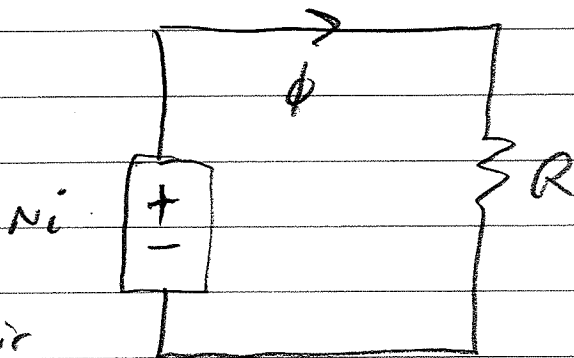Equivalent magnetic circuitMMF (\mathcal{F}) \Rightarrow Voltage (v)Flux (ϕ) \Rightarrow current (i)Reluctance (R) \Rightarrow resistance (R)

Thumb in dir
of \vec{i} (in coil)


RHR fingers go - to +

$$Ni = R\phi$$

For $i = 2.95 \sin 2\pi 60t$, $N = 100$, $R = 64,961$

$$\phi = \frac{100 \times 2.95 \sin 2\pi 60t}{64,961} = 0.00455 \sin 2\pi 60t \quad \checkmark$$

Add an air gap to iron

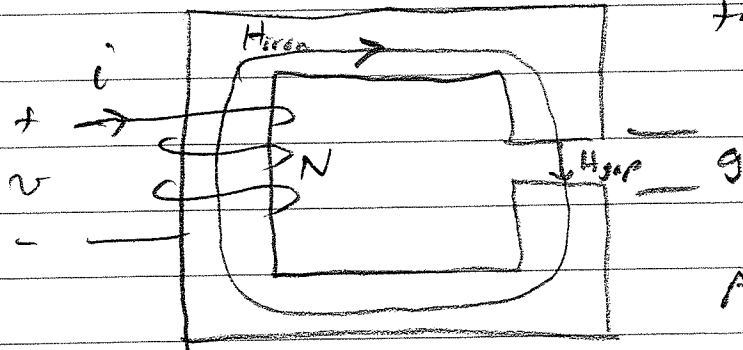

Assume all flux takes full path

Conservation of flux
One B; two H

Area A

Ampere's law

$$\oint_C \underline{H} \cdot d\underline{l} = \int_S \underline{J} \cdot d\underline{a}$$

S encircling wire $\Delta \perp$ to S EAW RHR dir of C

$$H_{\text{iron}} l_{\text{iron}} + H_{\text{gap}} g = Ni \quad (\text{mean path } l)$$

Conservation of flux

$$\oint_S \underline{B} \cdot d\underline{a} = 0$$


$\Delta \perp$ to S OUT

$$\phi = B_{\text{iron}} A_{\text{iron}} = B_{\text{gap}} A_{\text{gap}}$$

$$B_{\text{iron}} = \mu_{\text{iron}} H_{\text{iron}} \quad B_{\text{gap}} = \mu_0 H_{\text{gap}}$$

$$H_{\text{iron}} = \frac{\phi}{\mu_{\text{iron}} A_{\text{iron}}} \quad H_{\text{gap}} = \frac{\phi}{\mu_0 A_{\text{gap}}}$$
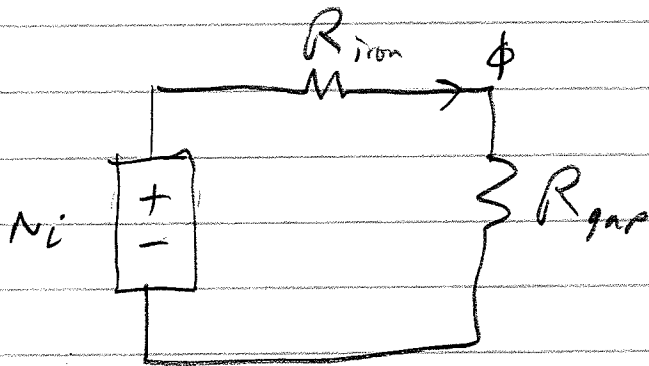
$$\left(\frac{\mu_{\text{iron}}}{\mu_0 A_{\text{iron}}} \right) \phi + \left(\frac{g}{\mu_0 A_{\text{gap}}} \right) \phi = Ni$$



NOTE

$$R_{\text{iron}} \ll R_{\text{gap}}$$

$$\phi = \frac{Ni}{R_{\text{iron}} + R_{\text{gap}}}$$

Faradays Law

$$\oint_C \vec{E} \cdot d\vec{l} = - \frac{d}{dt} \int_S \vec{B} \cdot \vec{n} \, da$$

S curl C, n ⊥ to S IAW RHR DIR OF C


$$-v + 0 = - \frac{d}{dt} \lambda = - \frac{d}{dt} N\phi$$

$$v = N \frac{d\phi}{dt} = \underbrace{\frac{N^2}{R_{\text{iron}} + R_{\text{gap}}}}_{L} \frac{di}{dt}$$

Let $\mu_{\text{iron}} \rightarrow \infty$

$$L \approx \frac{N^2 \mu_0 A}{g} = N^2 R_{\text{gap}}$$

Fringing

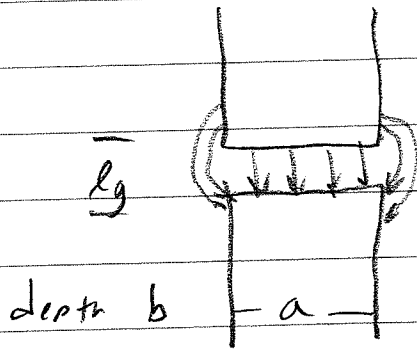

Flux forced to "outside" + b
gap makes the area bigger

$$A_c = ab$$

$$A_{gap} = (a + l_g)(b + l_g)$$


(empirical)

Explain what it means to have:

$$\mu \rightarrow \infty \quad (H = 0)$$

— Do parallel paths

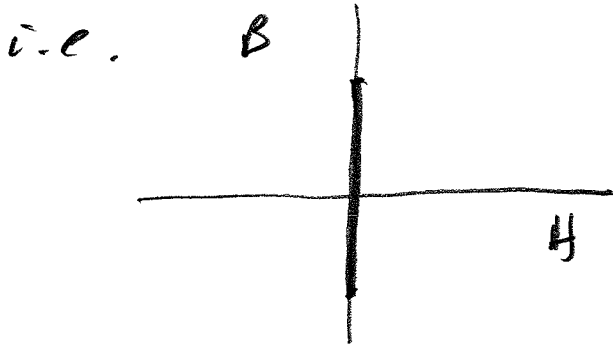NOTE: If $\mu \rightarrow \infty$, $H \rightarrow 0$




B is finite and

H is zero


R is zero

Example

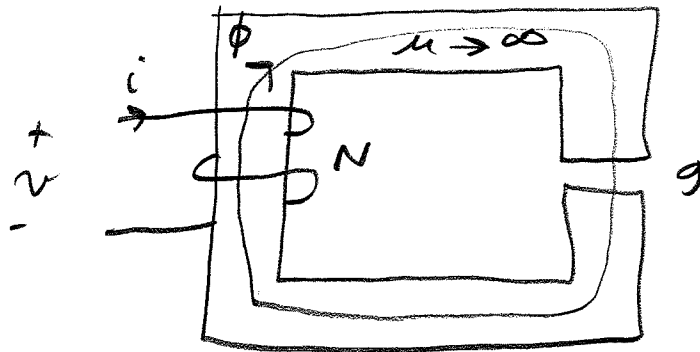

$$\mathcal{N} = N \frac{d\phi}{df}$$
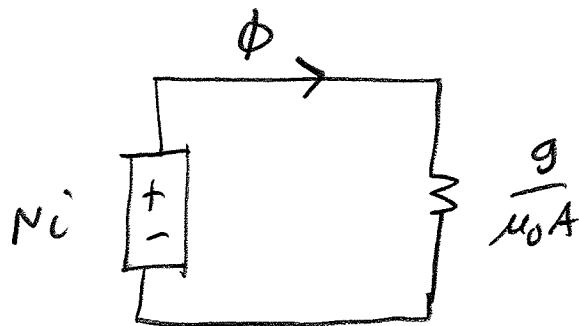
$$\phi = B_{\text{iron}} A = B_{\text{gap}} A$$




$$\phi = \frac{Ni}{(g/\mu_0 A)} = \frac{\mu_0 A N^2 i}{g}$$

$$\lambda = \frac{\mu_0 A N^2 i}{g}$$

Mutual Inductance

(Coupled coils)

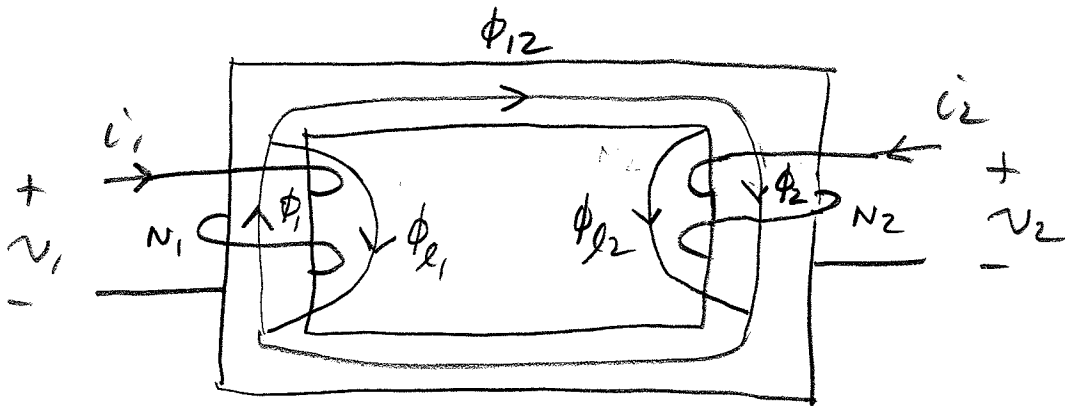

Consider 3 flux paths \Rightarrow 5 fluxes

ϕ_1 = total flux linking coil #1

ϕ_{12} = flux which links both coil #1 & coil #2


ϕ_{21} = flux which links coil #1 only

ϕ_2 = flux which links coil #2 only

Faraday's Law:
$$\left. \begin{aligned} v_1 &= \frac{d\lambda_1}{dt} & v_2 &= \frac{d\lambda_2}{dt} \\ \lambda_1 &= N_1 \phi_1 & \lambda_2 &= N_2 \phi_2 \end{aligned} \right\} \begin{array}{l} \text{depends on assumed} \\ \text{voltage polarities} \\ \text{and flux assumed} \\ \text{directions} \end{array}$$

(now find ϕ_1 and ϕ_2)

Magnetic Equivalent Circuit

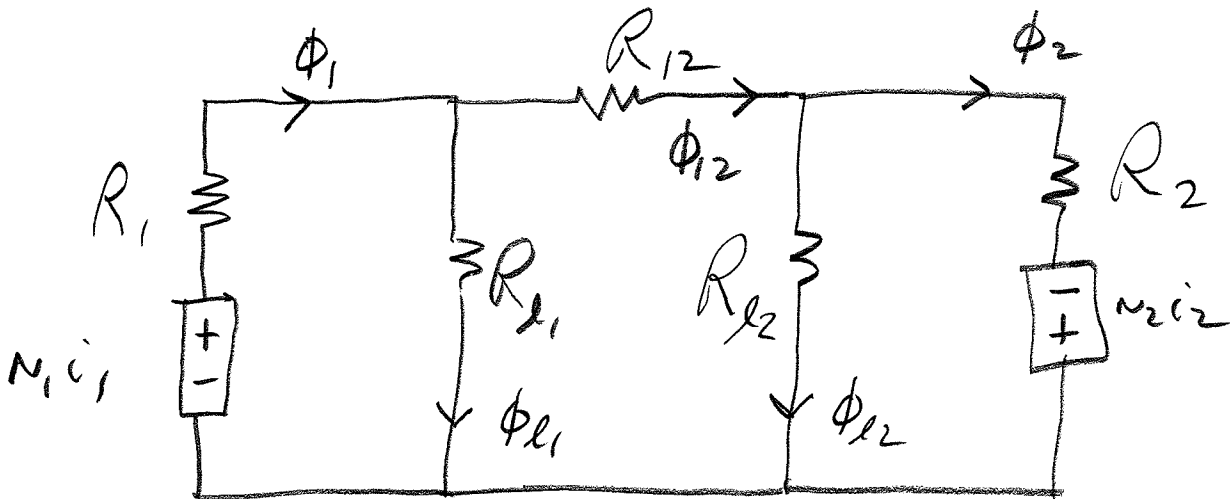

$$-N_1 i_1 + R_1 \phi_1 + R_{l1} \phi_{l1} = 0$$

$$R_{12} \phi_{12} + R_{l2} \phi_{l2} - R_{l1} \phi_{l1} = 0$$

$$R_2 \phi_2 - N_2 i_2 - R_{l2} \phi_{l2} = 0$$

$$\phi_1 - \phi_{12} - \phi_{l1} = 0$$

$$\phi_{12} - \phi_2 - \phi_{l2} = 0$$

Each $R = \frac{l}{\mu A}$

(not so obvious for leakage paths)

5 Equations

5 unknowns

Solve these 5 linear equations for the 5 fluxes

will get:

$$\phi_1 = a N_1 i_1 + b N_2 i_2$$

$$\phi_2 = b N_1 i_1 + c N_2 i_2$$

Then:

$$\lambda_1 = N_1 \phi_1 = a N_1^2 i_1 + b N_1 N_2 i_2$$

$$\lambda_2 = N_2 \phi_2 = b N_1 N_2 i_1 + c N_2^2 i_2$$

OR

$$\lambda_1 = \underbrace{L_{11}}_{\text{Self inductance Coil \#1}} i_1 + \underbrace{L_{12}}_{\text{mutual inductance 1 to 2}} i_2$$

$$\lambda_2 = \underbrace{L_{21}}_{\text{mutual inductance 2 to 1}} i_1 + \underbrace{L_{22}}_{\text{Self inductance Coil \#2}} i_2$$

mutual inductance
2 to 1

Self inductance
coil #2

In this case, $|L_{12}| = |L_{21}| = M$ (a positive number)

$$v_1 = L_1 \frac{di_1}{dt} + m \frac{di_2}{dt}$$

$$v_2 = m \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

X don't
show
this!

$$k \stackrel{\Delta}{=} \frac{m}{\sqrt{L_1 L_2}}$$

$$0 \leq k \leq 1$$

$k=0$ no coupling $\rightarrow M=0$
(all leakage)

$k=1$ full coupling $\rightarrow M = \sqrt{L_1 L_2}$
(no leakage)

NOTE: M is never negative

There may be cases where $L_{12} = -M$,

or $L_{21} = -M$, but M is always ≥ 0

For example:

In the last derivation, suppose

we change the sign on i_2

using $i_2' = -i_2$

The equations then are:

$$v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2'}{dt}$$

$$v_2 = M \frac{di_1}{dt} - L_2 \frac{di_2'}{dt}$$

and, if we reverse the polarity on v_2

using $v_2' = -v_2$

$$v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2'}{dt}$$

$$v_2' = -M \frac{di_1}{dt} + L_2 \frac{di_2'}{dt}$$