
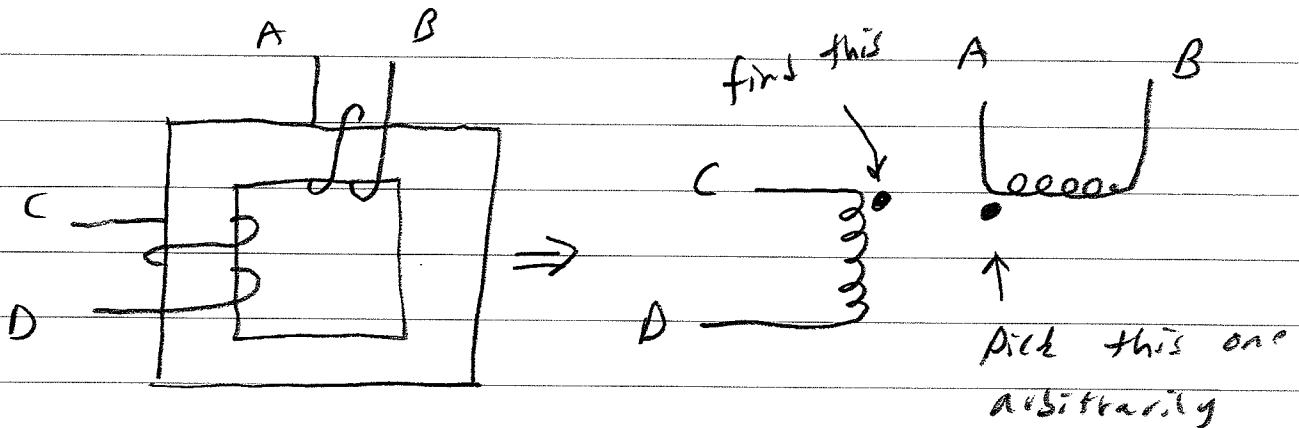


Polarity marks (The dot convention)


The dots are only needed when there are two or more coils.

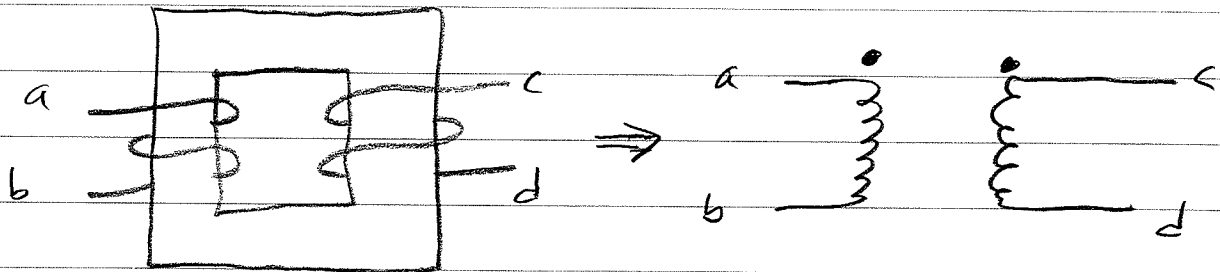The dots tell you how the coil is "wound"




TO find the second dot:

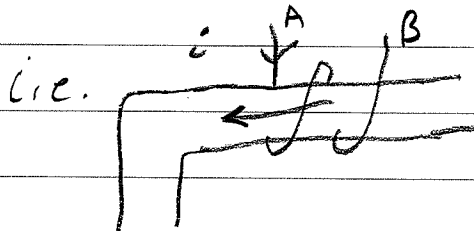1. Inject current into "first dot" and use Right Hand Rule to find flux direction in iron




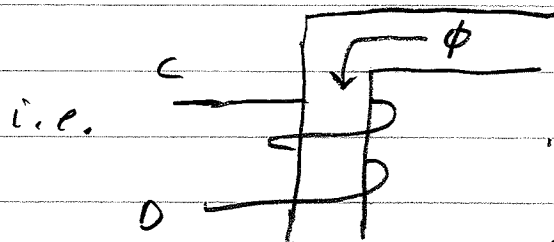2. Put "Second dot" on the terminal of the other coil whose injection current gives the same flux direction of iron




"Second dot" goes on C because if you inject current into C, it will create ϕ in same direction

Example

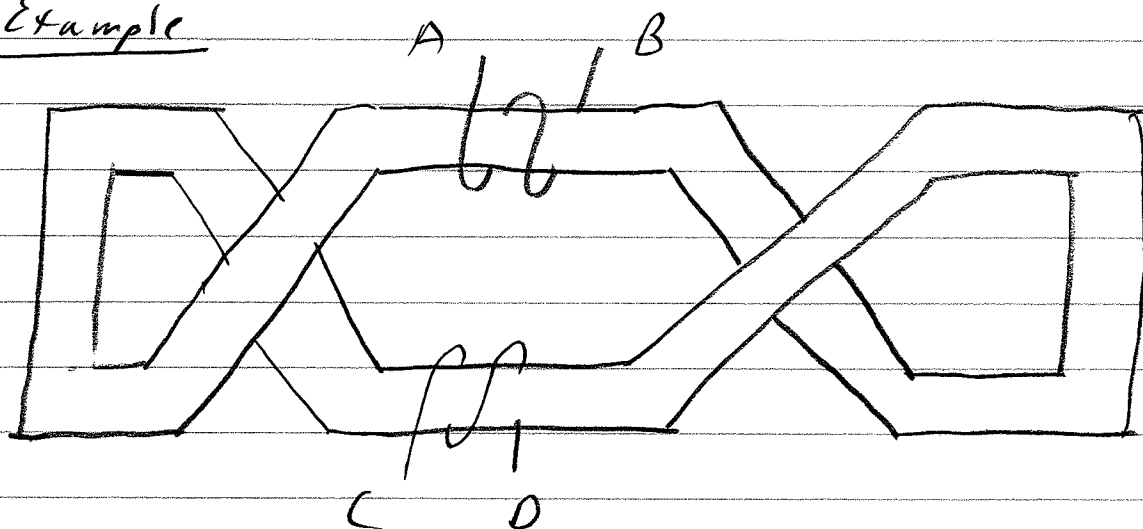

1. Pick terminal A for first dot
2. Inject current into A flux goes \rightarrow through iron of top coil and \leftarrow through bottom coil.
3. To get flux due to bottom coil to go \leftarrow , inject current into C: so dot on C

Writing equations

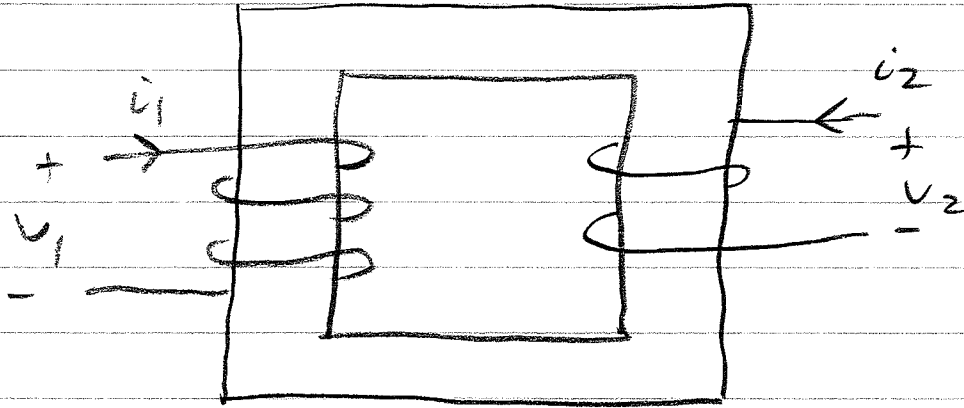

With resistance included,

$$v_1 = i_1 R_1 + \frac{d\lambda_1}{dt}$$

$$v_2 = i_2 R_2 + \frac{d\lambda_2}{dt}$$

magnetic analysis would show that

$$\left. \begin{aligned} \lambda_1 &= L_1 i_1 - m i_2 \\ \lambda_2 &= -m i_1 + L_2 i_2 \end{aligned} \right\} \begin{array}{l} \text{where } L_1, L_2, m \\ \text{are all positive} \end{array}$$

So:


$$v_1 = i_1 R_1 + L_1 \frac{di_1}{dt} - m \frac{di_2}{dt}$$

$$v_2 = i_2 R_2 - m \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

#13

13.1

The "circuit model" for this is:

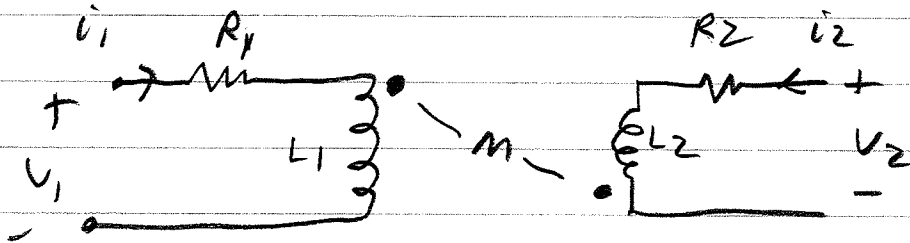


$$v_1 = i_1 R_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

nothing to do
with dots

minus because we are
summing drops in left
KVL and we want drop
from "dot" to "under"

So:

The mutual term will be
 M times the derivative
of the current entering
the dot of coil 2.
This is $-i_2$

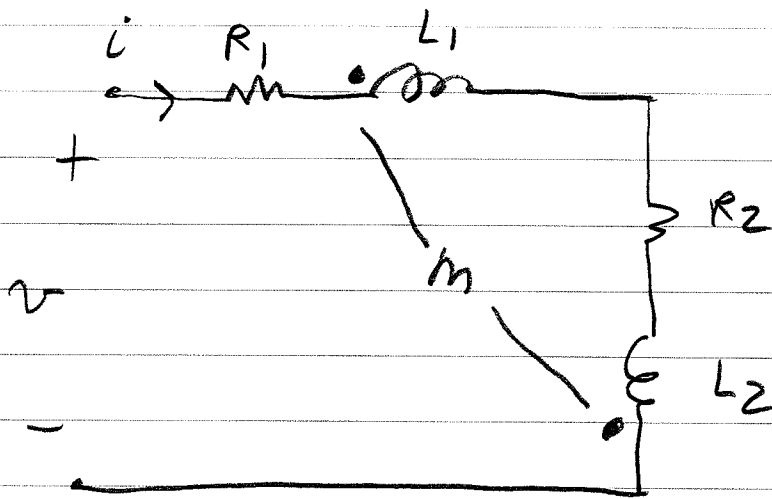Example

(Always assume
 L_1 L_2 M
 are positive)

$$-v + R_1 i + L_1 \frac{di}{dt} - M \frac{di}{dt} + R_2 i + L_2 \frac{di}{dt} - M \frac{di}{dt}$$

do not need dots for this
do not use dots for this

minus because we want voltage drop from dot to undot of coil 1, so we use the current "into" the dot of coil 2 - which is $-i$

minus because we want voltage drop from undot to dot of coil 2, so use the current "into" the undot of coil 1 - which is $-i$


Go through Example 3.6 if time allows

IDEAL TRANSFORMER

Active ideal model

$$\sigma = \infty$$

$$\mu = \infty$$

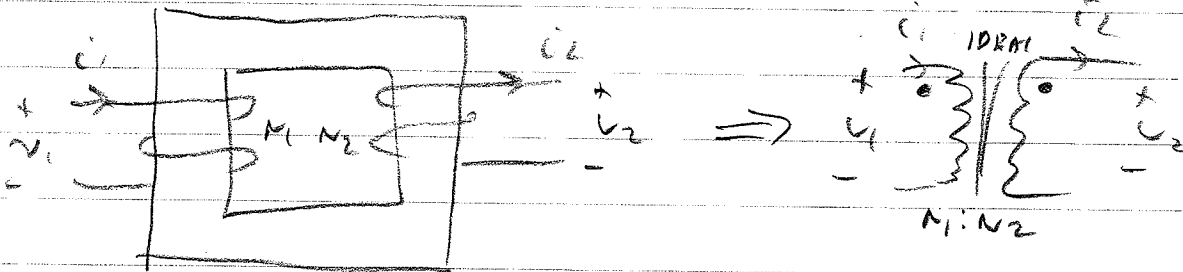

$$N_1 i_1 = N_2 i_2$$

$$v_2 = \frac{N_2}{N_1} v_1$$


$$a = \frac{N_1}{N_2}$$

- a) If you change label of i , change sign of i
- b) If " " " " " v_1 " " " " v
- c) If " " the dots, change sign of i & v

Can show this means $k=1$

$$L_1 = L_2 = M = \infty$$


"Refer" impedances across transformer

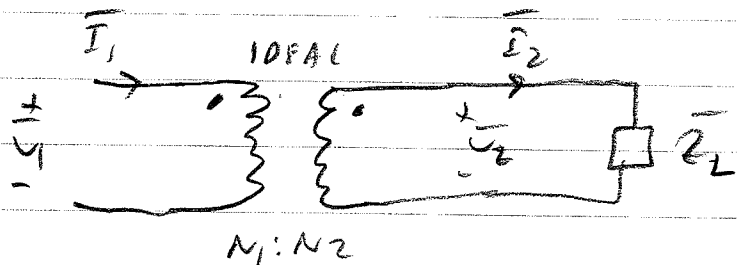


$$\bar{V}_2 = \bar{I}_2 \bar{Z}_L$$

$$\bar{V}_1 = \frac{N_1}{N_2} \bar{V}_2 = \frac{N_1}{N_2} (\bar{I}_2 \bar{Z}_L) = \frac{N_1}{N_2} \left(\left(\frac{N_1}{N_2} \bar{I}_1 \right) \bar{Z}_L \right)$$
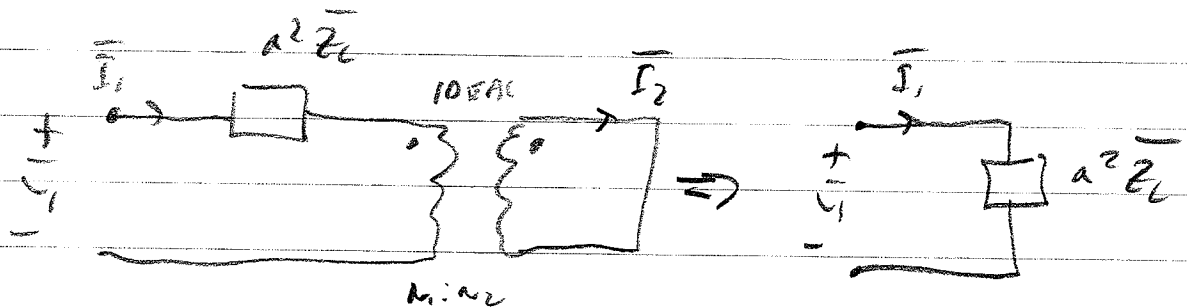
$$= \left(\frac{N_1}{N_2} \right)^2 \bar{Z}_L \bar{I}_1$$



Maximum Power Transfer

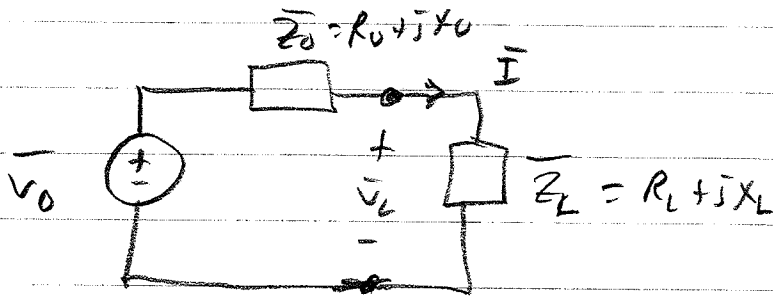

$$P_{TO} = \text{Real}(\bar{V}_L \bar{I}^*) \quad \text{OR}$$
$$= |\bar{I}|^2 R_L = \frac{|\bar{V}_0|^2 R_L}{((R_0 + R_L)^2 + (X_0 + X_L)^2)}$$

For fixed $|\bar{V}_0|$, R_0 , X_0 , what should R_L & X_L be?

maximize P_{TO} with respect to R_L & X_L
load

By inspection, set $X_L = -X_0$

$$P_{TO} = \frac{|\bar{V}_0|^2 R_L}{(R_0 + R_L)^2}$$

load
 $X_L = -X_0$

$$\frac{\partial P_{\text{To Load}}}{\partial R_L} = |\bar{V}_0|^2 \left(\frac{1}{(R_0 + R_L)^2} - \frac{2R_L}{(R_0 + R_L)^3} \right) = 0$$

multiply by $(R_0 + R_L)^2$ get $(R_0 + R_L) = 2R_L$

$$\boxed{R_L = R_0}$$

OR $\boxed{\bar{Z}_L = \bar{Z}_0^*}$

What if $X_L = 0$ (no reactance)?

$$P_{\text{To Load}} = \frac{|\bar{V}_0|^2 R_L}{(R_0 + R_L)^2 + X_0^2}$$

$$\frac{\partial P_{\text{To Load}}}{\partial R_L} = |\bar{V}_0|^2 \left(\frac{1}{(R_0 + R_L)^2 + X_0^2} - \frac{R_L (2(R_0 + R_L))}{((R_0 + R_L)^2 + X_0^2)^2} \right) = 0$$

multiply by $((R_0 + R_L)^2 + X_0^2)$ get

$$(R_0 + R_L)^2 + X_0^2 = 2R_L(R_0 + R_L)$$

$$R_0^2 + \cancel{2R_0R_L} + R_L^2 + X_0^2 = \cancel{2R_LR_0} + 2R_L^2$$

$$R_L^2 = R_0^2 + X_0^2$$

$$\boxed{R_L = \sqrt{R_0^2 + X_0^2} = |\bar{Z}_0|}$$

What if X_L cannot be changed?

$$P_{T0} = \frac{V_{01}^2 R_L}{(R_0 + R_L)^2 + (X_0 + X_L)^2}$$

For fixed X_L

$$\frac{2P_{T0}}{2R_L} = V_{01}^2 \left(\frac{1}{(R_0 + R_L)^2 + (X_0 + X_L)^2} - \frac{2R_L(R_0 + R_L)}{((R_0 + R_L)^2 + (X_0 + X_L)^2)^2} \right)$$

$$(R_0 + R_L)^2 + (X_0 + X_L)^2 = 2R_L R_0 + 2R_L^2$$

$$R_0^2 + \cancel{2R_0 R_L} + R_L^2 + (X_0 + X_L)^2 = \cancel{2R_L R_0} + 2R_L^2$$

$$R_L^2 = R_0^2 + (X_0 + X_L)^2$$

$$R_L = \sqrt{R_0^2 + (X_0 + X_L)^2}$$

What if R_L and X_L are constrained so

$$\frac{R_L}{X_L} = \text{constant?} \quad (\text{i.e. } X_L = c R_L)$$

$$P_{T0} = \frac{|V_0|^2 R_L}{(R_0 + R_L)^2 + (X_0 + c R_L)^2}$$

$$\frac{\partial P_{T0}}{\partial R_L} = |V_0|^2 \left(\frac{1}{(R_0 + R_L)^2 + (X_0 + c R_L)^2} - \frac{R_L (2(R_0 + R_L) + 2c(X_0 + c R_L))}{((R_0 + R_L)^2 + (X_0 + c R_L)^2)^2} \right)$$

$$= 0$$

$$\text{get } (R_0 + R_L)^2 + (X_0 + c R_L)^2 = 2R_0 R_L + 2R_L^2 + 2c R_L X_0 + 2c^2 R_L^2$$

$$R_0^2 + 2R_0 R_L + R_L^2 + X_0^2 + 2c R_L X_0 + c^2 R_L^2 = \quad //$$

$$R_0^2 + X_0^2 = c^2 R_L^2 + R_L^2 = R_L^2 (1 + c^2)$$



$$R_L = \frac{1}{\sqrt{1+c^2}} \sqrt{R_0^2 + X_0^2}$$

$$X_L = \frac{c}{\sqrt{1+c^2}} \sqrt{R_0^2 + X_0^2}$$

OR $R_L^2 + X_L^2 = R_0^2 + X_0^2$

$$|\vec{z}_L| = |\vec{z}_0|$$

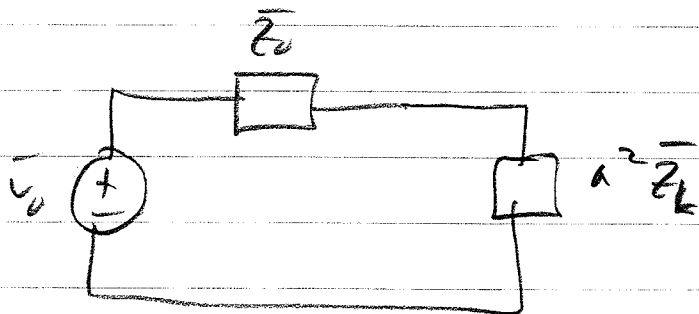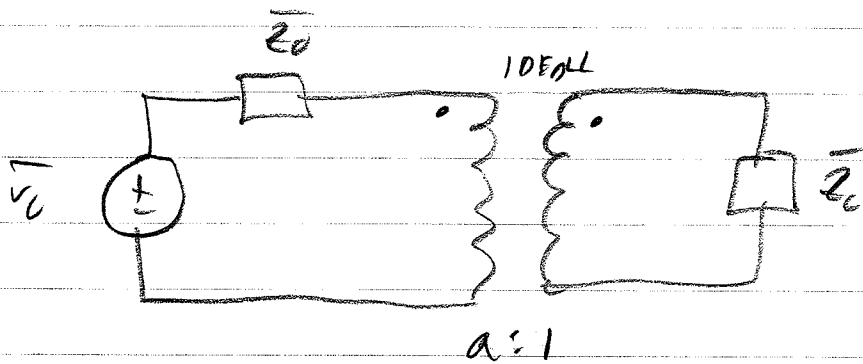USE THIS TO MAXIMIZE POWER TO FIXED \bar{Z}_L
USING A TRANSFORMER



Select a so that $|a^2 \bar{Z}_L| = |\bar{Z}_0|$

$$a = \sqrt{\frac{|\bar{Z}_0|}{|\bar{Z}_L|}}$$

#15

Power Transformer

Design consideration #1 = flux level

$$v_1 = v_{m1} \cos \omega t = N_1 \frac{d\phi}{dt}$$

$$\phi = \frac{v_{m1} \sin \omega t}{N_1 \omega}$$

$$\phi_{max} = \frac{v_{m1}}{2\pi f N_1}$$

$$v_{m1} = 2\pi f N_1 \phi_{max}$$

$$v_{RMS} = \sqrt{2} \pi f N_1 \phi_{max}$$

$$= 4.44 f N_1 \phi_{max}$$

Given Specified $v_{RMS} = 230$ v, $f = 60$ Hz

$$\phi_{max} = \frac{230}{4.44 \times 60 N_1}$$



$$B_{max} = \frac{\phi_{max}}{Area}$$

Given $N_1 = 200$ $Area = .005 \text{ m}^2$

$$B_{max} = 0.864 \text{ T}$$


Now add winding resistance, leakage L & magnetic flux

Recall

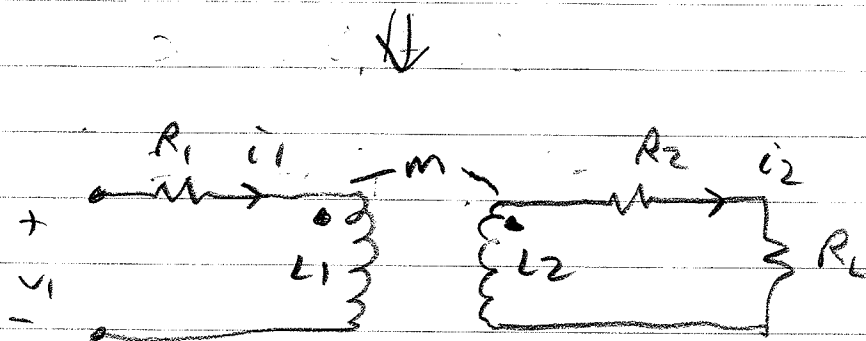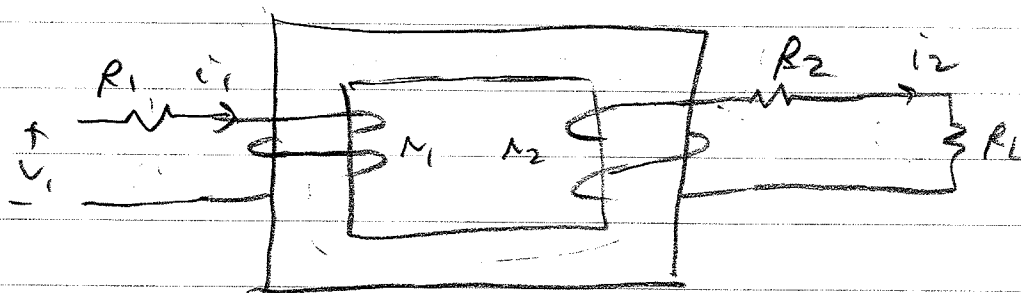


$$v_1 = i_1 R_1 + L_1 \frac{di_1}{dt} - m \frac{di_2}{dt}$$
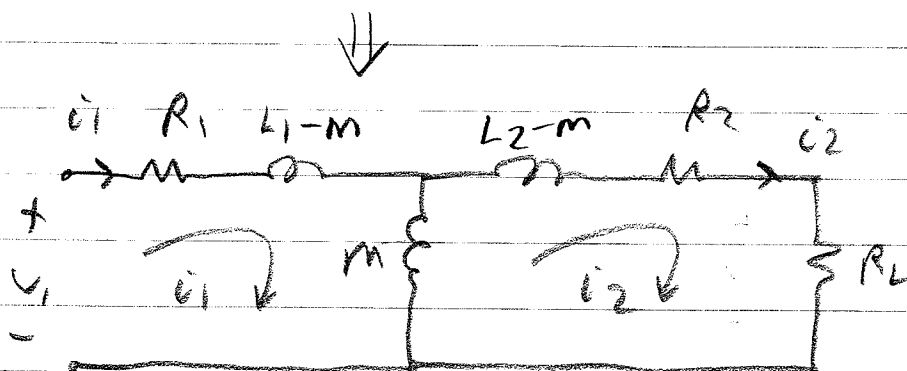
$$0 = i_2 R_2 + i_2 R_L + L_2 \frac{di_2}{dt} - m \frac{di_1}{dt}$$



OR

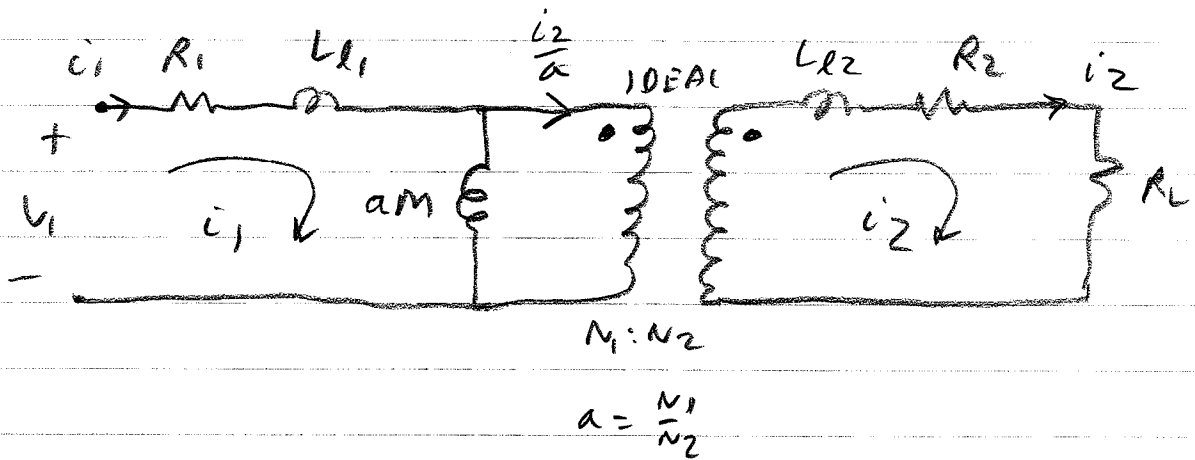


$$v_1 = R_1 i_1 + L_{l1} \frac{di_1}{dt} + aM \left(\frac{di_1}{dt} - \frac{1}{a} \frac{di_2}{dt} \right)$$

$$aM \left(\frac{di_1}{dt} - \frac{1}{a} \frac{di_2}{dt} \right) = a \left[L_{l2} \frac{di_2}{dt} + R_2 i_2 + R_L i_2 \right]$$

$$\left(\begin{array}{l} L_{l1} + aM = L_1 \\ L_{l2} + \frac{M}{a} = L_2 \end{array} \Rightarrow \begin{array}{l} L_{l1} = L_1 - aM \\ L_{l2} = L_2 - \frac{M}{a} \end{array} \right)$$


Core losses

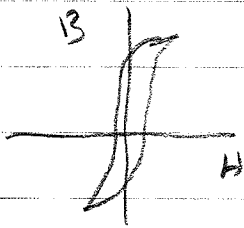1. Hysteresis $P_h \approx k_h f B_m^{1.6}$ (Heunster)



realize magnetic domain

2. Eddy currents

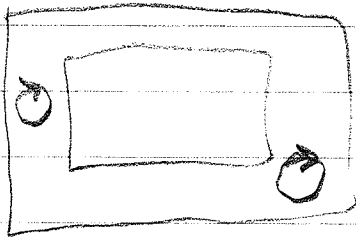

circulating currents in iron
Laminations reduce this in
the "depth" direction

$$P_e \approx k_e f^2 B_m^2$$


Since B_m depends on voltage,

$$B_m \propto V_{source}$$


Add as shunt resistor

Sinusoidal Steady State (Phasors etc.)

(and "refer" to 1 side)

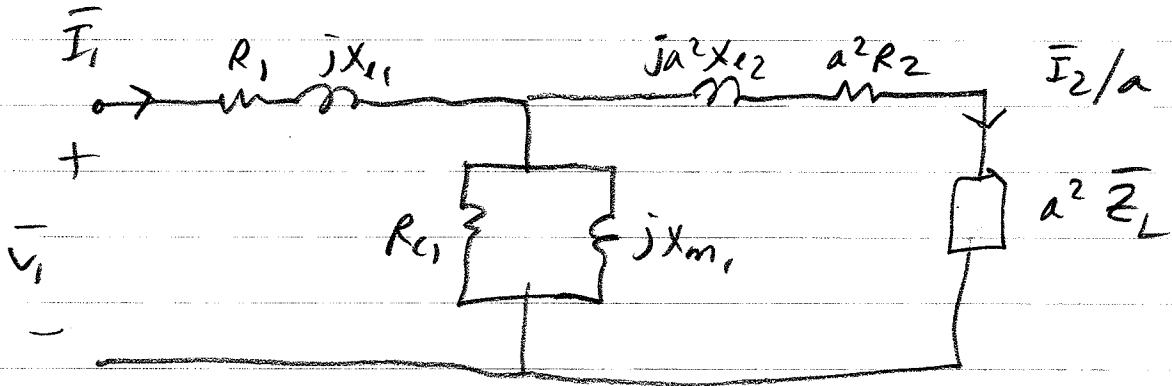

Approximate equivalent circuit

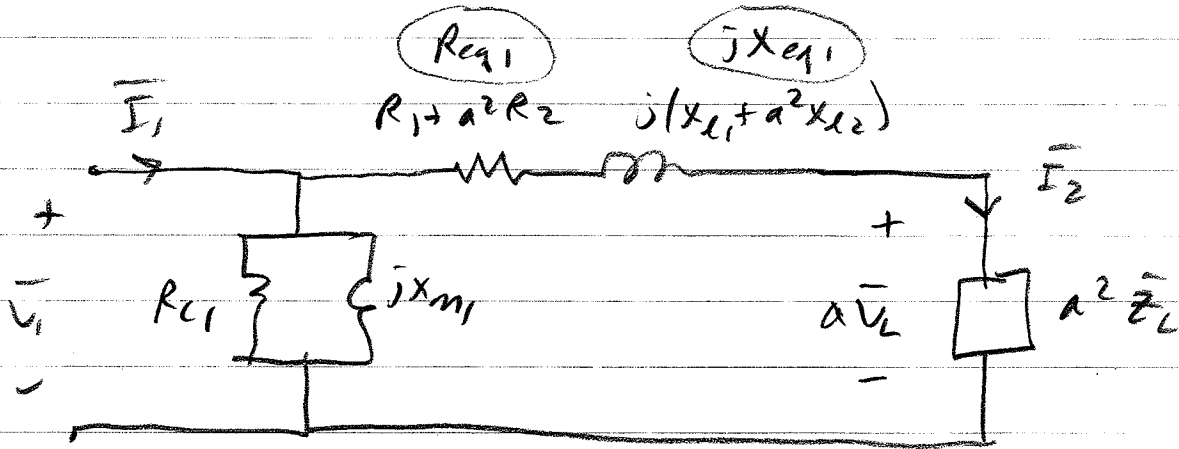

Efficiency $\eta = \frac{P_{out}}{P_{in}} \times 100$

Voltage regulation $VR = \frac{|\bar{V}_L|_{no\ load} - |\bar{V}_L|_{load}}{|\bar{V}_L|_{no\ load}} \times 100$

Nameplate

(SC TEST
OC TEST)

Rated V_1 / V_2

Rated KVA

% Z

$$\% Z \equiv \frac{\sqrt{R_{e1}^2 + X_{e1}^2}}{Z_{\text{rated}}} \times 100$$

$$Z_{\text{rated}} = \frac{V_{\text{rated}}}{I_{\text{rated}}} = \frac{V_{\text{rated}}}{S_{\text{rated}} / V_{\text{rated}}} = \frac{V_{\text{rated}}^2}{S_{\text{rated}}}$$

Can show if $|V_1| = V_{\text{rated}}$ and secondary is

shorted,

$$I_{\text{sc}} = \frac{100}{\% Z} \times I_{\text{rated}}$$