

* First quiz Friday September 7, 2018

Covers HW #1

* Section 2.4 in textbook

Last Time:

$$P = VI \cos(\theta_v - \theta_i)$$

$$Q = VI \sin(\theta_v - \theta_i)$$

$$\bar{S} = \bar{V} \bar{I}^* = VI \angle(\theta_v - \theta_i) = P + jQ$$

$$PF = \cos(\theta_v - \theta_i) \Rightarrow PF = \cos(\theta)$$


Today: 1) Why do reactances give Q?

2) Power triangle method for calculating power

3) Conservation of complex power

4) Specifying power

Ex)

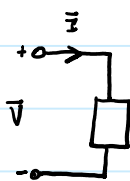


$$\bar{V} = 100 \angle 10^\circ$$

$$\bar{I} = 5 \angle 130^\circ$$

$$\bar{S} = \bar{V} \bar{I}^* = 500 \angle -120^\circ \text{ VA}$$

$$\bar{S} = -250 - j433.01 \text{ VA}$$

Reality

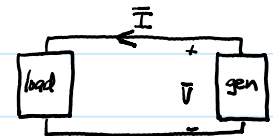

* P is negative, meaning power is generated, not consumed.


To correct equations, flip direction for defining \bar{I} .

* PF only defined for $|\theta| < 90^\circ$



Reactances:

1) Inductor:

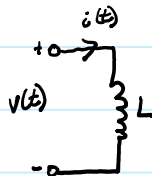

$$V = L \frac{di}{dt} \Rightarrow v = L \frac{d}{dt} (I_m \cos(\omega t + \theta_i))$$

$$v = \omega L I_m (-\sin(\omega t + \theta_i))$$


$$v = \omega L I_m \sin(\omega t - \theta_i)$$

$$v = \omega L I_m \cos(-\omega t - \theta_i - 90^\circ)$$

$$v = \omega L I_m \cos(\omega t + (\theta_i + 90^\circ))$$

$$\bar{V} = \omega L I_{RMS} \angle \theta_i + 90^\circ$$

2) Capacitor

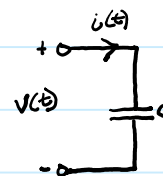

$$i(t) = C \frac{dv}{dt} \Rightarrow i = C \frac{d}{dt} (V_m \cos(\omega t + \theta_v))$$

$$i = \omega C V_m (-\sin(\omega t + \theta_v))$$

$$i = \omega C V_m \sin(-\omega t - \theta_v)$$

$$i = \omega C V_m \cos(-\omega t - \theta_v - 90^\circ)$$

$$i = \omega C V_m \cos(\omega t + (\theta_v + 90^\circ))$$

$$\bar{I} = \omega C V_{RMS} \angle \theta_v + 90^\circ$$

$$\bar{I} = -x + jy \quad | \bar{I} | = | -\bar{I} |$$

$$-\bar{I} = x - jy \quad \theta_i + 180^\circ = \theta_i - I$$

$$\bar{S}_L = \bar{V}_L \bar{I}_L^* = \omega L I_{RMS}^2 \angle (\theta_v + 90^\circ - \theta_i)$$

$$\bar{S}_L = \omega L I_{RMS}^2 \angle 90^\circ = 0 + j\omega L I_{RMS}^2$$


PF = 0 lag ($\theta > 0$)

$$\bar{S}_C = \bar{V}_C \bar{I}_C^* = \omega C V_{RMS}^2 \angle (\theta_v - (\theta_v + 90^\circ))$$

$$\bar{S}_C = \omega C V_{RMS}^2 \angle -90^\circ = 0 - j\omega C V_{RMS}^2$$

PF = 0 lead ($\theta < 0$)

Plot Phasors in Complex Plane

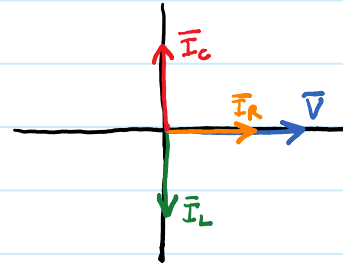


- * Resistor is in phase with voltage
- * Inductor current lags voltage by 90°
- * Capacitor current leads voltage by 90°

Power Triangle:

$$|\bar{S}| = S = \sqrt{P^2 + Q^2} = VI$$

$$P = S \cos(\theta)$$

$$Q = S \sin(\theta)$$

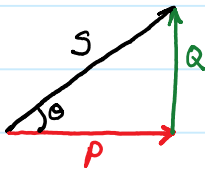

* The diagram above is the power triangle

Ex] $\bar{V} = 100 \angle 10^\circ \text{ V}$

$$\bar{I} = 10 \angle -26.8^\circ \text{ A}$$

Find: a) S and θ


b) Draw the power triangle to find P and Q

Solution: a) $S = VI$

$$\theta = 10^\circ - (-26.8^\circ)$$

$$S = 1000 \text{ VA}$$

$$\theta = 36.8^\circ$$

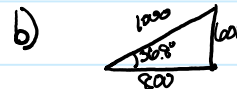

$$P = 800 \text{ W}$$

$$Q = 600 \text{ VAR}$$

Ex] $\bar{V} = 100 \angle 10^\circ \text{ V}$


$$\bar{I} = 10 \angle 46.8^\circ \text{ A}$$

Find: a) S and θ

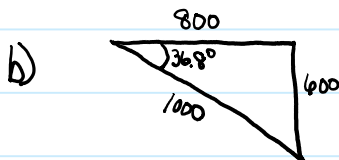b) Draw power triangle to find P and Q

Solution: a) $S = VI$ $\theta = \theta_v - \theta_i$

$$S = 1000 \text{ VA} \quad \theta = -36.8^\circ$$




$$P = 800 \text{ W}$$

$$Q = -600 \text{ VAR}$$

* Up to now, examined a single load. What if there are multiple loads?

Conservation of Complex Power


Series:

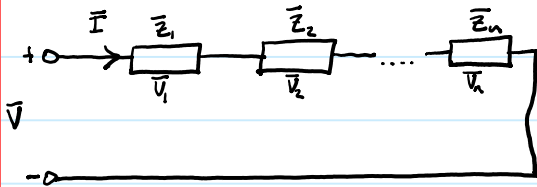

$$\bar{S}_{TOT} = \bar{V}_1 \bar{I}^* + \bar{V}_2 \bar{I}^* + \dots + \bar{V}_n \bar{I}^*$$

$$\bar{S}_{TOT} = \bar{S}_1 + \bar{S}_2 + \dots + \bar{S}_n$$

Parallel:

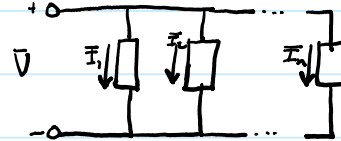

$$\bar{I}_{TOT} = \bar{I}_1 + \bar{I}_2 + \dots + \bar{I}_n$$

$$\begin{aligned} \bar{S}_{TOT} &= \bar{V} \bar{I}_{TOT}^* = \bar{V} (\bar{I}_1 + \bar{I}_2 + \dots + \bar{I}_n)^* \\ &= \bar{V} \bar{I}_1^* + \bar{V} \bar{I}_2^* + \dots + \bar{V} \bar{I}_n^* \end{aligned}$$


$$\bar{S}_{TOT} = \bar{S}_1 + \bar{S}_2 + \dots + \bar{S}_n$$

If: $\bar{S}_{TOT} = \sum_{j=1}^n \bar{S}_j$, Then:

$$\begin{aligned} P_{TOT} &= P_1 + P_2 + \dots + P_n \\ Q_{TOT} &= Q_1 + Q_2 + \dots + Q_n \end{aligned}$$

* We can use this for something called PF correction.

Ex

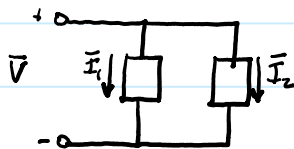

$$\bar{V} = 100 \angle 0^\circ \text{ V}$$

$$\bar{I}_1 = 10 \angle -26.8^\circ \text{ A}$$

$$\bar{I}_2 = 5 \angle 45^\circ \text{ A}$$

Find: a) \bar{S}_{TOT}

b) PF_{TOT}

c) Place a capacitor in parallel with the loads. How many VAR's added by capacitor for
 i) $PF = 0.95$ lag
 ii) $PF = 1$

Solution: a) $\bar{S}_{TOT} = \bar{S}_1 + \bar{S}_2$

$$\bar{S}_1 = V\bar{I}_1^*$$

$$\bar{S}_2 = V\bar{I}_2^*$$


$$\bar{S}_1 = 1000 \angle 26.8^\circ \text{ VA}$$

$$\bar{S}_2 = 500 \angle -30^\circ \text{ VA}$$

$$= 800 + j600 \text{ VA}$$

$$\bar{S}_2 = 433.01 - j250 \text{ VA}$$
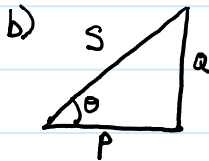
$$\boxed{\bar{S}_{TOT} = 1233.01 + j350 \text{ VA}}$$



$$\tan(\theta) = \frac{Q}{P}$$



$$\tan^{-1}\left(\frac{Q}{P}\right) = \theta$$

$$\theta = 15.85^\circ$$

$$PF = \cos(15.85^\circ) \Rightarrow$$

$$\boxed{PF = 0.962 \text{ lag}}$$

c) Adding capacitor only changes Q

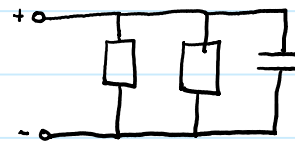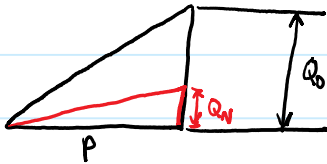

$$i) \cos^{-1}(PF_N) = \theta_N$$

$$\theta_N = 11.5^\circ$$

$$\tan(\theta_N) = \frac{Q_N}{P} \Rightarrow Q_N = P \tan(\theta_N) \Rightarrow Q_N = 250 \text{ VAR}$$

$$Q_0 + Q_c = Q_N$$

$$Q_c = Q_N - Q_0$$

$$\boxed{Q_c = -100 \text{ VAR}}$$

$$ii) PF = 1, Q = 0$$

$$\boxed{Q_c = -350 \text{ VAR}}$$

$$PF = 1 \quad \cos(\theta) = 1 \Rightarrow \theta = 0$$

$$Q = VI \sin \theta \Rightarrow Q = 0$$

Specifying Power:6 total quantities: V, I, PF, P, Q, S We need a reference. Take: $\bar{V} = V \angle 0$ This gives: $\bar{I} = I \angle \theta$

$$\theta = \begin{cases} \cos^{-1}(PF) & \text{lag} \\ -\cos^{-1}(PF) & \text{lead} \end{cases}$$

Different ways of specifying:

1) \bar{V} and \bar{I} given. This is the same as $V, I,$ and PF given2) V, PF, P given.

$$\theta = \begin{cases} \cos^{-1}(PF) & \text{lag} \\ -\cos^{-1}(PF) & \text{lead} \end{cases} \quad I = \frac{P}{V \cos \theta} \quad Q = P \tan \theta$$


$$\bar{S} = P + jQ$$

3) V, PF, S given

$$\theta = \begin{cases} \cos^{-1}(PF) & \text{lag} \\ -\cos^{-1}(PF) & \text{lead} \end{cases} \quad I = \frac{S}{V} \quad P = S \cos \theta \quad \bar{S} = S \angle \theta \\ Q = S \sin \theta$$

4) V, P, Q given

$$PF = \frac{P}{\sqrt{P^2 + Q^2}} \quad S = P + jQ \quad \theta = \tan^{-1}\left(\frac{Q}{P}\right) \\ I = \frac{\sqrt{P^2 + Q^2}}{V}$$

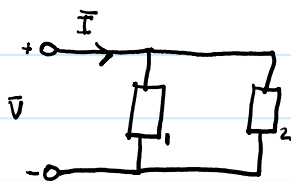Ex

$$\bar{V} = 100 \angle 0^\circ$$

$$S_1 = 20 \text{ kVA} \quad PF = 0.6 \text{ leading}$$

$$P_2 = 4 \text{ kW} \quad PF = 0.8 \text{ lagging}$$

Find: a) \bar{I} b) Input \bar{S} c) Input PF

Solution: a) V_1, S_1, PF given

$$I_1 = \frac{S_1}{V_1} \Rightarrow I_1 = 20 \text{ A}$$

$$\theta = -\cos^{-1}(0.6) \Rightarrow \theta = -53.13$$

$$\bar{I}_1 = 20 \angle -53.13^\circ \text{ A}$$

$$\bar{I}_1 = 12 + j16 \text{ A}$$

$$\bar{I} = \bar{I}_1 + \bar{I}_2 \Rightarrow \bar{I} = 16 + j13 \text{ A}$$

$$\bar{I} = 20.62 \angle 39.09^\circ \text{ A}$$

V_2, P_2, PF given

$$I_2 = \frac{P_2}{V_2 \cdot PF} \Rightarrow I_2 = 5 \text{ A}$$

$$\theta = \cos^{-1}(0.8) \Rightarrow \theta = 36.87^\circ$$

$$\bar{I}_2 = 5 \angle -36.87^\circ$$

$$\bar{I}_2 = 4 - j3 \text{ A}$$


b) $\bar{S} = V \bar{I}^*$

$$= (1000 \angle 0^\circ)(20.62 \angle -39.09^\circ)$$

$$\bar{S} = 20.62 \angle -39.09^\circ \text{ kVA}$$

$$\bar{S} = 16 - j13 \text{ kVA}$$

c)

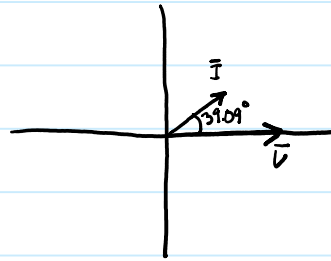

$$PF = \cos(39.09^\circ)$$

$$PF = 0.776 \text{ leading}$$