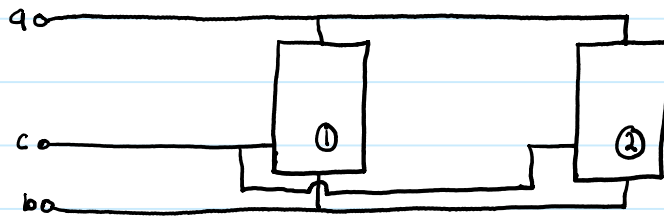


2018-09-14-1

Exl Problem 2.22



$$S_1 = 15 \text{ kVA} \quad \text{PF}_1 = 0.8 \text{ leading}$$

$$P_2 = 72 \text{ kW} \quad \text{PF}_2 = 0.8 \text{ lagging}$$

$$V_L = 2000 \text{ V}$$

- Find: a) I_L and PF_{TOT}
b) Q_c for $\text{PF} = 1$

Solution: a) $\bar{S}_{\text{TOT}} = \bar{S}_1 + \bar{S}_2$

$$S_2 = \frac{P_2}{\text{PF}} = 90 \text{ kVA}$$

$$\bar{S}_{\text{TOT}} = (12 - j9) + (72 + j54)$$

$$\bar{S}_{\text{TOT}} = 84 + j45 \text{ kVA}$$

$$= 95.3 \angle 28.18^\circ \text{ kVA}$$

$$S_{3\phi} = \sqrt{3} V_L I_L$$

$$I_L = \frac{S_{3\phi}}{\sqrt{3} V_L} \Rightarrow \boxed{I_L = 27.51 \text{ A}}$$

$$\boxed{\text{PF}_{\text{TOT}} = 0.881 \text{ lag}}$$


b) $Q_{3\phi} = 45 \text{ kVAR}$

$$\boxed{Q_c = -45 \text{ kVAR}}$$

2018-09-14-2

Ex] Problem 2.23

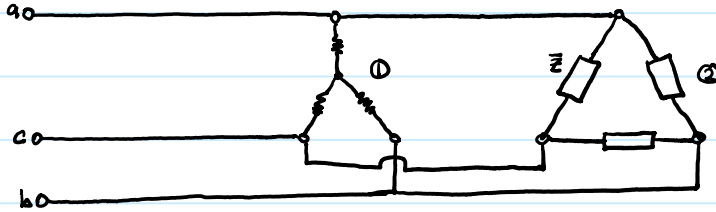Given: $S_{TOT} = 1000 \text{ kVA}$ $PF = 0.8 \text{ lag}$
 $V_L = 4160 \text{ V}$



$P_1 = 200 \text{ kW}$

Find: a) \bar{S}_2
b) \bar{Z}


Solution: a) $\bar{S}_{TOT} = \bar{S}_1 + \bar{S}_2$
 $\bar{S}_{TOT} = 1000 \angle 36.87^\circ \text{ kVA}$
 $= 800 + j600 \text{ kVA}$

$\bar{S}_2 = \bar{S}_{TOT} - \bar{S}_1$
 $\bar{S}_2 = 800 + j600 - (200 + j0)$
 $\bar{S}_2 = 600 + j600 \text{ kVA}$
 $\bar{S}_2 = 600\sqrt{2} \angle 45^\circ \text{ kVA}$

b) $S_2 = \sqrt{3} V_L I_\phi$
 $S_2 = 3 V_L I_\phi$
 $I_\phi = \frac{S_2}{3 V_L} \Rightarrow I_\phi = 67.99 \text{ A}$

$I_\phi = \frac{V_L}{Z} \Rightarrow Z = \frac{V_L}{I_\phi} \Rightarrow Z = 61.19 \Omega$
 $\theta = 45^\circ$

$\bar{Z} = 61.19 \angle 45^\circ \Omega$

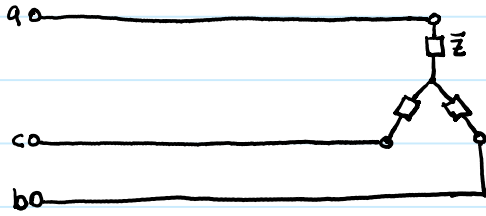Ex Problem 2.24

$$V_{\phi} = 1000 \text{ V}$$


$$\bar{Z} = 50 + j37.7 \Omega$$

Find: a) $\bar{I}_a, \bar{I}_b, \bar{I}_c$

b) $\bar{V}_{ab}, \bar{V}_{bc}, \bar{V}_{ca}$

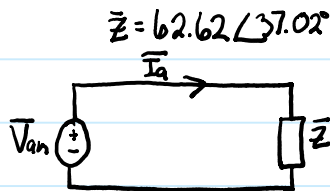c) \bar{S}_{TOT}

Solution: a) $\bar{V}_{an} = 1000 \angle 0^\circ$



$$\bar{Z} = 62.62 \angle 37.02^\circ$$

$$\bar{I}_a = \frac{\bar{V}_{an}}{\bar{Z}} = \frac{1000 \angle 0^\circ}{62.62 \angle 37.02^\circ}$$

$$\bar{I}_a = 15.97 \angle -37.02^\circ \text{ A}$$

$$\bar{I}_b = 15.97 \angle -157.02^\circ \text{ A}$$

$$\bar{I}_c = 15.97 \angle 82.98^\circ \text{ A}$$

b) $\bar{V}_{an} = 1000 \angle 0^\circ$ $\bar{V}_{bn} = 1000 \angle -120^\circ$

$$\bar{V}_{ab} = \sqrt{3} 1000 \angle 30^\circ \text{ V}$$

$$\bar{V}_{bc} = \sqrt{3} 1000 \angle 90^\circ \text{ V}$$

$$\bar{V}_{ca} = \sqrt{3} 1000 \angle 150^\circ \text{ V}$$

c) $\bar{S}_{TOT} = 3 \bar{V}_{\phi} \bar{I}_a^* = 3(1000 \angle 0^\circ)(15.97 \angle 37.02^\circ) \Rightarrow$

$$\bar{S}_{TOT} = 47,910 \angle 37.02^\circ \text{ VA}$$

$$= 38,253 + j28,846 \text{ VA}$$

2018-09-14-4

Ex | Problem 2.25

$$P_{3\phi} = 300 \text{ kW} \quad \text{PF} = 0.6 \text{ lag}$$

Find: Q_c for $\text{PF} = 0.9 \text{ lag}$

Solution: $S_{3\phi} = \frac{P_{3\phi}}{\text{PF}} \Rightarrow S_{3\phi} = 500 \text{ kVA}$

$$Q_{3\phi} = S_{3\phi} \sin(\theta) \Rightarrow Q_{3\phi} = S_{3\phi} (0.8) \Rightarrow Q_{3\phi} = 400 \text{ kVAR}$$

$$P = S_2 (\text{PF}_2)$$

$$S_{3\phi_2} = \frac{P}{\text{PF}_2} \Rightarrow S_{3\phi_2} = 333.33 \text{ kVA}$$

$$\theta_2 = \cos^{-1}(0.9) \Rightarrow \theta_2 = 25.942^\circ$$

$$Q_2 = S_{3\phi_2} \sin(\theta_2)$$

$$Q_2 = 145.30 \text{ kVAR}$$

$$Q_2 = Q_1 + Q_c$$

$$Q_c = Q_2 - Q_1$$

$$Q_c = -254.7 \text{ kVAR}$$