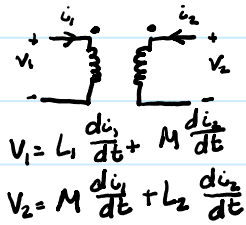



Last time: Dot Convention

\* Dot location doesn't effect self inductance term voltage drop.




$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$
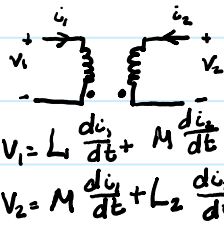
$$V_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$




$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$
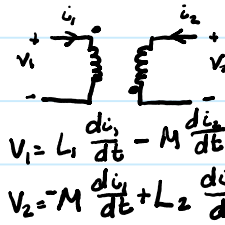
$$V_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$



$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

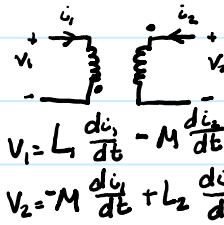
$$V_2 = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$



$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_2 = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

Ideal transformer:

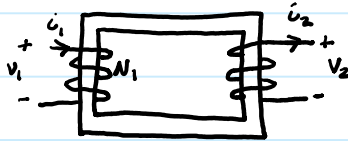


$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = a$$

$$\frac{i_1}{i_2} = \frac{N_2}{N_1} = \frac{1}{a}$$

$$P_1 = P_2$$

- Today:
- 1) Ideal transformer and impedances
  - 2) Max power transfer
  - 3) Equivalent circuit for transformer

Impedances and Transformers:

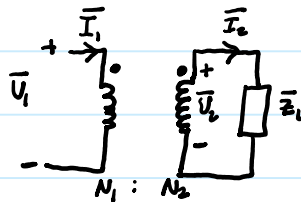

$$V_2 = Z_L I_2$$


$$V_1 = a V_2$$

$$I_1 = \frac{1}{a} I_2 \Rightarrow I_2 = a I_1$$

$$V_1 = a Z_L I_2$$


$$V_1 = a^2 Z_L I_1$$

$$\boxed{V_1 = (a^2 Z_L) I_1}$$

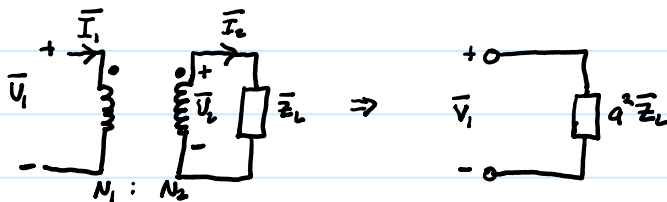

\* Impedance on 2 side can be moved to 1 side by multiplying by  $a^2$ .

Maximum power transferred to the load

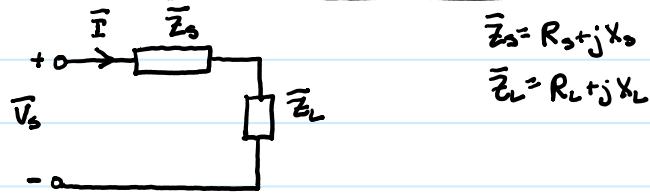

$$\bar{Z}_s = R_s + jX_s$$

$$\bar{Z}_L = R_L + jX_L$$


$$P_L = |\bar{I}|^2 R_L$$

$$\bar{I} = \frac{\bar{V}_s}{\bar{Z}_s + \bar{Z}_L} \Rightarrow \bar{I} = \frac{\bar{V}_s}{(R_s + R_L) + j(X_s + X_L)}$$

$$P_L = \frac{|\bar{V}_s|^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$$

\* Can show that for max  $P_L$ ,  $\bar{Z}_L = \bar{Z}_s^*$  or  $|\bar{Z}_L| = |\bar{Z}_s|$  (for  $\frac{R_L}{X_L}$  fixed as a constant)

\* Imposing  $|\bar{Z}_L| = |\bar{Z}_s|$  can easily be done by using a transformer

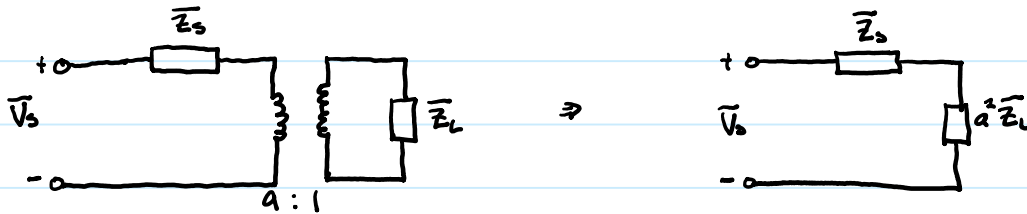


$$|a^2 \bar{Z}_L| = |\bar{Z}_s| \Rightarrow a^2 |\bar{Z}_L| = |\bar{Z}_s|$$

$$a^2 = \frac{|\bar{Z}_s|}{|\bar{Z}_L|} \Rightarrow$$

$$a = \sqrt{\frac{|\bar{Z}_s|}{|\bar{Z}_L|}}$$


Ex

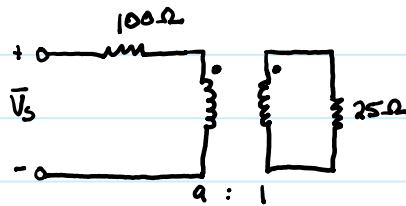

Find: a for max power transfer

$$a = \sqrt{\frac{100}{25}} = a = \sqrt{4} \Rightarrow \boxed{a=2}$$

Ex

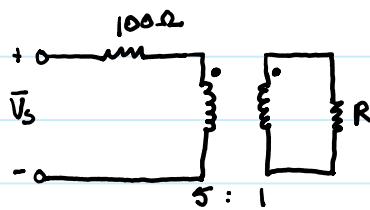


Find: R for max power transfer

$$5^2 R = 100 \Rightarrow 25R = 100 \Omega$$

$$\boxed{R=4 \Omega}$$

### Equivalent circuits for transformers

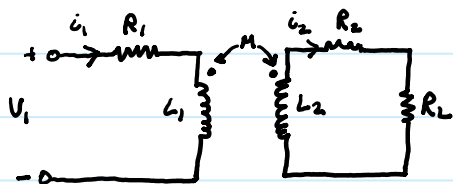


$$V_1 = i_1 R_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$0 = i_2 R_2 + i_2 R_L + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

$$\Rightarrow V_1 = i_1 R_1 + (L_1 - M) \frac{di_1}{dt} + M \frac{d}{dt}(i_1 - i_2)$$

$$\Rightarrow 0 = i_2 R_2 + (L_2 - M) \frac{di_2}{dt} + M \frac{d}{dt}(i_2 - i_1) + i_2 R_L$$

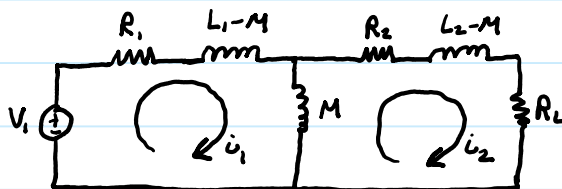\*  $i_1$ : dot  $\rightarrow$  no dot. Coil 2: current into dot =  $-i_2$   
 \*  $i_2$ : no dot  $\rightarrow$  dot. Coil 1: current into no dot =  $-i_1$



\* if  $L_1 - M$  or  $L_2 - M$  are less than 0, then the above equation shouldn't be used.

\* More generally:

$$V_1 = i_1 R_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$


$$0 = i_2 R_2 + i_2 R_L + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

$$\Rightarrow V_1 = i_1 R_1 + L_1 \frac{di_1}{dt} - aM \frac{d}{dt}\left(\frac{i_2}{a}\right)$$


$$0 = a^2 \left(\frac{i_2}{a}\right) R_2 + a \left(\frac{i_2}{a}\right) R_L + aL_2 \frac{d}{dt}\left(\frac{i_2}{a}\right) - M \frac{di_1}{dt}$$

$$\Rightarrow V_1 = i_1 R_1 + (L_1 - aM) \frac{di_1}{dt} + aM \frac{d}{dt}\left(i_1 - \frac{i_2}{a}\right)$$
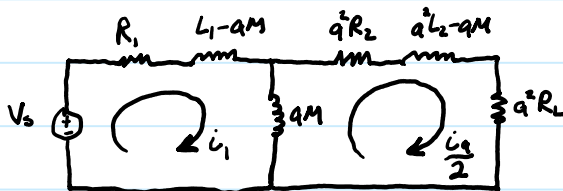
$$0 = a^2 \left(\frac{i_2}{a}\right) R_2 + (a^2 L_2 - aM) \frac{d}{dt}\left(\frac{i_2}{a}\right) + aM \left(\frac{i_2}{a} - i_1\right) + a^2 \left(\frac{i_2}{a}\right) R_L$$



### Thevenin Equivalent

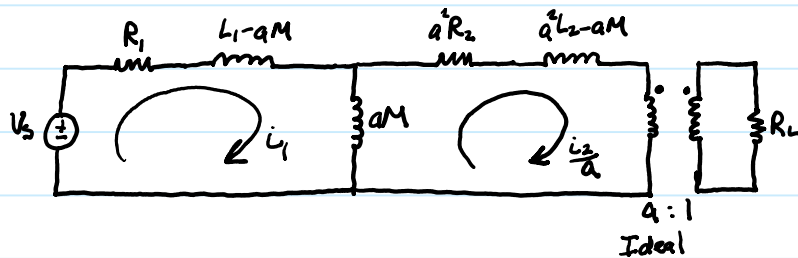


2018-09-26-4

### Analysis for sinusoidal steady state

$$\bar{V}_i = V_m \cos(\omega t + \theta_i)$$



Steps: 1) Convert all inductances to reactances

$$X_L = \omega L$$

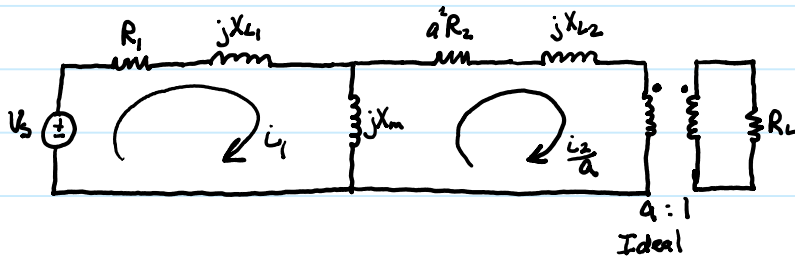

2) Solve the circuit using phasors.

### Ex Problem 3.12

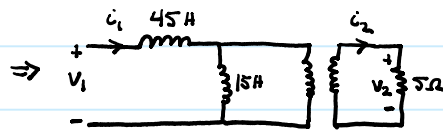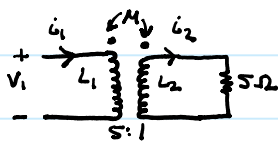

$$aM = 15\text{H} \Rightarrow M = 3\text{H}$$

$$L_1 - aM = 45\text{H} \Rightarrow L_1 = 60\text{H}$$

$$a^2 L_2 - aM = 0 \Rightarrow L_2 = \frac{M}{a} \Rightarrow L_2 = \frac{3}{5} = 0.6\text{H}$$

$$k = \frac{M}{\sqrt{L_1 L_2}} \Rightarrow k = 0.5$$