

* $S_1 = 3 \text{ kVA}$ $PF_1 = 0.5 \text{ lag}$

* $\bar{Z}_2 = 3+j3 \Omega$

* $I_3 = 10A$ $P_3 = 1 \text{ kW}$ leading PF

Find: a) \bar{S}_{tot}

b) $i_3(t)$

c) Q_c for $PF=1$ and C

Solution: a) $\theta_1 = \cos^{-1}(0.5) \Rightarrow \theta_1 = 60^\circ$

$\bar{S}_1 = 3000 \angle 60^\circ \text{ VA}$

$\bar{S}_2 = \frac{V^2}{\bar{Z}}$

$\bar{Z} = 3\sqrt{2} \angle 45^\circ$

$\bar{S}_2 = \frac{120^2}{3\sqrt{2} \angle 45^\circ} \Rightarrow \bar{S}_2 = 3394.11 \angle 45^\circ$

$P_3 = VI_3 \text{ PF} \Rightarrow P_3 = VI_3 \cos(-\theta_3) \Rightarrow \cos(-\theta_3) = \frac{P_3}{VI_3} \Rightarrow \theta_3 = -\cos^{-1}\left(\frac{P_3}{VI_3}\right) \Rightarrow \theta_3 = -33.56^\circ$

$\bar{S}_3 = 1200 \angle -33.56^\circ$

$$\bar{S}_{\text{tot}} = \bar{S}_1 + \bar{S}_2 + \bar{S}_3 \Rightarrow \boxed{\bar{S}_{\text{tot}} = 4899.97 + j4334.70 \text{ VA}} \\ = 6542.12 \angle 41.50^\circ \text{ VA}$$

b) $\bar{S}_{\text{tot}} = V \bar{I}_3^* \Rightarrow \bar{I}_3 = \left(\frac{\bar{S}_{\text{tot}}}{V}\right)^* \Rightarrow \bar{I}_3 = 54.52 \angle -41.50^\circ \text{ A}$


$$\boxed{i_3(t) = \sqrt{2}(54.52) \cos(2\pi(60)t - 41.50^\circ) \text{ A}}$$

c) for $PF=1$, $Q_c = -4334.70 \text{ VAR} \Rightarrow \boxed{Q_c = 4334.70 \text{ of capacitance}}$

$Q_c = \frac{V^2}{-X} \Rightarrow X = \frac{V^2}{Q_c} \Rightarrow X = 3.32 \Omega = \frac{1}{\omega C}$

$C = \frac{1}{\omega(3.32 \Omega)}$

$$\boxed{C = 7.99 \times 10^{-4} \text{ F}}$$

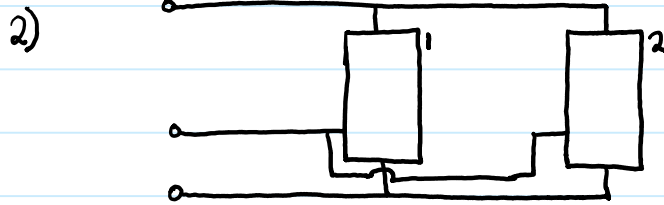

* Load 1: wye connected $\bar{Z}_{1\phi} = 60 \angle 25^\circ \Omega$
 * Load 2: delta connected $\bar{Z}_{1\phi} = 90 \angle 10^\circ \Omega$
 $V_L = 4.16 \text{ kV}$


Find: a) Draw per phase equivalent circuit

b) $\bar{I}_a, \bar{I}_b, \bar{I}_c, \bar{V}_{an}, \bar{V}_{bn}, \bar{V}_{cn}$

c) Draw phasor diagram

d) How would diagram in (c) change for a negative phase sequence

e) $\bar{S}_{3\phi}$

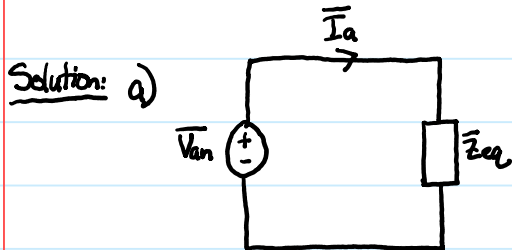

$$\bar{Z}_2 = \frac{\bar{Z}_\Delta}{3} \Rightarrow \bar{Z}_2 = 30 \angle 10^\circ \Omega$$

$$\bar{Z}_{eq} = \left(\frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} \right)^{-1} \Rightarrow \bar{Z}_{eq} = \left(\frac{1}{60 \angle 25^\circ} + \frac{1}{30 \angle 10^\circ} \right)^{-1}$$


$$\bar{Z}_{eq} = 20.15 \angle 15^\circ$$

b) $\bar{V}_{an} = \frac{4.16}{\sqrt{3}} \angle 0^\circ \Rightarrow \bar{V}_{an} = 2401.78 \angle 0^\circ \text{ V}$
 $\bar{V}_{bn} = 2401.78 \angle -120^\circ \text{ V}$
 $\bar{V}_{cn} = 2401.78 \angle 120^\circ \text{ V}$

$$\bar{I}_a = \frac{\bar{V}_{an}}{\bar{Z}_{eq}} \Rightarrow \bar{I}_a = 119.19 \angle -15^\circ \text{ A}$$

$$\bar{I}_b = 119.19 \angle -135^\circ \text{ A}$$

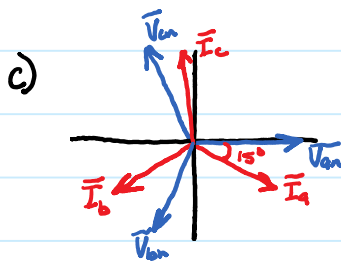
$$\bar{I}_c = 119.19 \angle 105^\circ \text{ A}$$



d) \bar{V}_{bn} and \bar{V}_{cn} switch
 \bar{I}_b and \bar{I}_c switch

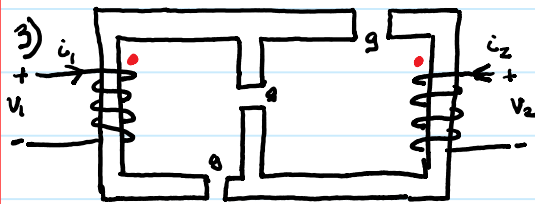e) $\bar{S}_{3\phi} = 3 \bar{V}_{an} \bar{I}_a^* = 3(2401.78 \angle 0^\circ)(119.19 \angle 15^\circ)$


$$\bar{S}_{3\phi} = 858.8 \angle 15^\circ \text{ kVA}$$



* immersed in gas $\mu_r = 2$
 $\mu_c = \infty$ $g = 5\text{mm}$ $A = 20\text{cm}^2$
 $\mu_0 = 4\pi \times 10^{-7} \text{H/m}$ $N_1 = 20$ $N_2 = 40$

- Find:
- a) R_g
 - b) Draw magnetic circuit
 - c) λ_1 and λ_2
 - d) L_1, L_2, M
 - e) k
 - f) dot marks
 - g) V_1 in terms of i_1 and i_2

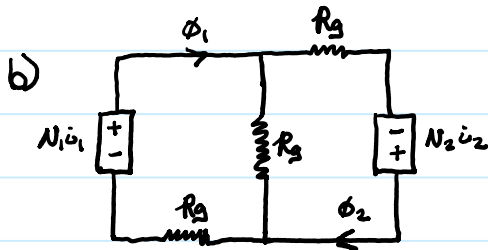Solution: a) $R_g = \frac{g}{\mu_0 \mu_r A} \Rightarrow R_g = 9.95 \times 10^8 \text{ AT/Wb}$



c) $N_1 i_1 = R_g \phi_1 + R_g (\phi_1 - \phi_2)$ $N_2 i_2 = R_g \phi_2 + R_g (\phi_2 - \phi_1)$

$+ N_2 i_2 = R_g \phi_2 - R_g (\phi_1 - \phi_2)$

$N_1 i_1 + N_2 i_2 = R_g (\phi_1 + \phi_2) \Rightarrow \phi_1 + \phi_2 = \frac{N_1}{R_g} i_1 + \frac{N_2}{R_g} i_2 \Rightarrow \phi_1 = -\phi_2 + \frac{N_1}{R_g} i_1 + \frac{N_2}{R_g} i_2$

$N_2 i_2 = R_g \phi_2 + R_g (2\phi_2 - \frac{N_1}{R_g} i_1 - \frac{N_2}{R_g} i_2) \Rightarrow N_2 i_2 = 3R_g \phi_2 - N_1 i_1 - N_2 i_2$

$3R_g \phi_2 = N_1 i_1 + 2N_2 i_2$

$\phi_2 = \frac{N_1}{3R_g} i_1 + \frac{2N_2}{3R_g} i_2$

$\phi_1 = \frac{2N_1}{3R_g} i_1 + \frac{N_2}{3R_g} i_2$

$\lambda_1 = \frac{2N_1^2}{3R_g} i_1 + \frac{N_1 N_2}{3R_g} i_2$
 $\lambda_2 = \frac{N_1 N_2}{3R_g} i_1 + \frac{2N_2^2}{3R_g} i_2$

d) $L_1 = 0.268 \text{ mH}$

$L_2 = 1.07 \text{ mH}$


$M = 0.268 \text{ mH}$

e) $k = \frac{M}{\sqrt{L_1 L_2}}$

$k = 0.5$

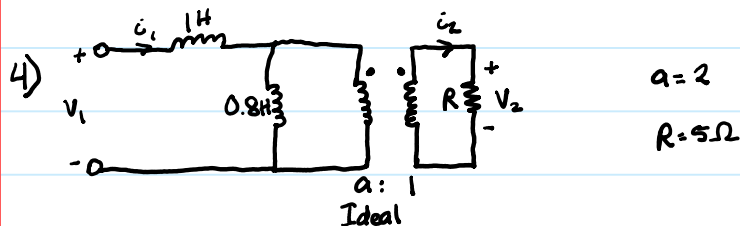
g) $V_1 = \frac{d\lambda_1}{dt}$

$V_1 = 2.68 \times 10^{-4} \frac{di_1}{dt} + 2.68 \times 10^{-4} \frac{di_2}{dt}$



Find: a) Loop equations in time domain

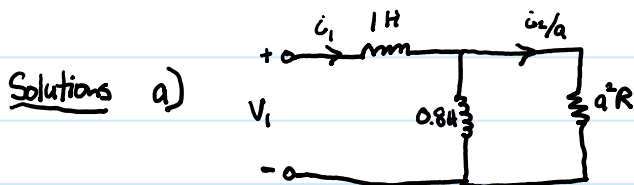b) If $v_1 = \sqrt{2}(120)\cos(10t)$, $v_2(t)$



$$v_1 = 1 \frac{di_1}{dt} + 0.8 \left(\frac{di_1}{dt} - \frac{1}{a} \frac{di_2}{dt} \right)$$

$$0 = \frac{i_2}{a} (a^2 R) + 0.8 \left(\frac{1}{a} \frac{di_2}{dt} - \frac{di_1}{dt} \right)$$

\Rightarrow

$$v_1 = \frac{di_1}{dt} + 0.8 \left(\frac{di_1}{dt} - \frac{1}{2} \frac{di_2}{dt} \right)$$

\Rightarrow

$$0 = 10i_2 + 0.8 \left(\frac{1}{2} \frac{di_2}{dt} - \frac{di_1}{dt} \right)$$

b) $\bar{V}_1 = 120\angle 0^\circ \text{ V}$

$$120\angle 0^\circ = j10\bar{I}_1 + j8 \left(\bar{I}_1 - \frac{1}{2}\bar{I}_2 \right)$$

$$0 = 10\bar{I}_2 + j8 \left(\frac{1}{2}\bar{I}_2 - \bar{I}_1 \right)$$

$$10\bar{I}_2 + j4\bar{I}_2 = j8\bar{I}_1$$

$$\bar{I}_2 = \left(\frac{j8}{10+j4} \right) \bar{I}_1 \Rightarrow \bar{I}_2 = (0.2759 + j0.6997) \bar{I}_1$$

$$(120 + j0) = j10\bar{I}_1 + j8 \left(\bar{I}_1 - \frac{1}{2}\bar{I}_2 \right)$$

$$\bar{I}_1 = \frac{120 + j0}{2.7588 + j16.8964}$$

$$\bar{I}_1 = 1.130 - j6.918$$

$$\bar{I}_2 = 5.083 - j1.130$$

$$\bar{V}_2 = \bar{I}_2 R$$

$$\bar{V}_2 = 25.415 - j5.65$$

$$= 26.04 \angle -12.53^\circ \text{ V}$$

$$v_2(t) = \sqrt{2}(26.04) \cos(10t - 12.53^\circ)$$