

Section (Check One) MWF _____ TTH _____

1. _____ / 25 2. _____ / 25
 3. _____ / 25 4. _____ / 25 Total _____ / 100



Useful information

$\sin(x) = \cos(x - 90^\circ)$ $\bar{V} = \bar{Z}\bar{I}$ $\bar{S} = \bar{V}\bar{I}^*$ $\bar{S}_{3\phi} = \sqrt{3}V_L I_L \angle \theta$

$0 < \theta < 180^\circ$ (lag) $I_L = \sqrt{3}I_\phi$ (delta) $\bar{Z}_Y = \bar{Z}_\Delta / 3$ $\mu_0 = 4\pi \cdot 10^{-7}$ H/m
 $-180^\circ < \theta < 0$ (lead) $V_L = \sqrt{3}V_\phi$ (wye)

$\int_C \mathbf{H} \cdot d\mathbf{l} = \int_S \mathbf{J} \cdot \mathbf{n} da$ $\int_C \mathbf{E} \cdot d\mathbf{l} = -\frac{\partial}{\partial t} \int_S \mathbf{B} \cdot \mathbf{n} da$ $\mathfrak{R} = \frac{l}{\mu A}$ $MMF = Ni = \phi \mathfrak{R}$

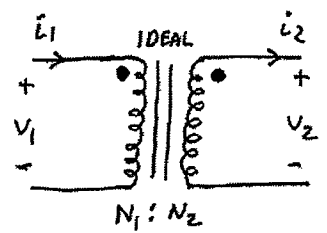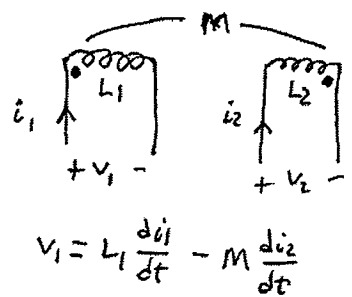$\phi = BA$ $\lambda = Li = N\phi$ $k = \frac{M}{\sqrt{L_1 L_2}}$ 1 hp = 746 Watts



$a = \frac{N_1}{N_2}$ $N_1 i_1 = N_2 i_2$
 $\frac{v_1}{v_2} = \frac{N_1}{N_2}$

1. (25 points)

A single-phase residential electric service has two lines plus one neutral (single phase, 3 wire).


The voltage from line 1 to neutral is 120 volts angle zero.

The voltage from line 2 to neutral is 120 volts angle 180 degrees.

The voltage from line 1 to line 2 is 240 volts angle zero.

One load is connected between line 1 and neutral and draws 10 Amps at 0.9 power factor lag. A second load is connected between line 1 and line 2 and draws 15 Amps at 0.85 power factor lag.

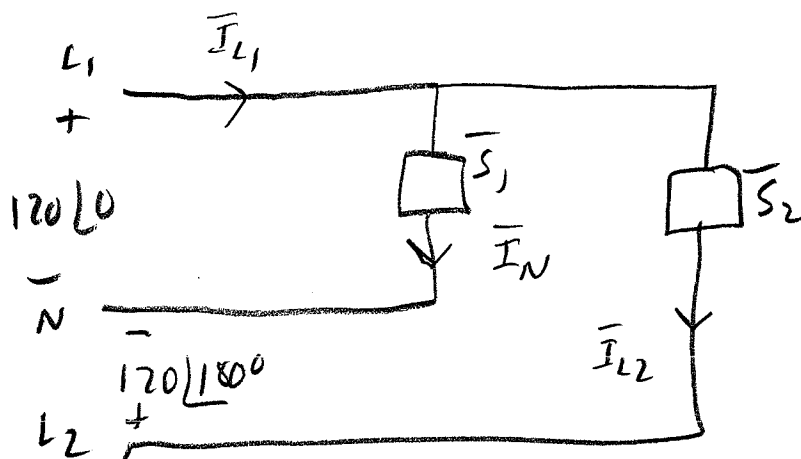- Find the magnitude of the current in the line 1 conductor (call this I_{L1})
- Find the magnitude of the current in the line 2 conductor (call this I_{L2})
- Find the magnitude of the current in the neutral conductor (call this I_N)
- Find the total real power consumed by both of the loads



$$\bar{I}_1 = 10 \angle -25.8^\circ$$

$$\bar{I}_{L2} = 15 \angle -31.8^\circ$$

$$\bar{I}_{L1} = 9 - j4.35 + 12.7 - j7.9$$

$$= 21.7 - j12.3$$

$$= 24.9 \angle -29.5^\circ$$

$$P = 120 \times 10 \cos 25.8^\circ$$

$$+ 240 \times 15 \cos 31.8^\circ$$


$$= 4140 \text{ W}$$

a) 24.9 A,

b) 15 A

c) 10 A

d) 4140 W

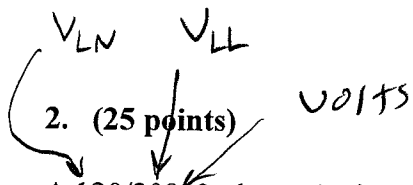

A 120/208, 3-phase, 4 wire, wye-connected, ABC sequence, 60 HZ source supplies the following 2 loads:

Load #1 10 Amps (line current) 3200 Watts (3-phase), wye-connected, lagging power factor
 Load #2 8 Amps (phase current) 0.9 power factor lag, delta connected

- What is the total line current being supplied by the source?
- How many capacitive VARS 3-phase need to be supplied at the load to reduce the total source line current to 22 Amps?

$$|\bar{S}_1| = \sqrt{3} \times 208 \times 10 = 3603$$

$$P_1 = 3200 \text{ W}$$

$$Q_1 = + \sqrt{3603^2 - 3200^2}$$

$$= 1656 \text{ vars}$$

$$\bar{S}_2 = 3 \times 208 \times 8 \angle 25.8^\circ$$

$$= 4494 + j2173$$

$$\bar{S}_{TOT} = 7694 + j3829$$

$$= 8594 \angle 26.5^\circ$$

$$\sqrt{3} \times 208 \times I_L = 8594$$

$$I_L = 23.9 \text{ A}$$

$$\bar{S}_{new} = \sqrt{3} \times 208 \times 22 \angle \theta \stackrel{\text{must}}{=} 7694 + jQ_{new}$$

$$\sqrt{3} \times 208 \times 22 \cos \theta = 7694 \quad \theta = 13.9^\circ$$



$$Q_{new} = \sqrt{3} \times 208 \times 22 \sin \theta = 1904$$

$$Q_{add} = -1925 \text{ vars}$$

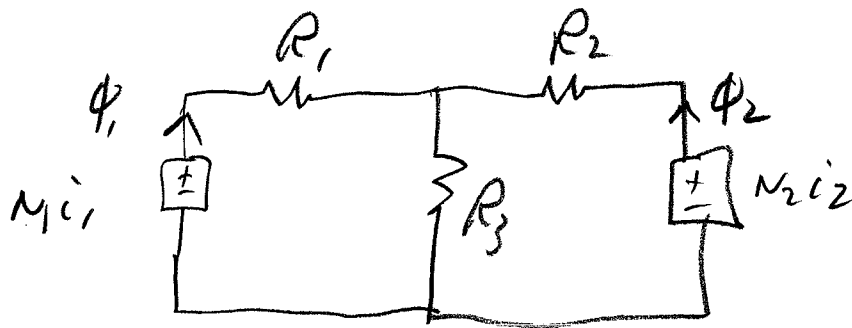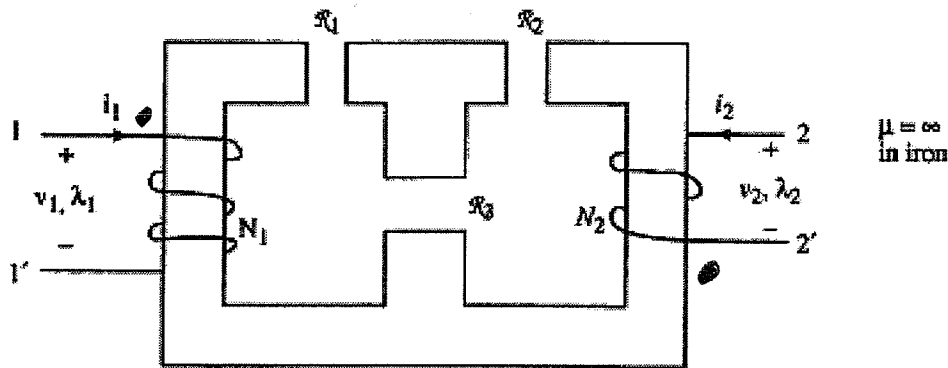3. (25 points)

Two coils are coupled through the iron of the magnetic circuit shown below.

- Place the dots on the appropriate terminals of the two coils
- Write all of the equations that you would need to find the two flux linkages in terms of the two currents (do not solve).




$$\mathcal{F}_1 = N_1 \phi_1$$

$$\mathcal{F}_2 = N_2 \phi_2$$

$$-N_1 i_1 + R_1 \phi_1 + R_3 (\phi_1 + \phi_2) = 0$$

$$-N_2 i_2 + R_2 \phi_2 + R_3 (\phi_1 + \phi_2) = 0$$

4. (25 points)

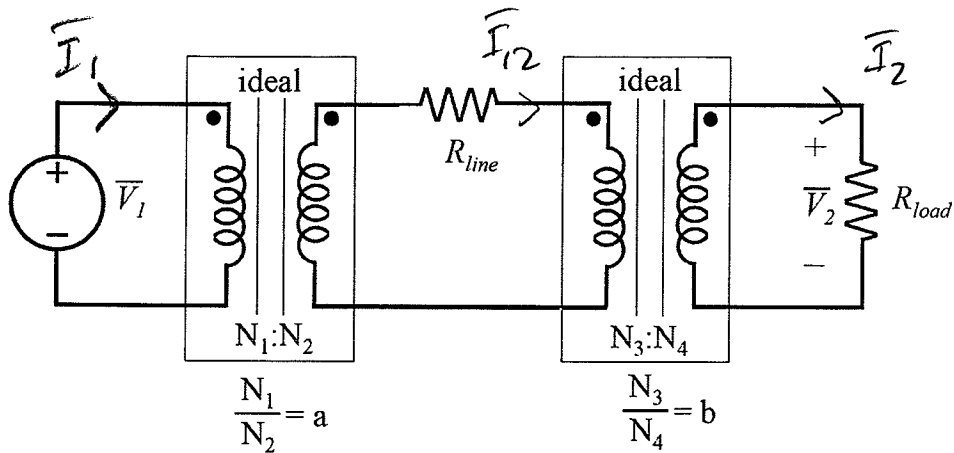

For the circuit shown above:

- Find the equivalent resistance as seen by the source \bar{V}_1
- Find the voltage \bar{V}_2 as a function of \bar{V}_1

a) $a^2 (R_{line} + b^2 R_{load})$

b) $\bar{I}_1 = \frac{\bar{V}_1}{a^2 (R_{line} + b^2 R_{load})}$

$$N_1 \bar{I}_1 = N_2 \bar{I}_{12}$$

$\bar{I}_{12} = \frac{\bar{V}_1}{a^2 (R_{line} + b^2 R_{load})}$

$$N_3 \bar{I}_{12} = N_4 \bar{I}_2$$

$$\bar{I}_2 = \frac{b \bar{V}_1}{a (R_{line} + b^2 R_{load})}$$

$$\bar{V}_2 = \frac{b \bar{V}_1 R_{load}}{a (R_{line} + b^2 R_{load})}$$