

ECE 330 Exam #1, Fall 2016 Name: Solution
 90 Minutes

Section (Check One) MWF 9 am _____ MWF 10 am _____

1. _____ / 25 2. _____ / 25

3. _____ / 25 4. _____ / 25 Total _____ / 100

Useful information

$$\sin(x) = \cos(x - 90^\circ) \quad \bar{V} = \bar{Z}\bar{I} \quad \bar{S} = \bar{V}\bar{I}^* = P + jQ \quad \bar{S}_{\phi} = \sqrt{3}V_L I_L \angle \theta$$



$$0 < \theta < 180^\circ \text{ (lag)} \quad I_L = \sqrt{3}I_\phi \text{ (delta)} \quad \bar{Z}_Y = \bar{Z}_\Delta / 3 \quad \mu_0 = 4\pi \cdot 10^{-7} \text{ H/m}$$

$$-180^\circ < \theta < 0 \text{ (lead)} \quad V_L = \sqrt{3}V_\phi \text{ (wye)}$$

ABC sequence has A at zero, B at minus 120 degrees, and C at plus 120 degrees


$$\int_C \mathbf{H} \cdot d\mathbf{l} = \int_S \mathbf{J} \cdot \mathbf{n} da \quad \int_C \mathbf{E} \cdot d\mathbf{l} = -\frac{\partial}{\partial t} \int_S \mathbf{B} \cdot \mathbf{n} da \quad \mathcal{R} = \frac{l}{\mu A} \quad MMF = Ni = \phi R$$

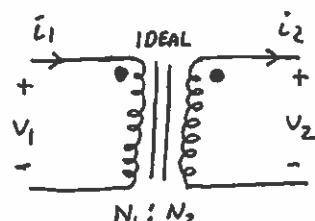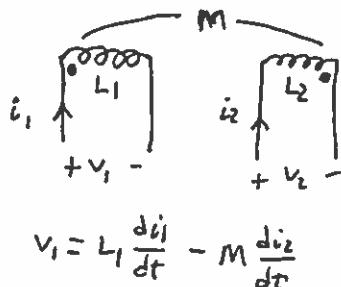
$$\phi = BA \quad \lambda = N\phi = Li \text{ (if linear)} \quad v = d\lambda/dt \quad k = \frac{M}{\sqrt{L_1 L_2}} \quad 1 \text{ hp} = 746 \text{ Watts}$$



$$\alpha = \frac{N_1}{N_2} \quad N_1 i_1 = N_2 i_2$$

$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$

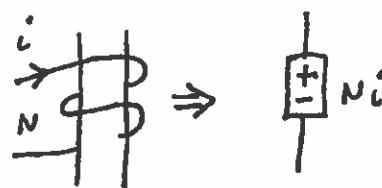

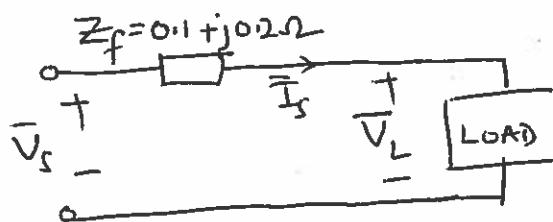

Problem 1. (25 points)

A feeder with an impedance of $0.1+j0.2$ Ohms supplies a single-phase 20kW, 0.85 lagging power factor load. The voltage across the load is $v(t) = \sqrt{2} (120) \sin(377t + \pi/3)$ V Calculate:

- The source current phasor \bar{I}_s and the instantaneous $i_s(t)$
- The source (sending end) voltage phasor \bar{V}_s
- The power factor angle at the sending end
- The total complex power supplied by the source, S_{total}
- The magnitude of the voltage at the receiving end if the load is removed (open circuited)

$$a) \bar{V}_L = 120 \angle 60^\circ - 90^\circ V = 120 \angle -30^\circ V$$

$$\bar{S} = \frac{20k}{0.85} \angle \cos^{-1}(0.85) VA = 23529 \angle 31.79^\circ VA$$

$$\bar{I}_s = \bar{I}_L = \left(\frac{\bar{S}}{\bar{V}_L}\right)^* = \frac{23529 \angle -31.79^\circ}{120 \angle 30^\circ} = 196.1 \angle -61.79^\circ A$$

$$i_s(t) = 196.1 \sqrt{2} \cos(377t - 61.79^\circ) A$$

$$b) \bar{V}_s = \bar{V}_L + \bar{I}_s \bar{Z}_f = 120 \angle -30^\circ + (196.1 \angle -61.79^\circ)(0.1 + j0.2)$$

$$= 159 \angle -21.68^\circ V$$

$$c) \text{pf. angle} = \theta_{V_s} - \theta_{I_s} = -21.68^\circ + 61.79^\circ = 40.1^\circ$$

$$d) \bar{S}_{\text{total}} = \bar{V}_s \cdot \bar{I}_s^* = (159 \angle -21.68^\circ)(196.1 \angle -61.79^\circ)$$

$$= 31176 \angle 40.1^\circ VA$$

$$e) \bar{I}_s = 0 \Rightarrow \bar{V}_{L_{\text{new}}} = \bar{V}_s = 159 \angle -21.68^\circ V$$

(extra paper at the end)

Problem 2. (25 points)


A balanced 3-phase, 208 Volt (line-line), Wye-connected source serves a balanced, 3-phase, Wye-connected, lagging power factor load. A variable 3-phase capacitor bank is connected across the load in a Delta configuration. Measurements of the source line current for various values of capacitor Vars (3-phase) give the following test results for tests T1 to T8:

	T1	T2	T3	T4	T5	T6	T7	T8
Capacitor Vars (3-phase):	0	200	400	600	800	1,000	1,200	1,400
Source line current:	3.75	3.43	3.17	3.00	2.92	2.95	3.07	3.29


- a) By just looking at the numbers in the table above, about how many Vars (3-phase) would you say the original load (without the capacitors) consumes?
 - b) Approximately how many Watts (3-phase) would you say the original load (without the capacitors) consumes?
 - c) What is the exact value of the original load $P + jQ$ (3-phase --- without the capacitors)?
 - d) What would the source line current be in test T4 if the same capacitors used in test T4 were connected in a Wye rather than a Delta?
- a) minimum line current means unity power factor for constant P . So 2.92A is min, so $\boxed{Q = 800 \text{ VARS}}$
- b) $\sqrt{3} \times 208 \times 2.92 = \boxed{1052\text{W} = P}$
- c) $|P + jQ| = \sqrt{3} \times 208 \times 3.75 = \sqrt{P^2 + Q^2} = 1351$
 $|P + j(Q - 600)| = \sqrt{3} \times 208 \times 3 = \sqrt{P^2 + (Q - 600)^2} = 1081$
- $(OK \quad OTHER \quad TEST)$ $P^2 + Q^2 = 1351^2 \text{VA}$ $P^2 + Q^2 - 1200Q + 3600K = 1081^2 \text{VA}$
 $0 - 1200Q + 3600K = 1081^2 - 1351^2 = -656,640$
- $-1200Q = -1,016,640$ $\boxed{Q = 847 \text{ VARS}}$
- d) $Q_{cap} = 600/3 = 200 \text{ VARS}$ $\boxed{P = 1052\text{W}}$
- $\boxed{So I_L = 3.43\text{A}}$
- (extra paper at the end)

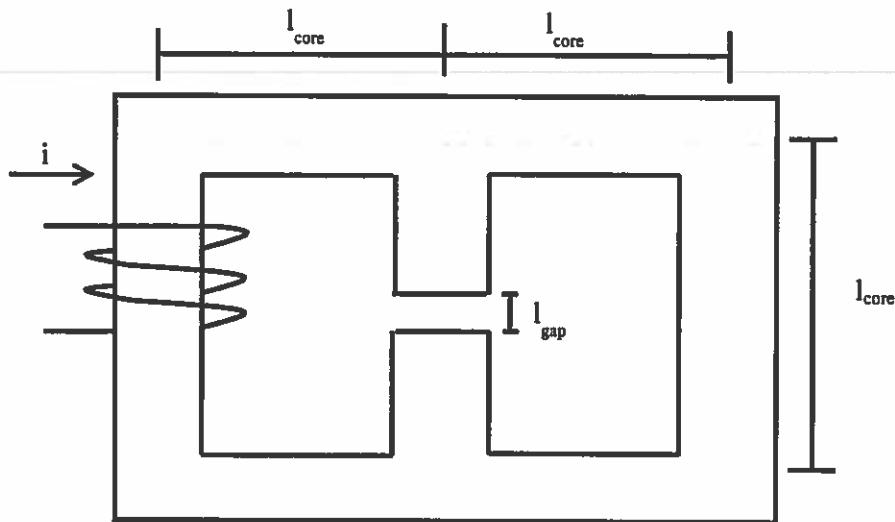Problem 3. (25 points)

Consider the iron geometry given in the figure below. Assume μ_r of the iron core = 1000, l_{core} = 10 cm, l_{gap} = 0.1 cm, the cross section of the core is 1cm by 1cm, and number of turns is 100. Account for air gap fringing in the following calculations.



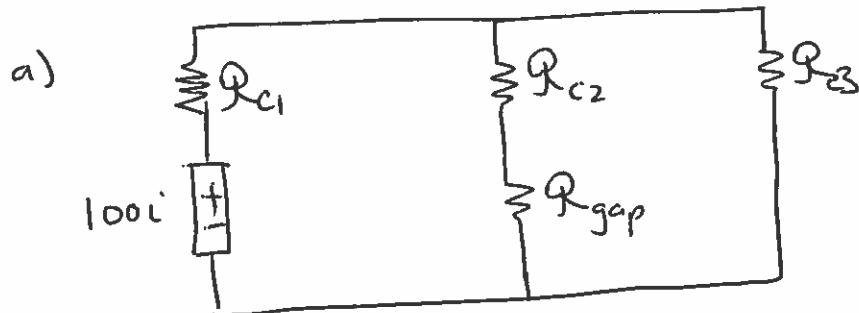- Draw the equivalent magnetic circuit and calculate and label all reluctances.
- Calculate the inductance of the coil.
- Find the current (assume dc) needed to generate a flux density in the left leg of 0.5 Tesla.
- With this same current, what is the flux density in the center and right legs?



$$R_{C1} = R_{C3} = \frac{0.3}{1000\mu_0 \times 1 \times 10^{-4}} \\ = 2.387 \times 10^6 \text{ H}^{-1}$$

$$R_{C2} = \frac{(0.1 - 0.001)}{1000\mu_0 \times 1 \times 10^{-4}} \\ = 7.878 \times 10^5 \text{ H}^{-1}$$

Accounting for fringing,

$$A_{gap} = 1.1 \times 1.1 = 1.21 \text{ cm}^2$$

$$R_g = \frac{0.001}{\mu_0 \times 1.21 \times 10^{-4}} \\ = 6.577 \times 10^{+6} \text{ H}^{-1}$$

(extra paper at the end)

$$b) L_{coil} = \frac{N^2}{R_T}$$

$$\text{Total reluctance, } R_T = R_{c1} + (R_{c2} + R_{gap}) // R_{c3}$$

$$= 4.19 \times 10^6 \text{ H}^{-1}$$

$$L_{coil} = \frac{100^2}{4.19 \times 10^6} = 2.387 \text{ mH}$$

$$c) \text{ Flux through left leg, } \phi_1 = BA = 0.5 \times 10^{-4} \text{ Wb}$$

$$100i = R_T \times \phi_1 \Rightarrow i = 2.095 \text{ A}$$

$$d) \text{ Flux through right leg} = \frac{100i - \phi_1 R_{c1}}{R_{c3}} = 3.78 \times 10^{-5} \text{ Wb}$$

$$\text{Flux through middle leg} = \phi_1 - 3.78 \times 10^{-5} = 1.22 \times 10^{-5} \text{ Wb}$$

$$B_{right} = \frac{3.78 \times 10^{-5}}{10^{-4}} = 0.378 \text{ T}$$


$$B_{center} = \frac{1.22 \times 10^{-5}}{10^{-4}} = 0.122 \text{ T}$$

Problem 4. (25 points)

Two identical coils (each with zero resistance) are located near each other.

When a 60Hz sinusoidal voltage of 120 Volts (RMS) is applied to coil #1, the coil #1 current is 0.5 Amps (RMS) and the voltage measured on the open-circuited coil #2 is 60 Volts (RMS).

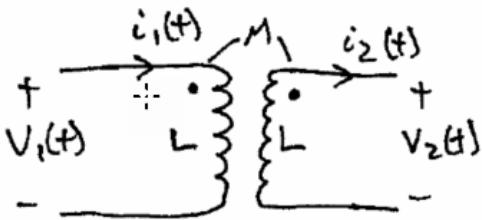- (a) What are the self inductances of coil #1 and #2 in Henries?



$$i_{1rms} := 0.5 \text{ A} \quad i_{1peak} := i_{1rms} \sqrt{2} = 0.707 \text{ A}$$

$$v_{1rms} := 120 \text{ V} \quad v_{1peak} := v_{1rms} \sqrt{2} = 169.706 \text{ V}$$

In this problem $L_1 = L_2$.

Some important consts and units:

$$f := 60 \text{ Hz} \quad \omega := 2 \cdot \pi \cdot f \quad \frac{\text{Wb}}{\text{A}} = 1 \text{ H}$$

$$120 \pi = 376.991 \quad \text{H} \cdot \text{A} = 1 \text{ Wb}$$

$$\text{V} \cdot \text{s} = 1 \text{ Wb} \quad j := \sqrt{-1}$$

$$v_1(t) = 120 \sqrt{2} \cdot \cos(120 \pi \cdot \text{Hz} \cdot t) \cdot \text{V}$$

$$v_2(t) = 60 \sqrt{2} \cdot \cos(120 \pi \cdot \text{Hz} \cdot t) \cdot \text{V}$$

$$i_1(t) = \frac{\sqrt{2}}{2} \cdot \cos(120 \pi \cdot t) \cdot \text{A}$$

$$V := 120 \text{ V}$$

$$V^1 := 60 \text{ V}$$

Equations for the two loops are given in (1) and (2)

$$(1) \quad v_1(t) = L_1 \cdot \frac{d}{dt} i_1(t) - M \cdot \frac{d}{dt} i_2(t)$$

$$(2) \quad v_2(t) = -L_2 \cdot \frac{d}{dt} i_2(t) + M \cdot \frac{d}{dt} i_1(t)$$

This can be solved by integration but assume steady state and use phasors.

$$120 \cdot \text{V} = j \cdot 120 \pi \cdot \text{Hz} \cdot L_1 \cdot \frac{1}{2} \text{ A} \xrightarrow{\text{solve}, L_1} -\frac{2i \cdot \text{V}}{\pi \cdot \text{A} \cdot \text{Hz}}$$

$$L_1 := \frac{2 \cdot \text{V}}{\pi \cdot \text{A} \cdot \text{Hz}} = 0.637 \text{ H}$$

$$L_2 := L_1 = 0.6366 \text{ H}$$

Note j gives 90 degree phase shift, it is not included in the magnitude of L.

- (b) What is the magnitude of the mutual inductance between coil #1 and coil #2 in Henries?

$$60 \text{ V} = j \cdot 120 \pi \cdot \text{Hz} \cdot M \cdot \frac{1}{2} \text{ A} \xrightarrow{\text{solve}, M} \text{undefined}$$

$$M := \frac{\text{V} \cdot 1}{\pi \cdot \text{A} \cdot \text{Hz}} = 0.318 \text{ H}$$

$$M = 0.318 \text{ H}$$

Note j gives 90 degree phase shift, it is not included in the magnitude of M.

- (c) What is the coefficient of coupling for these two coils?

$$k := \frac{M}{\sqrt{L_1 \cdot L_2}} = 0.5$$

$$k = 0.5$$

- (d) What are the current magnitudes in coil #1 and #2 if a resistive load of 10 Ohms is placed across coil #2 while the given voltage is applied across coil #1?

When the load is added to the secondary side, there are two loops, two equations, two unknowns.

$$v_1(t) = L_1 \cdot \frac{d}{dt} i_1(t) - M \cdot \frac{d}{dt} i_2(t)$$

$$v_2(t) = -L_2 \cdot \frac{d}{dt} i_2(t) + M \cdot \frac{d}{dt} i_1(t) \quad \text{Due to the load } v_2(t) = i_2(t) \cdot R$$

$$\begin{aligned} V_1 &= j \cdot 120 \pi \cdot L_1 \cdot I_1 - j \cdot 120 \pi \cdot M \cdot I_2 \\ I_2 \cdot 10 &= -j \cdot 120 \pi \cdot L_2 \cdot I_2 + j \cdot 120 \pi \cdot M \cdot I_1 \end{aligned}$$

$$\begin{aligned} 120 \pi \cdot L_1 &= 240 \text{ H} \\ \text{substituions: } 120 \pi \cdot L_2 &= 240 \text{ H} \\ 120 \pi \cdot M &= 120 \text{ H} \end{aligned}$$

$$120 = 240 I_1 - 120 \cdot I_2 \quad (1)$$

$$0 = 120 \cdot I_1 - 240 \cdot I_2 - 10 I_2 \quad (2)$$



$$I_{matrix} := \text{rref} \left(\begin{bmatrix} 240 & -120 & 120 \\ 120 & -250 & 0 \end{bmatrix} \right) = \begin{bmatrix} 1 & 0 & 0.658 \\ 0 & 1 & 0.316 \end{bmatrix}$$

$$I := \text{submatrix}(I_{matrix}, 1, 2, 3, 3) \cdot A = \begin{bmatrix} 0.658 \\ 0.316 \end{bmatrix} A$$

$$I_1 = 0.658 \text{ A}$$


$$I_2 = 0.316 \text{ A}$$

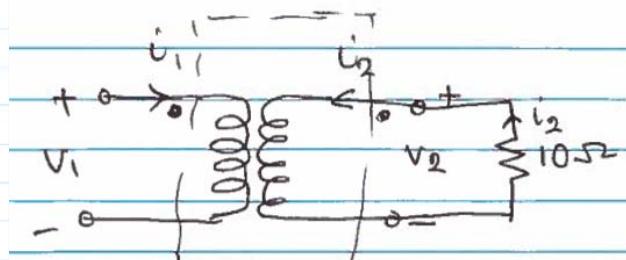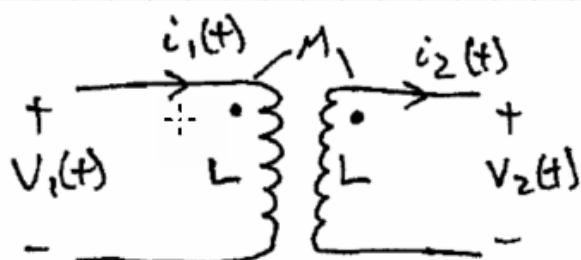See the next 3 pages for an alternate approach. **But note the solutions are the same!** See the models below. Can you spot the difference?



(4)

(a)

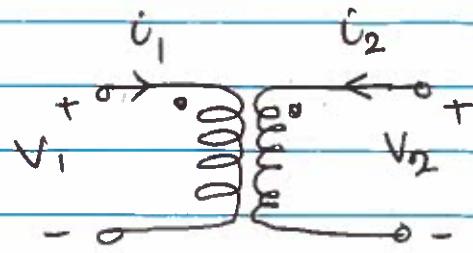

$$V_1 = 120 \text{ V (rms)}$$

$$i_1 = 0.5 \text{ A (rms)}$$

$$V_2 = 60 \text{ V}$$

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad \text{--- (1)}$$

$$V_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \quad \text{--- (2)}$$

Winding 2 open circuit \Rightarrow

$$i_2 = 0$$

(1) Boils down to

$$\therefore V_1 = L_1 \frac{di_1}{dt}$$

in phasors

$$\bar{V}_1 = j\omega L_1 \bar{I}_1$$

\leftarrow peak magnitude

$$\therefore L_1 = \left| \frac{\bar{V}_1}{j\omega \bar{I}_1} \right| = \left| \frac{120}{2\pi \times 60 \times 0.5} \right|$$

$$L_1 = 0.6366 \text{ H}$$

$$L_2 = 0.6366 \text{ H}$$

$L_1 = L_2$ because

the coils are identical.

(b) . (2) Boils down to .

$$V_2 = \frac{M di}{dt} \quad (\text{as winding 2 is still open circuit})$$

In. Phasor form

~~6000E~~

$$\bar{V}_2 = j\omega M \bar{I}_1$$


$$M = \left| \frac{\bar{V}_2}{j\omega \bar{I}_1} \right| = \sqrt{\frac{60}{80j^2\pi \times 60 \times 0.5}}$$

$$M = 0.318 \text{ H}$$

(c) Coefficient of coupling ,

$$K = \frac{M}{\sqrt{L_1 L_2}} = \frac{0.318}{\sqrt{0.6366 \times 0.6366}}$$

$$K = 0.5$$

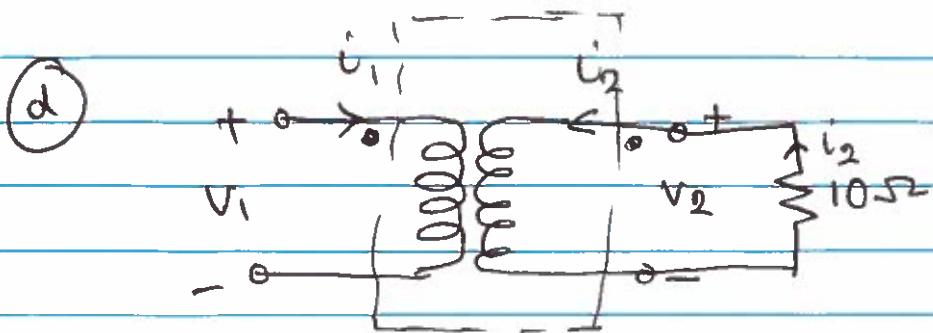

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad \text{--- (1)}$$

$$V_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \quad \text{--- (2)}$$

$$\text{and } V_2 = -10i_2 \quad \text{--- (3)}$$

Use (2) and (3)

$$-10i_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \quad \text{--- (4)}$$

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad \text{--- (5)}$$

Substitute $\frac{di}{dt}$ with $j\omega$.
for phasors.

(5) Boils down to

$$\bar{V}_1 = j\omega L_1 \bar{I}_1 + j\omega M \bar{I}_2$$

(4) Boils down to

$$j\omega L_2 \bar{I}_2 + j\omega M \bar{I}_1 + 10 \bar{I}_2 = 0$$