

ECE430
Exam #1
Fall 2006

Name Nick
(Print Name)

Section: (Circle One) 2 MWF 3 MWF

Problem 1 _____ Problem 2 _____ Problem 3 _____

TOTAL: _____

USEFUL INFORMATION

$$\sin(x) = \cos(x - 90^\circ)$$

$$\bar{V} = \bar{Z}\bar{I}$$

$$\bar{S} = \bar{V}\bar{I}^*$$

$$\bar{S}_{3\phi} = \sqrt{3}V_L I_L \angle \theta$$

$$0 < \theta < 180^\circ \text{ (lag)}$$

$$I_L = \sqrt{3}I_\phi \text{ (delta)}$$

$$1 \text{ hp} = 746 \text{ W}$$

$$-180^\circ < \theta < 0 \text{ (lead)}$$

$$V_L = \sqrt{3}V_\phi \text{ (wye)}$$

$$\int_C \mathbf{H} \cdot d\mathbf{l} = \int_S \mathbf{J} \cdot \mathbf{n} da$$

$$\int_C \mathbf{E} \cdot d\mathbf{l} = -\frac{\partial}{\partial t} \int_S \mathbf{B} \cdot \mathbf{n} da$$

$$\mathfrak{R} = \frac{l}{\mu A}$$

$$\mu_0 = 4\pi \cdot 10^{-7} \text{ H/m}$$

$$MMF = Ni = \phi \mathfrak{R}$$

$$\lambda = Li = N\phi$$

$$\phi = BA$$

$$k = \frac{M}{\sqrt{L_1 L_2}}$$

Problem 1 (30 pts.)

A single-phase, 60 Hz, sinusoidal source is supplying two loads at 120Volts (RMS). When load number one is connected all by itself, the source current is 5 Amps (RMS) and the load consumes 550 Watts. When load number 2 is connected all by itself, the source current is 7 Amps (RMS) and the load consumes 750 Watts. Find two different possible values of the source line current when both loads are connected at the same time.

$$|S_1| = 120(5) = 600$$

$$P_1 = 550 \text{ W} \rightarrow Q_1 = \pm \sqrt{600^2 - 550^2} = \pm 239.8 \text{ VAR}$$

$$|S_2| = 120(7) = 840$$

$$P_2 = 750 \quad Q_2 = \pm \sqrt{840^2 - 750^2} = \pm 378 \text{ VAR}$$

4 possible loads

2 possible current magnitudes

Both negative

$$S_T = 1300 - j618$$

$$|S_T| = 1439 \text{ VA}$$

$$|I| = 12 \text{ A}$$

Q_1 neg Q_2 pos

$$S_T = 1300 + j138$$

$$|S_T| = 1307 \text{ VA}$$

$$|I| = 10.9 \text{ A}$$

Problem 2 (30 pts)

A balanced 3-phase, 208 Volt (line-line), Wye-connected source serves a balanced, 3-phase, Wye-connected, passive load. A variable 3-phase capacitor bank is connected across the load in a Delta configuration. Measurements of the source line current for various values of capacitor Vars (3-phase) give:

Capacitor Vars (3-phase):	0	200	400	600	800	1,000	1,200	1,400
Source line current:	3.75	3.43	3.17	3.00	2.92	2.95	3.07	3.29

- (a) By just looking at the numbers in the table above, about how many Vars (3-phase) would you say the original load (without the capacitors) consumes?

Put answer here: ≈ 800 Vars

Note: $|I| = \frac{|S|}{V} = \frac{\sqrt{P^2 + Q^2}}{V}$

- (b) Approximately how many Watts (3-phase) would you say the original load (without the capacitors) consumes?

$P \approx 3 \cdot \left(\frac{208}{\sqrt{3}}\right) (2.92) \approx 1052 \text{ W}$

- (c) What is the exact value of the original load $P + jQ$ (without the capacitors)?

$|S_1| = 3.75 \cdot 3 \frac{208}{\sqrt{3}} = 1351$

$|S_2| = 3.43 \cdot \sqrt{3} \cdot 208 = 1236$

$|S_1|^2 - |S_2|^2 = P^2 + Q_1^2 - P^2 - Q_2^2$

$Q_2 = Q_1 - 200$

$|S_1|^2 - |S_2|^2 = Q_1^2 - (Q_1 - 200)^2 = Q_1^2 - Q_1^2 + 400Q_1 - 40000$

$297505 = 400Q_1 - 40000$

$Q_1 = +844 \text{ VAR}$

$P_1 = \sqrt{S_1^2 - Q_1^2} \rightarrow P_1 = 1055 \text{ W}$

$S_1 = 1055 + j844 \text{ VA}$

Problem 3 (40 points)

5 cm depth



Given the magnetic device below, considering uniform flux in the iron only, calculate

- (1) The absolute value of the mutual inductance relating the current in coil #2 to the flux linkage in coil #1.

$M = 0.0013 \text{ H}$

- (2) The flux linkage in coil #1 if the currents are $i_1 = 5 \text{ A}$ and $i_2 = -3 \text{ A}$.

$\lambda_1 = 0.0144 \text{ Wb Tm}$

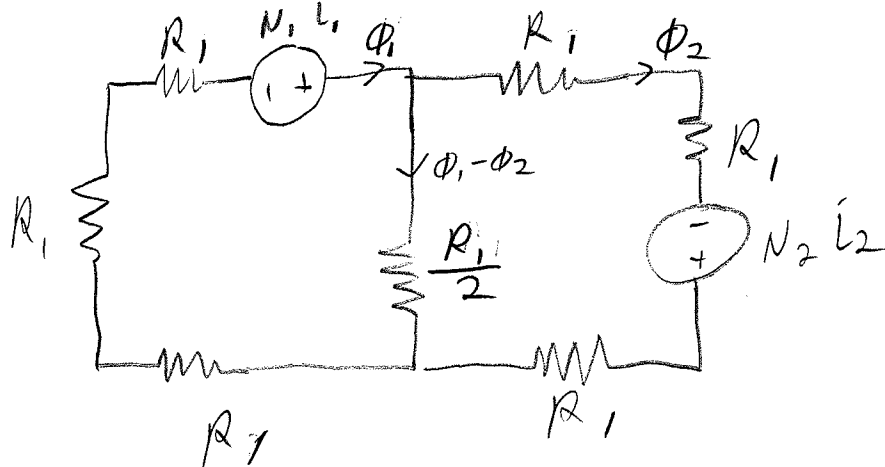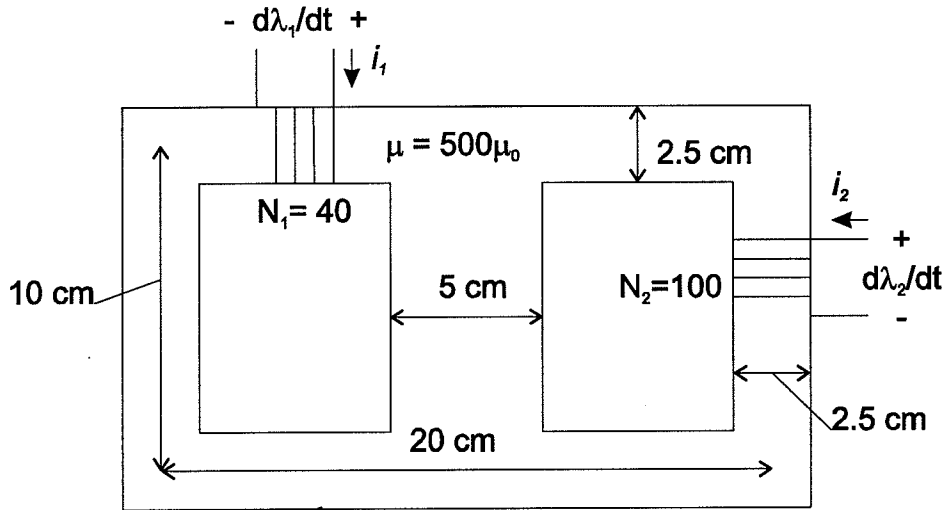

$$R_1 = \frac{0.1 \text{ m}}{500 \mu_0 (0.025)(0.05)} = 127 \times 10^3 \frac{\text{AT}}{\text{Wb}}$$

$$N_1 i_1 = \frac{R_1}{2} (\phi_1 - \phi_2) + 3 \phi_1 R_1 \rightarrow \phi_2 = \frac{2}{R_1} \left(\frac{7}{2} R_1 \phi_1 - N_1 i_1 \right)$$

$$N_2 i_2 = \frac{R_1}{2} (\phi_2 - \phi_1) + 3 \phi_2 R_1 \rightarrow \phi_1 = \frac{2}{R_1} \left(\frac{7}{2} R_1 \phi_2 - N_2 i_2 \right)$$

Blank page for extra workspace

$$\Phi_1 = \frac{2}{R_1} \left(\frac{7}{2} R_1 \left(\frac{2}{R_1} \left(\frac{7}{2} R_1 \Phi_1 - N_1 \bar{i}_1 \right) \right) - N_2 \bar{i}_2 \right)$$

$$\Phi_1 = \frac{2}{R_1} \frac{7}{2} R_1 \frac{2}{R_1} \frac{7}{2} R_1 \Phi_1 - \frac{2}{R_1} \frac{7}{2} R_1 \frac{2}{R_1} N_1 \bar{i}_1 - \frac{2}{R_1} N_2 \bar{i}_2$$

$$\Phi_1 = 49 \Phi_1 - \frac{14}{R_1} N_1 \bar{i}_1 - \frac{2}{R_1} N_2 \bar{i}_2$$

$$48 \Phi_1 = \frac{14}{R_1} N_1 \bar{i}_1 + \frac{2}{R_1} N_2 \bar{i}_2$$

$$\Phi_1 = \frac{14}{48 R_1} N_1 \bar{i}_1 + \frac{2}{48 R_1} N_2 \bar{i}_2$$

$$\lambda_1 = N_1 \Phi_1 = \underbrace{\frac{14}{48 R_1} N_1^2}_{L_1} \bar{i}_1 + \underbrace{\frac{2}{48 R_1} N_1 N_2}_{M} \bar{i}_2$$

$$\boxed{M = 0.00131 \text{ H}}$$

$$L_1 = 0.00367 \text{ H}$$

$$\lambda_1 = L_1 \bar{i}_1 + M \bar{i}_2$$

$$\lambda_1 = 0.00367(5) + 0.00131(-3) = \boxed{0.144 \text{ WbTm}}$$