

Section (Check One) MWF 10am _____ MWF 2pm _____

1. _____ / 25 2. _____ / 25

3. _____ / 25 4. _____ / 25 Total _____ / 100

Useful information

$$\sin(x) = \cos(x - 90^\circ)$$

$$\bar{V} = \bar{ZI}$$

$$\bar{S} = \bar{VI}^*$$

$$\bar{S}_{3\phi} = \sqrt{3}V_L I_L \angle \theta$$

$$0 < \theta < 180^\circ \text{ (lag)}$$

$$I_L = \sqrt{3}I_\phi \text{ (delta)}$$

$$\bar{Z}_Y = \bar{Z}_\Delta / 3$$

$$\mu_0 = 4\pi \cdot 10^{-7} \text{ H/m}$$

$$-180^\circ < \theta < 0 \text{ (lead)}$$

$$V_L = \sqrt{3}V_\phi \text{ (wye)}$$

$$\int_C \mathbf{H} \cdot d\mathbf{l} = \int_S \mathbf{J} \cdot \mathbf{n} da$$

$$\int_C \mathbf{E} \cdot d\mathbf{l} = -\frac{\partial}{\partial t} \int_S \mathbf{B} \cdot \mathbf{n} da \quad \mathfrak{R} = \frac{l}{\mu A}$$

$$MMF = Ni = \phi \mathfrak{R}$$


$$\phi = BA$$

$$\lambda = N\phi$$


$$v = d\lambda/dt$$

$$k = \frac{M}{\sqrt{L_1 L_2}}$$

$$1 \text{ hp} = 746 \text{ Watts}$$

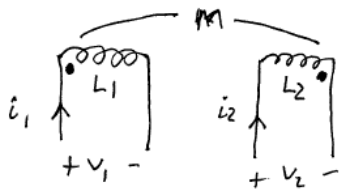

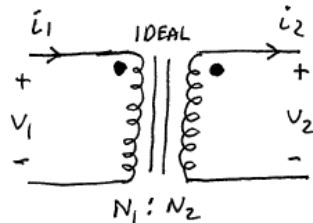
$$v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$



$$a = \frac{N_1}{N_2} \quad N_1 i_1 = N_2 i_2$$

$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$

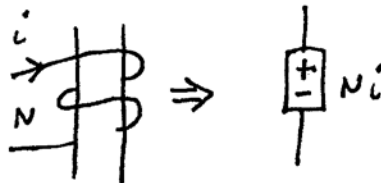

Problem 1. (25 points)

Three single-phase loads are connected in parallel across a 60Hz source of 120 Volts (RMS).

Load #1: 3 KVA at 0.8 power factor lagging

Load #2: 20 Amps (RMS) and 2 KW real power (inductive load)

Load #3: $(10 + j10) \Omega$

- a) Find the total complex power consumed by these three loads.
- b) Find the equivalent impedance as viewed from the source.
- c) Find the value of capacitive VARS that should be added in parallel to these three loads to make the overall power factor 0.95 lag.


Problem 2. (25 points)

A balanced, 60 Hz, 120/208 Volt, 3 phase, 4 wire source is supplying impedance loads in parallel. One is 4-wire, Wye connected and draws 10 Amps line current and 3,100 Watts (3-phase) of real power (inductive). The other is 3-wire Delta connected and draws 8 Amps of line current and zero VARs (3-phase) of reactive power.

- a) What is the source total line current magnitude?
- b) What is the total real power (3-phase) delivered by the source?
- c) Repeat a) and b) if the second load is rewired (same impedances) to be 4-wire, Wye connected.

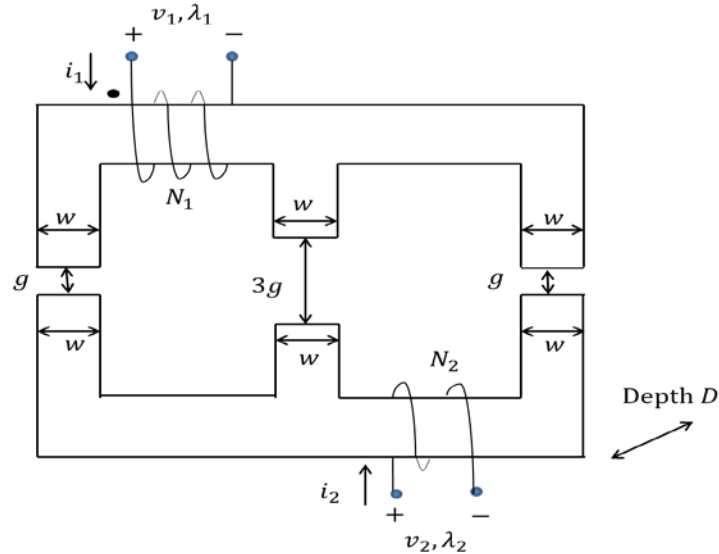Problem 3. (25 points)

An electric device has both upper and lower pieces composed of infinitely permeable magnetic material. It has depth D , and all other lengths are shown in the figure: $D = 2\text{cm}$, $w = 3\text{cm}$, and $g = 3\text{mm}$. The number of turns are $N_1 = 100$, $N_2 = 50$. Assume no fringing or flux leakage.



- Given the dot marking for coil 1, finish the dot marking for coil 2 in the above figure;
- Draw the magnetic equivalent circuit, and find the specific value of each reluctance in the magnetic circuit. Write two “loop” equations that you could use to find the *flux* through the two coils in terms of i_1 and i_2 — do not simplify or solve ;
- Ignore coil 2, and find the inductance L_1 of coil 1;
- Ignore coil 1, and find the inductance L_2 of coil 2;
- Assume the self-inductance values of coils 1 and 2 are given by L_1 and L_2 as in Parts c) and d), and their coupling coefficient is $k = 0.75$. Write v_1 and v_2 in terms of i_1 and i_2 .

Blank page provided next for work

Problem 4. (25 points)

A voltage of $17,633\cos(377t)$ Volts (12,470 V RMS) is applied to a single-phase transformer coil primary (source side). The primary coil has 6,500 turns.

- a) What is the magnitude of flux density in the transformer primary coil iron core that has a cross-section area of 0.008 square meters?
- b) If this is an ideal transformer, with 125 turns on the secondary (load side), how much current (RMS) will a 7 Ohm load draw on the secondary side?
- c) For part b), what will this impedance look like (how many Ohms) from the high voltage side?