

ECE330: Power Circuits & Electromechanics Review. Three-phase AC circuits

Prof. Richard Y. Zhang
Univ. of Illinois at Urbana-Champaign
ryz@illinois.edu



1


Schedule

- Mon 2/24: Review
- Wed 2/26: Review
- **Thu 2/27: Exam 1**
- Fri 2/28: No class

2

3 ϕ models


Important

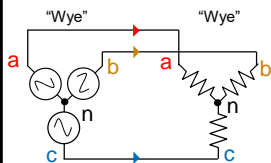

- Assumption 1 (Balanced)**
- Same phase-neutral voltage
 - Same phase current

- Assumption 2 (Positive sequence)**
- Phase b lags phase a by 120°
 - Phase c leads phase a by 120°
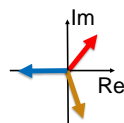
$$\begin{aligned}\bar{V}_{an} &= V \angle \theta_v & \bar{I}_a &= I \angle \theta_i \\ \bar{V}_{bn} &= V \angle (\theta_v - 120^\circ) & \bar{I}_b &= I \angle (\theta_i - 120^\circ) \\ \bar{V}_{cn} &= V \angle (\theta_v + 120^\circ) & \bar{I}_c &= I \angle (\theta_i + 120^\circ)\end{aligned}$$



Implications
(Assumption 1)


- Zero neutral current
- Identical load per phase
- Total power = **3x** power per phase

3

3

Single phase Equivalence

Important

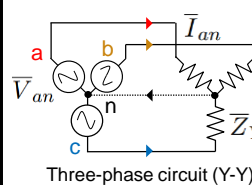

Line voltage / line current


$$V_L = |\bar{V}_{ab}| = \sqrt{3} |\bar{V}_{an}|$$

$$I_L = |\bar{I}_{an}|$$

Three-phase power

$$\bar{S}_{3\phi} = 3\bar{S}_\phi$$

Three-phase circuit (Y-Y)

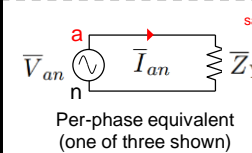

Phase-neutral quantities

$$|\bar{V}_{an}| = |\bar{V}_{ab}| / \sqrt{3} = V_L / \sqrt{3}$$

$$|\bar{I}_{an}| = I_L$$

One-phase power

$$\bar{S}_\phi = \bar{S}_{3\phi} / 3$$

Per-phase equivalent
(one of three shown)

4

4


2.22 A three-phase load of 15 kVA at 0.8 PF leading is connected in parallel with a three-phase 72 kW load at 0.8 PF lagging. The line-to-line voltage is 2000 V.

- Find the line current and the PF of the combined total load.
- Find the total kVAR needed to bring the PF to unity.

5

Wye-Delta Equivalence

Important

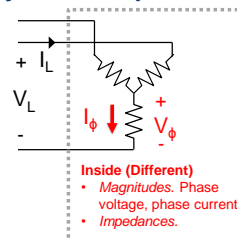

Inside (Different)

- Magnitudes. Phase voltage, phase current
- Impedances.

Inside (Different)

- Magnitudes. Phase voltage, phase current
- Impedances.

Outside (Same)

- Magnitudes. Line voltage (aka line-to-line voltage), line current
- Phasors. Phase-to-phase voltage, phase-to-neutral voltage, phase-to-phase voltage, phase-to-neutral voltage
- Power. Power factor, complex power, PF angle, P, Q.

6

6

Important

Wye-Delta equivalence

Power
 $\bar{S}_\Delta = \bar{S}_Y$

Current
 $\sqrt{3}|\bar{I}_\Delta| = |\bar{I}_Y|$
 $\text{PowFac}_\Delta = \text{PowFac}_Y$

Impedance
 $\bar{Z}_\Delta = 3\bar{Z}_Y$

7

Warm-up

What is the equivalent per-phase Wye impedance?

$2j\ \Omega$, $-6j\ \Omega$, $-6j\ \Omega$, $1j\ \Omega$, $1j\ \Omega$, $2j\ \Omega$, $-6j\ \Omega$, $1j\ \Omega$, $2j\ \Omega$, $-2j\ \Omega$, $1j\ \Omega$

$2j + \left(\frac{1}{-2j} + \frac{1}{j} \right)^{-1} = 4j$

8

Warm-up

2.16) A 345 kV three-phase line supplies 750 MVA at 0.8 PF lagging to a three-phase load which is delta connected.

- Find the complex impedance per phase. **"equivalent Delta current"**
- Find the magnitudes of the line and phase currents.
- Compute real and reactive power per phase.
- Compute the total complex power.

- 1 → Draw and label the 3-phase circuit diagram
- 2 → Draw and label the equivalent wye-wye diagram
- 3 → Draw and label the equivalent 1-phase diagram
- 4 → Solve the 1-phase problem
- 5 → Convert back to wye-wye, then back to orig 3-phase

9

A three-phase wye-connected load draws 100 kW at a PF of 0.80 lagging from a 240 V (line-line) three-phase system. Three capacitors are delta-connected across the load. The total kVAR of the capacitors is 35 kVAR.

- Find the line current before and after the capacitors are added.
- Find the new power factor.

10

A three-phase, 100 V (line-line) delta-connected generator delivers 625 VA at 0.8 PF leading to the following two loads in parallel:

- A purely capacitive three-phase wye-connected load that consumes 875 VAR
- A balanced delta-connected three-phase impedance

Find the impedance of each of the legs of the delta-connected load.

11