


Schedule

Mon 2/24: ReviewWed 2/26: ReviewThu 2/27: Exam 1

• Fri 2/28: No class


2

 $\begin{array}{c|c} \textbf{Mmf and back-emf} \\ \textbf{(Back-emf just means negative emf)} \\ \hline \\ \textbf{Magnetic flux (ϕ)} \\ \hline \\ \textbf{I}_1 \bigotimes \bullet I_2 \\ \hline \\ \textbf{Electric current l} \\ \hline \\ \textbf{Electric current l} \\ \hline \\ \textbf{Faraday's law} \\ \textbf{V}_L = \frac{d}{dt}(\phi_1 - \phi_2) \\ \hline \\ \textbf{Magnetic flux} \\ \hline \\ \textbf{V}_L = \frac{d}{dt}(\phi_1 - \phi_2) \\ \hline \\ \textbf{Current into} + \text{terminal} \\ \\ \textbf{Seck-emf''} \\ \hline \\ \textbf{Seck-emf''} \\ \hline \\ \textbf{Seck-emf''} \\$

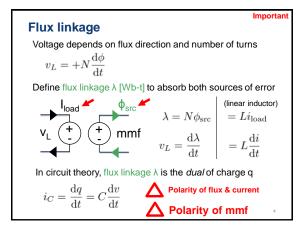



Δ


6

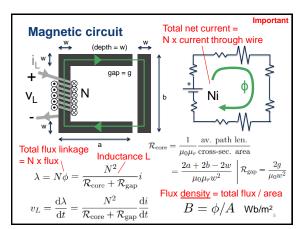


5

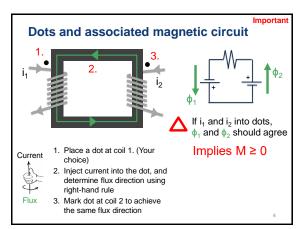

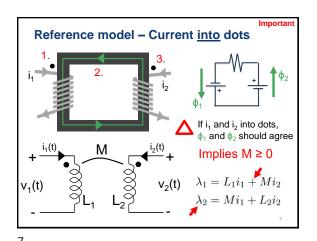

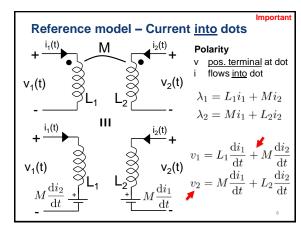

8

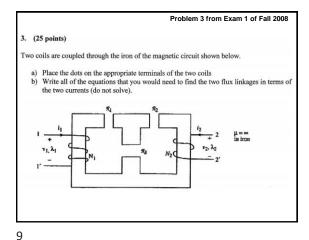

Problem 4. (25 points)

A multi-coil magnetic circuit is illustrated in the diagram below. The cross-sectional area of the magnetic core is A everywhere. The permeability of the magnetic core is infinite. There are two air gaps with lengths ga and ga as shown and permeability µs. You may neglect fringing. Label the voltages and currents - you may define the two voltages and two currents any way that you like.

a) (5 pts) Put the polarity "dots" on the proper side of each coil
b) (10 pts) Find expressions for L1, L2, and M in terms of the parameters
c) (5 pts) Find an expression for the coefficient of coupling in terms of only g1 and g2
d) (5 pts) What happens to the coefficient of coupling as g1 gets smaller and g2 gets bigger?

Problem 4 from Exam 1 of Fall 2013

Problem 4. (25 points)

Two identical coils (each with zero resistance) are located near each other. Coil #2 is open circuited.

When a 60Hz sinusoidal voltage of 120 Volts (RMS) is applied to coil #1, the coil #1 current is 6 Amps (RMS) and the voltage measured on the open-circuited coil #2 is 70 Volts (RMS).

- (a) What are the self inductances of coil #1 and #2 in Henries?
- (b) What is the magnitude of the mutual inductance between coil #1 and coil #2 in Henries?
- c) What are the current magnitudes in coil #1 and #2 if a short circuit is placed across coil #2 while the given voltage is applied across coil #1?

10

11