

ECE 430 Exam #1, Spring 2010
90 Minutes

Name: Solution

Section (Check One) MWF 10am _____ MWF 2pm _____

1. 25 / 25 2. 25 / 25
3. 25 / 25 4. 25 / 25 Total 100 / 100
first two



Useful information

$\sin(x) = \cos(x - 90^\circ)$ $\bar{V} = \bar{Z}\bar{I}$ $\bar{S} = \bar{V}\bar{I}^*$
 $\bar{S}_{3\phi} = \sqrt{3}V_L I_L \angle \theta$


$0 < \theta < 180^\circ$ (lag) $I_L = \sqrt{3}I_\phi$ (delta) $\bar{Z}_Y = \bar{Z}_\Delta / 3$ $\mu_0 = 4\pi \cdot 10^{-7}$ H/m
 $-180^\circ < \theta < 0$ (lead) $V_L = \sqrt{3}V_\phi$ (wye)

$\int_C \mathbf{H} \cdot d\mathbf{l} = \int_S \mathbf{J} \cdot \mathbf{n} da$ $\int_C \mathbf{E} \cdot d\mathbf{l} = -\frac{\partial}{\partial t} \int_S \mathbf{B} \cdot \mathbf{n} da$ $\mathfrak{R} = \frac{l}{\mu A}$ $MMF = Ni = \phi \mathfrak{R}$

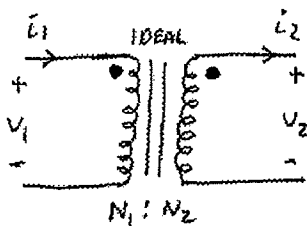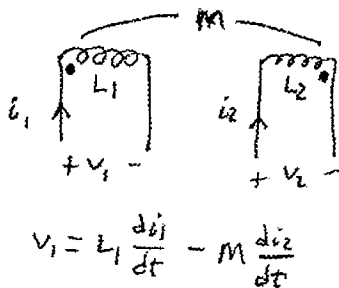$\phi = BA$ $\lambda = Li = N\phi$ $k = \frac{M}{\sqrt{L_1 L_2}}$ 1 hp = 746 Watts





$a = \frac{N_1}{N_2}$ $N_1 i_1 = N_2 i_2$
 $\frac{v_1}{v_2} = \frac{N_1}{N_2}$

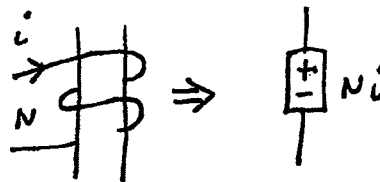

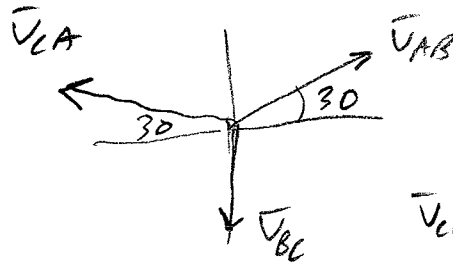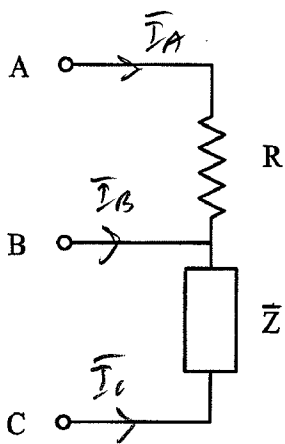Problem 1. (25 points)

A balanced, symmetrical 208 V (RMS Line to Line), 3-phase, 60 Hz source with ABC sequence is supplying the three-wire (not balanced 3-phase) load shown below.



Assume $\angle V_{AB} = 30^\circ$

$$\bar{I}_A = \frac{208 \angle 30^\circ}{100} = 2.08 \angle 30^\circ$$

$$\bar{V}_{CB} = -\bar{V}_{BC} = 208 \angle 90^\circ$$

$$\bar{I}_C = \frac{\bar{V}_{CB}}{100 \bar{k}}$$

Resistor R is fixed at 100 Ohms. Impedance \bar{Z} is specified as a multiple $\bar{k}R$, where \bar{k} could be positive, negative, or even complex.

a) If $\bar{k} = 1$, what are the three line current magnitudes, and what is the total three-phase real power consumed by this load? (12 points)

$$\text{If } \bar{k} = 1, \quad \bar{I}_C = \frac{208 \angle 90^\circ}{100} = 2.08 \angle 90^\circ$$

$$\bar{I}_A = 2.08 \angle 30^\circ \text{ (above)}$$

$$\bar{I}_B = -\bar{I}_A - \bar{I}_C = -2.08 \angle 30^\circ - 2.08 \angle 90^\circ = -1.801 - j1.04 - j2.08 = -1.801 - j3.12$$

$$\bar{I}_B = 3.60 \angle 240^\circ$$

$$P = \frac{208^2}{100} + \frac{208^2}{100} = 865 \text{ W}$$

b) What value of \bar{k} , if any, will produce balanced three-phase line currents with this connection? (13 points)

Using $\angle V_{AB} = 30^\circ$, $\bar{I}_A = 2.08 \angle 30^\circ$

Or, $\bar{k} = 1 \angle -60^\circ$ will also shift

\bar{I}_C to $2.08 \angle 150^\circ$. This would be ABC sequence currents.

From a), we found that $\bar{k} = 1$ gives $\bar{I}_C = 2.08 \angle 90^\circ$. So, if we use $\bar{k} = -1$ then \bar{I}_C will be $2.08 \angle -90^\circ$ and that will

give $\bar{I}_B = 2.08 \angle 150^\circ$ which is a balanced 3 ϕ set. (ACB seq.)

Problem 2. (25 pts)

Three loads are connected in parallel across a 60Hz, 3-phase source at 208 Volts (RMS Line-Line).

Load #1: Delta-connected load with 12 Amps phase current at 0.9 power factor lag

Load #2: Wye-connected load with 20 Ohms per phase pure resistance

Load #3: Delta-connected load with 3,000 Watts plus 1,500 Vars of power (3-phase)

- Find the line current magnitude for each of the three loads (8 points)
- Find the source line current magnitude (8 points)
- Find the value of capacitive VARS (3-phase) that should be added in parallel to these three loads to make the overall power factor 0.95 lag (9 points).

$$a) \quad I_{L1} = \sqrt{3} I_{\phi} = \boxed{20.784 \text{ A}} \quad I_{L2} = \frac{208/\sqrt{3}}{20} = \boxed{6 \text{ A}}$$

$$I_{L3} = \frac{\sqrt{3000^2 + 1500^2}}{\sqrt{3} \times 208} = \boxed{9.31 \text{ A}}$$

$$b) \quad \bar{S}_{TOT} = 3 \times 12 \times 208 \angle 25.8^\circ + 3 \times 120 \times 6 + 3000 + j1500$$
$$= 6742 + j3259 + 2160 + 3000 + j1500 = 11902 + j4759 = 12818 \angle 21.8^\circ$$


$$12818 = \sqrt{3} \times 208 \times I_L \quad \boxed{I_L = 35.58 \text{ A}}$$

$$c) \quad \bar{S}_{3\phi} = \frac{11902}{0.95} \angle +\cos^{-1} 0.95 = 11902 + j3912$$


$$\boxed{Q_{add} = 3912 - 4759 = -847 \text{ VARS}}$$

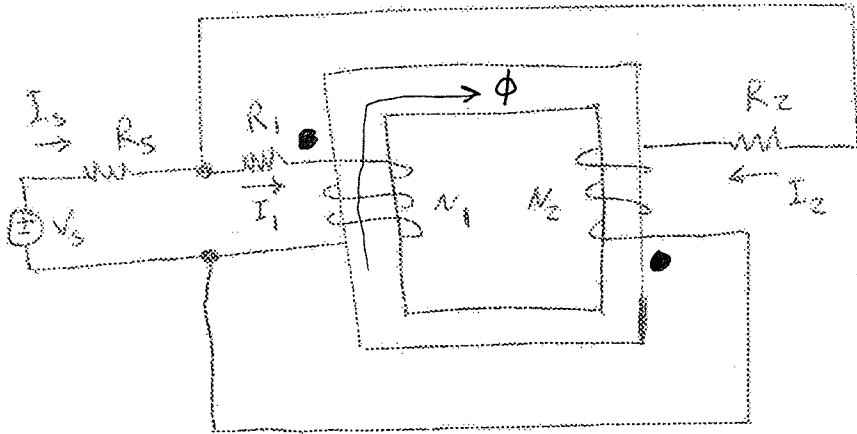Problem 3. (25 points)

A magnetic core with two coils is shown below. Magnetic core reluctance, R_C , electrical resistances, R_S, R_1, R_2 , and winding turns, N_1, N_2 are known.



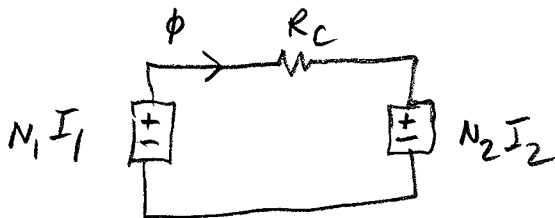- a) Label the dots on both coils (4 points) (See figure)
 b) Draw the magnetic equivalent circuit (Neglect leakage flux) (4 points)



$$-N_1 I_1 + \phi R_C + N_2 I_2 = 0$$

$$\phi = \frac{N_1 I_1 - N_2 I_2}{R_C}$$

- c) Solve for inductances, L_1, L_2 , mutual inductance, M , and coupling factor, k (9 points)

$$v_1 (+ \text{ on top}) = N_1 \frac{d\phi}{dt} = \frac{N_1^2}{R_C} \frac{dI_1}{dt} - \frac{N_1 N_2}{R_C} \frac{dI_2}{dt}$$

$$v_2 (+ \text{ on top}) = -N_2 \frac{d\phi}{dt} = -\frac{N_1 N_2}{R_C} \frac{dI_1}{dt} + \frac{N_2^2}{R_C} \frac{dI_2}{dt}$$

$$L_1 = \frac{N_1^2}{R_C} \quad L_2 = \frac{N_2^2}{R_C}$$

$$M = \frac{N_1 N_2}{R_C}$$

- d) Write the two equations for V_S in terms of I_1 and I_2 (8 points)


$$V_S = (I_1 + I_2)R_S + R_1 I_1 + v_1 \text{ (above)}$$

$$V_S = (I_1 + I_2)R_S + R_2 I_2 + v_2 \text{ (above)}$$

$$k = \frac{N_1 N_2 / R_C}{\sqrt{\frac{N_1^2}{R_C} \frac{N_2^2}{R_C}}} = 1$$

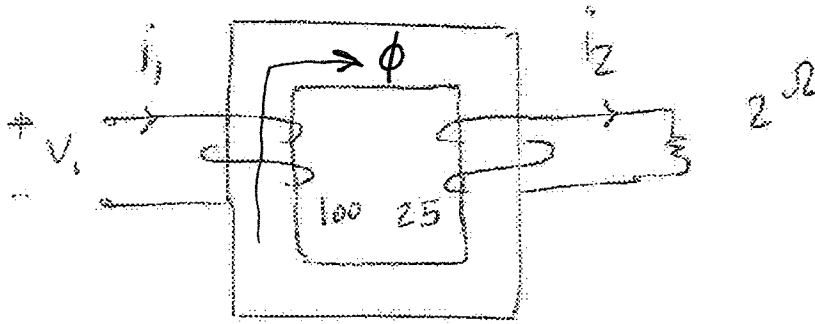Problem 4. (25 points)

A two-coil system is shown below. You can neglect the leakage flux, but the core has some reluctance that you need to compute.



System parameters are:

- $N_1 = 100$ $N_2 = 25$
- Mean length = 0.4m
- Area = 0.005 m²
- $\mu_r = 1000$
- Coil resistances are negligible

$$v_1 = 120\sqrt{2} \cos(2\pi 60t)$$

If a 120 V (RMS), 60 Hz sinusoidal voltage source is applied to coil 1, and a 2 ohm resistor is connected across the terminals of coil 2. Find the following quantities in time domain:

- a) The magnetic flux, ϕ , in the iron core (5 points) use cw flux

$$v_1 = N_1 \frac{d\phi}{dt} = 120\sqrt{2} \cos(2\pi 60t) \quad \phi = \frac{120\sqrt{2}}{100 \times 2\pi 60} \sin(2\pi 60t)$$

$$i_1 = 4.26\sqrt{2} \cos(2\pi 60t - 28^\circ)$$

$$\phi = 0.0045 \sin 2\pi 60t \text{ webers}$$

- b) The magnetic flux density, B, in the iron core (5 points)

$$\vec{I}_1 = \frac{2.86}{\sqrt{2}} \angle -90^\circ + \frac{5.3}{\sqrt{2}} \angle 0$$

$$B = \frac{\phi}{A} = \frac{0.0045}{0.005} \sin 2\pi 60t = 0.9 \sin 2\pi 60t \text{ Tesla (or webers/m}^2\text{)}$$


- c) The secondary coil current, i_2 (7 points)

$$\begin{aligned} &= 3.75 - j2.02 \\ &= 4.26 \angle -28^\circ \end{aligned}$$

$$v_2 (+ \text{ on top}) = 25 \frac{d\phi}{dt} = 25 \times 0.0045 \times 2\pi 60 \cos 2\pi 60t$$

$$v_2 = 42.42 \cos 2\pi 60t = 2i_2$$

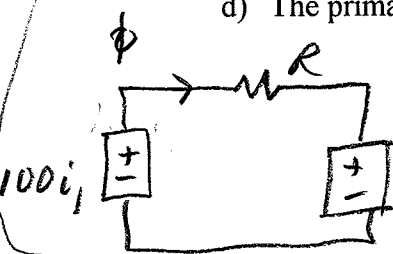- d) The primary coil current, i_1 (8 points)



$$R = \frac{0.4}{4\pi \times 10^{-7} \times 1000 \times 0.005} = 63662$$

$$i_2 = 21.21 \cos 2\pi 60t$$

$$100i_1 = 63662 \times 0.0045 \sin 2\pi 60t + 25 \times 21.21 \cos 2\pi 60t$$

$$i_1 = 2.86 \sin 2\pi 60t + 5.3 \cos 2\pi 60t$$