

**Problem 1 (20 pts.)**

- a) A single-phase 460 V, 60 Hz load uses 12 kW at a lagging PF of 0.75. Taking voltage as reference the current  $\bar{I}$  is \_\_\_\_\_ and the complex power is \_\_\_\_\_.

$$\bar{V} = 460 \angle 0^\circ \text{ V}$$

$$\bar{I} = \frac{P}{V \cdot \text{PF}} \angle -\cos^{-1} 0.75 = \frac{12 \times 10^3}{460 \times 0.75} \angle -41.4^\circ \text{ A} = \boxed{34.78 \angle -41.4^\circ \text{ A}}$$

$$\bar{S} = P + jQ = P + jP \tan(41.4^\circ) = 12 (1 + j0.88) = \boxed{12 + j10.6 \text{ kVA}}$$

- b) Two loads in parallel have the complex powers as  $141.4 \angle 45^\circ$  kVA and  $50 + j50$  kVA. The total complex power is \_\_\_\_\_. The value of Q required to make PF unity is \_\_\_\_\_.

$$\bar{S}_1 = 141.4 \angle 45^\circ = 100 + j100$$

$$\bar{S}_2 = 50 + j50$$

$$\bar{S}_T = \bar{S}_1 + \bar{S}_2 = \boxed{150 + j150 \text{ kVA}}$$

$$Q_{\text{required}} = \boxed{-150 \text{ kVAR}}$$

- c) The voltage across a two terminal network is  $100 \cos(t-30^\circ)$  V and the current into the network is  $500 \cos(t+30^\circ)$  A. The power factor is 0.5 and is leading or lagging (circle one).

$$\text{PF} = \cos(-60^\circ) = 0.5$$

- d) A 2300 V three-phase power system supplies 2 kW to a delta connected balanced load at a PF of 0.8 lagging. The magnitude of line current is 0.628 A, the magnitude of phase current is 0.362 A and the complex impedance of each leg (phase) is 6348 / 37° Ω.

$$P_{3\phi} = \sqrt{3} V_{l-l} I_l \text{ PF}$$

$$I_l = \frac{P_{3\phi}}{\sqrt{3} V_{l-l} \text{ PF}} = \frac{2 \times 10^3}{\sqrt{3} \times 2300 \times 0.8} = 0.628 \text{ A}$$

$$I_\phi = \frac{I_l}{\sqrt{3}} = 0.362 \text{ A}$$

$$|Z| = \frac{2300}{0.362} = 6348 \Omega \Rightarrow Z = 6348 \angle \cos^{-1} 0.8 = 6348 \angle 36.9^\circ \Omega$$



- e) A coil of 1000 turns is wound on an iron core whose reluctance  $\mathcal{R} = 4.6 \times 10^6 \text{ At/W}$ . The inductance of the coil is 0.217 H.

$$L = \frac{N^2}{\mathcal{R}} = \frac{1000^2}{4.6 \times 10^6} = 0.217 \text{ H}$$

- f) Two coils which are coupled have self-inductances of 10 and 20 mH respectively and a coupling coefficient of 0.9. The mutual inductance is 12.73 mH.

$$M = k \sqrt{L_1 L_2} = 0.9 \sqrt{10 \times 20} = 12.73 \text{ mH}$$

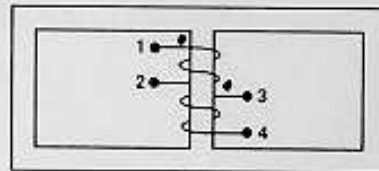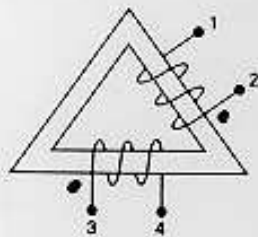- g) Put the dot markings on the coils in the structures below.



- b) If  $\lambda = \frac{i}{x^2}$ ,  $W_m(\lambda, x) = \frac{x^2 \lambda^2}{2}$ ,  $W'_m(i, x) = \frac{i^2}{2x^2}$ .

$$W_m = \int_0^\lambda i d\lambda' = \int_0^\lambda x'^2 \lambda'^2 d\lambda' = \frac{x^2 \lambda^2}{2}$$

$$W'_m = \int_0^i \lambda di' = \int_0^i \frac{i'}{x^2} di' = \frac{i^2}{2x^2}$$

- i) An 8 pole induction motor with 5% slip ( $s = 0.05$ ) is supplied by a 60 Hz generator. The speed of the motor is 855 RPM and the frequency of rotor current is 3 Hz.

$$N_s = \frac{120 f}{P} = \frac{120 \times 60}{8} = 900 \text{ RPM}$$

$$N_{act} = N_s (1 - s) = 900 (1 - 0.05) = 855 \text{ RPM}$$

$$f_r = s f_s = 0.05 \times 60 = 3 \text{ Hz}$$

2

2

- j) The rotor copper losses of a three phase, 6 pole, 60 Hz induction motor running at 1100 RPM is 5 kW. The input power to the motor is 60 kW and the torque of electric origin is 477.5 N-m. Neglect stator copper losses.

$$N_s = \frac{120 \times 60}{6} = 1200 \text{ RPM}$$


$$s = \frac{N_s - N_{act}}{N_s} = \frac{1200 - 1100}{1200} = \frac{1}{12}$$

$$P_r = s P_{ag} \Rightarrow P_{ag} = \frac{P_r}{s} = \frac{5 \text{ kW}}{1/12} = \boxed{60 \text{ kW}}$$

$$P_m = P_{ag} (1-s) = 60 \left(1 - \frac{1}{12}\right) = 55 \text{ kW}$$

$$T^e = \frac{P_m}{\omega_m} = \frac{55 \times 10^3}{2\pi \left(\frac{60}{60}\right) (1-s)} = \boxed{477.5 \text{ N-m}}$$

**Problem 2 (20 pts.)**

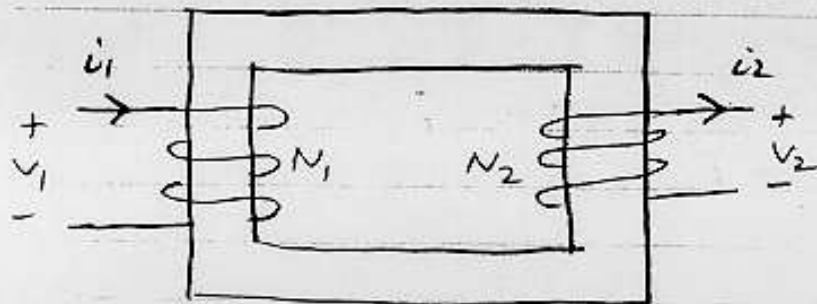


Given: cross-section area =  $10^{-3} \text{ m}^2$

Length of main flux path = 0.2 m

$v_1 = 170 \cos 377t$  volts

- Find  $N_1$  so that the flux density in the iron is limited to a peak value of 1.0 tesla in steady state with  $i_2 = 0$ . (Assume infinite permeability for the iron.)
- Using these turns, what will be the peak value of  $i_1$  if the iron permeability is  $500 \mu_0$  and  $i_2 = 0$ ? (Neglect leakage flux) ( $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$ )
- What is the peak value of  $i_1$  if  $N_2 = 900$  turns and an  $80 \Omega$  resistor is added on the "2" side? (Neglect leakage flux)

**Problem 3 (20 pts.)**

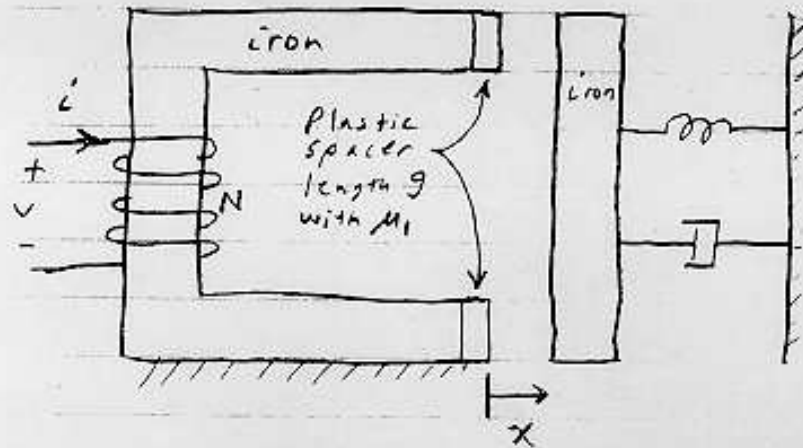

All materials have width  $w$  and depth  $d$ .  $\mu_{\text{iron}} = \infty$ . Consider only one flux path.

- (8 pts.) Find an expression for the force of electrical origin in the positive  $x$  direction when  $x = 0$ , as a function of current  $i$ .
- (8 pts.) Find the energy transferred from the electrical system into the coupling field when  $x$  moves from 0 to  $x_1$  while  $i$  is held constant at  $I_0$ .
- (2 pts.) Is the answer to (b) a positive number or negative?
- (2 pts.) In one sentence, give a physical explanation for the sign on the force of electrical origin in part (a).

**Problem 4 (20 pts.)**

For the following state space model

$$\begin{aligned}\dot{x}_1 &= x_2 \\ \dot{x}_2 &= -0.1x_2x_3 - x_1^3 + x_1 \\ \dot{x}_3 &= (-2x_2x_3 - x_3 + 5)\end{aligned}$$

the initial conditions are  $x_1(0) = 1$ ,  $x_2(0) = 0.5$  and  $x_3(0) = 10$  at  $t = 0$ .

- a) (10 pts.) With a time step of  $\Delta t = 0.1$  sec, integrate the system to obtain  $x_1$ ,  $x_2$ ,  $x_3$  at  $t = 0.1$  sec.  
b) (5 pts.) Find the equilibrium points.  
c) (5 pts.) Find the linearized model, i.e., matrix  $A$  at any one of the equilibrium points. (No eigenvalue computation needed.)

$$\begin{aligned}a) \quad x_1(0.1) &= x_1(0) + \Delta t \dot{x}_1|_0 = 1 + 0.1 \times 0.5 = \boxed{1.05} \\ x_2(0.1) &= x_2(0) + \Delta t \dot{x}_2|_0 = 0.5 + 0.1 \left( -0.1 \times 0.5 \times 10 - 1^3 + 1 \right) = \boxed{0.45} \\ x_3(0.1) &= x_3(0) + \Delta t \dot{x}_3|_0 = 10 + 0.1 \left( -2 \times 0.5 \times 10 - 10 + 5 \right) = \boxed{8.5}\end{aligned}$$

$$b) \quad \begin{cases} 0 = x_2 \\ 0 = -0.1x_2x_3 - x_1^3 + x_1 \\ 0 = -2x_2x_3 - x_3 + 5 \end{cases} \Rightarrow \begin{aligned} &x_2 = 0 \\ &x_1^3 - x_1 = 0 \Rightarrow x_1 = 0, 1, -1 \\ &x_3 = 5 \end{aligned}$$

3 equilibrium points:  $(0, 0, 5)$ ,  $(1, 0, 5)$ , and  $(-1, 0, 5)$   
#1 #2 #3

c) Linearized model

$$A = \begin{bmatrix} 0 & 1 & 0 \\ -3x_1^2 + 1 & -0.1x_3 & -0.1x_2 \\ 0 & -2x_3 & -2x_2 - 1 \end{bmatrix}$$

$$\#1 \begin{bmatrix} 0 & 1 & 0 \\ 1 & -0.5 & 0 \\ 0 & -10 & -1 \end{bmatrix}, \quad \#2 \begin{bmatrix} 0 & 1 & 0 \\ -2 & -0.5 & 0 \\ 0 & -10 & -1 \end{bmatrix}, \quad \#3 \begin{bmatrix} 0 & 1 & 0 \\ -2 & -0.5 & 0 \\ 0 & -10 & -1 \end{bmatrix}$$

**Problem 5 (20 pts.)**

A three-phase, 60 Hz, 6 pole, 550 V (line-line) wye connected synchronous generator is delivering 250 kW at rated voltage. The excitation voltage  $E_{ar}$  is 460 V per phase and the synchronous reactance  $x_s = 1.2 \Omega$  (Neglect stator resistance.)


- (7 pts.) Calculate the torque angle  $\delta$  and the torque of electrical origin (specify + or -).
- (5 pts.) Find the generator current magnitude, power factor and reactive generation  $Q$ .
- (5 pts.) For the same terminal voltage and active power generation  $P$  determine the excitation voltage  $E_{ar}$  to deliver power with a power factor of 0.8 lagging. What is the new value of the torque angle  $\delta$  in this case?
- (3 pts.) How many poles should an induction motor have to turn at 900 RPM at no load when served by this generator?

a)  $\bar{V}_a = \frac{550}{\sqrt{3}} = 317.5 \angle 0^\circ \text{ V}$

$$P = \frac{3 E_{ar} V_a \sin \delta}{x_s}$$

$$\sin \delta = \frac{P x_s}{3 E_{ar} V_a} = \frac{250 \times 10^3 \times 1.2}{3 \times 460 \times 317.5} = 0.6846$$
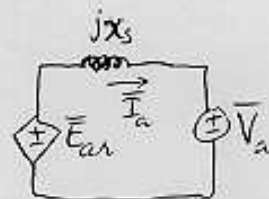
$$\delta = 43.2^\circ, \quad T^e = \frac{P}{\omega_m} = \frac{250 \times 10^3}{2\pi \left(\frac{60}{60}\right)} = 1989.4 \text{ N-m}$$



b)  $\bar{I}_a = \frac{\bar{E}_{ar} - \bar{V}_a}{j x_s} = \frac{460 \angle 43.2^\circ - 317.5 \angle 0^\circ}{j 1.2} = 262.8 \angle -3.24^\circ \text{ A}$

$$\bar{I}_a = 262.8 \text{ A}, \quad \text{PF} = \cos 3.24^\circ = 0.998, \quad Q = P \tan(3.24^\circ) = 14.15 \text{ kVAR}$$

c)  $\bar{S}_{\text{new}} = \frac{P/3}{0.8} \angle \cos^{-1} 0.8 = 104.2 \angle 36.9^\circ \text{ kVA}$

$$\bar{I}_{a,\text{new}} = \frac{\bar{S}_{\text{new}}^*}{\bar{V}_a^*} = \frac{104.2 \angle -36.9^\circ}{317.5} = 0.328 \angle -36.9^\circ \text{ kA}$$

$$\bar{E}_{ar,\text{new}} = 317.5 \angle 0^\circ + (j 1.2)(0.328 \angle -36.9^\circ) = 637 \angle 29.6^\circ \text{ V}$$

$$\delta_{\text{new}} = 29.6^\circ$$

d)  $\frac{P}{2} N_m = N_s$   
 $\frac{P}{2} 900 = 3600$

$$P = 8$$