

Problem 1 (25 pts.)

The following three-phase balanced loads are connected in parallel across a three-phase wye-connected, 50 Hz source of 480 V (line to line)

Load #1 94 kVA (3-phase) at 0.8 PF lag (Wye connected)

Load #2 67 kW (3-phase) at 0.7 PF lag (Wye connected)

Load #3 75 Amps phase current, with 0.9 power factor lag (Delta connected)

Find the following things:

- The total complex power (3-phase) consumed by the three loads
- The total source line current (magnitude).
- The capacitive reactive power needed per phase (for a delta connection) so that the overall power factor is 0.95 lag.
- The new source line current with the power factor correction of c) installed.

$$a) \bar{S} = 94k[37^\circ] + \frac{67k}{0.7}[46^\circ] + 3 \times 480 \times 75[26^\circ]$$

$$= [(75+j56) + (66+j69) + (97+j47)]k = 238+j172k$$

$$= \boxed{294k[36^\circ]}$$


$$b) 294k = \sqrt{3} \times 480 \times I_L \quad \boxed{I_L = 354A}$$

$$c) \bar{S} = \frac{238}{0.95}[18^\circ] = 239k+j77k$$

$$\text{Q}_{\text{per phase}} = \frac{172k - 77k}{3} = \boxed{32 \text{ kVAR per phase}}$$

$$d) \frac{238k}{0.95} = 251k = \sqrt{3} \times 480 \times I_L \quad \boxed{I_L = 302A}$$

Problem 2 (25 pts.)

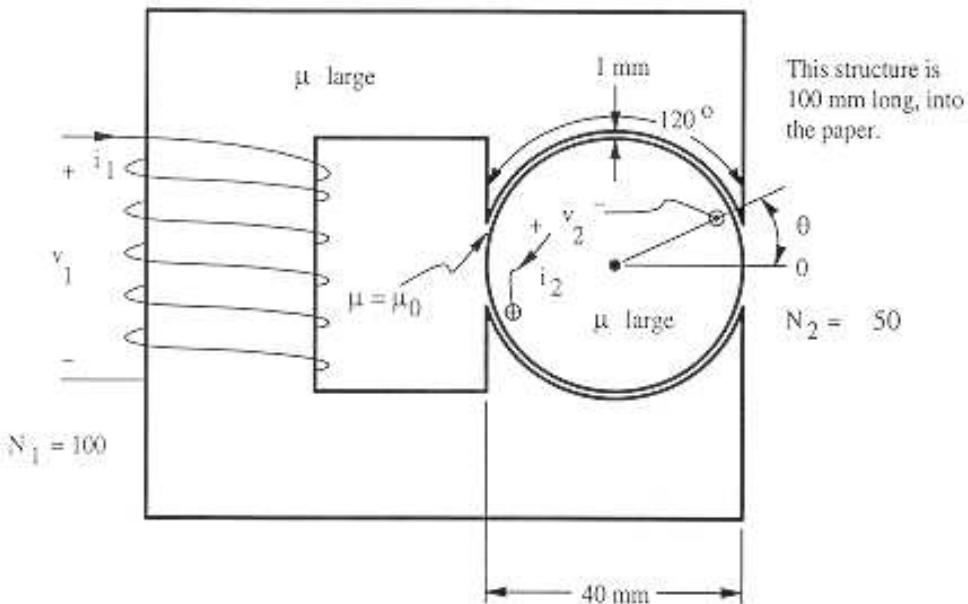

- a) For the structure above, find $\lambda_1(i_1, i_2, \theta)$ and $\lambda_2(i_1, i_2, \theta)$. The winding resistances are small. (Hint: consider the reluctance of the structure. You may use sinusoidal approximations for position effects as appropriate.)
- b) Let $i_1 = 6 \text{ A}$. If $d\theta/dt = 120\pi \text{ rad/s}$, what is the measured voltage $v_2(t)$ when $i_2 = 0$?

$$\mathcal{R} = \frac{\ell}{\mu A} \rightarrow \frac{\frac{2\pi r}{20}}{\frac{0.002}{\mu_0 (\frac{2\pi r}{3})^2}} = \frac{20 \text{ mm}}{\mu_0 (2.63 \times 10^{-2})} \quad R = 20 \text{ mm} \quad L = 100 \text{ mm}$$

$$= 3.90 \times 10^5 \text{ H}^{-1} \quad L_1 = \frac{N_1^2}{\mathcal{R}} = 2.63 \times 10^{-2}$$

$$\lambda_1 = L_1 i_1 + M_{12} i_2 \quad \lambda_2 = L_2 i_2 + M_{12} i_1$$

$$L_1 = \frac{N_1^2}{\mathcal{R}} = 2.63 \times 10^{-2} \quad M_{12} = \frac{N_1 N_2}{\mathcal{R}} \text{ for } i_2 = 0 \quad L_2 = \frac{N_2^2}{\mathcal{R}} = 6.58 \times 10^{-3}$$

$$\lambda_1 = 2.63 \times 10^{-2} i_1 + 1.32 \times 10^{-2} \sin \theta i_2 \quad \lambda_2 = 1.32 \times 10^{-2}$$

$$\lambda_1 = 2.63 \times 10^{-2} i_1 + 1.32 \times 10^{-2} \sin \theta i_2 \quad \lambda_2 = 6.58 \times 10^{-3} i_2 + 1.32 \times 10^{-2} \sin \theta i_1$$

$$i_1 = \omega_1 t, \quad i_2 = 0, \quad \frac{d\theta}{dt} = 120\pi \text{ rad/s} \quad v_2 = \frac{d\lambda_2}{dt} = -7.40 \times 10^{-2} \sin \theta \frac{d\theta}{dt}$$

$$= 29.8 \sin(120\pi t + \theta_0)$$

Problem 3 (25 pts.)

An electromechanical system is described by the following flux-linkage vs current characteristic:

$$\lambda = \frac{.04}{x - .01} i$$

It is operated on the closed cycle a - b - c - d - e as indicated below, with x constant during a - b and also c - d. The current is constant during b - c and also d - e.

	a	b	c	d	e
i (Amps)	0	i_b	i_b	0	0
λ (Wb turns)	0	8	λ_c	0	0
x (meters)	.03	.03	.02	.02	.03

$$\omega_m^2 = \frac{.02 i^2}{x - .01}$$

$$f^2 = \frac{- .02 i^2}{(x - .01)^2}$$

Find the following things:

- i_b and λ_c .
- Energy transferred from the electrical system into the coupling field during a - b.
- Energy transferred from the mechanical system into the coupling field during b - c.
- Energy transferred from the electrical system into the coupling field during c - d.
- Energy transferred from the mechanical system into the coupling field during d - e.

a) $\theta = \frac{.04}{.02} i_b$ $i_b = 4 \text{ A}$ $\lambda_c = \frac{.04}{.01} 4 = 16 \text{ Wb Tn}$

b) $EFE_{a-b} = \int_0^8 \frac{\lambda}{2} d\lambda = \frac{\lambda^2}{4} \Big|_0^8 = 16 \cdot 0 = 16 \text{ J}$

c) $EFM_{b-c} = \left(+ \frac{.02 \times 16}{(4 - .01)^2} dx \right) \Big|_{.03}^{.02} = - \frac{.32}{(x - .01)} \Big|_{.03}^{.02} = - 32 + 16 = - 16 \text{ J}$

d) $EFE_{c-d} = \int_{.02}^0 \frac{\lambda}{4} d\lambda = \frac{\lambda^2}{8} \Big|_{.02}^0 = - 32 \text{ J}$

e) $EFM_{d-e} = 0$ $EFE_{b-c} = \int_8^{16} 4 d\lambda = 32 \text{ J}$


$FFM_{a-b} = 0$

$FFM_{c-d} = 0$

$EFE_{d-e} = 0$ $EFE_{c-e} = 16 \text{ J}$

$FFM_{cycle} = - 16 \text{ J}$

Problem 4 (25 pts.)

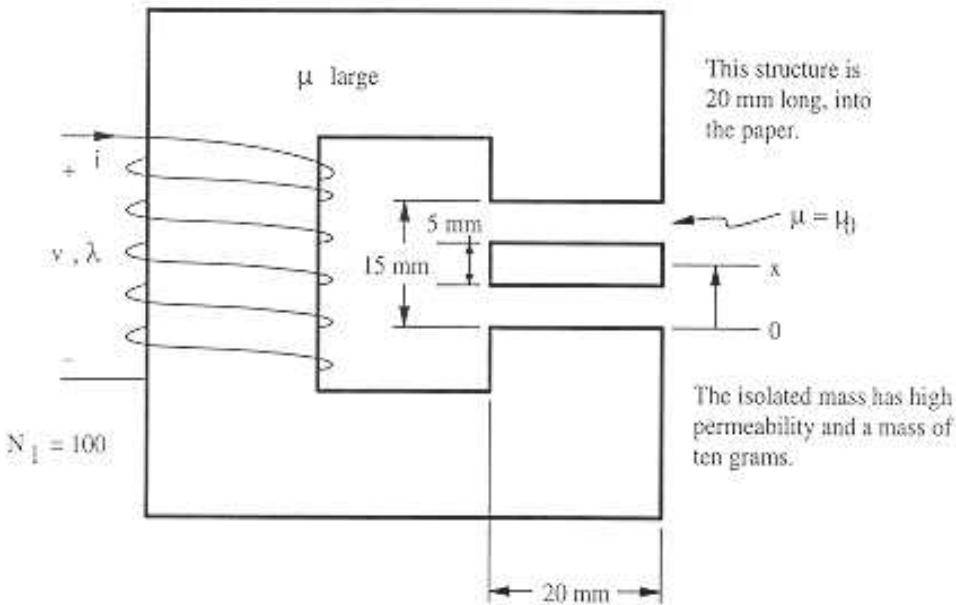

The physical arrangement shown is proposed as a way to levitate an object. The following analysis tries to determine whether this will work. Use the acceleration due to gravity (pointed down) as 10 m/s^2 .

- Find $\lambda(i, x)$ for this structure.
- Find either the stored energy $W_m(\lambda, x)$ or co-energy $W_m'(i, x)$ for this structure.
- It is proposed that if the position of the ten gram object is sensed, and a current $i(x) = 20000x^2$ (with x in meters and i in amps) is imposed, then the object can be levitated (held stable and stationary in open space). What is $i^*(x)$ for this choice of current?
- Write equations for $d\lambda/dt$, $dx/dt = V$ (velocity) and dV/dt for this system, in state-space form, given that $i = i(x) = 20000x^2$. Use λ , x , and V as state variables.
- Linearize your result about the point $x = 5 \text{ mm}$. Do you think it will work?

a) $\mathcal{Q} = \frac{\lambda}{\mu_0 A} = \frac{0.1 \text{ N}}{\mu_0 (400 \times 10^{-6})} = 19.7 \times 10^6 \quad \frac{\text{N}^2}{\text{A}} = 0.503 \text{ mH} = L \quad \lambda = 5.03 \times 10^{-9} i$

b) $W_m' = \frac{1}{2} L i^2 = 2.51 \times 10^{-7} i^2$

c) $W_m' = 10^5 \chi^4 \quad \{ \epsilon = \frac{\partial W_m'}{\partial x} = 4 \times 10^5 x^3$

d) $\frac{d\lambda}{dt} = 10 \frac{\lambda}{\omega} = 10 V \quad \frac{dV}{dt} = 4 \times 10^5 x^3 - 0.1$
 $\frac{dx}{dt} = V$

AT $x = 5 \text{ mm}$:
 $i = 5.03 \times 10^{-9} \times -0.05$
 $\sqrt{FALLING}$

$x = -0.05 + \Delta x$

$\frac{dx}{dt} = \frac{dx}{dt} + \frac{dx}{dt}$

$\frac{dx}{dt} = V$

$\frac{dV}{dt} = 300x - 0.05$
 $= 0.05 + 30 \Delta x$

Extra work space (please show which problem is involved).

$$\begin{aligned} & (-.005 + \Delta x)^2 (-.005 + \Delta x) \\ &= (.005^2 + .01\Delta x + \Delta x^2)(-.005 + \Delta x) \\ &\quad + .005^3 + 50\pi 10^{-6}\Delta x + .005\Delta x^2 \\ &\quad + .005^2\Delta x + .01\Delta x^2 + \Delta x^3 \\ & 4\pi 10^5 \quad (.005^3 + 75\pi 10^{-6}\Delta x) \\ & \quad 0.05 + 30\Delta x \end{aligned}$$

$$\begin{bmatrix} \dot{\Delta x} \\ \dot{\Delta v} \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ 30 & 0 \end{bmatrix} \begin{bmatrix} \Delta x \\ \Delta v \end{bmatrix} = \begin{bmatrix} 0 \\ -0.05 \end{bmatrix}$$

$$(S\mathbf{I} - A)^{-1}$$

$$\begin{bmatrix} 3 & 0 \\ 0 & 5 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ 30 & 0 \end{bmatrix}$$


$$e^{j\omega t} \begin{bmatrix} 3 & -1 \\ -30 & 5 \end{bmatrix}$$

$$\begin{aligned} s^2 + 3s + 0 \\ s = \pm \sqrt{30} \quad \text{N.S.} \end{aligned}$$

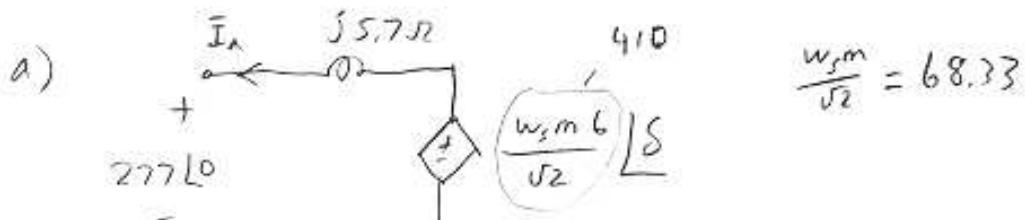Problem 5 (25 pts.)

A three-phase, 60 Hz, 4 pole, wye connected synchronous generator is delivering 30 kW (3-phase) into a system at the rated voltage of 277 V (line to neutral). The field current $I_f = 6 \text{ ADC}$ produces an internal excitation voltage magnitude E_{ar} of 410 V (line to neutral). The synchronous reactance $X_s = 5.7 \text{ Ohms}$. Compute the following things (neglect stator (armature) resistance and saturation of the iron):

- The torque angle δ and the torque in NM.
- The generator line current magnitude
- The power factor of the power being delivered by the generator
- Is the generator over-excited or under-excited? (explain your answer)



$$30 \text{ k} = \frac{3 \times 277 \times 410}{5.7} \sin \delta$$

$$T = \frac{30 \text{ k}}{377 \frac{2}{\sqrt{2}}} = 159 \text{ N-m}$$

$$\delta = 30^\circ$$

b) $\bar{I}_A = \frac{410 L^0 - 277 L^0}{j 5.7} = 72 L^{-60^\circ} - 48.6 L^{-90^\circ}$

$$= 36 - j62 + 0 + j48.6 = 36 - j13.4 = 38 L^{-20^\circ}$$

c) $\text{pf} = \cos(0 + 70^\circ) = 0.94 \text{ lag}$

d) Over-excited because $Q_{\text{out}} > 0$

Problem 6 (25 pts.)

An industrial plant is supplied by the electric utility with $3\ \phi$, 4160 V (line-line), 60 Hz. The total plant load is 5000 kW (3-phase). Each major process in the plant now runs with an induction motor that has a power factor of 0.85 lagging. It has been suggested that one of these major processes can be converted over to a synchronous motor, which would also improve the overall power factor. The proposed machine has a series reactance per phase $X_s = 6\ \Omega$. It will serve a process that requires 2000 kW (3-phase) after installation.

- Find the current delivered to the plant by the utility before the replacement of the induction motor by the synchronous motor.
- The motor is installed, and set up to draw 2000 kW (out of the same 5000 kW total) and $S = 2750$ kVA, with leading power factor. What is the current delivered to the plant now? What is the plant's overall power factor?
- With the motor in place, drawing $P = 2000$ kW and $S = 2750$ kVA, find the torque angle and the internal voltage magnitude E_{ar} in the machine.

$$a) P = 5000 \text{ kW}, S = 5832 \text{ kVA} = \sqrt{3} V_L I_L \quad I_L = 816.4 \quad Q = 3099 \text{ kVAR}$$

$$b) P = 5000 \text{ kW} \quad Q_{synch} = 1887$$

$$Q_{load} = 3099 \text{ kVAR}$$

$$Q_{TOTAL} = 28.45 \text{ kVAR LOAD}$$

$$S_{TOTAL} = 5000 \text{ kVA} \quad I_L = 694 \text{ A}$$

$$\text{OVERALL pf} = 1$$

$$c) P = \frac{3(V_{as}/E_{ar}) \sin \delta}{6} = \frac{|V_L| |E_{ar}| \sin \delta}{6} = 2000 \text{ kW}$$

$$E_{ar} \sin \delta = 1665$$

$$Q = \frac{3 V_{as}^2}{6} - \frac{3 V_{as} E_{ar}}{6} \cos \delta = 1887 \text{ kVAR}$$

$$9.97 \times 10^5 = \frac{3 V_{as} E_{ar}}{6} \cos \delta$$

$$830.4 = E_{ar} \cos \delta \quad \tan \delta = \frac{1665}{830.4} = 2$$

$$1665 = E_{ar} \sin \delta \quad \delta = 63.5^\circ$$

$$9.968 \times 10^5 = \frac{3 V_{as} E_{ar}}{6} \cos \delta \quad 1665$$

$$830 = E_{ar} \cos \delta \quad \frac{1665}{3973}$$

$$3973 = E_{ar} \cos \delta$$

$$E_{ar} = 4308 \quad \tan \delta = 0.419$$


$$\delta = 22.73^\circ \checkmark$$

Problem 7 (25 pts.)

A 3-phase, 6-pole, 60 Hz, 440 V (line-line) wye-connected squirrel cage induction motor is running at 1120 RPM. The shunt magnetizing reactance (on the stator side) is 20 Ohms per phase, the stator a rotor series leakage reactances are each 1.5 Ohms per phase (on the stator side), and the rotor resistance referred to the stator is 0.5 Ohms per phase. Neglect stator resistance, iron core losses and rotational losses. Find the following things:

- The frequency of the rotor currents in Hz at this level of load
- The magnitude of the stator line current at this level of load
- The torque to the shaft of the machine in N-m at this level of load
- What is the starting current if this machine was started with full voltage suddenly applied while it is at standstill?
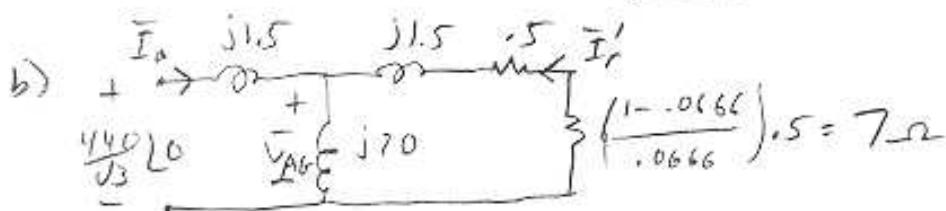
$$a) f_r = sf_s = \left(\frac{1200 - 1120}{1200} \right) 60 = \boxed{4 \text{ Hz}} \quad s = .0666$$



$$\bar{Z}_{tot} = j1.5 + \frac{j70(7.5 + j1.5)}{7.5 + j21.5} = j1.5 + 5.8 + j3.35 = 7.56 \angle 40^\circ$$

$$|I_a| = \frac{254}{7.56} = \boxed{33.6 \text{ A}} \quad \theta = -40^\circ$$

$$c) -254 \angle 6 + j1.5 \times 33.6 \angle -40^\circ + \bar{V}_{A6} = 0 \quad \bar{V}_{A6} = 254 \angle 0 - 50.4 \angle 50^\circ$$

$$\bar{V}_{A6} = 222 - j29 = 225 \angle -10^\circ \quad \bar{I}_r' = \frac{225 \angle -10^\circ}{7.5 + j1.5} = 29.4 \angle$$


$$T = \frac{3 \times 29.4^2 \left(\frac{.5}{.0666} \right)}{1200 \times \frac{7\pi}{60}} = \boxed{155 \text{ N-m}}$$

$$d) s = 1 \quad \bar{Z} = j1.5 + \frac{(1.5 + j1.5)j70}{.5 + j21.5} = 1.43 + j2.9 = 2.93 \angle 9^\circ \quad |I_a| = \frac{254}{2.93} = \boxed{87 \text{ A}}$$

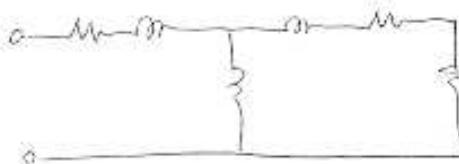Problem 8 (25 pts.)

An induction machine has nameplate ratings of 3ϕ , 60 Hz, 230 V (line to line), 24 A, 1740 RPM, 10 HP (horsepower). This motor has been tested, and is known to have $R_s = 0.1 \Omega$ and $X_{ls} = 0.6 \Omega$. The motor operates at rated voltage. When it is unloaded, it draws 10 A and total power of 32 W while running at a speed just slightly under 1800 RPM. When it is running at rated load and speed, it draws 24 A and 7890 W. Recall that 1 HP = 746 W. You may ignore magnetic losses and rotational losses.

- Find X_m (hint: consider the unloaded information).
- Find R_t' and X_b' . What is the efficiency of this motor at rated load and speed?



a)

$$|Z| = 13.5 \Omega = \sqrt{0.1^2 + (0.6 + X_m)^2}$$

$$176.3 = (0.6 + X_m)^2$$

$$13.28 = 0.6 \times X_m$$

$$X_m = 12.68 \Omega$$

b)

$$\zeta = \sqrt{3} V_s I_s$$

$$= 9561 \quad \theta = 7890$$

$$Q = 5400$$

$$4. I = -34.37^\circ$$

$$= 19.81 - j 23.56$$

$$\eta = \frac{7460}{7890} = 94.6\%$$