

NAME SOLN

e. (2 pts) Compute the phase voltage at the turbine's terminals.

$$\begin{aligned}
 V_{\text{turbine}} &= V_{\text{load}} + \bar{I} \cdot (R + jX) \\
 &= 277 \angle 0 + 80.22 \angle -25.84 (0.1 + j0.5) \\
 &= 277 + 40.9 \angle 52.8 = \underline{\underline{303.45 \angle 6.16^\circ}} \text{ ANS.}
 \end{aligned}$$

f. (3 pts) Compute the per phase real power at the turbine terminals?


$$\begin{aligned}
 S &= \bar{V} \bar{I} = (303 \angle 6.1^\circ) (80.22 \angle -25.8)^\ast = (303 \angle 6.1) (80.22 \angle 25.8) \\
 &= 24,337 \angle 31.96^\circ = 20,646 + j 12,885
 \end{aligned}$$

$$P = \underline{\underline{20.646 \text{ kW}}} \text{ ANS.}$$



g. (3 pts) Draw and label the power triangle for one-phase at the turbine terminals with computed S, P, Q, and angle values.

From f

$$S = 24,337 \angle 31.96^\circ$$

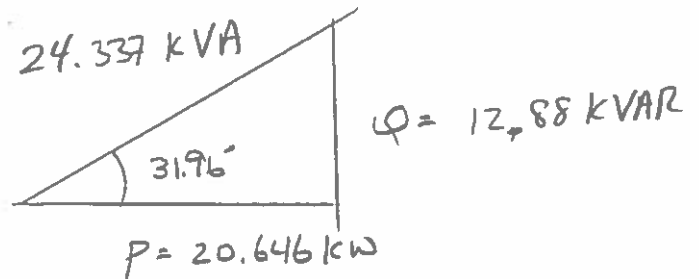

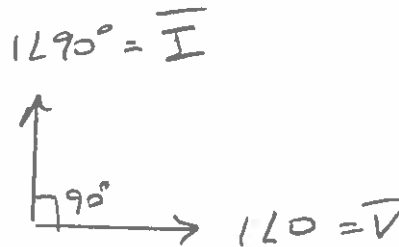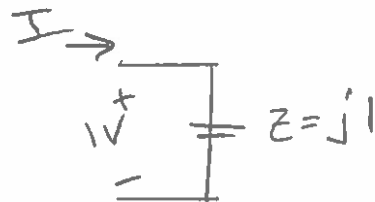BONUS (2 pts) Draw and label a phasor diagram showing the relationship between current through and voltage across a capacitor. The voltage is 1 V per unit. The capacitor's impedance magnitude is 1 per unit.




$$\bar{I} = \frac{\bar{V}}{Z} = \frac{1 \angle 0}{1 \angle 90} = \underline{\underline{1 \angle -90^\circ}} \text{ ANS.}$$

$$Z = \frac{1}{j1} = -j1 = 1 \angle -90^\circ$$

Quiz 2

1. A small wind turbine is delivering 60 kW through a 3-phase power line to a load having a power factor of 0.9 lagging power factor.
- The line voltage is 480 V at the load.
  - Each transmission line phase has inductive reactance  $X = 0.5 \Omega$  and resistance  $R = .1 \Omega$
  - The system is operating at 60 Hz
  - Assume the zero reference is phase "a" voltage at the load.

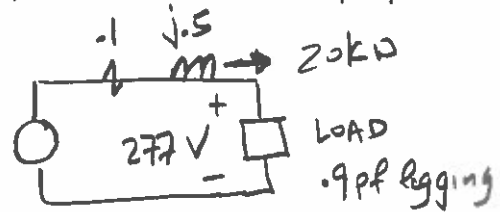- a. (3 pts) Draw and label the circuit per-phase diagram. Use this diagram for all subsequent computations.



$$V_p = \frac{480}{\sqrt{3}} = 277V$$

$$P_{1\phi} = \frac{60kW}{3} = 20kW$$

- b. (3 pts) Compute the voltage phasor on phase "a" at the load terminals.

$$\underline{\underline{V_a}} = 277 \angle 0^\circ \text{ ANS}$$



- c. (3 pts) Compute the phasor line current at the load.

$$ELI \rightarrow$$

$$pf = .9 = \cos \theta$$

$$\theta = \cos^{-1}(.9) = 25.84^\circ$$

$$P = 20kW = VI \cos(25.84^\circ) = VI pf$$

$$I = \frac{20000}{277(.9)} = \underline{\underline{80.22A}} \text{ ANS}$$

- d. (3 pts) Write the current equation time-domain current equation  $i(t)$

$$i(t) = \sqrt{2}(80.22) \cos(\omega t - 25.84^\circ) ; \omega = 2\pi f \rightarrow 2\pi 60$$