BALL RETURN PUTTING MAT WITH SCOREKEEPER

Team 69: Ben Cannistraro and Chris Bell ECE 445 Design Document Spring 2019 TA: Soumithri Bala

1 Introduction

1.1 Objective

Golf is a sport that requires a lot of time and practice in order to improve. However, it is a very weather dependent sport and many players are not able to practice during the winter months or during rainy days without spending a lot of money to go to indoor practice facilities or to purchase practice mats for their homes. There are some cheaper practice mats available, especially for putting, but they do not return the ball to the player or allow you to keep track of made putts.

Our goal is to build a low-cost putting mat that will allow players to practice indoors. This putting mat will include a mechanism that returns made putts to the user, allowing for more efficient practice time. It will also utilize a control circuit that will operate the return mechanism as well as keep count of all made putts by the user. This circuit will transmit a signal to a hex display via bluetooth every time a putt is made. This hex display will keep track of the number of putts made, as well as include a timer for competitive purposes.

1.2 Background

In sports, there are a lot of advancements being made with analytics and statistics to help players to track progress and continue to improve. Our device would allow a user to practice and track progress in the number of putts made over a given time span or to practice through competition. Our putting mat would allow users to do just that, as there is no putting mat available on the market that will track the number of putts made and return the ball to the user.

1.3 High Level Requirements

- The scoreboard will increment when a ball has entered the hole. It will keep score up to 63 made putts and can be reset to 0 when a pushbutton is pressed.
- The scoreboard will take an input from a pushbutton allowing the time to be set, up to 9 minutes. The timer will count down and keep an accurate time, within 5%, for each game.
- The return mechanism will hold the ball for no more than 10 seconds and be released and returned to the player.

2 Design

Living in the midwest, it is hard to practice or compete in golf during the winter. One of the most important parts of a player's game is putting so the ability to practice indoors during the winter is important in improving one's game. On the market there are lots of indoor putting mats including some that will return the ball to you, however there isn't a mat that keeps score and allows to compete against a friend.

2.1 Block Diagram


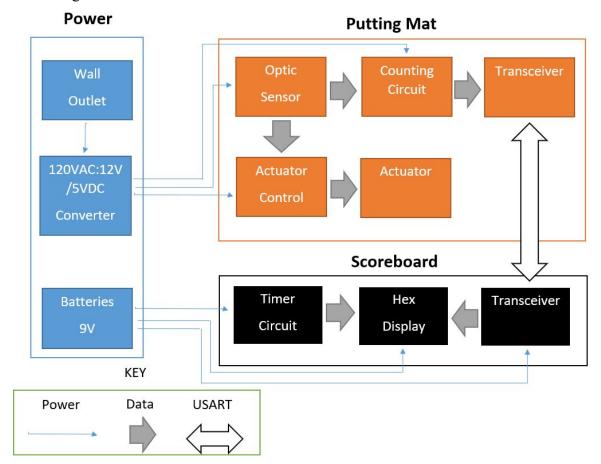


Figure 1: Block Diagram

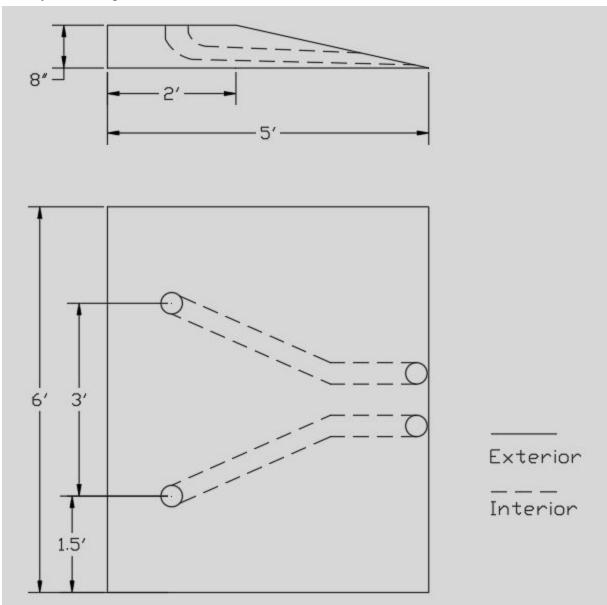

2.2 Physical Design

Figure 2: Physical Design Diagram

2.3.1 Power Supply

The Putting Mat and Scoreboard will be powered by too separate sources. The Putting Mat will be powered by a wall plug and the Scoreboard will be powered by a battery pack.

1 AC/DC Converter

The 120V AC will need to be converted to 12V DC and 5V DC to be used to power our counting circuit, microcontroller, actuator control circuit and actuator.

Requirement	Verification	
 A transformer and bridge circuit will be used to get an output of 12V DC ±3V. 	1. To test the transformer and bridge converter, use an oscilloscope to measure the output waveform.	
 Voltage regulator (MC78L12) will be used to output 5V DC ±5%. 	2. Use an oscilloscope to measure the output of the regulator.	
 Voltage regulator (LM78L05) will be used to output 12VDC ±5%. 	3. Use an oscilloscope to measure the output of the regulator.	

2 Batteries

This pack will use a 9V battery to power the circuits and transceiver.

Requirement	Verification	
1. Use a 9V DC battery as our power source.	 Verify voltage using oscilloscope or multimeter. 	

2.3.2 Putting Mat

We will use the space underneath the mat to house our circuitry that will allow a made to be counted and transmitted and then return the ball to the user.

1 Optic Sensor

This will sit inside the edge of the hole, when the ball is detected it will output a logical high that go to the solenoid control circuit and the counting circuit. We will use an infrared optical sensor.

Requirement	Verification	
1. When there is no ball in the hole, the sensor output voltage is in a range of 0V to 0.5V.	1. Place the sensor inside the hole and check the output voltage with multimeter.	
2. When there is a ball in the hole, the sensor output is a voltage in the range of 4V to 5.5V.	2. With the sensor inside, place a ball in the hole and check the output voltage of sensor using a multimeter. If the voltage is out of range, adjust the placement of the sensor.	

2 Counting Circuit

Counter will be implemented on an ATmega328p microcontroller. One microcontroller per hole, this will increment a count each time the ball enters the respective hole.

Requirement	Verification
1. Counting circuit will increment the current count by one each time the sensor produces a high output.	 Verify high output by connecting LED to sensor and seeing if it lights up.
 Counting circuit will have the ability to count within a range of 0-63 (6-bits). 	2. Connect counter to 6 hex displays and check that it increments and resets at 63.
 Counting will circuit will halt counting when it receives the halt signal. 	3. Send a halt input to the microcontroller and test that circuit will not increment when sensor is high.
 Count will reset to zero when reset signal is received. 	 Increment count to a number greater than zero and send a high reset signal to the processor, the count will reset to zero.

3 Transceiver

Two microcontroller in putting mat will send 6 bit count to the scoreboard and receive two 1-bits signal to tell when to halt and reset the counter. We will be using the ATmega328p to accomplish this.

Requirement	Verification	
1. Microcontroller will communicate with another microcontroller to send and receive a max of an 8-bit string.	 Test connection between microcontroller by sending signal to light an led on the board of the other microcontroller. Next, test by sending 6-bit and testing that proper 8-bit BCD is output. 	

4 Actuator Control

This circuit will be design to have the solenoid extended to block the ball from initially returning. Once the sensor has seen the ball, it will cause the solenoid to retract and drop the ball allowing it to return. A fet (MTP3055EL) will be used as a switch, when sensor is high, detecting ball, solenoid will power up.

	Requirement Verification	
1.	When sensor is high, 4-5.5V, the solenoid circuit will allow the current to pass through the actuator. When high the source and drain resistance need to be less than one ohm.	1. Set gate side to 5V and measure resistance across the drain and source of the fet.
2.	The actuator will be driven within 10 seconds of the ball entering the cup.	2. Test the ball triggering the sensor and measure the time it takes for the ball to be dropped.

5 Actuator

The actuator will need to extend to cover the 4" hole to prevent the ball from passing. This will be powered on a 12V supply.

Requirement	Verification	
1. When current is passed through the actuator, the actuator arm will draw back and allow the ball to	1. Put 12V on the actuator with a pull down resistor, the actuator arm will draw back.	

pass.	
-------	--

2.3.3 Scoreboard

1 Timer Circuit

This circuit will count down from a time that is set by the user, the time can be set using a push button and another pushbutton to start the timer. A microcontroller will be used to set the initial time to four IC4026 ic's that will be used to do the actual counting. This count will be displayed on a seperate hex display.

Requirement	Verification	
 Starting timer will increment by 1 minute when increment pushbutton is pressed. Max starting time will be 9 minutes. 	 Press pushbutton to test that time will increase by 1 minute on 7 segment displays. 	
2. Timer will count down time accurately, within ±5%	2. Begin timer and track how long the timer takes compared to a digital timer.	
3. Circuit will output a halt signal when the timer is done counting.	3. When timer is complete, test that halt pin will output 5V signal.	

2 Seven Segment Display

This will consist of seven hex displays and will require seven hex drivers. Four of these will be used to display the score of the users, two per user. The other three will be used to display the time of the counter.


Requirement	Verification
 Circuit will receive an 8-bit string for each score, decoders will convert this string and display values on 7 segment displays. 	 Hook decoders up to switches and test that the corresponding values are displayed.


3 Transceiver

There will be two microcontrollers, each will communicate with a microcontroller in the putting mat. This microcontroller will receive a 6-bit string, score, and send a 2-bit string, halt and reset.

Requirement	Verification	
1. Microcontroller will receive a max of an 8-bit string from a microcontroller in the putting mat.	 Test connection between microcontroller by sending signal to light an led on the board of the other microcontroller. Next, test by sending 6-bit and testing that proper 8-bit BCD is output. 	

2.3.4 Supporting Documents

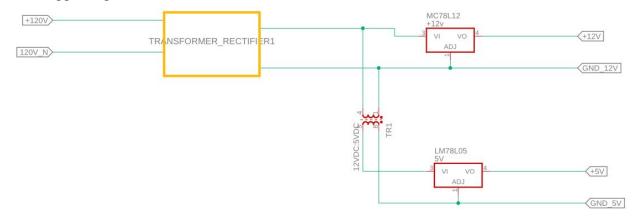

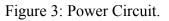

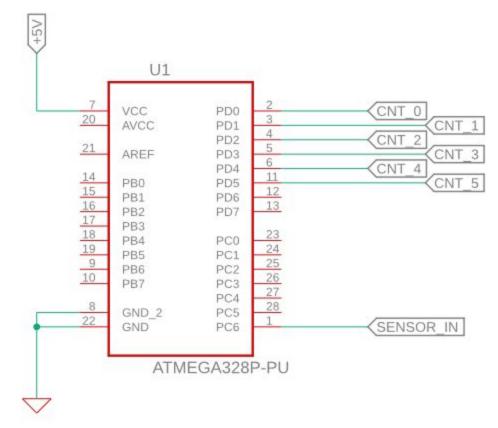


Figure 4: Counter Circuit, one for each hole.

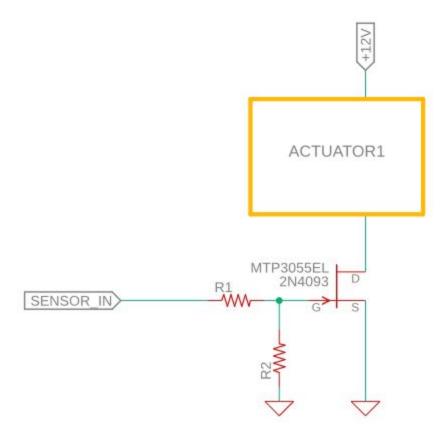


Figure 5: Actuator Circuit.

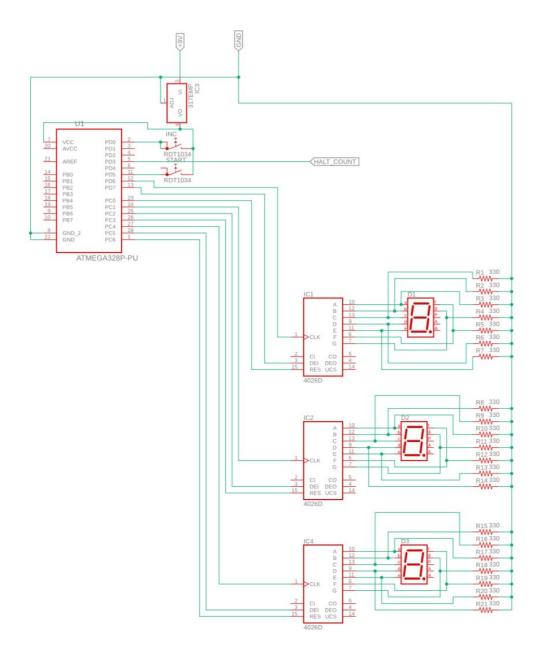


Figure 6: Timer circuit

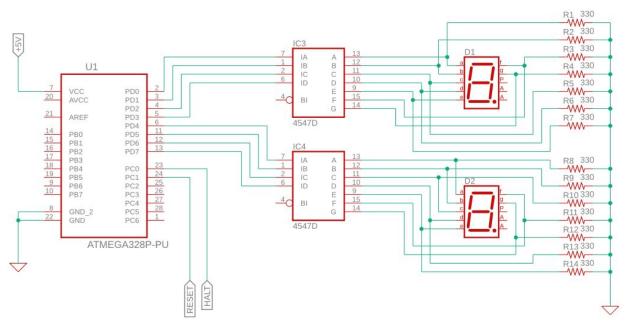


Figure 7: Scoreboard

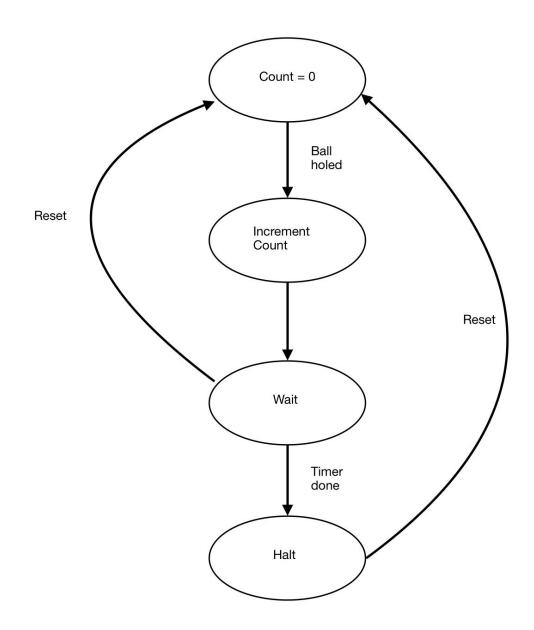


Figure 8: Counter State Diagram

2.4 Tolerance Analysis

The most important component to our project is the optical sensor that reads when a ball has entered the hole. This sensor drives the counting circuit and the actuator control circuits, which control the main functions of our design. If the sensor cannot read when the ball has entered the hole, it will not send the high signal needed to start the counter and activate the actuator control. We are most concerned with the effect that distance from the sensor has with its ability to read the golf ball and output a high signal. We cannot control how the golf ball lands inside the hole and how close to the sensor that it is.

3 Cost and Schedule

3.1 Cost Analysis

In order to determine our fixed labor costs, we assumed that we would be making the average EE salary found on the ECE website[1]. We also assumed that the average salary based worker works 40 hours a week for 50 weeks out of the year. We also figured we would be working for 16 weeks and around 10 hours a week. For the two of us this comes out to be:

 $\frac{\$71,000}{year} * \frac{1 \ year}{50 \ weeks} * \frac{1 \ week}{40 \ hours} * \frac{10 \ hours}{week} * 16 \ weeks * 2 * 2.5 = \$28,400$

We also have to factor in manufacturing costs from the machine shop. We were given a quote of \$55/hr for labor. They predicted a total job time of 8 hours. This comes out to \$440 in manufacturing costs.

Item	Unit Price	Quantity	Total Price
Artificial surface	\$2.59 / sqft	19	\$49.21
10' PVC	\$18.29	1	\$18.29
90 degree PVC	\$8.99	2	\$17.98
45 degree PVC	\$8.30	2	\$16.60
.5 x 4 x 8 Plywood	\$15.95	2	\$31.90
2 x 4, 8ft	\$5.00	2	\$10.00
ATmega328p	\$1.22	5	\$6.10
IRA-S210 Sensor	\$3.12	1	\$3.12
Actuator	\$14.95	1	\$14.95
РСВ	\$5.00	5	\$25.00
7-segment Display	\$.94	7	\$6.58

Below is a list of the costs for the parts needed to build our design:

Assorted resistors, capacitors, ICs, push buttons	\$10.00	N/A	\$10.00
DC-DC Converter (12V - 5V)	\$7.00	1	\$7.00
AC-DC Converter (120V - 12V, 5A max)	\$24.95	1	\$24.95
Total Sum:			\$241.68

Our total manufacturing and labor costs come out to be \$29,081.70. In the future, some of these costs could be lowered if there was ever a decision to mass produce.

3.2 Schedule

Week	Ben	Chris
2/18/19	Design document	Design document
2/25/19	Start programming microcontrollers	Start PCB design for counter circuit
3/4/19	Continue programming, start PCB design for timer circuit	Continue PCB design for counter, start PCB design for hex display circuit
3/11/19	Finish programming and timer PCB	Finish counter and hex PCB design
Spring Break	Progress assignment	Progress assignment
3/25/19	Connect microcontrollers to each circuit and begin testing data transmission	Start actuator and sensor design
4/1/19	Finish microcontroller connections	Finish actuator and sensor design
4/8/19	Begin connecting parts to exterior design	Begin connecting parts to exterior design
4/15/19	Finish exterior and begin	Finish exterior and begin

	testing	testing
4/22/19	Prepare for presentation	Prepare for presentation
4/29/19	Final report	Final Report

4 Ethics and Safety

In accordance with the IEEE Code of Ethics, #1, we are responsible for making sure our project is safe for the public to use and that we disclose any potential factors that might endanger the public [2]. The main concern for safety in our project is the ball return mechanism. We do not want to design this in such a way that the user can be harmed by the ball while it is being returned. Our design addresses this concern by returning the ball under the putting surface and at a slow speed.

The main safety concern is our 120V AC/DC converter. At the moment, we are unsure how much power this will need to pull which means there could be dangers in overheating of parts in this converter. Heat syncs can be used as well as housing the converter outside of the mat. There is also a potential hazard in using this much voltage.

5 Citations

- [1]E. I. T. S. Services, "Rankings and Statistics," *Fields of Specialization :: ECE ILLINOIS*.
 [Online]. Available: https://ece.illinois.edu/about/rankings-and-statistics.asp. [Accessed: 22-Feb-2019].
- [2] IEEE.org, "IEEE IEEE Code of Ethics", 2019. [Online]. Available: http://www.ieee.org/about/corporate/governance/p7-8.html. [Accessed: 7- Feb- 2019].