MICROMOUSR

ECE 445 - Team 77 Andrew Betbadal, Nicholas Radler, Katelyn Schoedl TA: Amr Martini



Introduction

- An innovative startup device.
- A robot cat toy to entertain pets and owners alike.
- Voted Best Cat Toy 2018.




Mousr in Action




Objectives for MicroMousr

- 1. Sensor components must exist on one board and be capable of fitting in the physical body of the Mousr product (3.4 x 2.2 x 1.4 inches).
- 2. Must be able to demonstrate basic movements and control while in Autonomous Mode, and respond to user control when in Manual mode.
- 3. Electronic components must cost less than the current Mousr model.

MicroMousr System

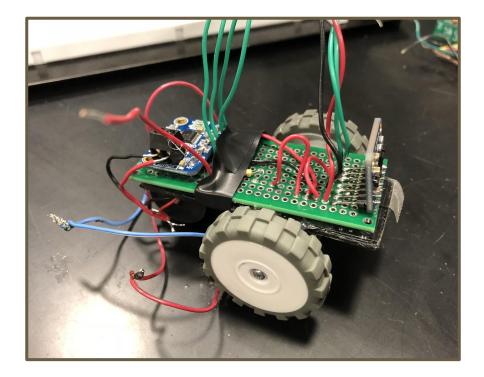

High Level Design

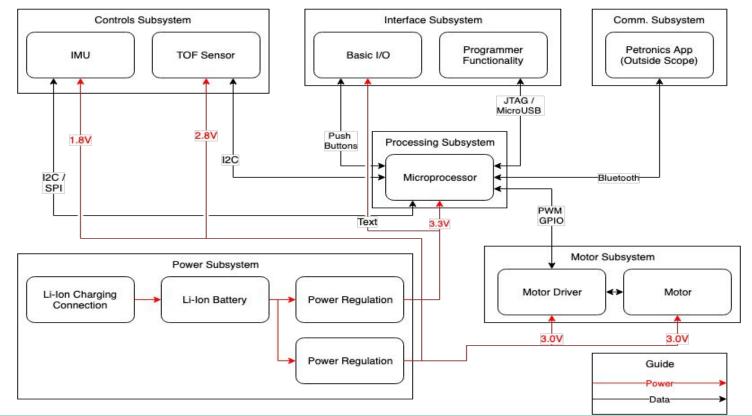


Power

- Power is stored in a 4.2 V battery
- Charging circuit includes reverse voltage protection
- Distributed through two LDO voltage regulators
 - Main components and sensors
- Provides for separate ON and OFF modes




Power Distribution Network

Regulator to Processor

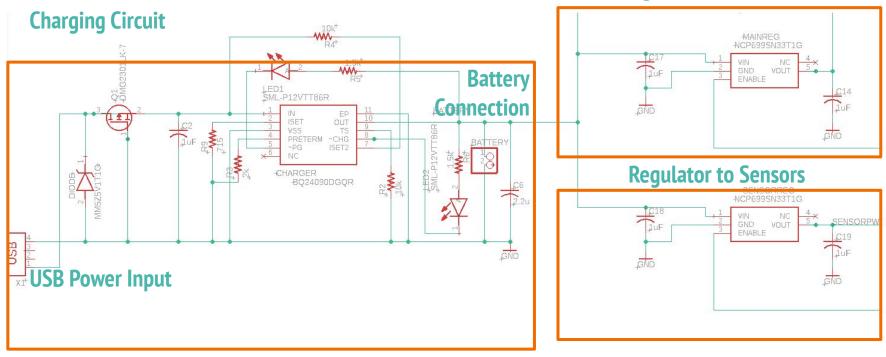



Enable

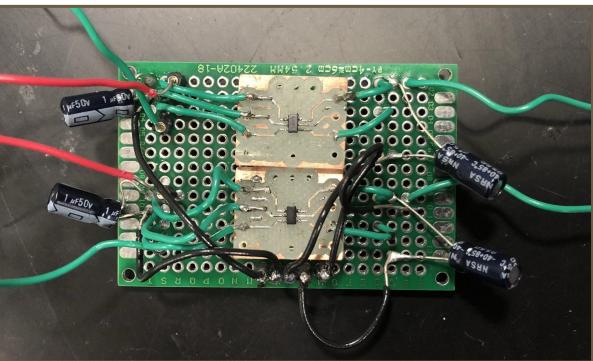

Output to Sensors


Output to Main

Enable

Power from

Battery

LDO Response Time

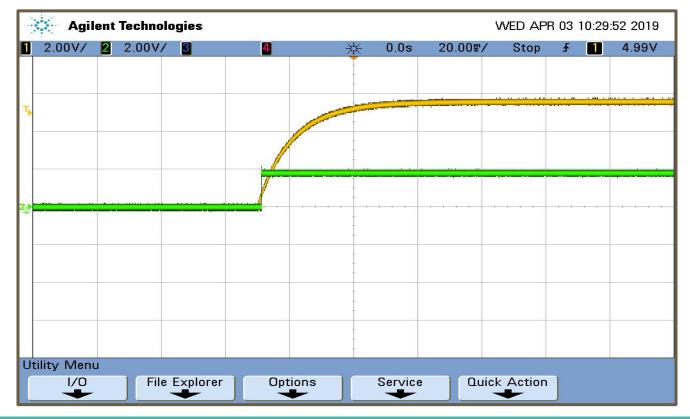


Power Consumption

Load	Voltage (Typical)	Voltage Range	Current (Active)	Current (OFF / SLEEP)	Power Consumption (Active)	Power Consumption (OFF / SLEEP)	
Processor	3.0	1.7-3.9	5.4mA	.7μΑ	16.2mW	.0021mW	
ToF	+2.8V	2.6V-3.5V	19mA	0A	20mW	0W	
IMU	1.8V	1.71V-3.6 V	.45mA	0A	0.81mW	0W	
Motor Driver		[Reference	Calculation 2]	769.2mW	0W		
LED	2V	2V-5V	20mA	0A	75mW	0W	
Push Button	3V	1V-24V	15μΑ	15µA	.045mW	.045mW	
Voltage Regulator (x2)	4.2V	2.1V-6V	40μΑ	0A	.168mW	0W	
Total Power Co	nsumption	821.186mW	0.05799 mW				


Microprocessor

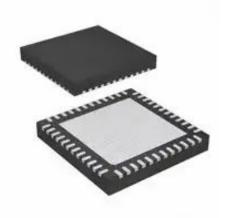- Cortex-M4 ARM Processor
- Bluetooth Low Energy compatibility






Microprocessor Schematic

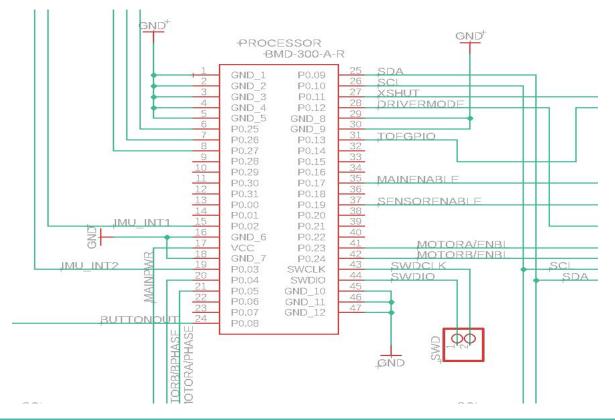


13

Time of Flight

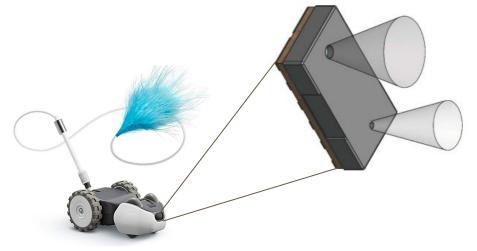
- Optical sensor that uses infrared filters to measure distance
- Used for obstacle avoidance
- Smallest ToF sensor on the market
- Extremely accurate within a 0.7 meter range



Time of Flight

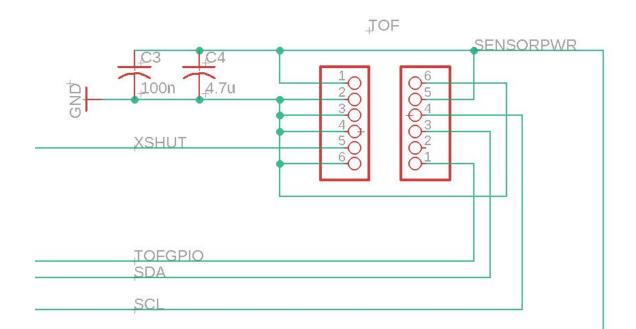




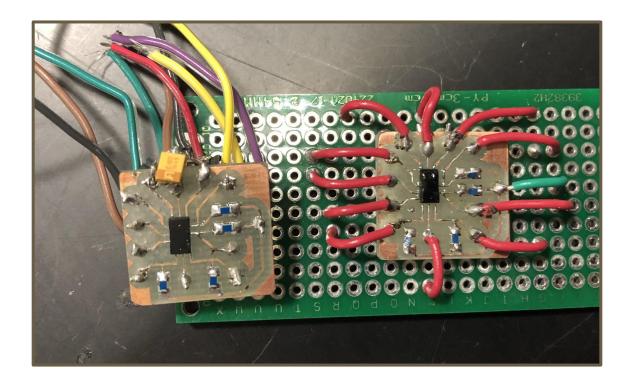




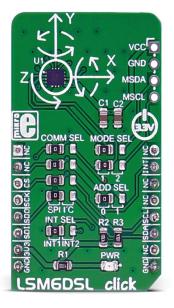- Inertial Measurement Unit
- 3-Axis Accelerometer
 - Pitch, roll and yaw are rotation around X, Y and Z axis
- 3-Axis Gyroscope
 - Delivers rotation values for each axis



Push Button

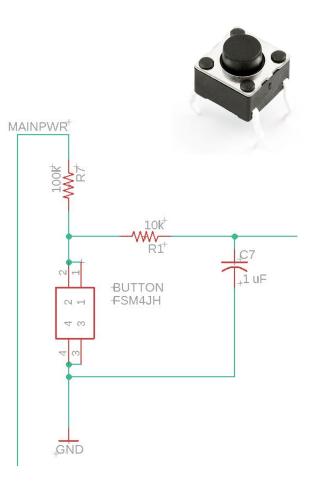- Switch between OFF and ON modes
- Debounce circuit




Push Button Debounce




RGB LED

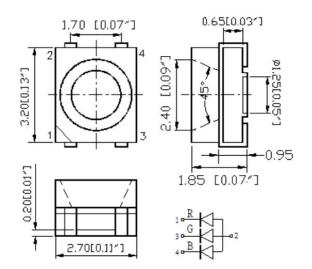- Signal direction of movement
- PWM Driven




Push Button and RGB

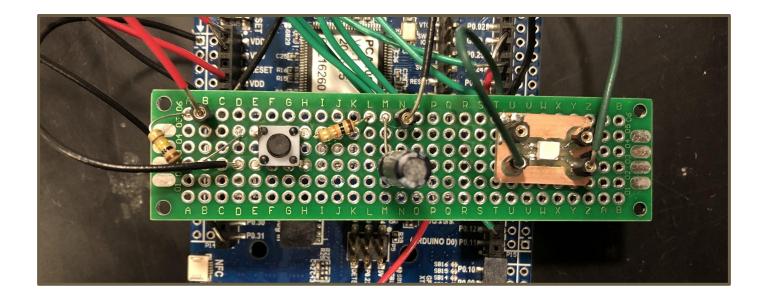



Motor Driver

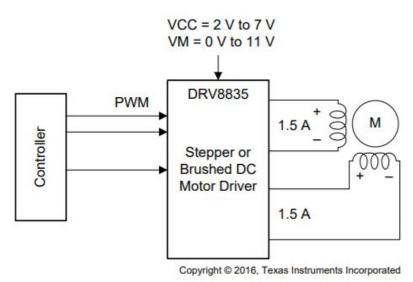- Dual H-Bridge Chip for two DC motors
- PWM signal from GPIO controls motor direction and speed
- Phase/Enable allows for bidirectional control



Hardware Design

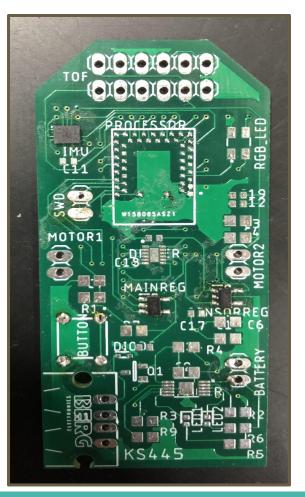


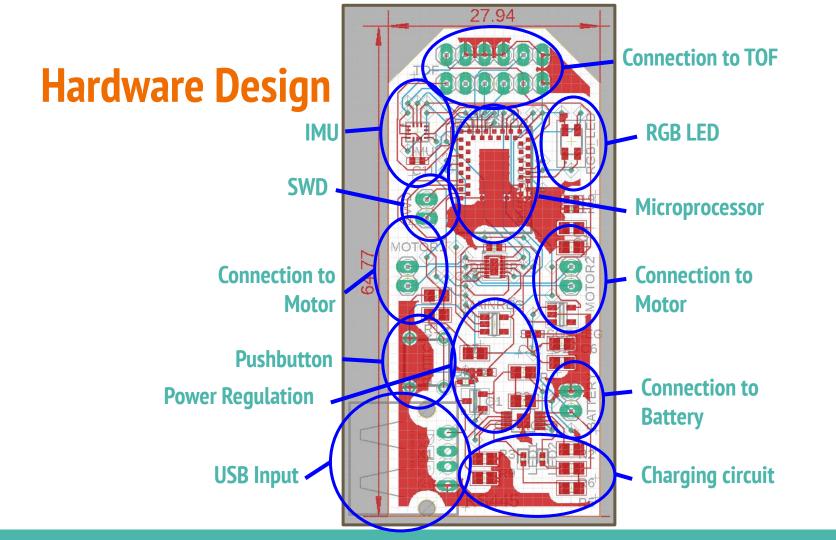


Communication

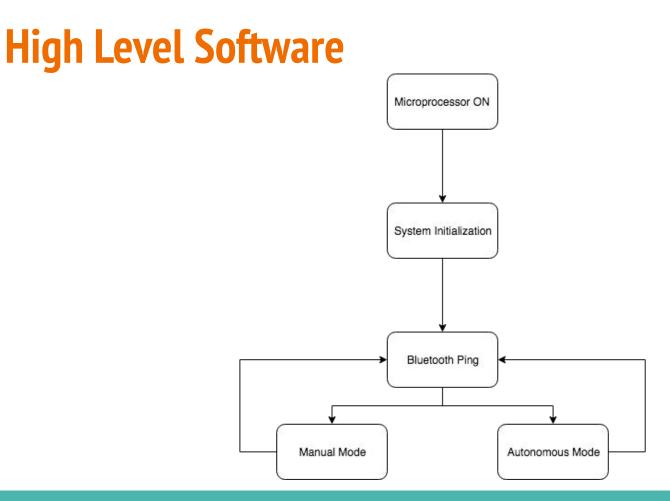• Bluetooth connection through Petronics app







System Initialization Procedure

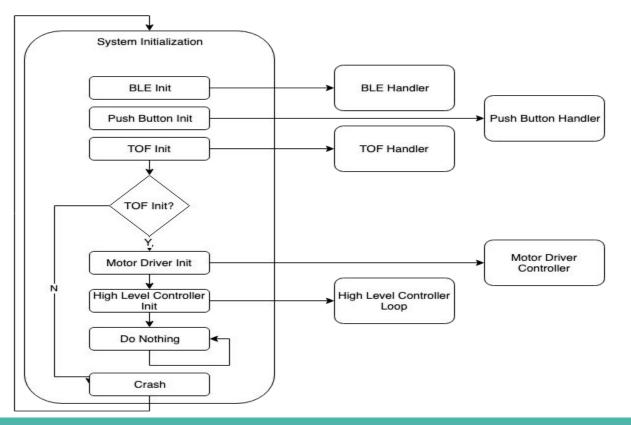

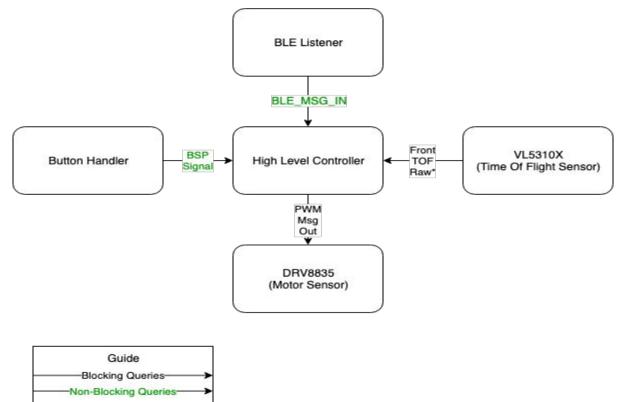
High Level Multithreaded System Description




ORB Message Passing Protocol

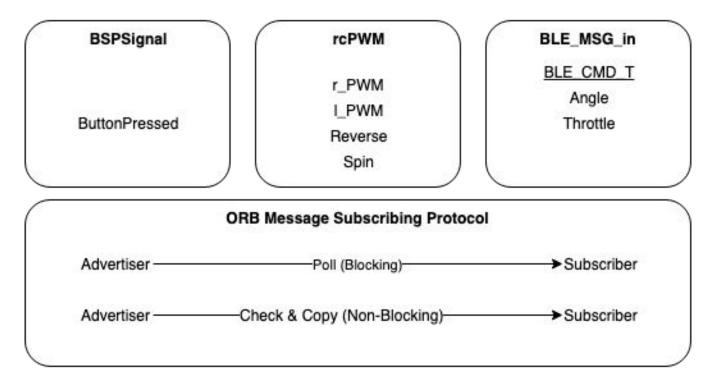

High Level Controller Design

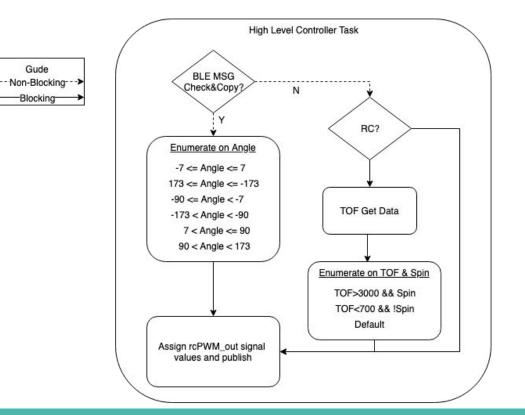

PWM Driver Design

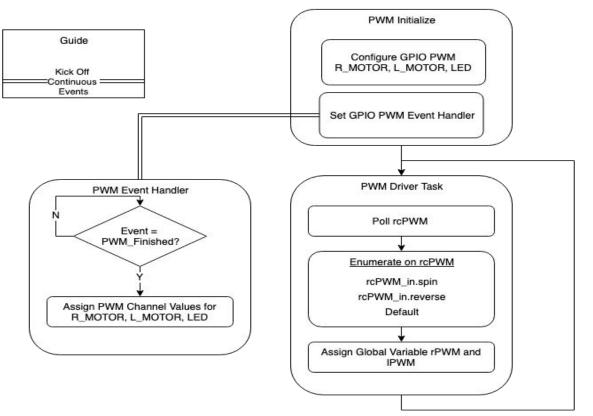

Dual Motor PWM control

Ag	ilent Techn	ologies					WED API	R 10 21:56	:21 2019
1.00V/	2 1.00	// 3	4	÷	🗧 0.0s	2.0005	/ Stop	£ 2	1.29V
1									
2									
RMS(2): 1.823V									
+1.58 DC	3750V 10.0:1	+2.80 DC	000V 10.0:1		.0V 1.00:1		0.0V 1.00:1		/ISa/s r 21:55

Cost Summary

- \$29 at non-bulk pricing
- \$17 at bulk pricing

Device	Quantity	Product	Cost	Footprint	Product Link
Microprocessor	1	NRF52832-QFAA-R	\$5.73	QFN48 (6 X 6)	https://www.digikey.com/
0.8pF Capacitor	1	500R07S0R8CV4T-ND	\$0.02	0402	https://www.digikey.com/
12pF Capacitor	2	CC0402JRNPO9BN120	\$0.01	0402	https://www.digikey.com/
100nF Capacitor	3	TMK105B7104KV-FR	\$0.12	0402	https://www.digikey.com/
100pF Capacitor	1	C0402X6S0G101K020E	\$0.30	0402	https://www.digikey.com/
4.7uF Capacitor	1	06034D475KAT2A	\$0.60	0603	https://www.digikey.com/
1.0uF Capacitor	1	GRM188R70J105KA01E	\$0.33	0603	https://www.digikey.com/
3.9nH Inductor	1	ATFC-0402-3N8B-T	\$0.12	0402	https://www.digikey.com
10uH Inductor	1	LQM18FN100M00D	\$0.15	0603	https://www.digikey.com/
15nH Inductor	1	ATFC-0402-15NG-T	\$0.12	0402	https://www.digikey.com
IMU	1	LSM6DSLTR	\$4.09	LGA-14(2.5x3x0.88)	https://www.digikey.com/pr
100nF Capacitor	2	TMK105B7104KV-FR	\$0.12	0402	https://www.digikey.com/pr
10k Ohm Resistor	2	RNCP0603FTD10K0	\$0.01	0603	https://www.digikey.com
ToF	1	VL53L0CXV0DH/1	\$4.10	VL53L0X (4.4mmx2.4mm)	https://www.mouser.com/P
100nF Capacitor	1	TMK105B7104KV-FR	\$0.12	0402	https://www.digikey.com/pi
4.7uF Capacitor	1	08034D475KAT2A	\$0.60	0603	https://www.digikev.com/p
Motor Driver	1	595-DRV8835DSSR	\$1.67	DRV8835 (2mmx3mm)	https://www.digikey.com/pr
1.0uF Capacitor	1	VJ0805Y105KXXTW1B(\$0.03	0805	https://www.digikey.com
Voltage Regulator	2	NCP699SN18T1G	\$0.47	NCP699	https://www.digikey.com
1.0uF Capacitor	4	CL05A105MQ5NNNC	\$0.00	0402	https://www.digikey.com
Battery Charger	1	BQ24090DGQR	\$1.30	BQ24090	https://www.digikey.con
1.0uF Capacitor	2	VJ0805Y105KXXTW1B(\$0.03	0805	https://www.digikey.con
1.5k Ohm Resistor	2	RR0510P-152-D	\$0.10	0402	https://www.digikey.com/p
1k Ohm Resistor	1	RR0510P-102-D	\$0.10	0402	https://www.digikey.com
2k Ohm Resistor	1	RT0402BRD072KL	\$0.40	0402	https://www.digikey.com
Attached LEDs	2				
Button Switch	1	1825910-6	S0.11	(6mmx6mm)	https://www.digikey.com
.1uF Capacitor	1	08053C104M4T4A	\$0.25	0805	https://www.digikey.com
100k Ohm Resistor	1	ERA-2AED104X	\$0.22	0402	https://www.digikey.com
10k Ohm Resistor	1	RNCP0603FTD10K0	\$0.01	0603	https://www.digikey.com
Inverter	1	SN74AHC1G04DBVR	\$0.43	SOT23-5 (2.9mmx1.6mn	https://www.digikey.com
LED	1	QBLP677-RGB	\$0.89	3.2mm x 2.7mm	https://www.digikey.com
Battery 3.7V Nominal	1	ASR00003	\$3.95	NA	https://www.digikey.com
Micro USB Connector	1	UX60-MB-5S8(01)	\$0.50	UX60-MB-5S8	https://www.digikey.com
		Total Cost	\$29.09		

Conclusions and Further Work

- Autonomous control based on ToF input
- Manual control with app input from Bluetooth
- Hardware connections intact
- Issues:
 - Processor module clock speed
 - Required libraries
 - IMU integration
 - Charging circuit
 - Motor wires

THANK YOU to Petronics and ECE Course Staff