


# ThereminFreaks – Theremin Rhythm Game

## Group 34

Esteban Looser-Rojas

Daniel Olivas Hernandez

Michael Recklein

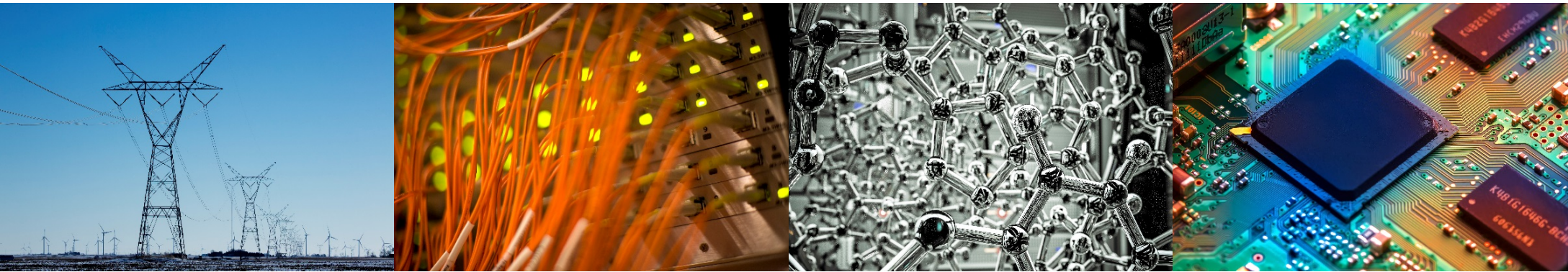

**I ILLINOIS**

Electrical & Computer Engineering

COLLEGE OF ENGINEERING


# Introduction

- Desire to make a video game with unique hardware
- No rhythm games out there for simulating theremin
- Very unique instrument to make a rhythm game for:  
no contact + wave hands around

# Objectives

- Create realistic and intuitive theremin simulator
- Responsive and enjoyable game
- Sound engine sounds like theremin and controls like one

# Block Diagram

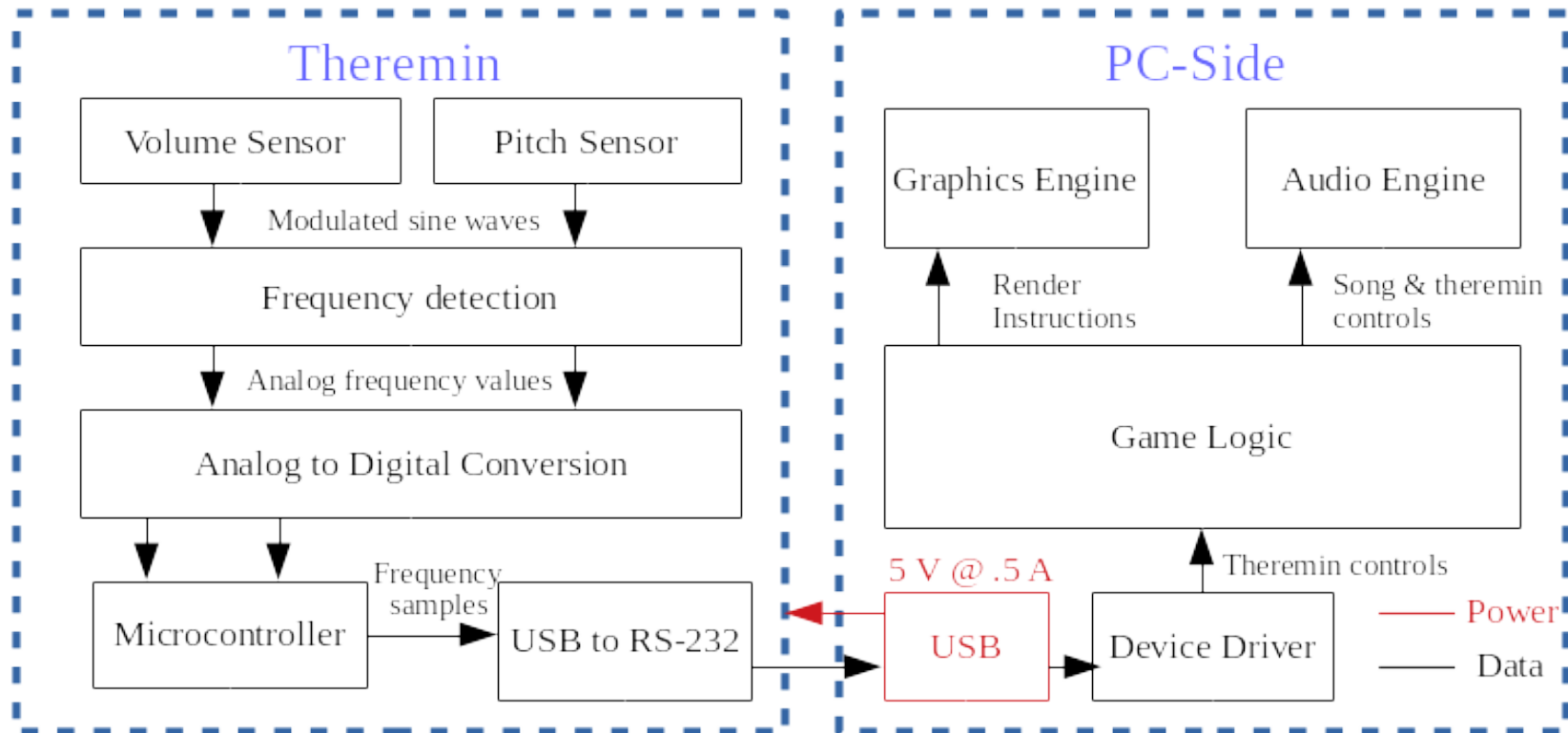





# Pitch and Volume Sensors

- Volume antenna: 6" wide; 10" long; 3/8" dia  
Pitch antenna: 2' long; 3/8" dia
- Design taken from DIY theremin guide
- Problem: unstable oscillators
- Theory: antennae load too large
- Solution: shorter antennae; better oscillator design



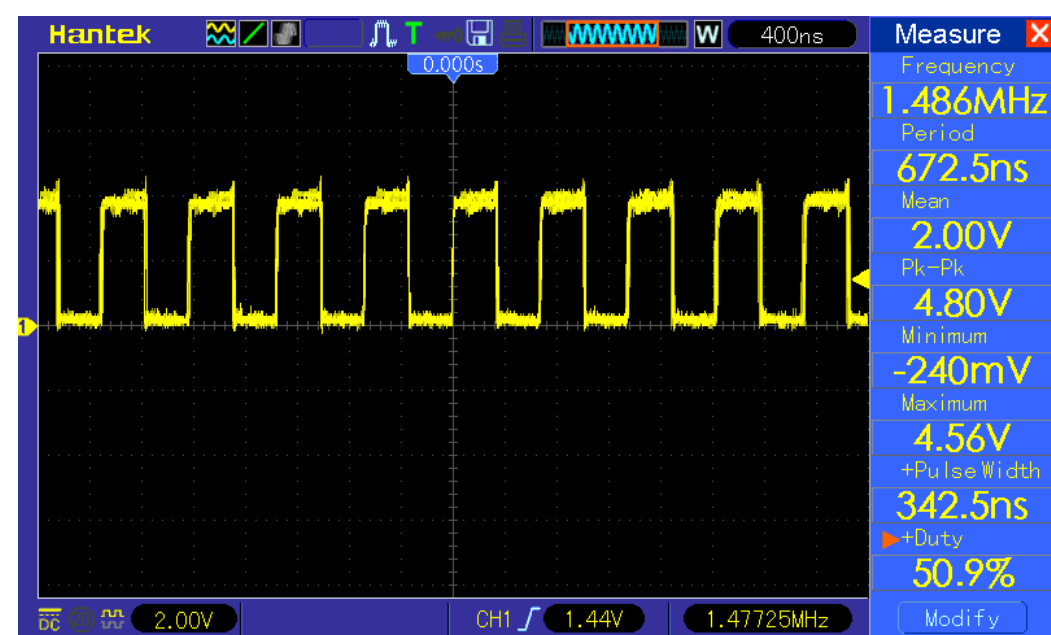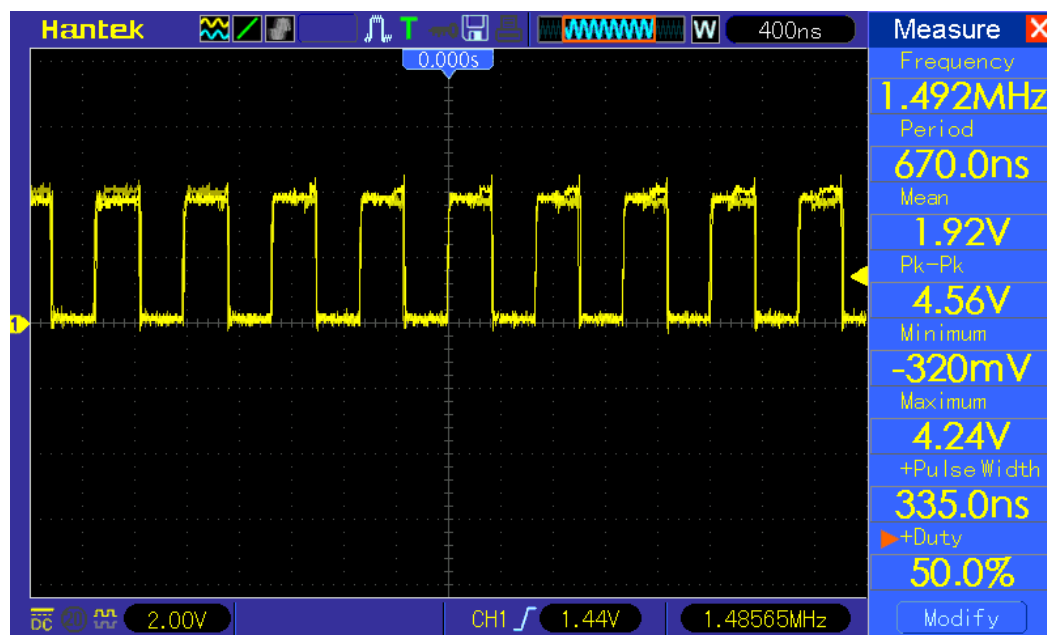
# Oscillators


- First used Hartley oscillators w/SMD transformer – very weak signal
- Change: Hartley → Colpitts (thru-hole inductors)
- Requirement: Antennae change osc. freq by 5-10 kHz from base freq
- Measured antenna freq from no hand near (left) to hand near (right): ~6 kHz difference



## Old design: Hartley Oscillator


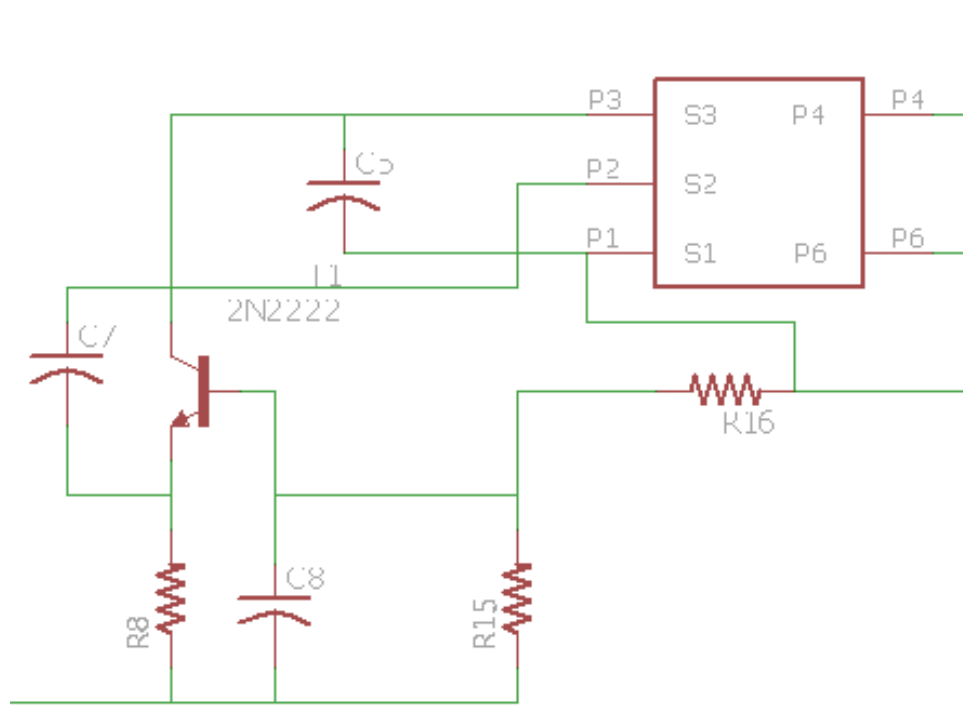


## New design: Colpitts Oscillator

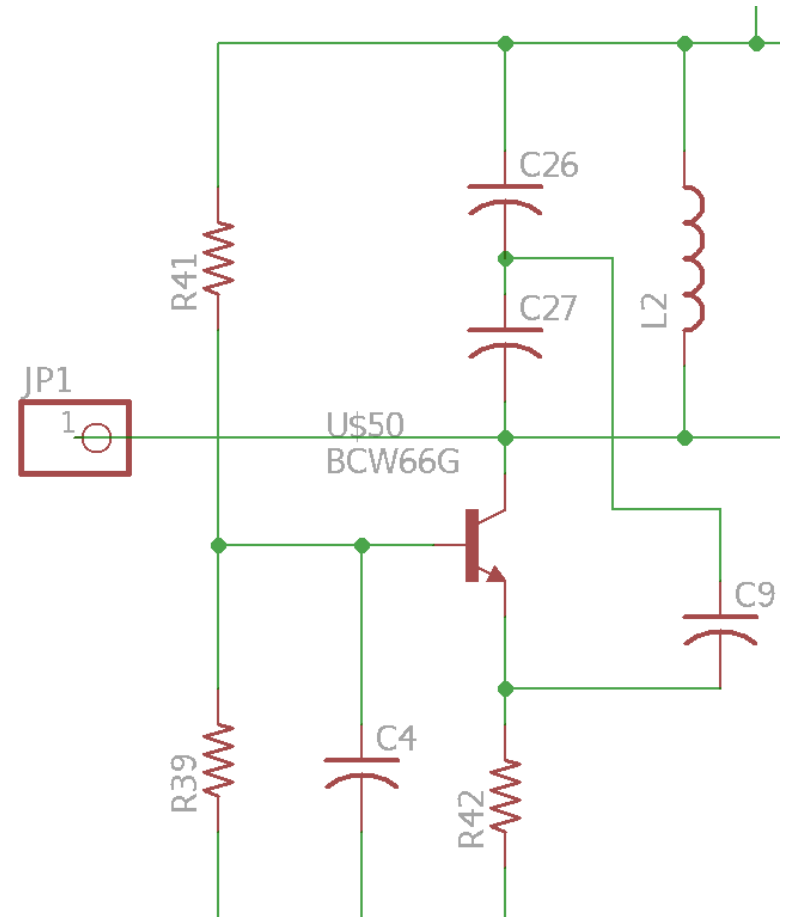

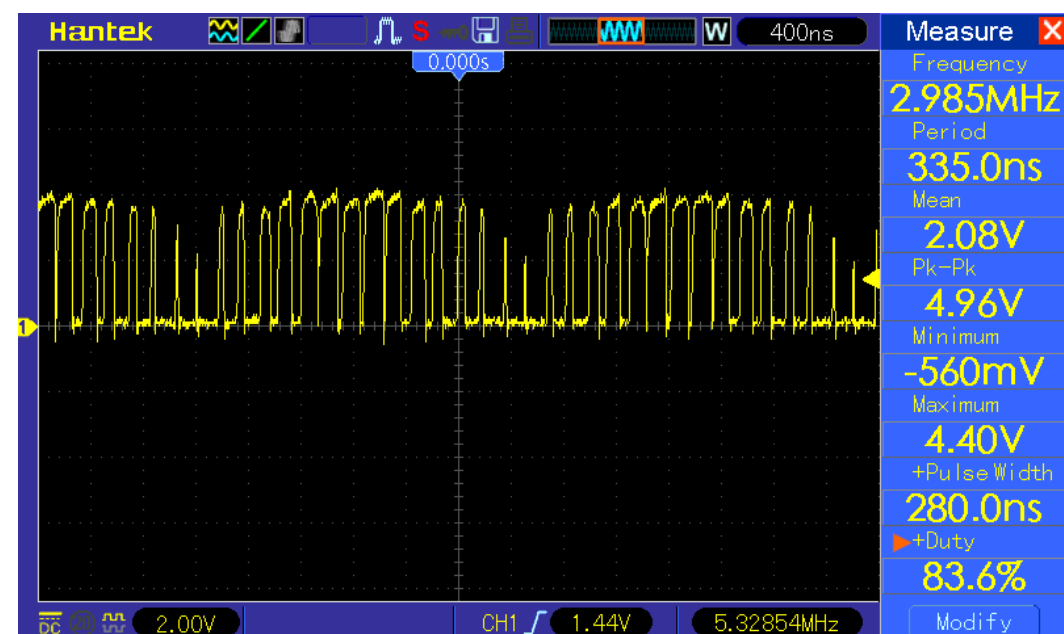
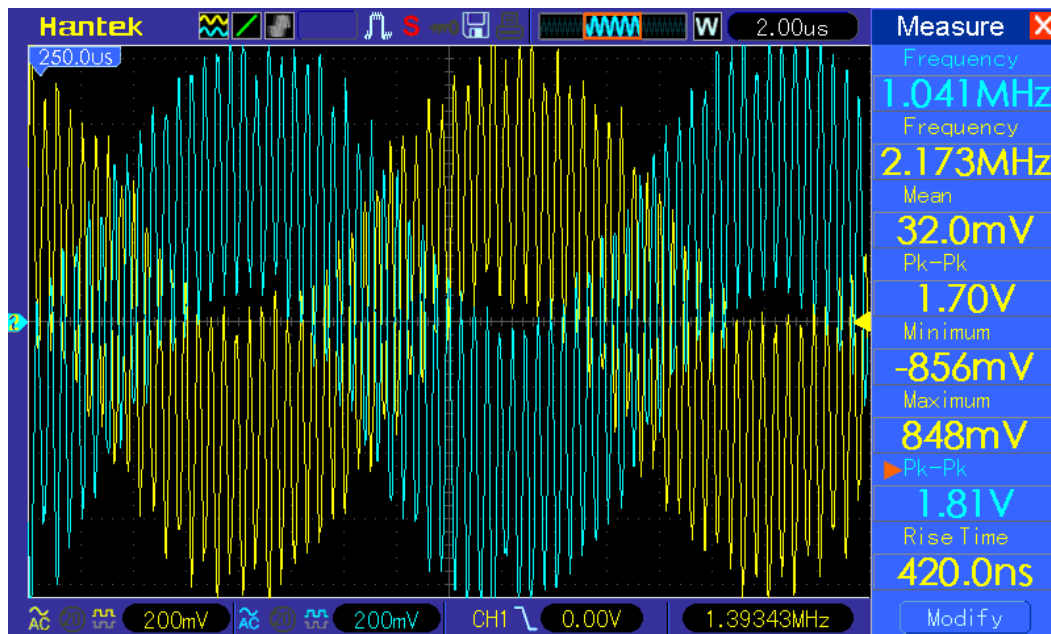
# Mixers

- Initially used Gilbert cells (on left) – sensitive; low output (1.7V pk-pk)
- Change: oscillator sine wave → square wave
- Requirement: modulated waves from 1-4 MHz input at logical high (2-5V)
- Use XOR gate to mix signals (on right) – get clean 5V output





## Square Wave & Digital XOR Mixer


### Gilbert Cell

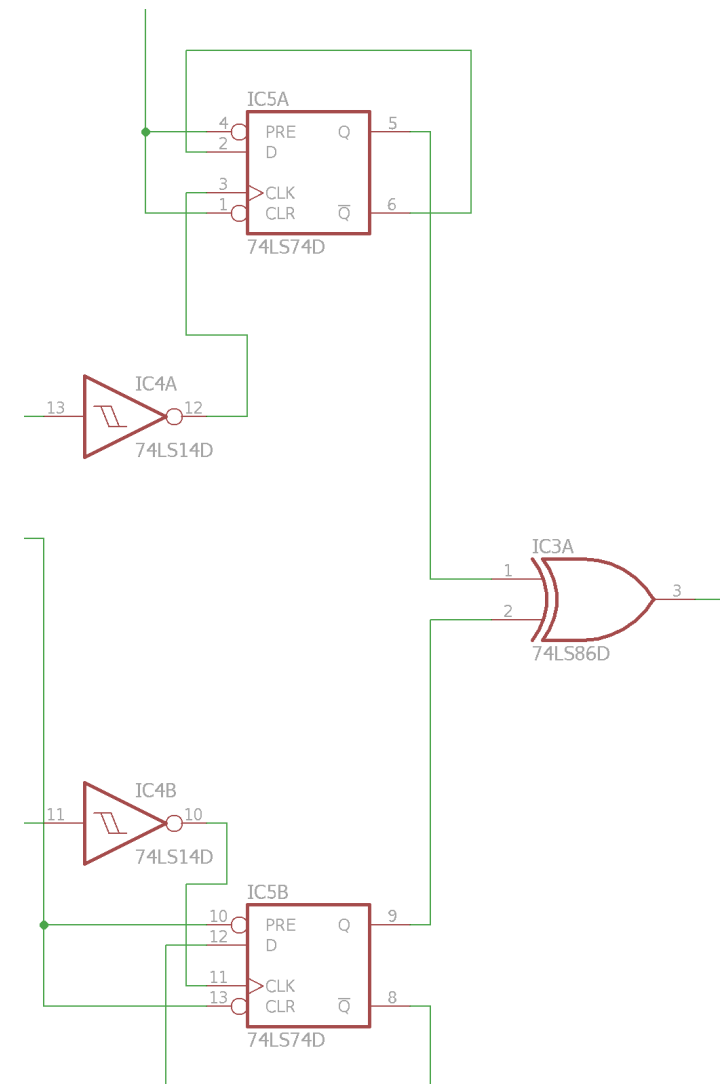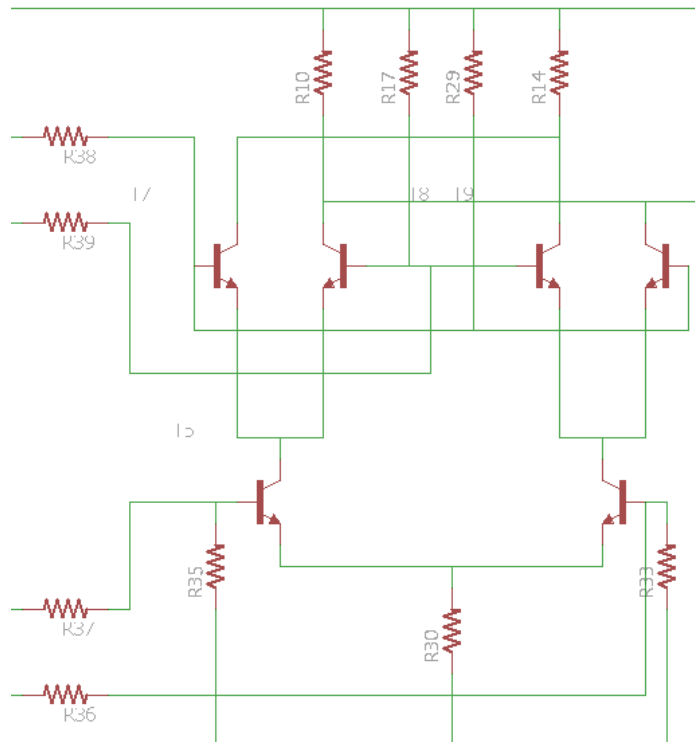

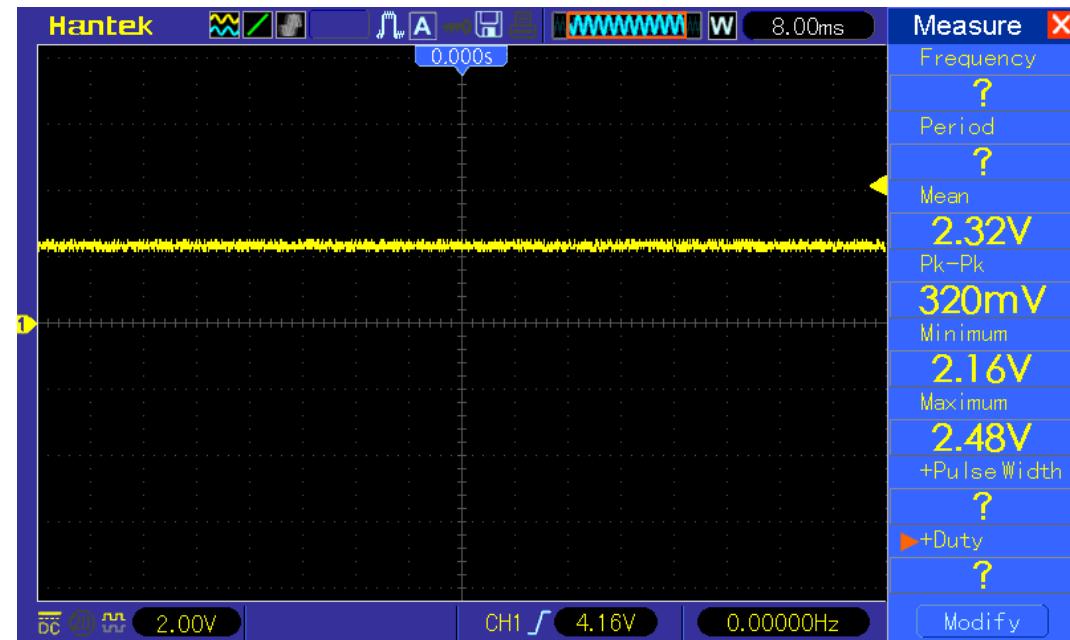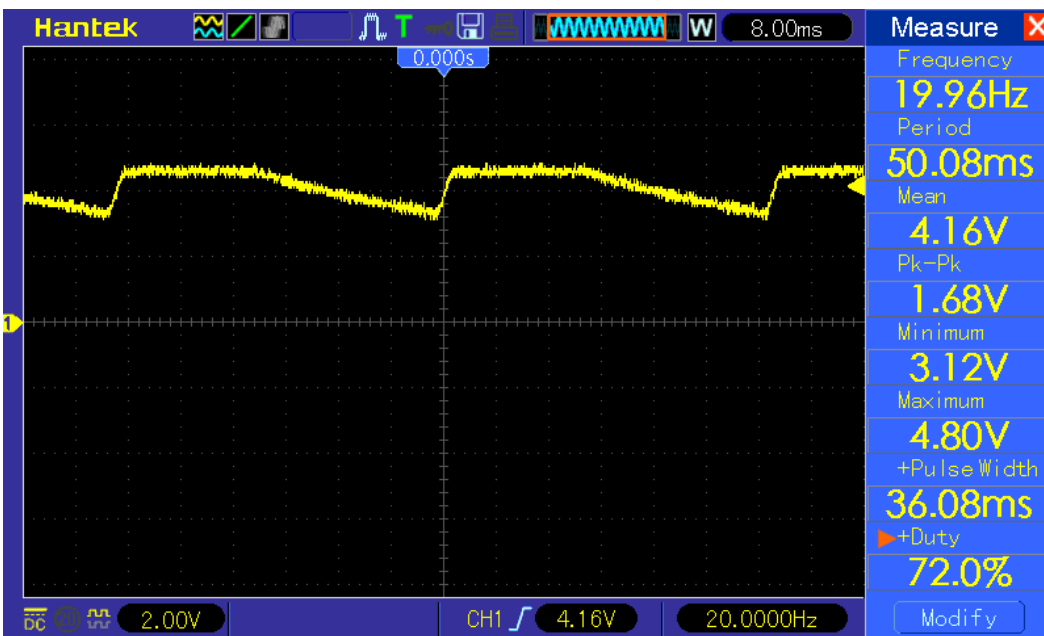
# Detector and Integrator

- Use BJTs for integrator circuit
- Simple diode and RC lowpass filter for detector
- Requirement: 30 kHz bandwidth
- Ran func. generator through 20 Hz - 30 kHz range




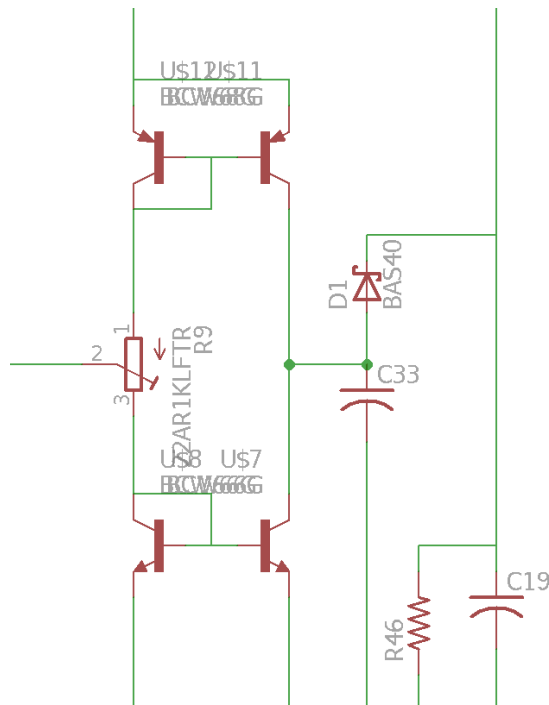

Integrator and Detector

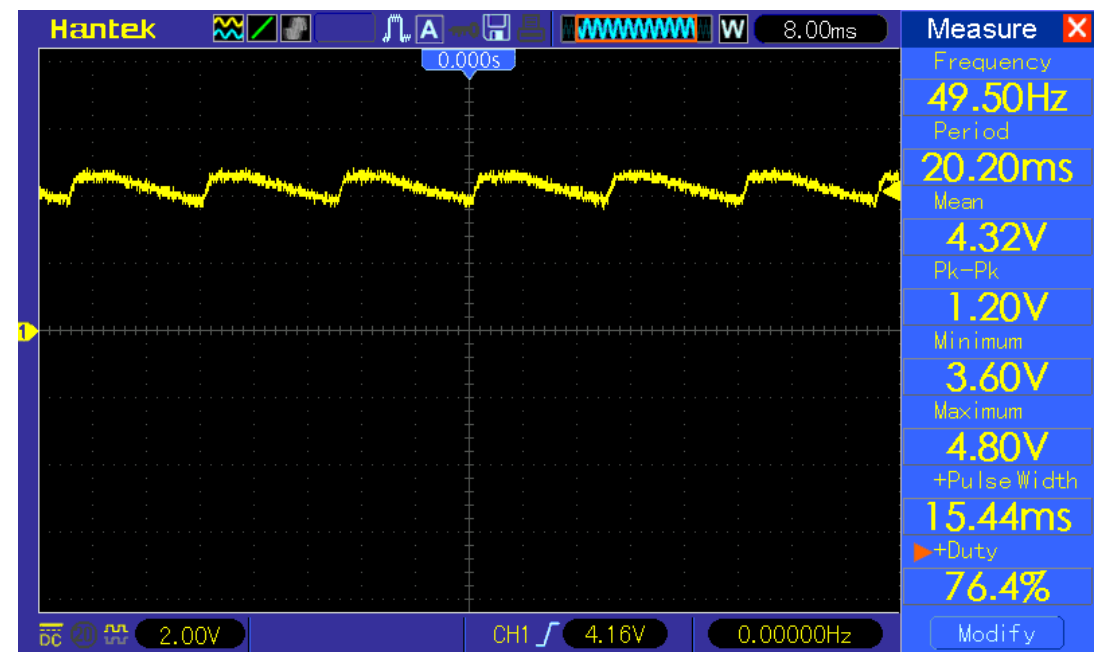


Above: 50 Hz input  
Below: 2 kHz input

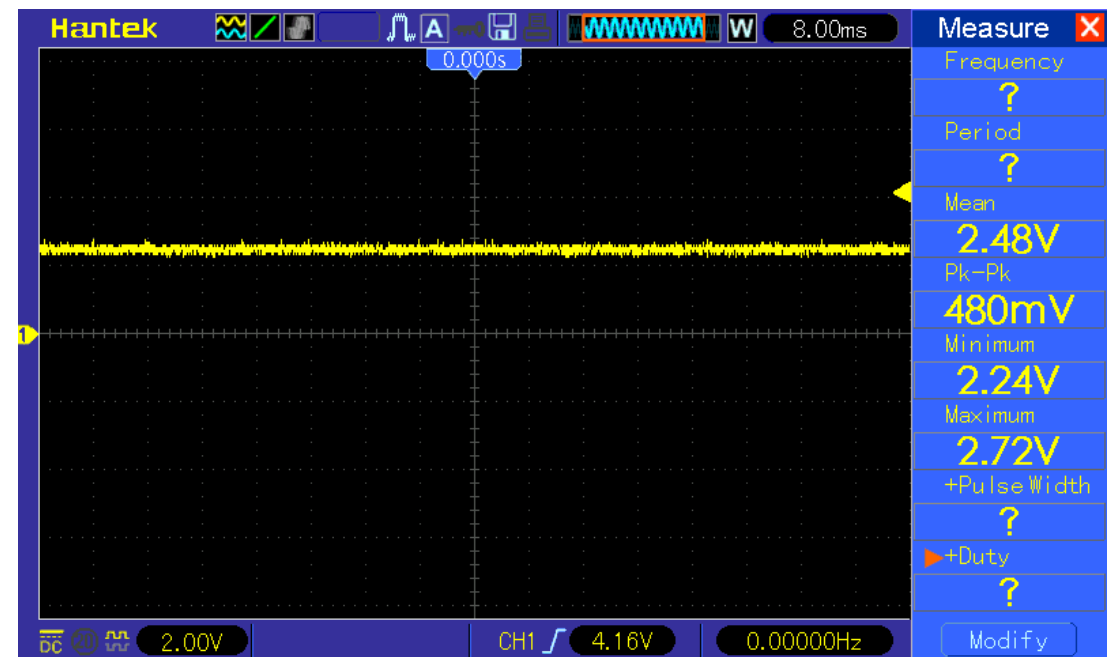



## Analog Circuit

Oscillators

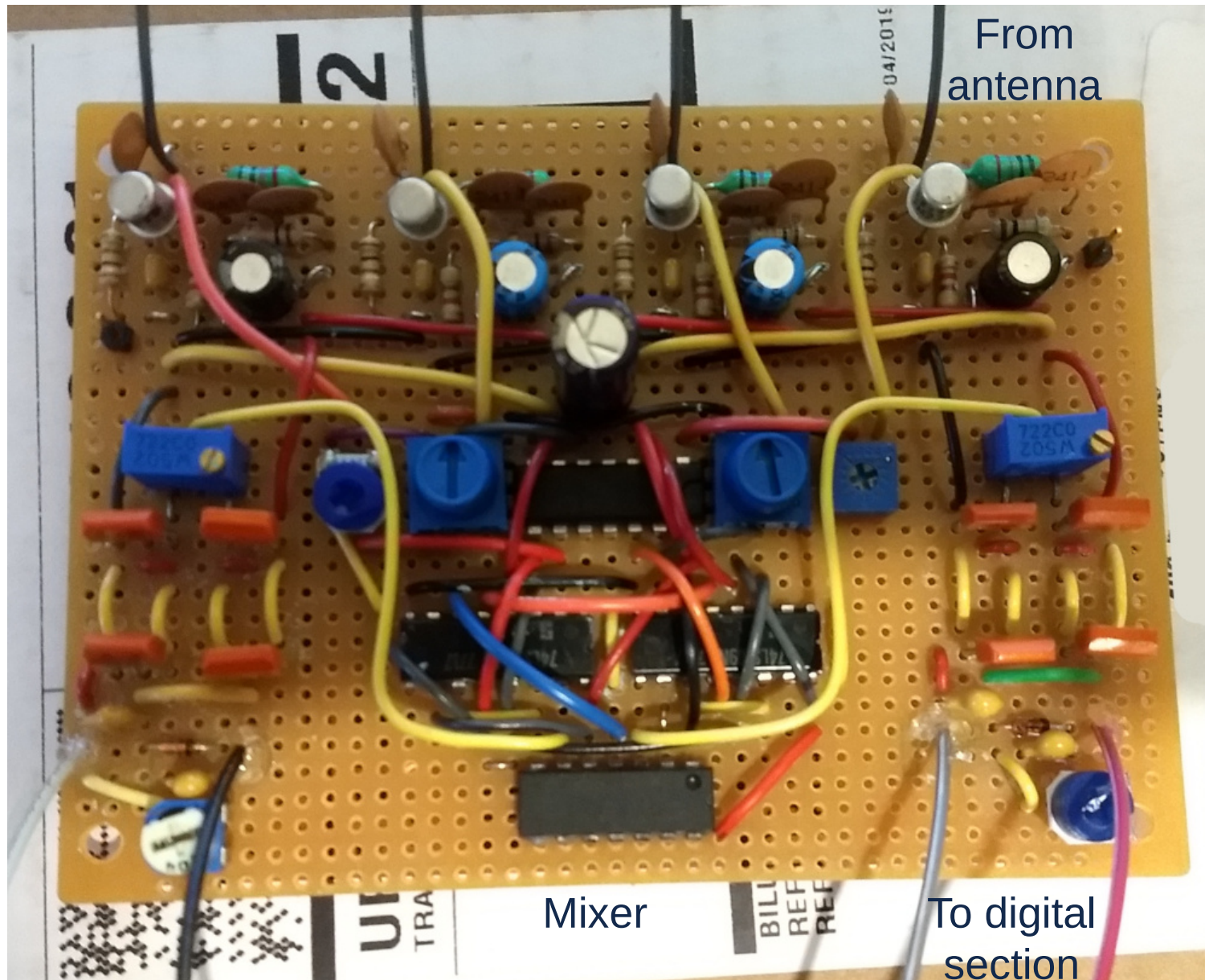

From  
antenna

Integrator

Detector


Mixer

To digital  
section


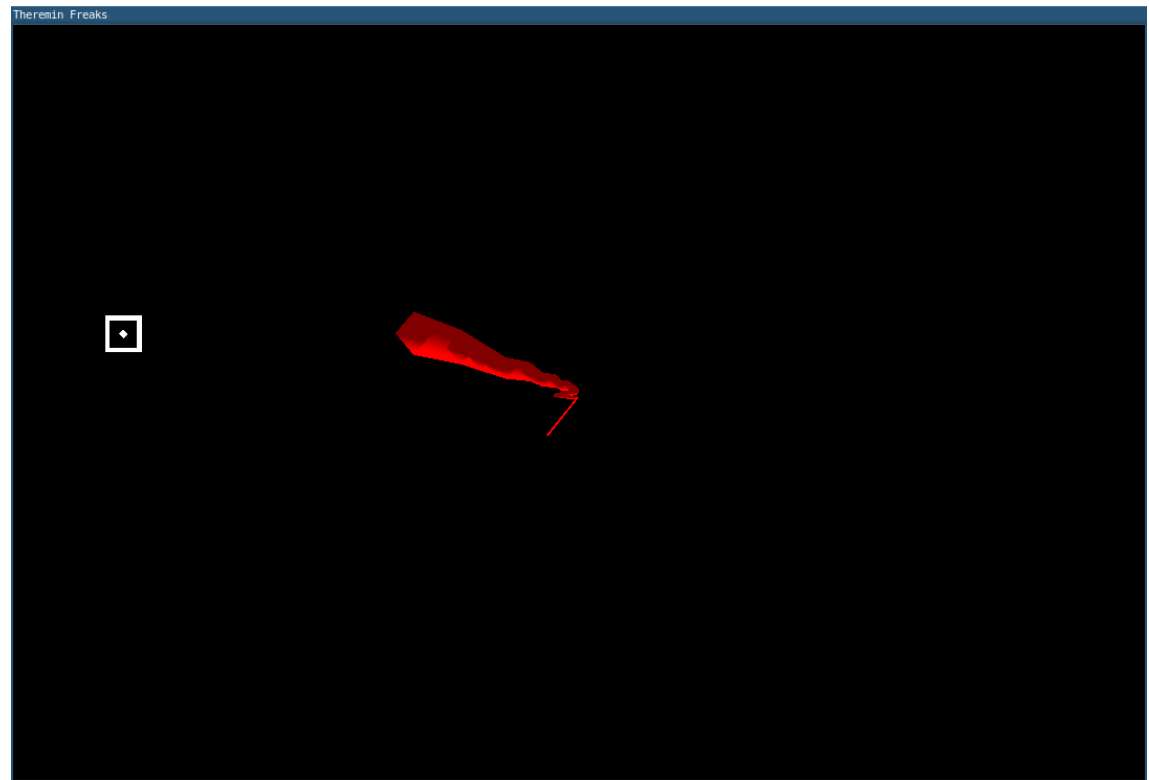
# Game Design: Rendering Engine

- Create mesh to signal required pitch and volume
- Generated from text file + primitive meshes
- Requirement: want ~60 fps consistently – achieved (checked FPS counter)




# Game Design: Game Logic

- Decoupled frame rate from game speed
- Scoring function based off cubic distance from “safe zone”
- Forgives shaky hands and sampling noise


```
f = Min[ 1/(Sqrt[x ^ 2 + y ^ 2] + .5) ^ 3, 1]
```

```
Plot3D[f, {x, -1, 1}, {y, -1, 1}, PlotRange -> All]
```
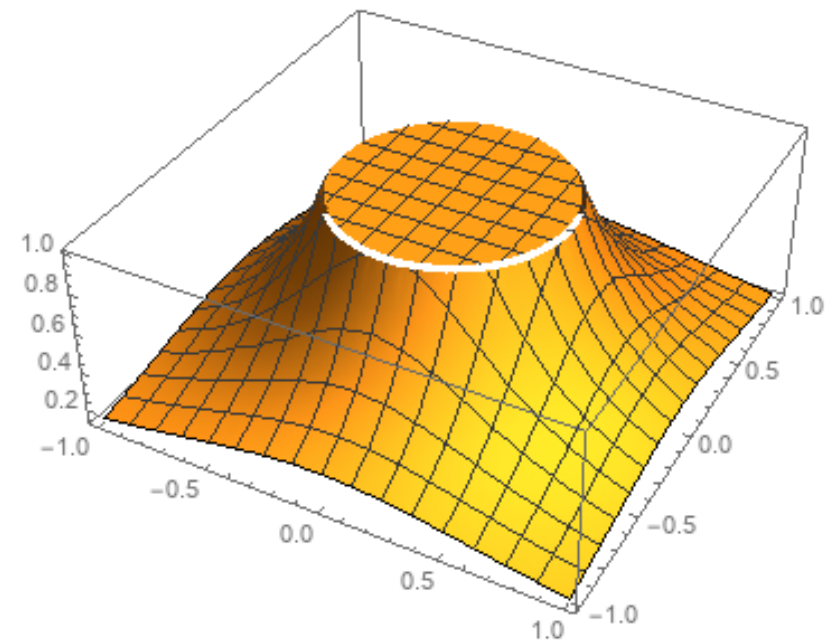
$$\text{Min}\left[1, \frac{1}{\left(0.5 + \sqrt{x^2 + y^2}\right)^3}\right]$$





# Game Flowchart

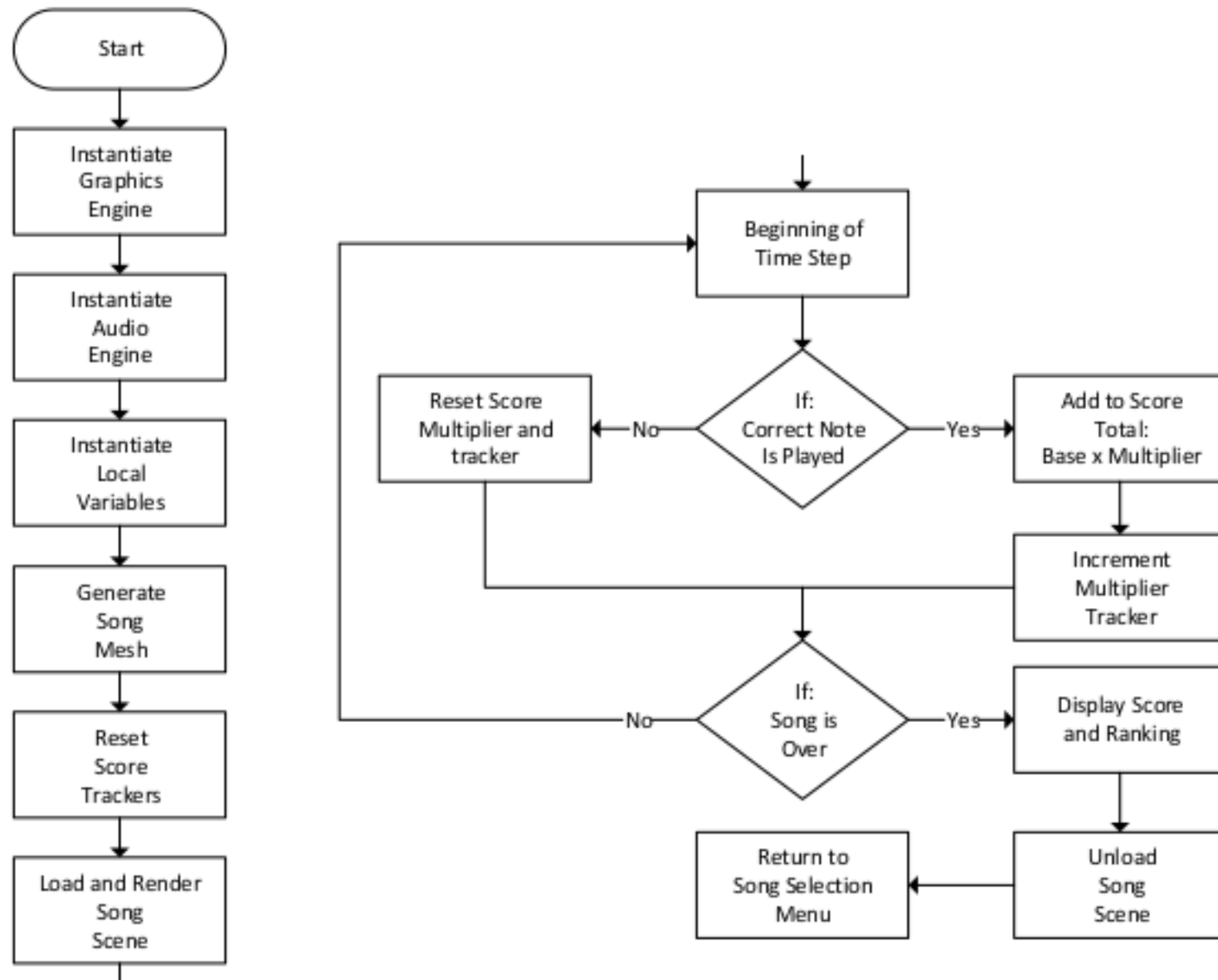

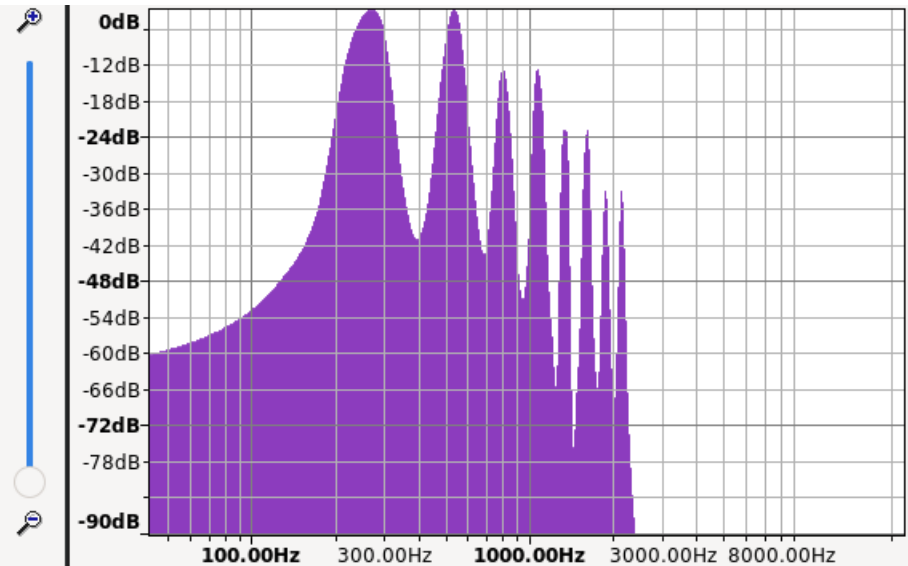
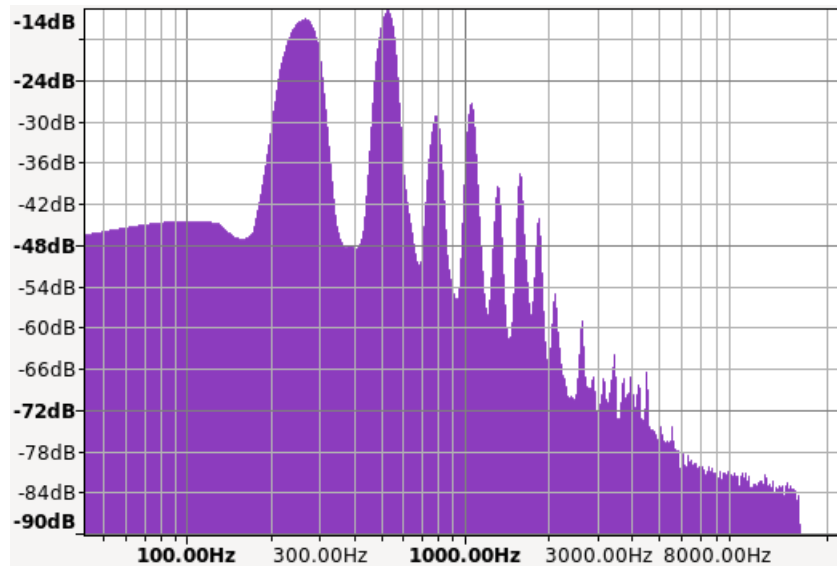
# Audio Engine

- Take ADC samples from driver and scale to a certain frequency range
- Analyzed recorded theremin sound with FFT (left)
- Simulate theremin sound using additive synthesis (right)



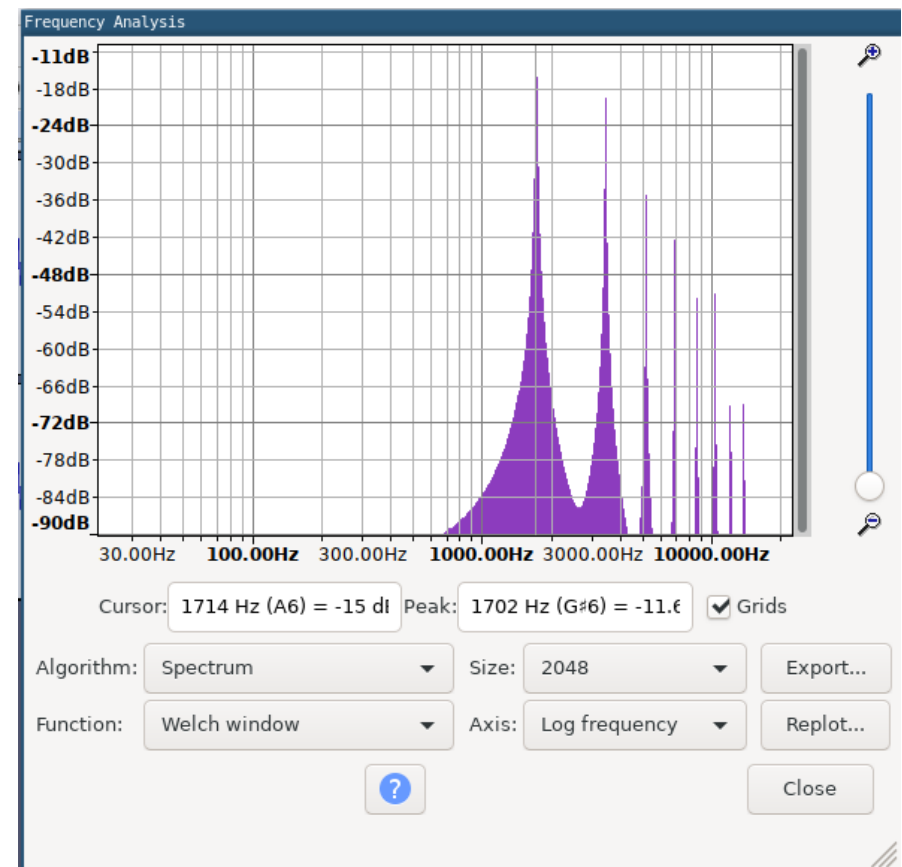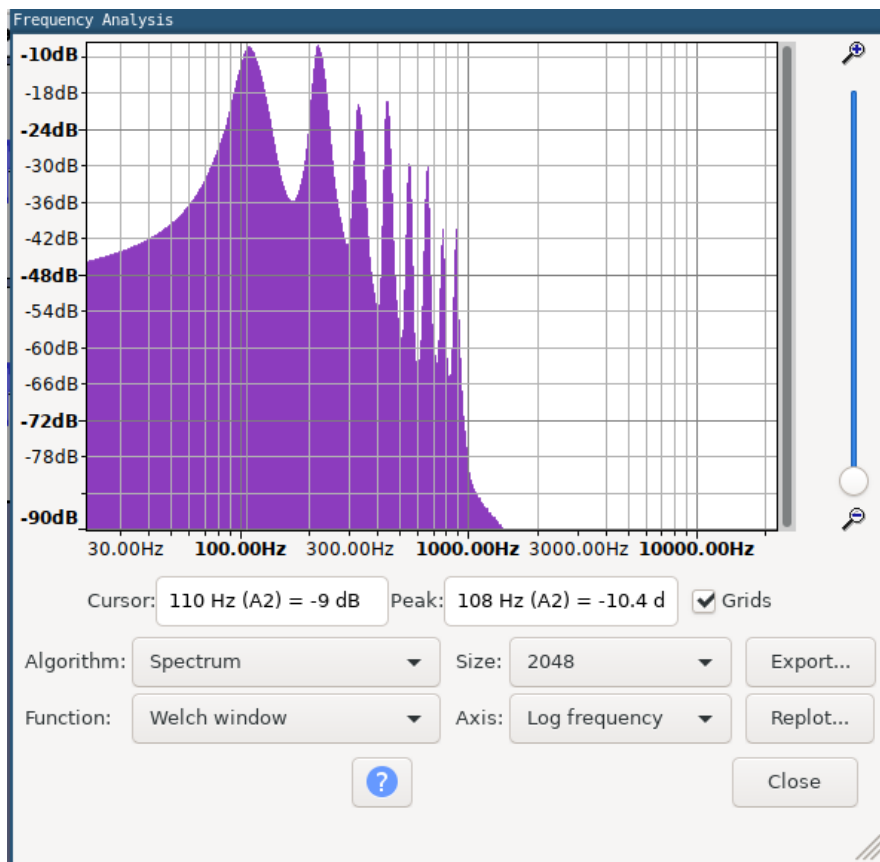
# Audio Engine cont.

- Requirement: have at least four-octave sound range
- Used 110 Hz as lowest note (A2, left) and 1710 Hz as highest note (A6, right)
- Five-octave sound range result



# Synthesis Flowchart

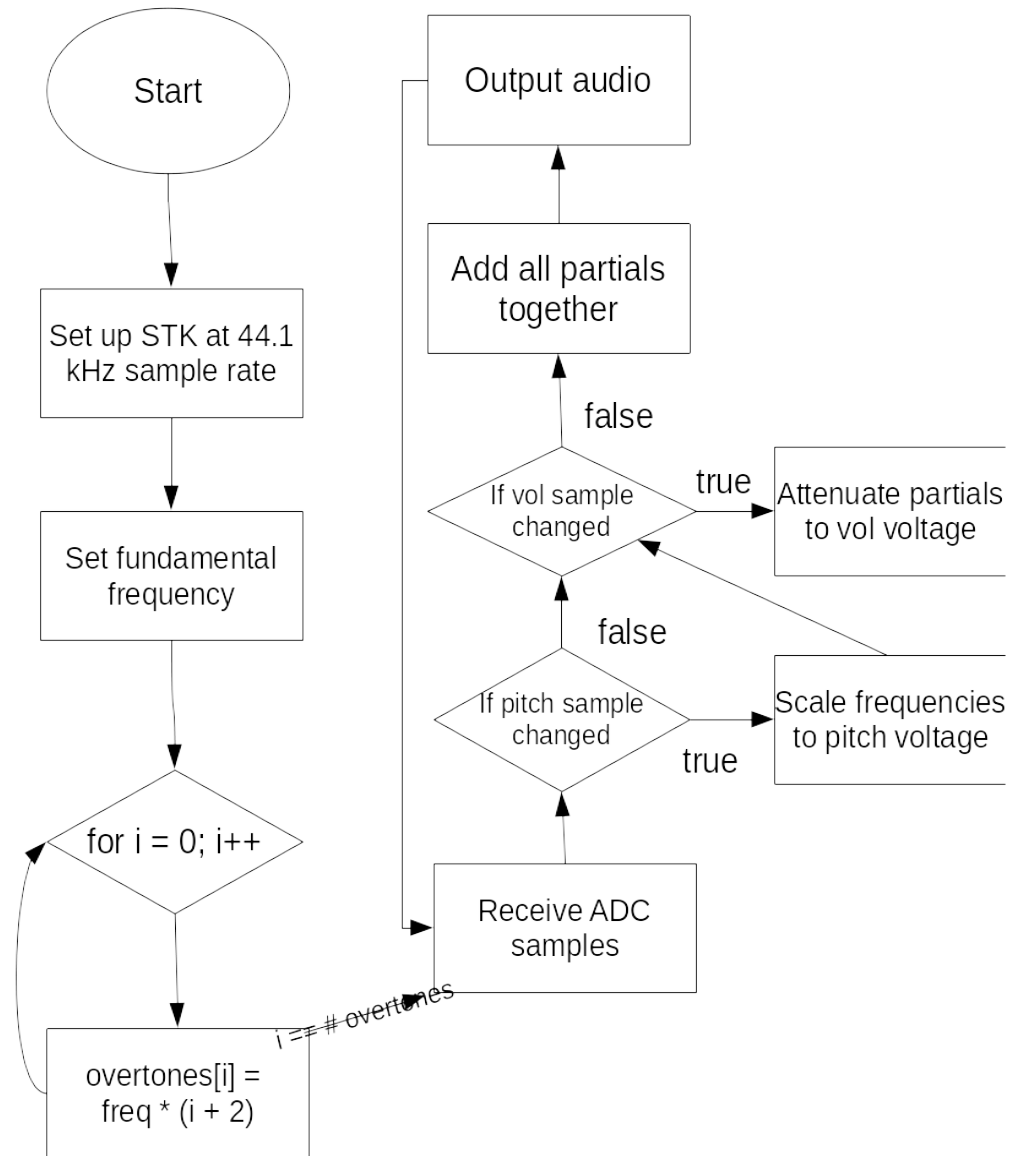

# Analog-to-Digital Converters

- Off-the-shelf 16-bit Maxim Integrated  $\sigma$ - $\delta$  converters

## Requirement

- ADCs can send at least 480 samples per second

## Verification


- Connect trimmer to ADC; ADC to Arduino

Program Arduino to manipulate ADC and send voltage reading

Verify trimmer position corresponds to value from ADC
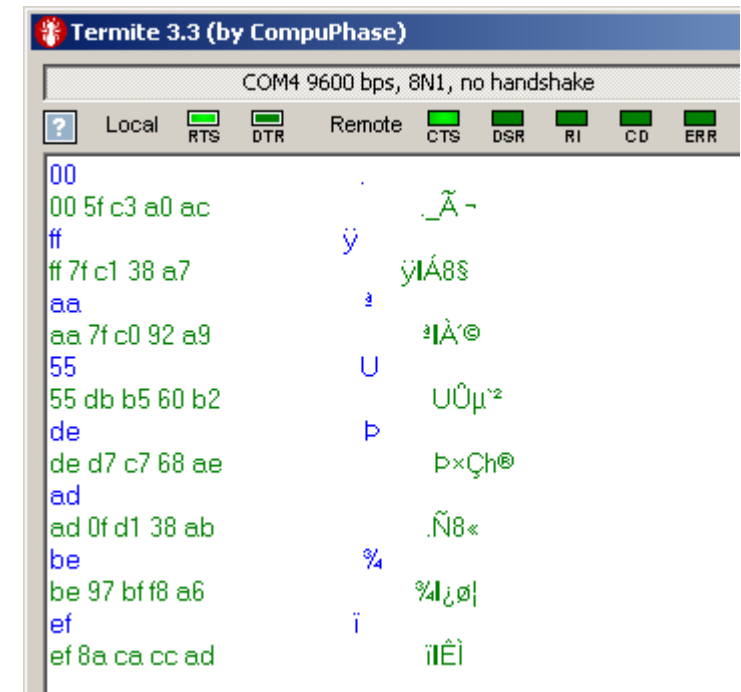
# PIC16 and RS-232 to USB chip


- PIC16 signals to ADC to take sample
- PIC16 then sends four bytes to PC thru RS-232 UART
- Requirement: PIC16 able to send samples from ADC to RS-232 interface at 9600 baud
- Verification: Send byte to PIC16, get same byte back + both ADC samples




The screenshot shows the Terminate 3.3 serial terminal window. The title bar reads "Termite 3.3 (by CompuPhase)". The status bar indicates "COM4 9600 bps, 8N1, no handshake". The window has a menu bar with "Local", "RTS", "DTR", "Remote", "CTS", "DSR", "RI", "CD", and "ERR". The main display area shows a data exchange. On the left, the data received from the PIC16 is shown in green text: "00", "00 5f c3 a0 ac", "ff", "ff 7f c1 38 a7", "aa", "aa 7f c0 92 a9", "55", "55 db b5 60 b2", "de", "de d7 c7 68 ae", "ad", "ad 0f d1 38 ab", "be", "be 97 bf f8 a6", "ef", "ef 8a ca cc ad". On the right, the data sent to the PIC16 is shown in blue text: "00", "y", "y", "U", "b", "4", "i". The data sent to the PIC16 is also shown in green text on the right: "y", "y", "U", "b", "4", "i".


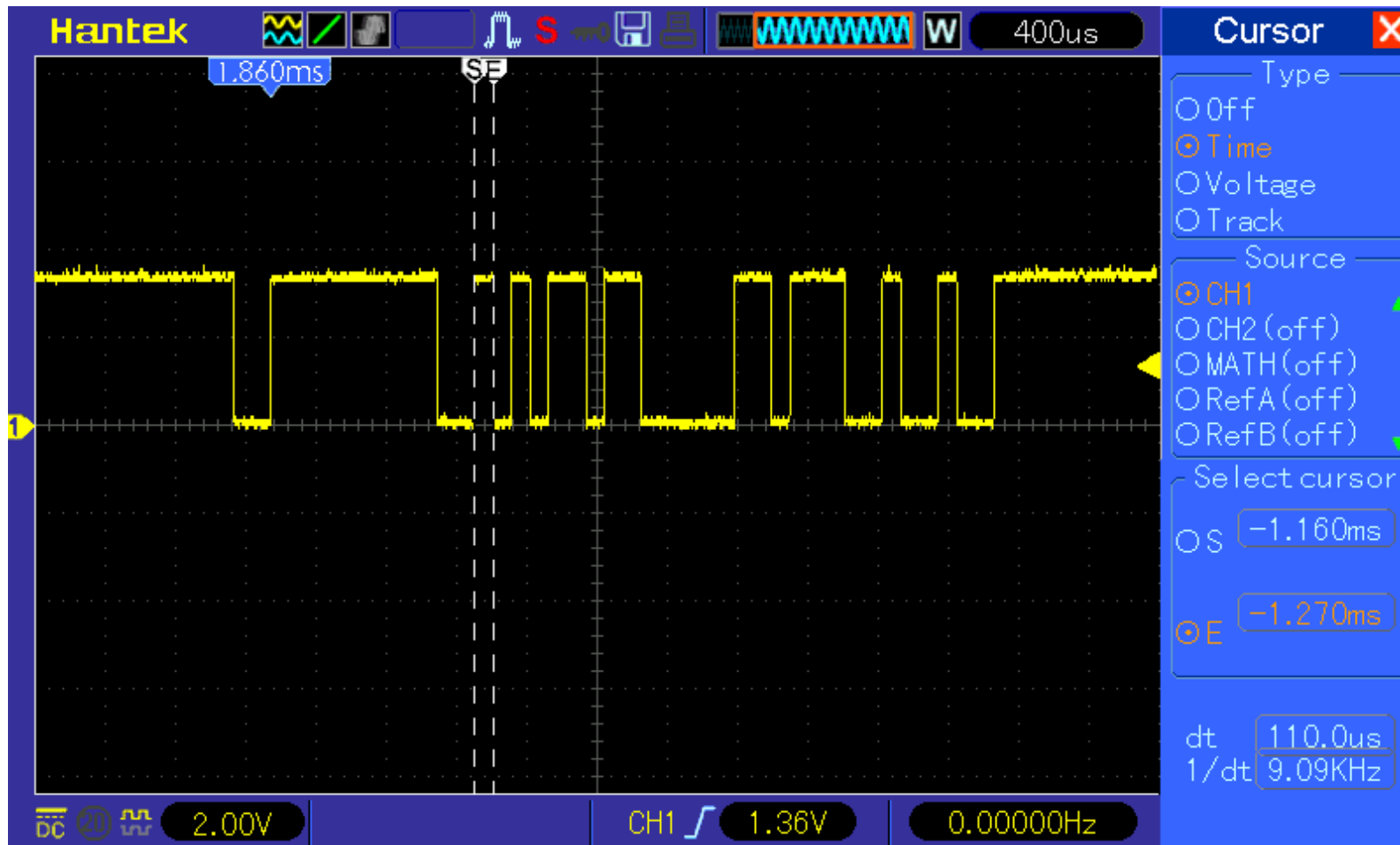
## Oscilloscope Trace of RS-232 Transmission



# Digital Circuit

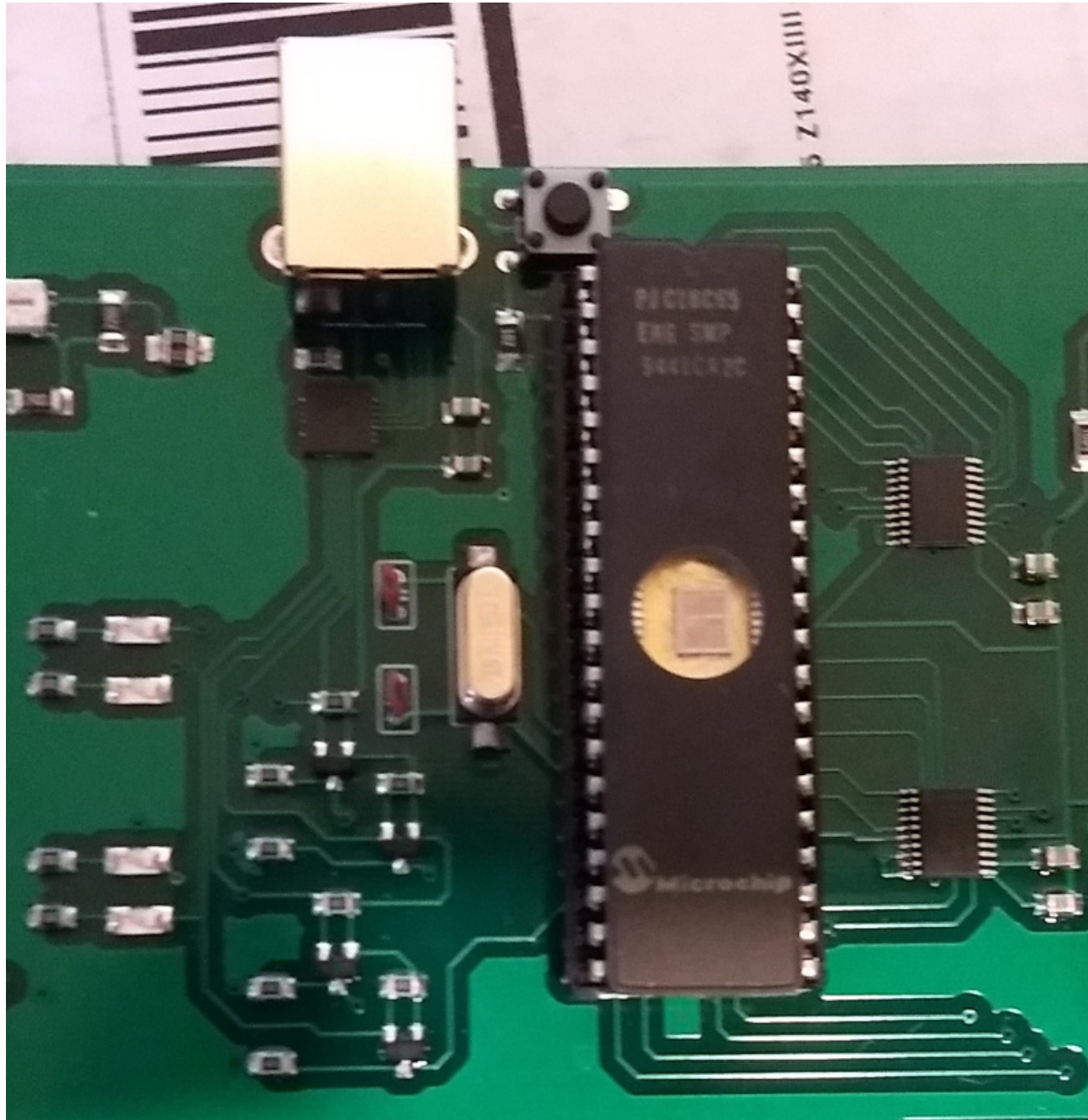

# PIC16

## ADCs



## Mixer

# Integrator

# Device Driver

- Uses system calls to open serial device and read/write from/to theremin controller
- Requirement: provide 2 16-bit samples from theremin with delay  $< 50$  ms
- Verification: take time difference between PIC sampling input and driver receiving input
- ~9.5 ms delay

```
~/U/E/E/usb driver $ stty -F /dev/ttyUSB3 cs8 9600 ignon -iexten -echo -echoe -echok -echoctl -echoke nof
~/U/E/E/usb driver $ ./test /dev/ttyUSB3
transmission time: 9623
voltage level from top ADC, right of PCB: 4.096000
voltage level from bottom ADC, left of PCB: 4.096000
~/U/E/E/usb driver $ ./test /dev/ttyUSB3
transmission time: 9552
voltage level from top ADC, right of PCB: 3.977811
voltage level from bottom ADC, left of PCB: 3.953060
~/U/E/E/usb driver $ ./test /dev/ttyUSB3
transmission time: 9475
voltage level from top ADC, right of PCB: 3.720307
voltage level from bottom ADC, left of PCB: 3.803058
~/U/E/E/usb driver $ ./test /dev/ttyUSB3
transmission time: 9498
voltage level from top ADC, right of PCB: 3.525304
voltage level from bottom ADC, left of PCB: 3.850059
~/U/E/E/usb driver $ ./test /dev/ttyUSB3
transmission time: 9591
voltage level from top ADC, right of PCB: 3.322551
voltage level from bottom ADC, left of PCB: 3.591055
```

# Conclusions

- Oscillators still need work done (detailed in next slide)
- Digital section of theremin reliable
- Synthesis engine decent
- Game barebones but working

# Future Work

- Fix transistor biasing with inductors before biasing inductor 6V pk-pk (left); 32.4V pk-pk after (right)
- Improve upon sound synthesis engine
- Flesh out game
- Actual controller enclosure and rigid antennae

