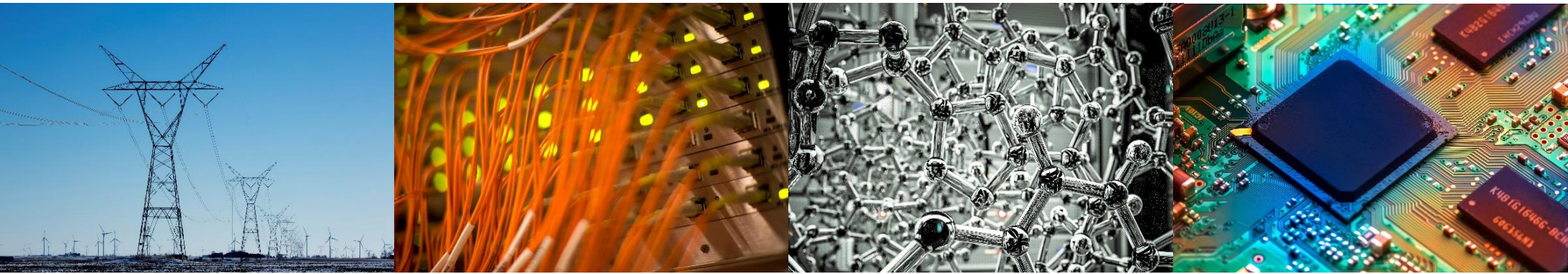


# Illini Theremixer

Karthik Achar, Shiv Kapur, Akhil Reddy

Team 15




**I ILLINOIS**

Electrical & Computer Engineering

COLLEGE OF ENGINEERING
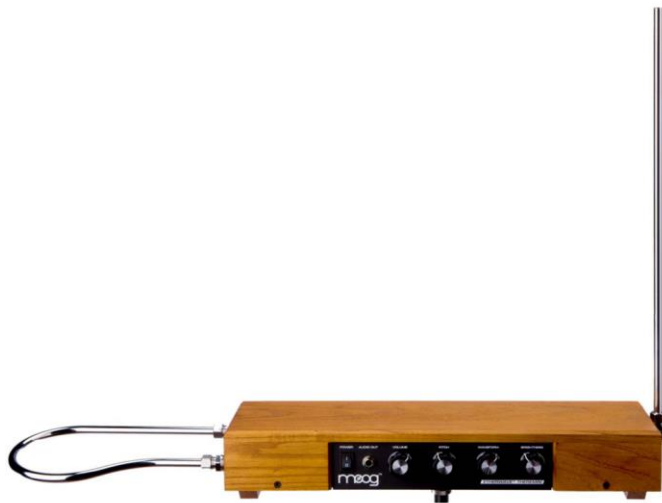
# Introduction – What is a Theremin?




- Created by Léon Theremin in the 1920s
- Project idea: repurposed analog theremin
  - Two outputs as control signals




# Objective

- Control Signals:
  - Frequencies from Oscillators  
*(Representing Relative Hand Placement)*
- Functions:
  - Increase/Decrease Bass, Mid, Treble, Volume
- Components:
  - Hardware: Etherwave Antennas & Oscillators, ADC (AD7352)
  - Software: Microcontroller (Teensy 3.2)

# Design Model

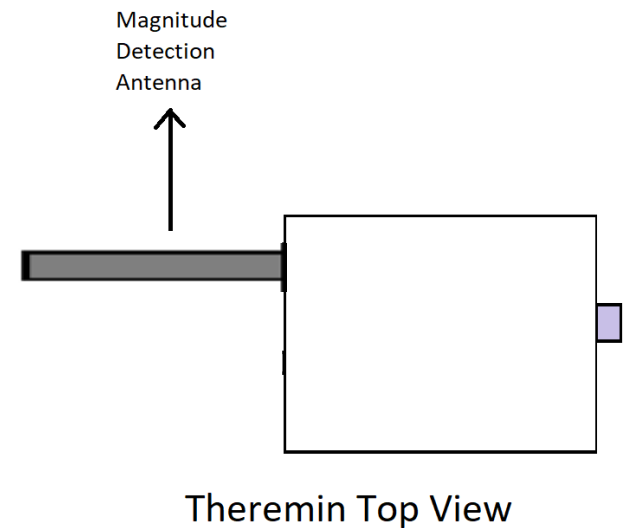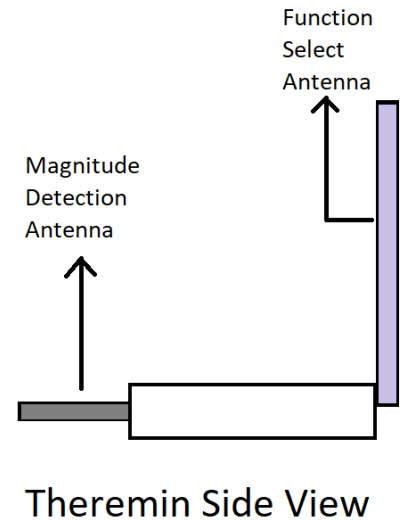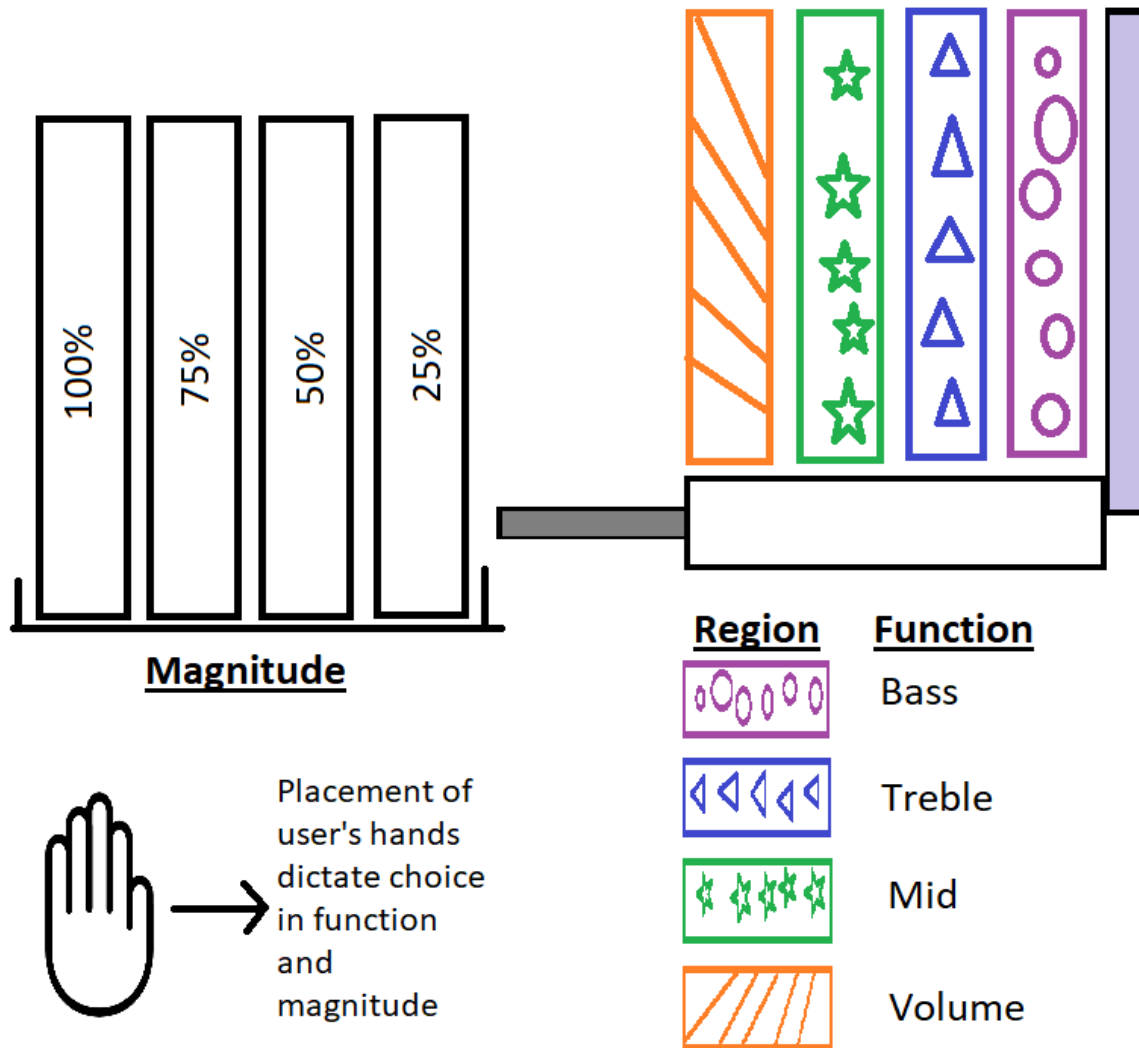

# Physical Model

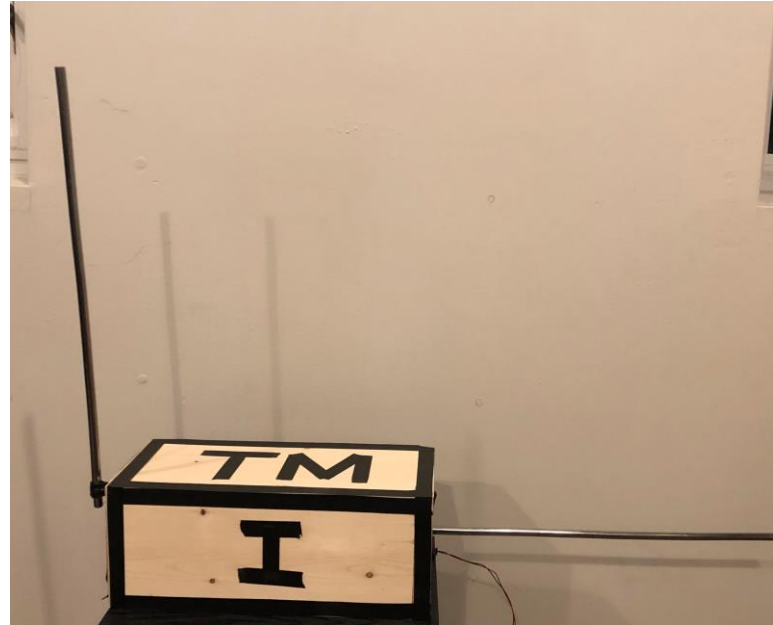


Front View





Side View
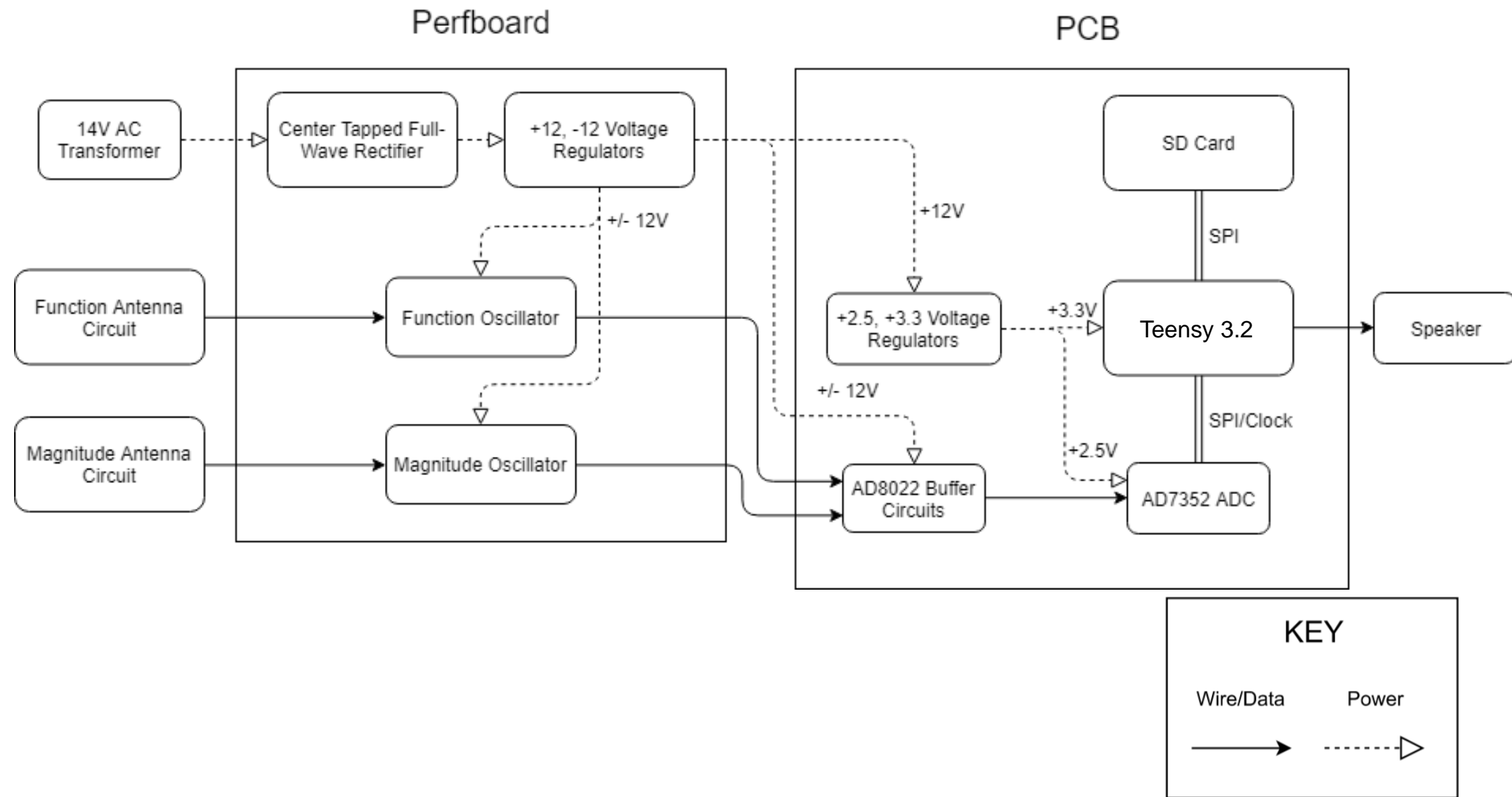
# Block Diagram




# Overview of Requirements and Verifications

Power Module	14 Volt AC Transformer	$\pm 12$ Voltage Regulator	+ 3.3 Voltage Regulator	+ 2.5 Voltage Regulator
Hardware Module	Magnitude Detection Antenna	Magnitude Detection Oscillator	Function Select Antenna	Function Select Oscillator
H/S Integration Module	Analog to Digital Converter			
Software Module	Micro-controller			


 Fully Meets Requirement  
 Partially Meets Requirement

# Hardware: Antennas


Function Oscillator Antenna Circuit:

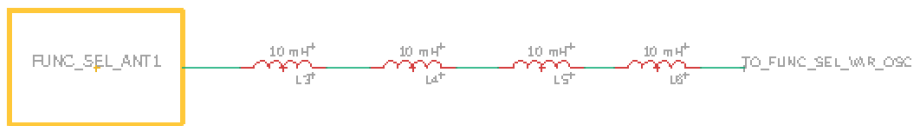

Magnitude Oscillator Antenna Circuit:

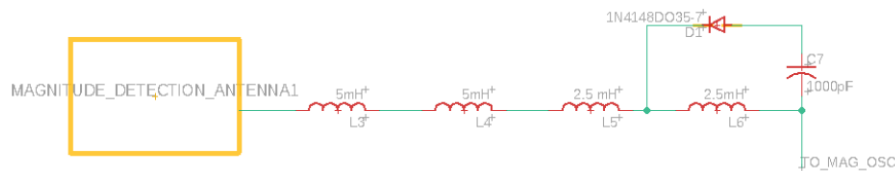



Antenna Capacitance

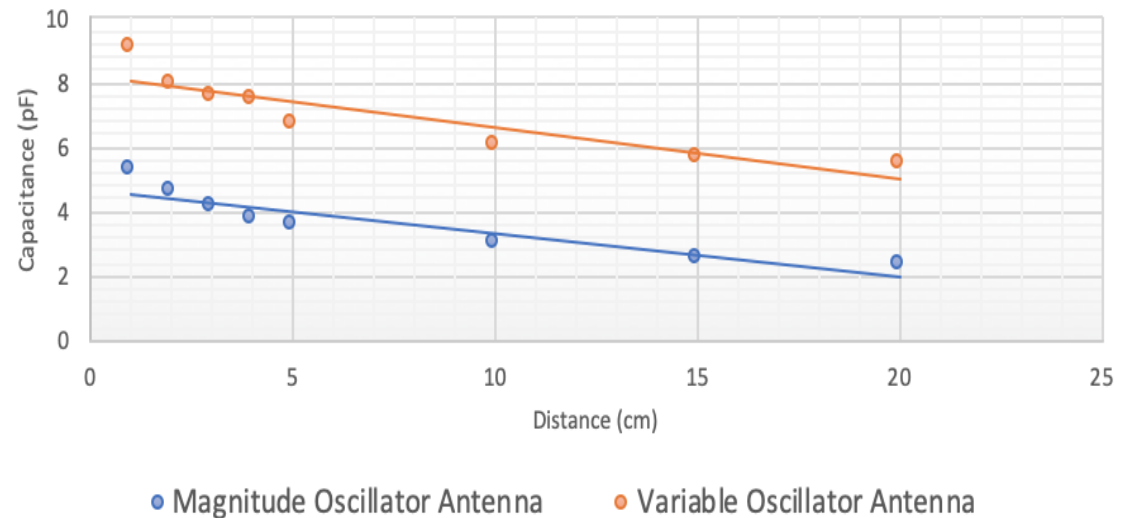

Distance (cm)	0	1	2	3	4	5	10	15	20
Magnitude Oscillator Antenna Capacitance (pF)	87.17	5.33	4.59	4.14	3.82	3.6	3.01	2.59	2.31
Variable Oscillator Antenna Capacitance (pF)	120.01	9.06	7.93	7.62	7.48	6.75	6.07	5.67	5.52





# Hardware: Function Oscillator

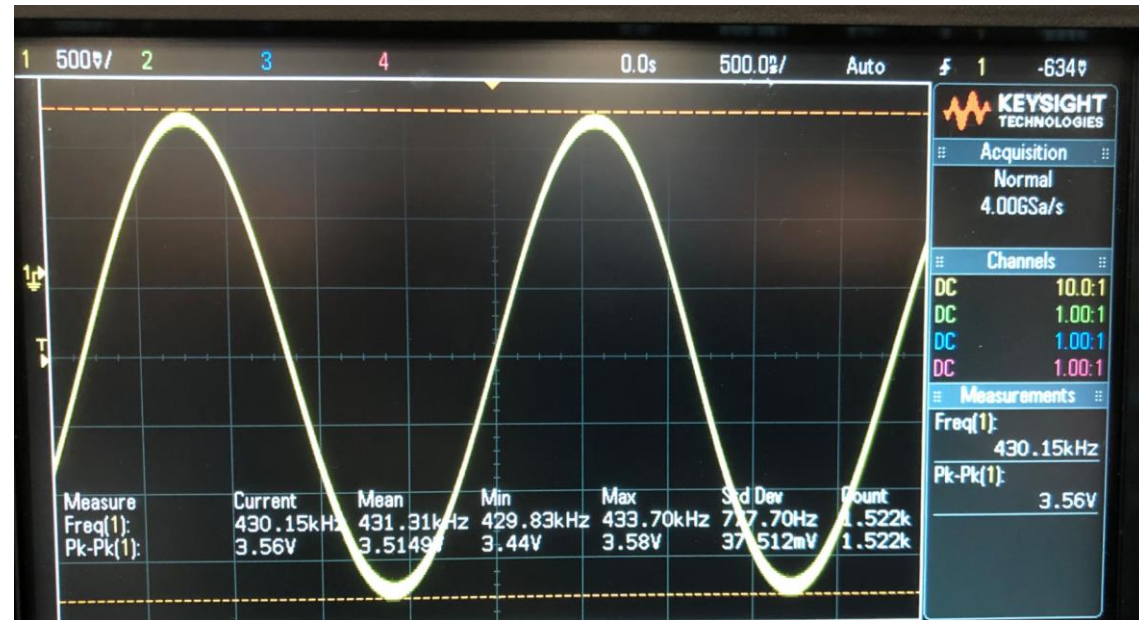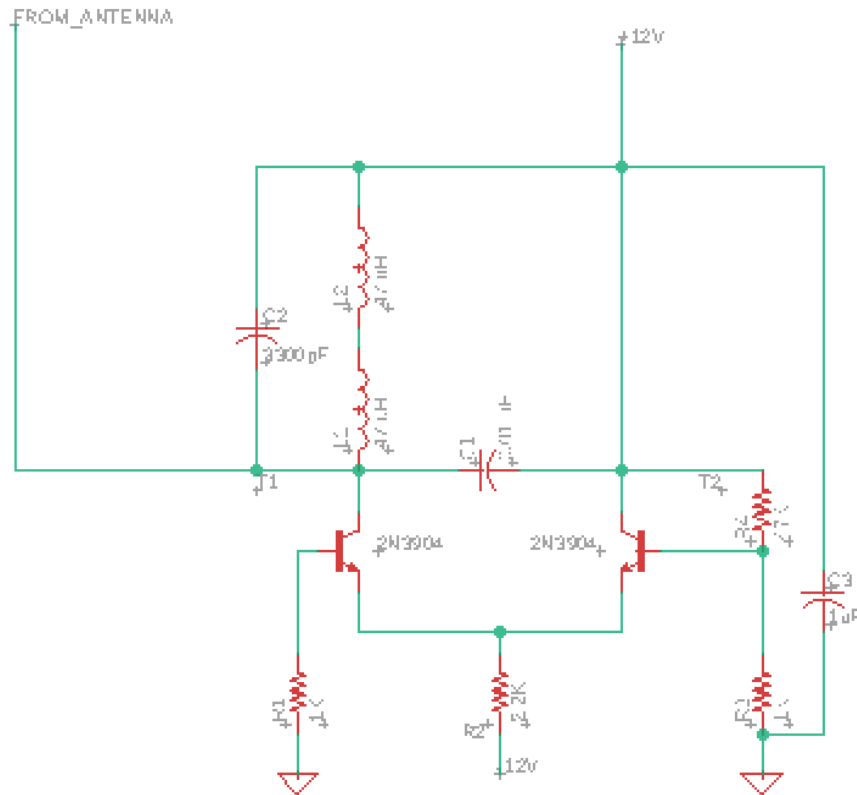



- Average Frequency: 431.31 kHz
- Average Peak to Peak: 3.51 V

# Hardware: Magnitude Oscillator

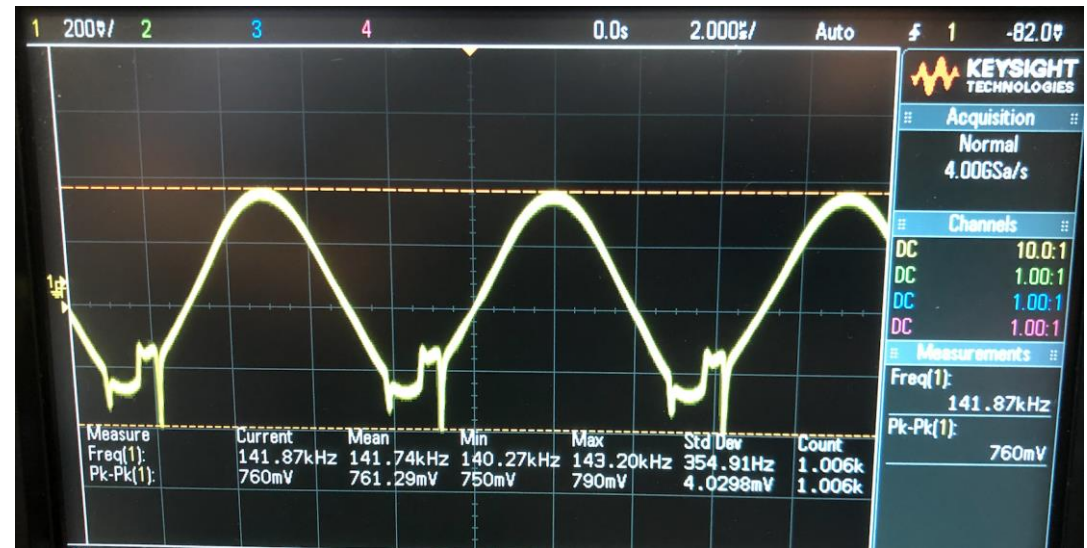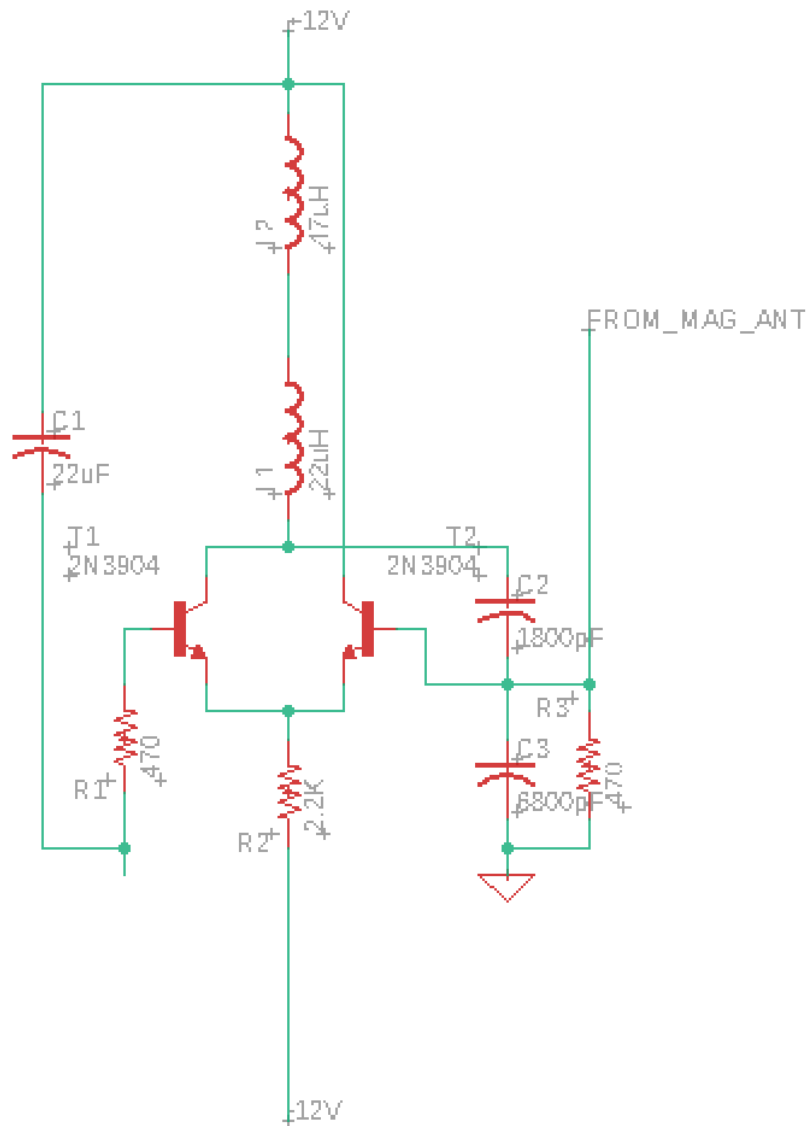

- Average Frequency: 141.76 kHz
- Average Peak to Peak: 761.29 mV


# Hardware: ADC

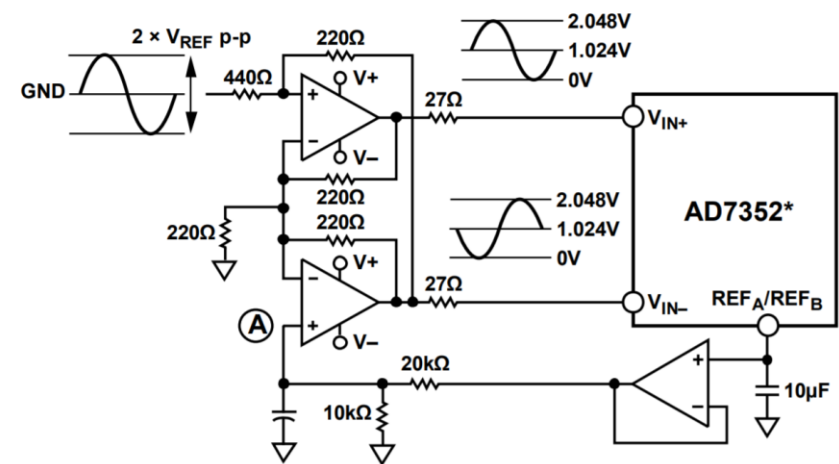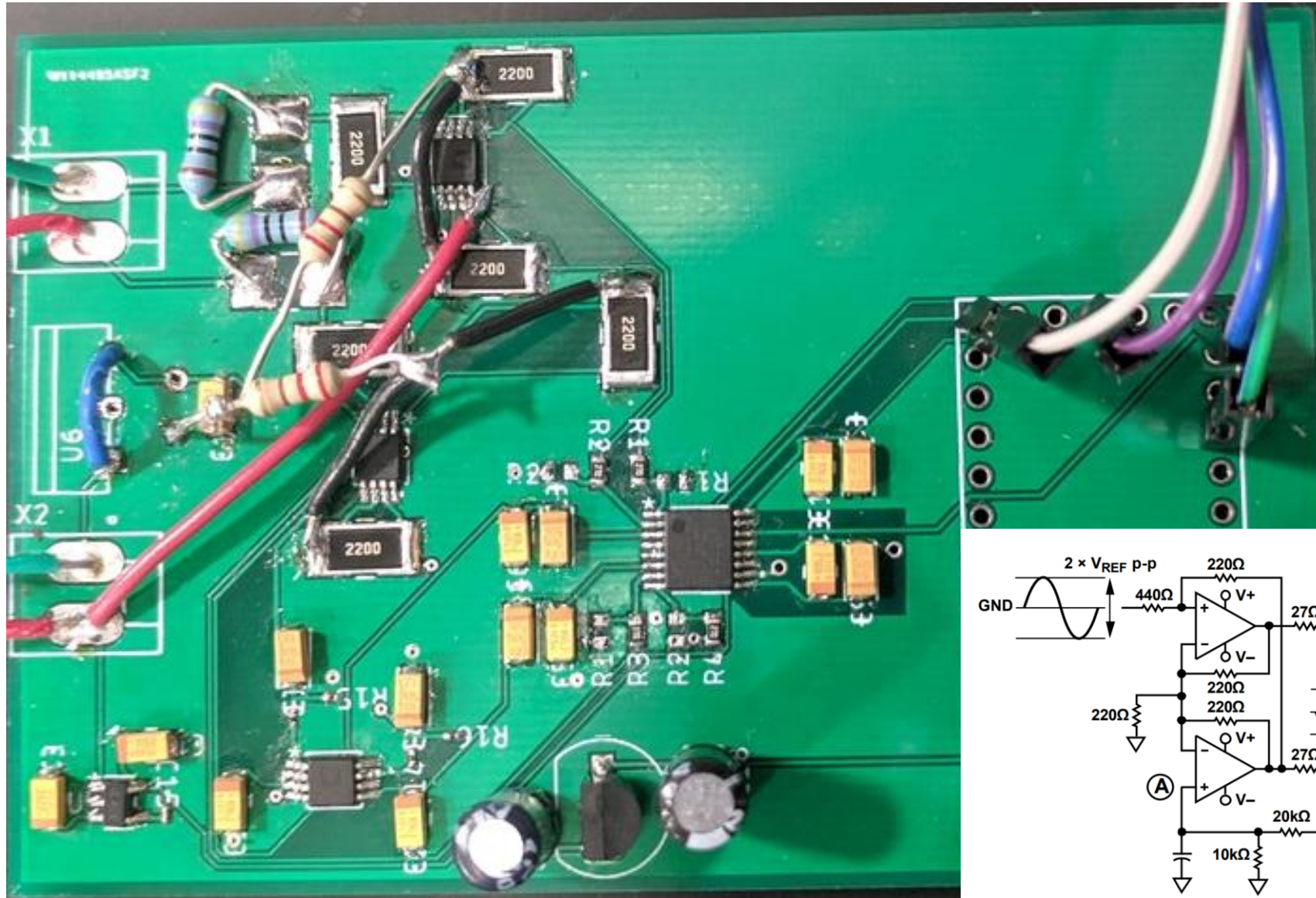
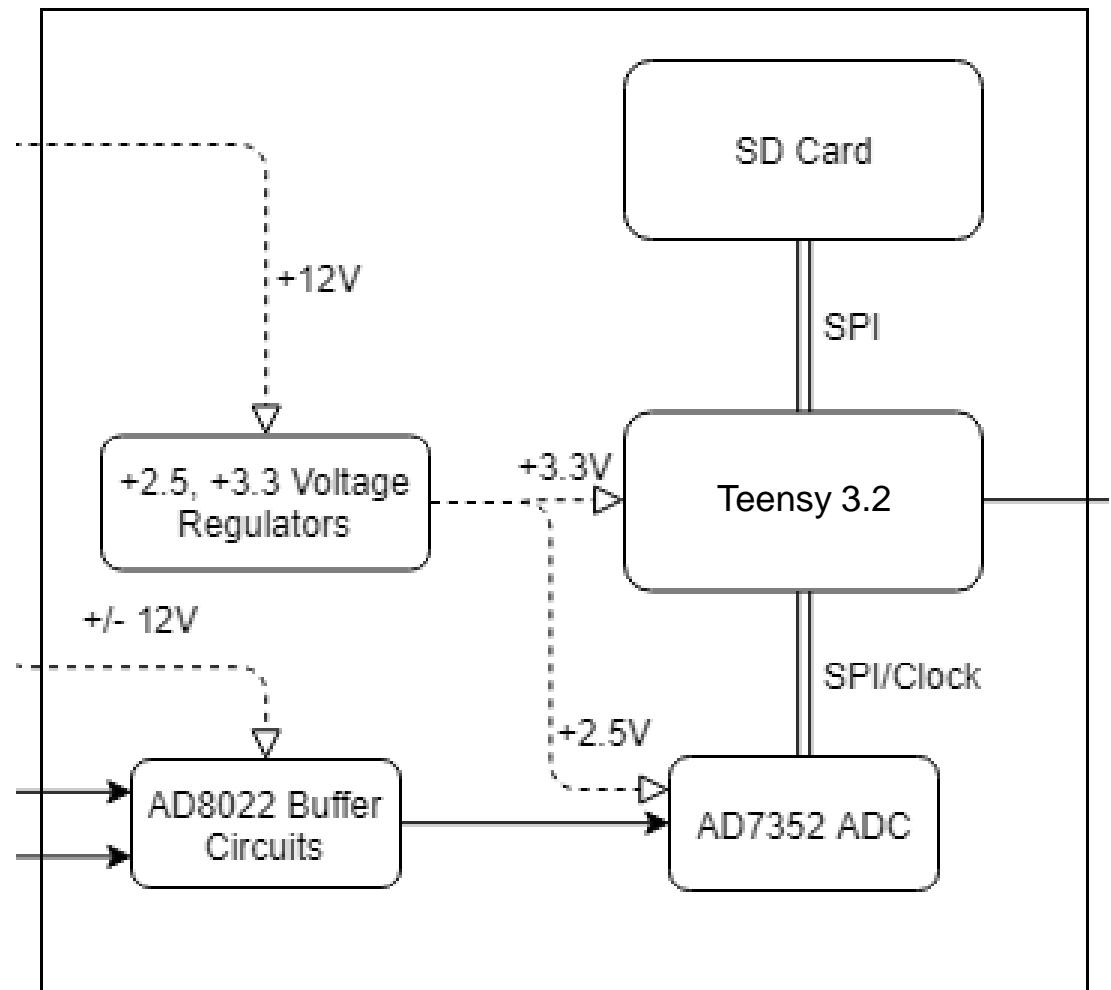
# Hardware/Software: Integration


PCB

- AD8022 opamps
- AD7352 12-bit ADC
  - Outputs data via SPI protocol
- Teensy Microprocessor






# Software: Flow Chart

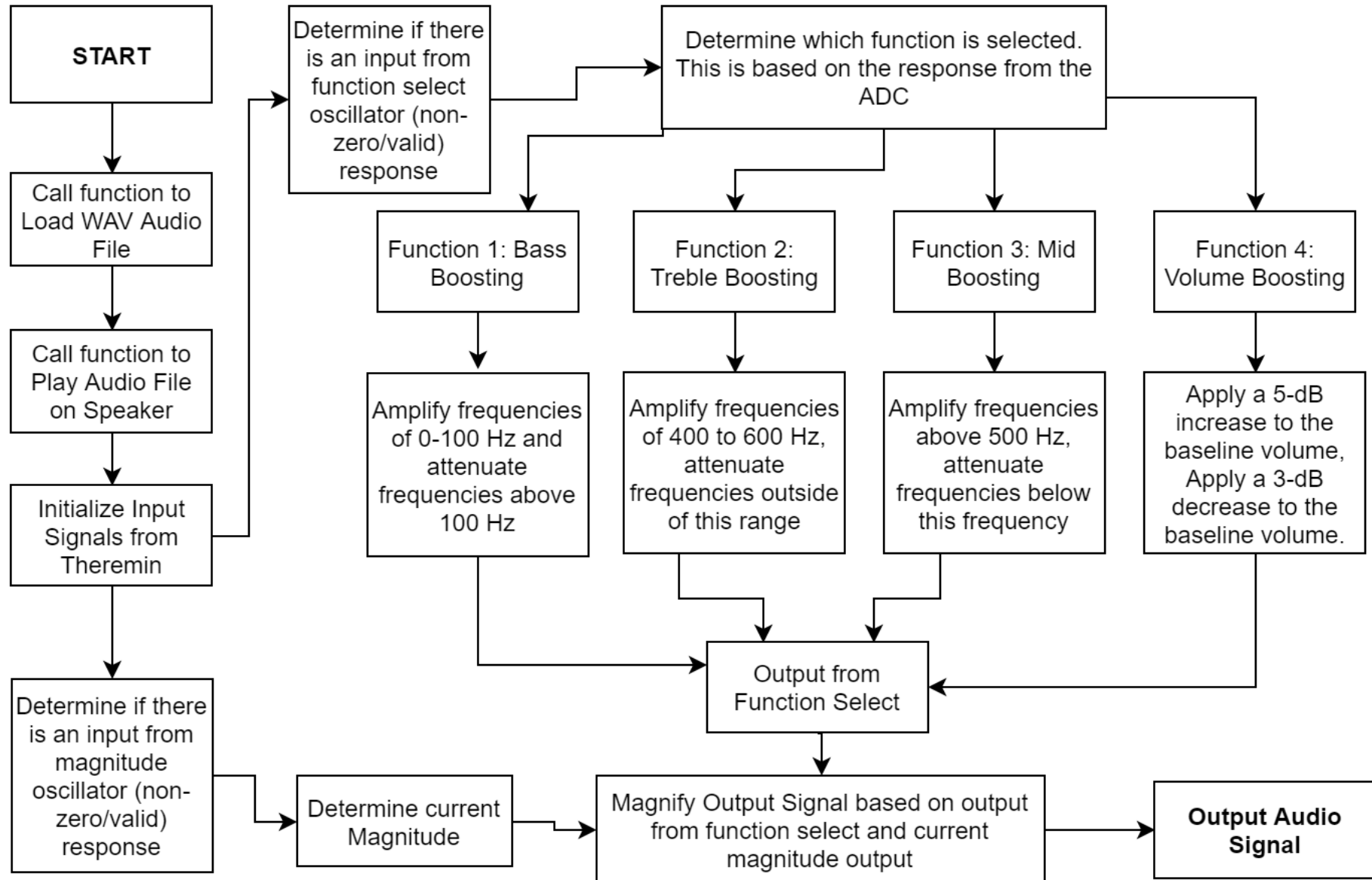


# Software: Filters

- Function Select Input Signal
  - Bass Boosting → Low Pass Filter (100 Hz)
  - Mid Boosting → Band Pass Filter (400 to 600 Hz)
  - Treble Boosting → High Pass Filter (800 Hz)
  - Volume Boosting → Modify Baseline Volume
- Magnitude Input Signal
  - Amplify output audio signal at higher frequencies
  - Attenuate output audio signal at lower frequencies


# Software: Outputs of Filters

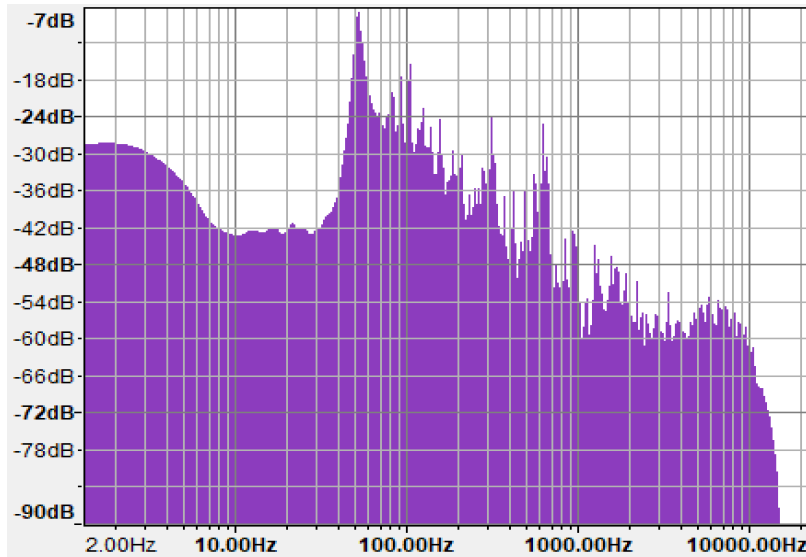


*Original Audio*

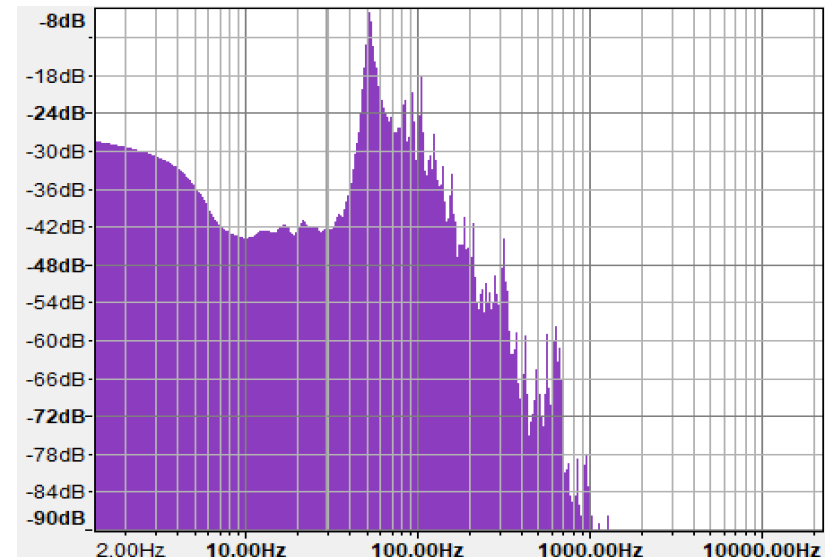

*Low Pass Filter*

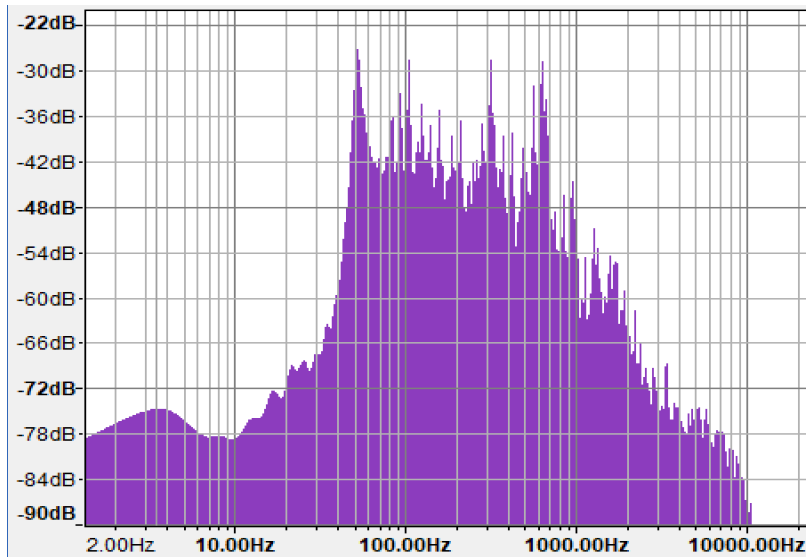

*Band Pass Filter*

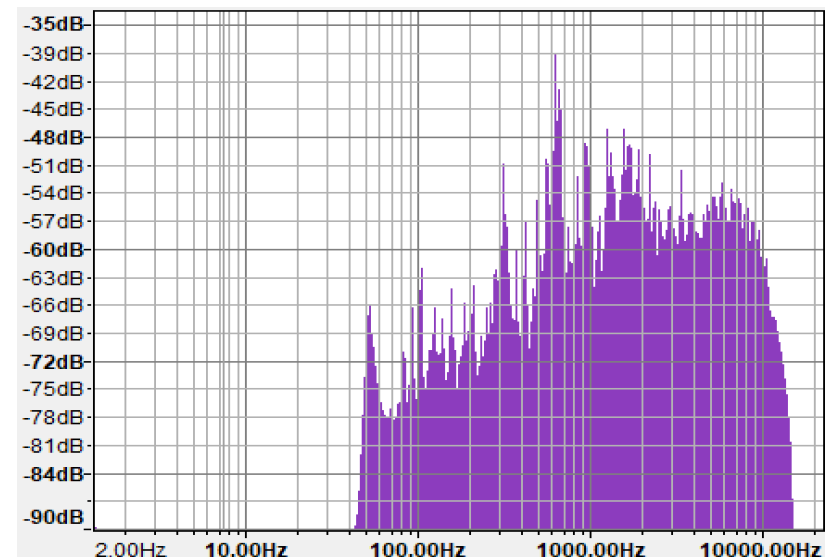

*High Pass Filter*

# Project Successes & Challenges

## Successes:

- Audio Filters
- ADC Sampling
- Oscillator Frequencies
- Antenna Sensitivity

## Challenges:

- Antenna & Oscillator Integration
- FFT at high frequencies
- Buffer implementation



# Hardware: Next Steps

- Enhance effect of antenna capacitance on oscillator frequency
- Design new PCB to reflect design changes and problems
  - Buffer circuits
  - Ground loops in mixed signal design

# Software: Next Steps

- Implement FFT to measure control signal frequency
- Provide Additional Features:
  - Cut-Off Frequency Selection using a Potentiometer
  - Reset/Pause/Play/Skip Options using Buttons
  - Visual Display of Current Filters
  - New Mixing Effects

# Conclusion: Lessons Learned

- Understanding individual modules and their role in the overall project
- Being adaptable to different circumstances and outcomes
- Teamwork and collaboration helps solve challenging problems

# Q & A



