



UNIVERSITY OF  
**ILLINOIS**  
URBANA-CHAMPAIGN

# Optimized Solar Charging Off Grid for Several Output Voltage Potentials

Team 7: Lukas Gollings, Kanin Tangchartsiri, WonJoon Lee

4/29/2022



# Problem Statement

**Problem:** In the event of electricity going out for several days during a natural disaster, people are left with no way to charge their phones, flashlight batteries, or any other tools they may desperately need.

## Essential Features:

- Provides an off-grid energy source
- Ability to charge electronic devices
- Can harvest energy from a renewable source
- Must be reliable within a wide range of conditions and environments
- Adhere to IEEE safety and ethics for battery charging
- Must be user friendly



Example Power Outage [1]



## Solution:



- Input Power Subsystem
- Microcontroller Subsystem
- Voltage and Current Regulation System
- User Interface


## Ethical Concerns:

- Battery management safety
- Accuracy of measurement
- Reproducibility




# Our Solution

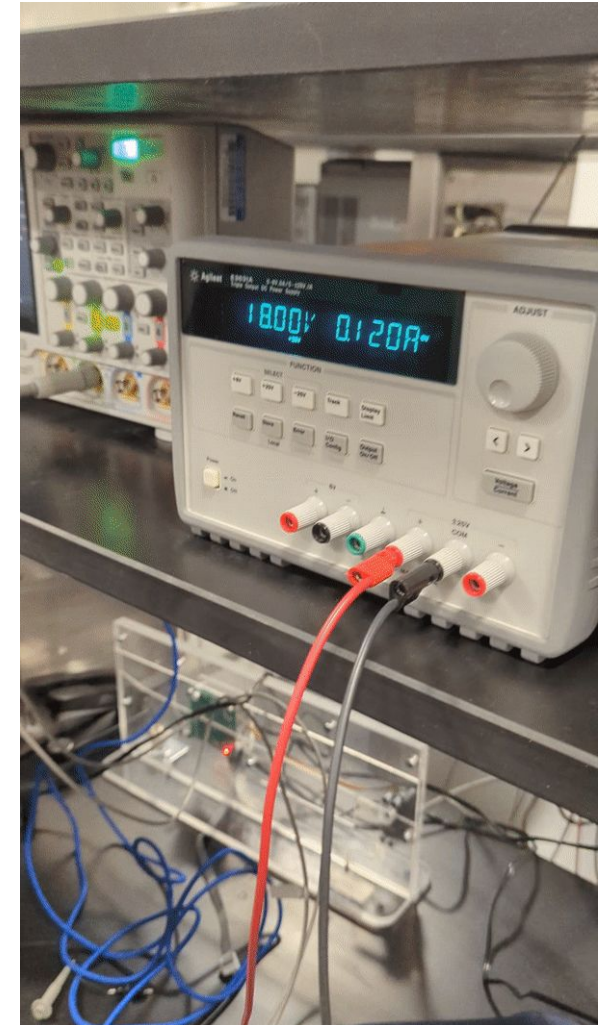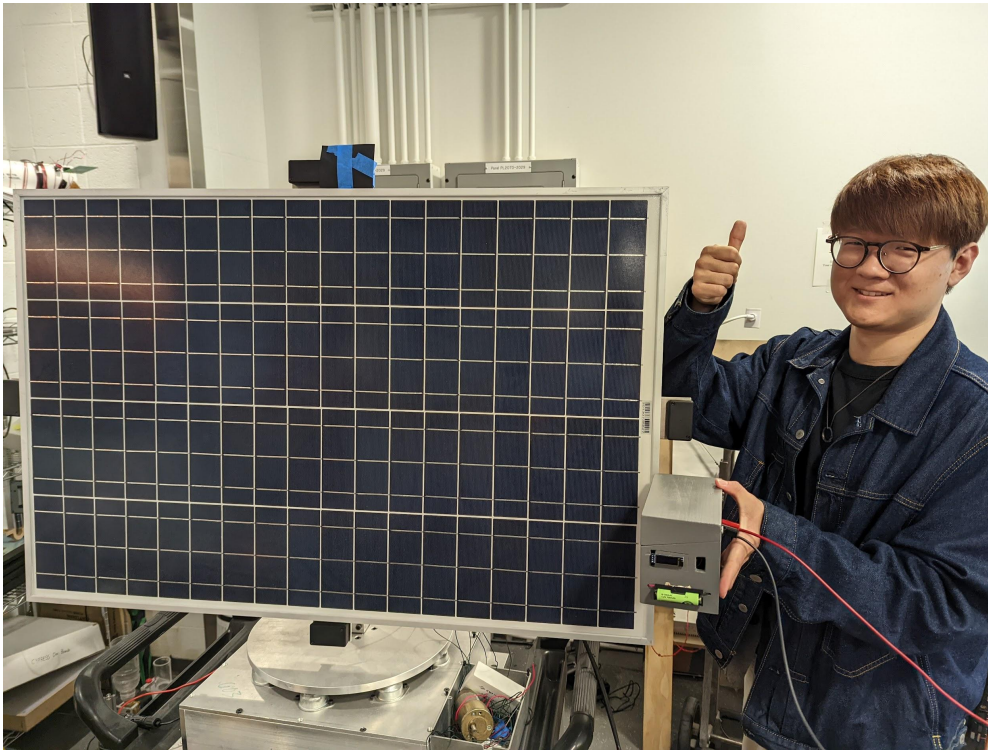

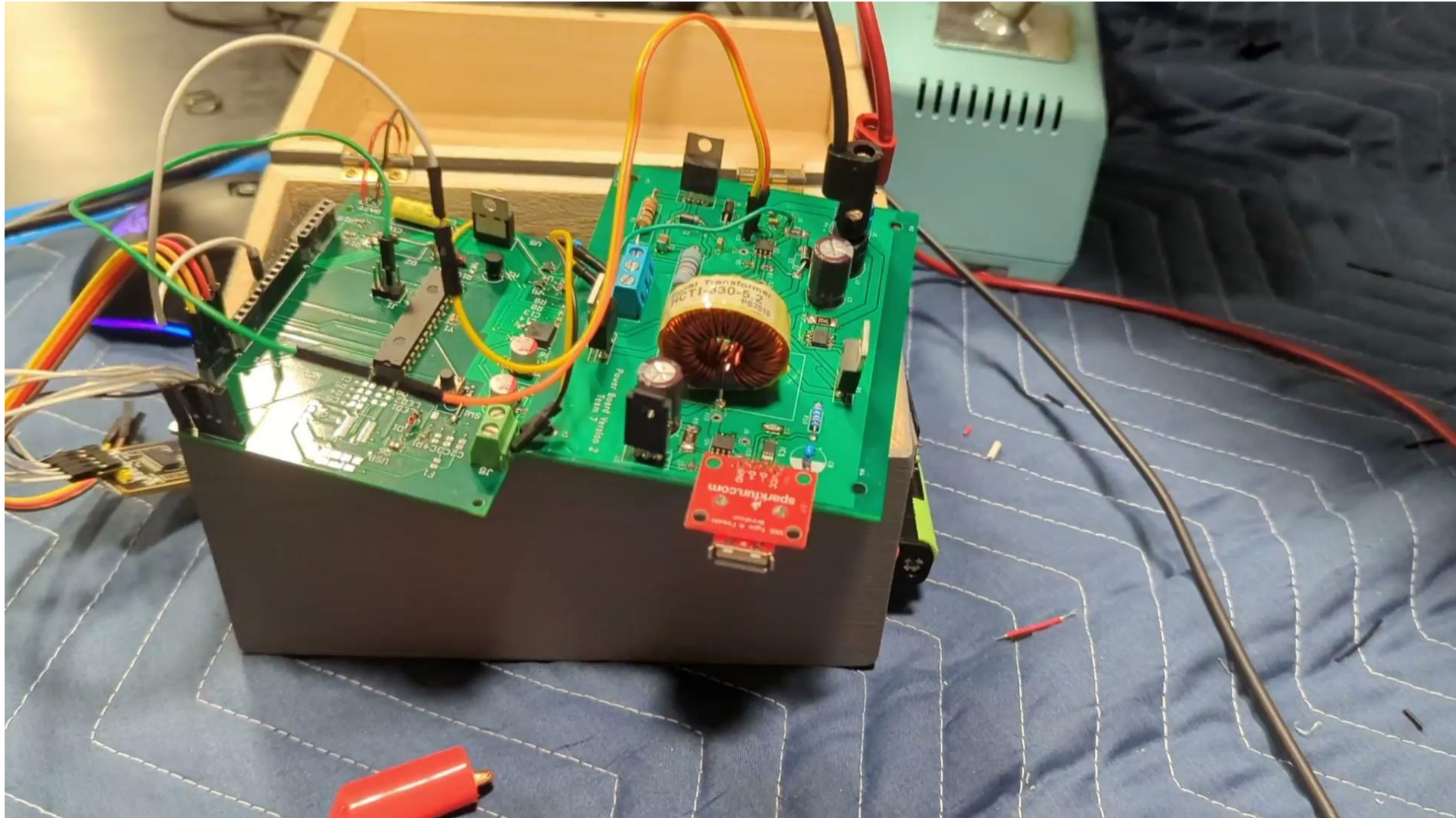

Output for Solar Charging



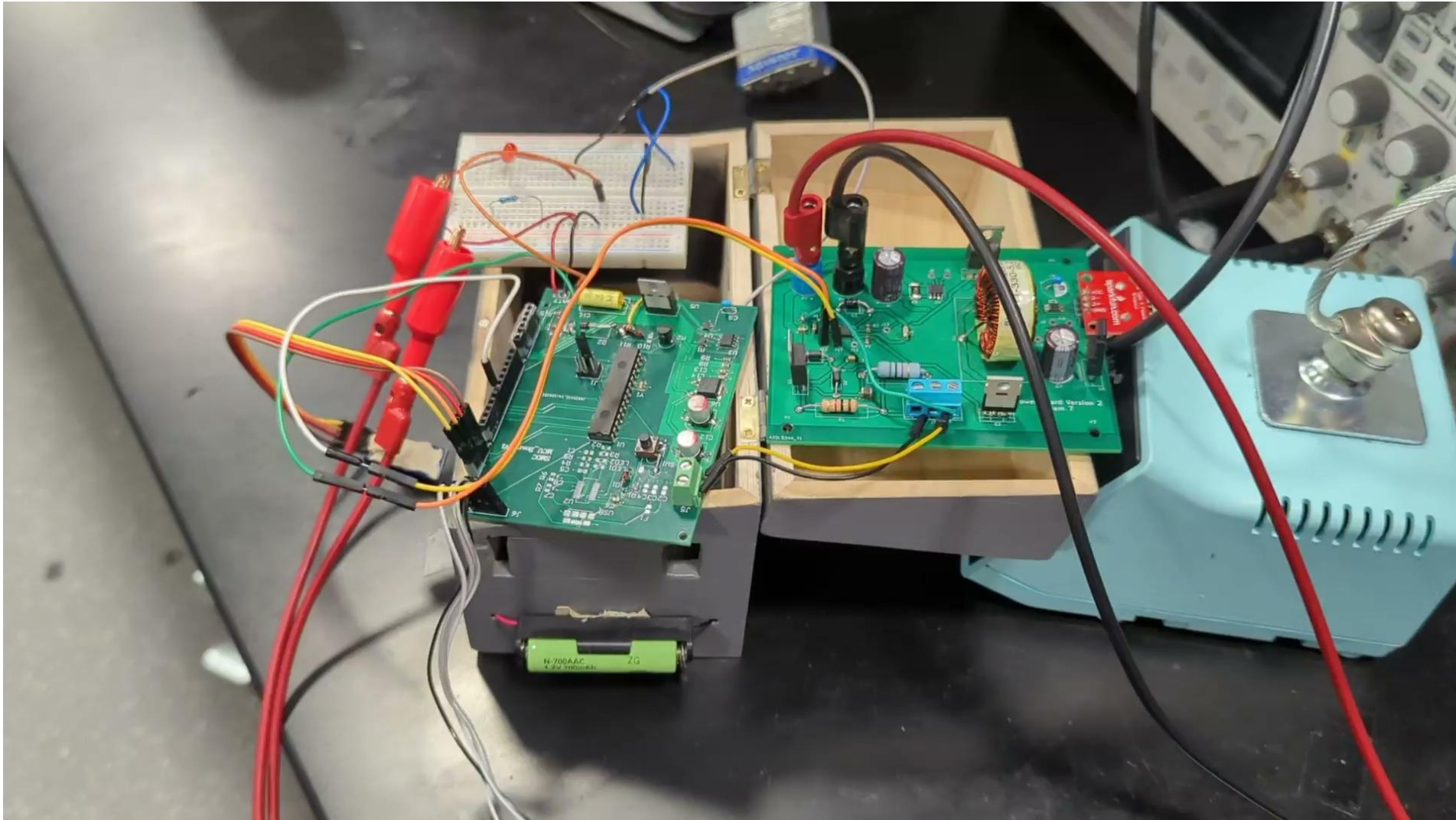


NiCd battery charging (70 mA output)



# Design and Considerations




# Block Diagram

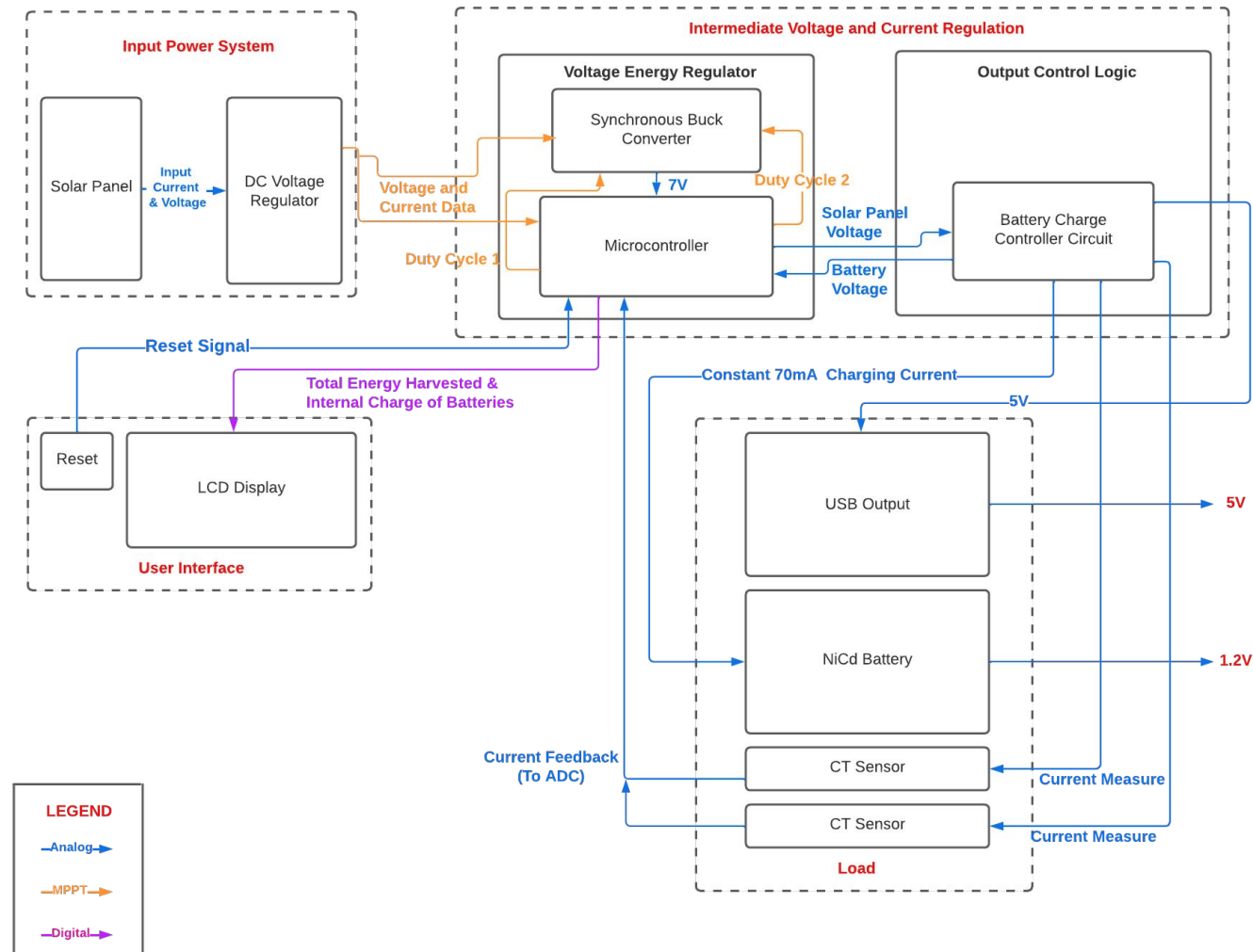


Block diagram with our different subsystems: input power system, intermediate voltage/current regulation, UI, and load

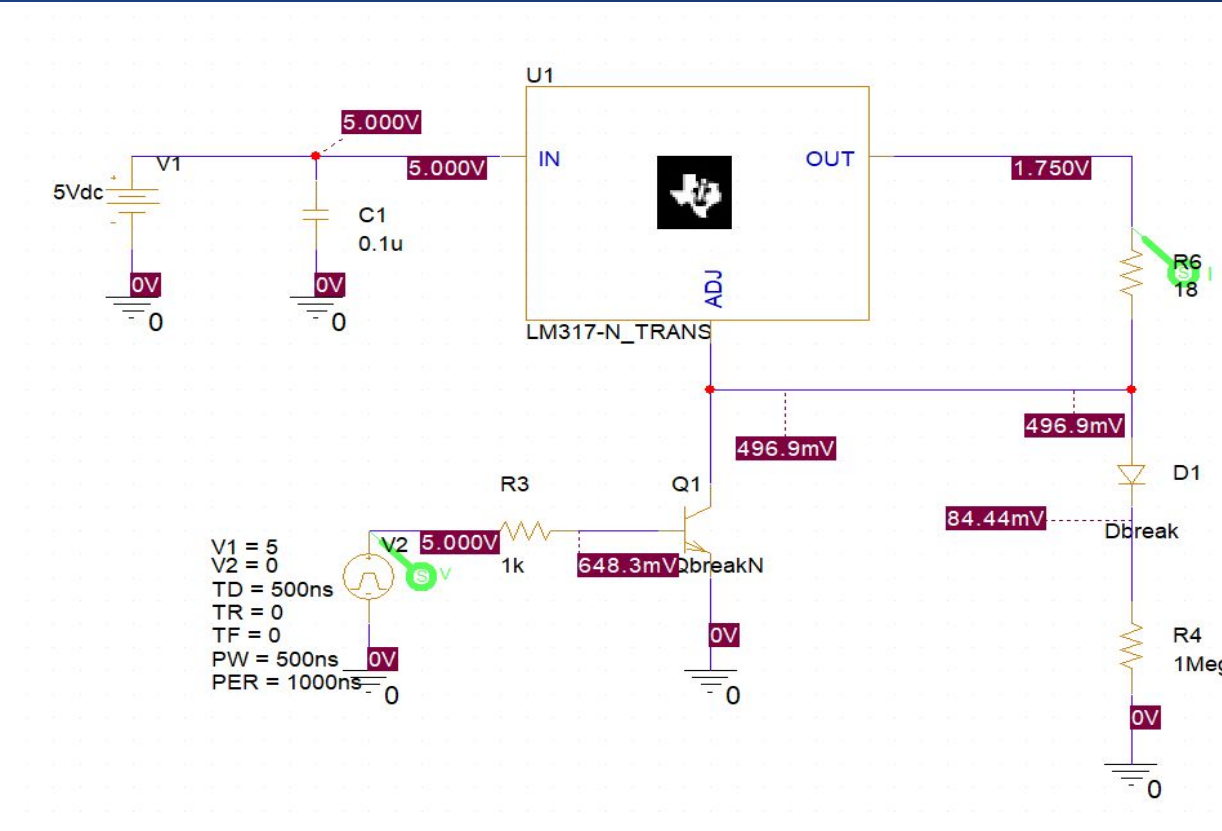
# NiCd Battery Charger Design Considerations



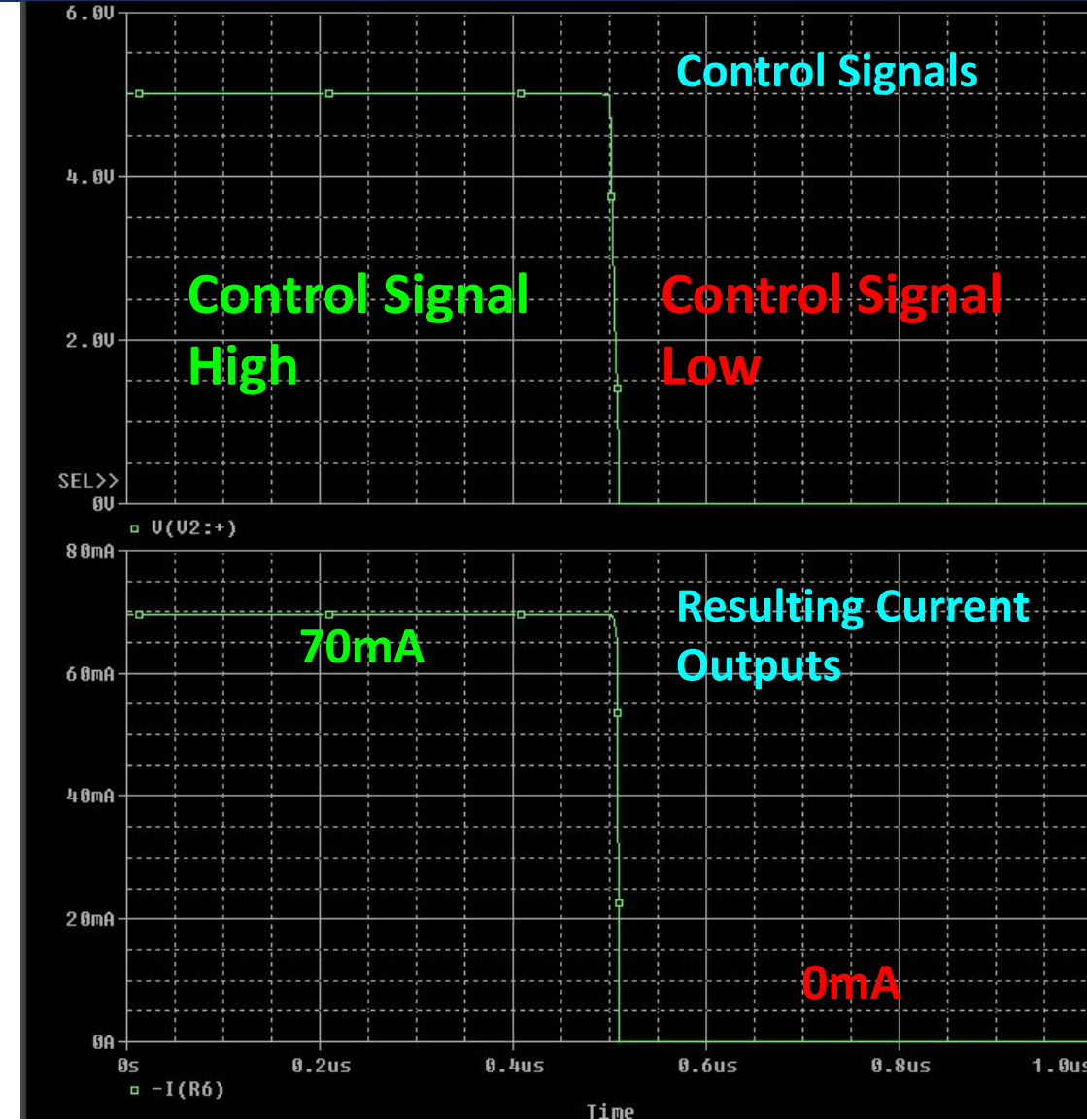
- NiCd Battery is recommended to charge with constant current rating that is 10% of the total capacity.
  - 700mAh with 70mA
- Solution: Constant current output configuration using LM317



# PCB Design: MCU Board

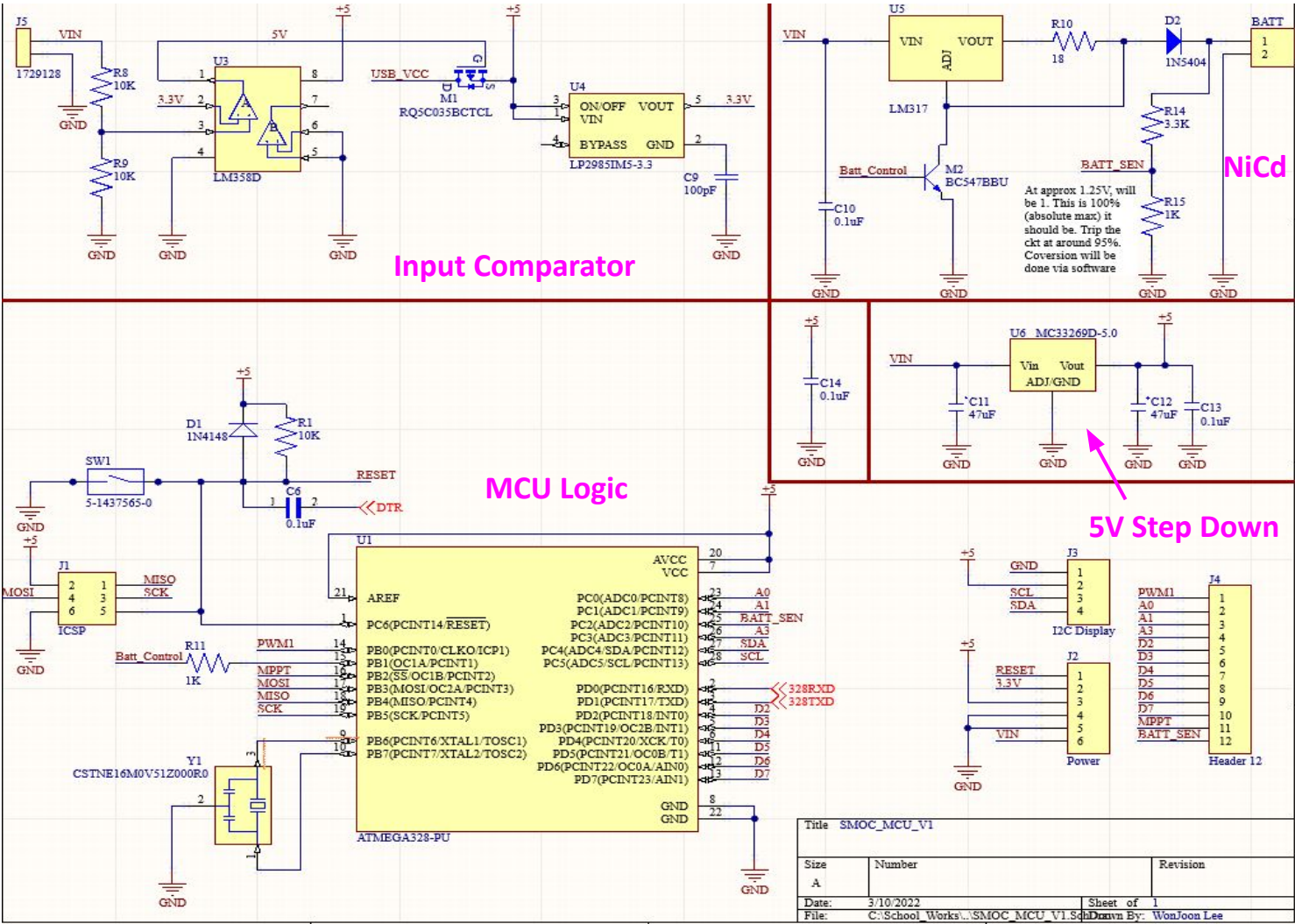


MCU Board Schematic

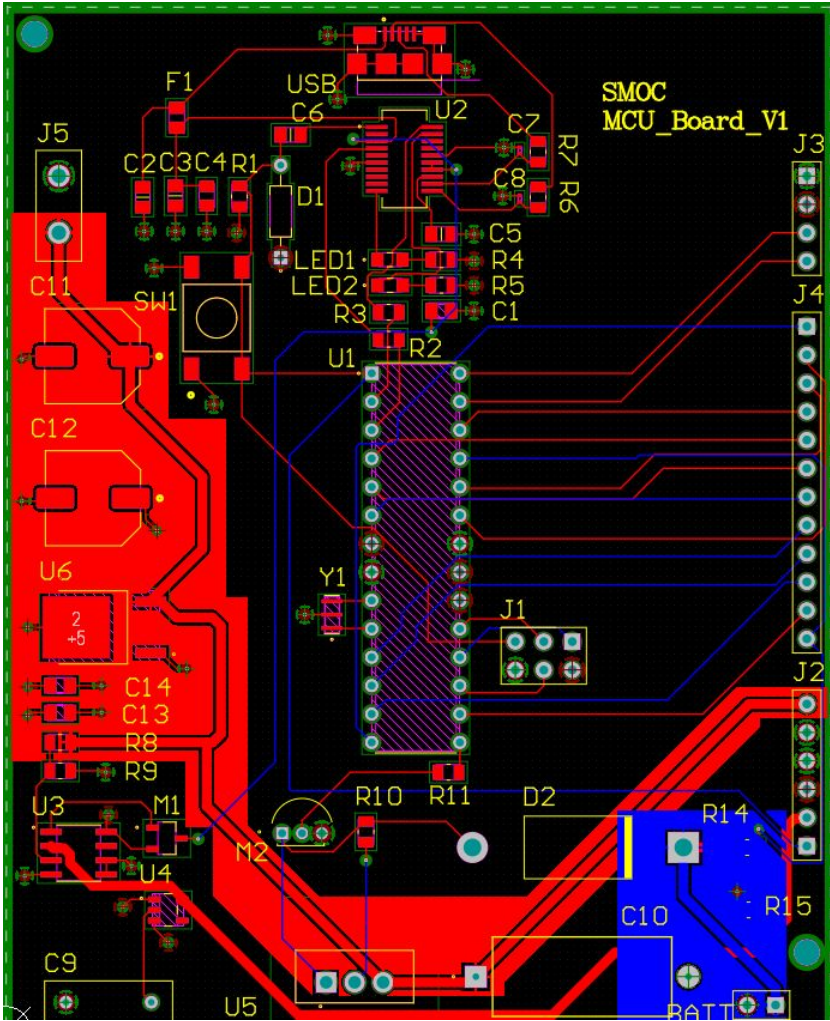


MCU Board Board Layout



# PCB Design: Power Board

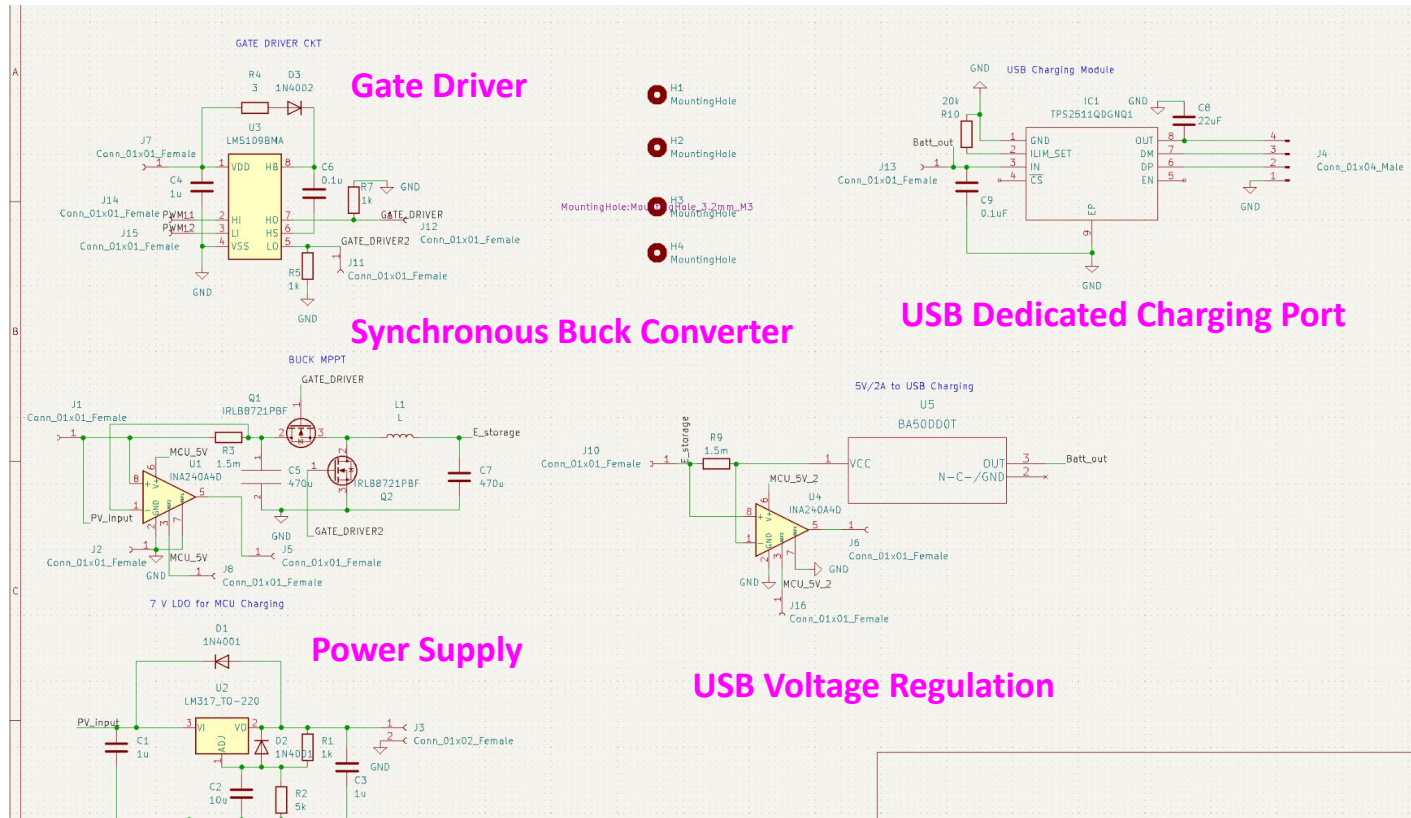


Power Board Schematic

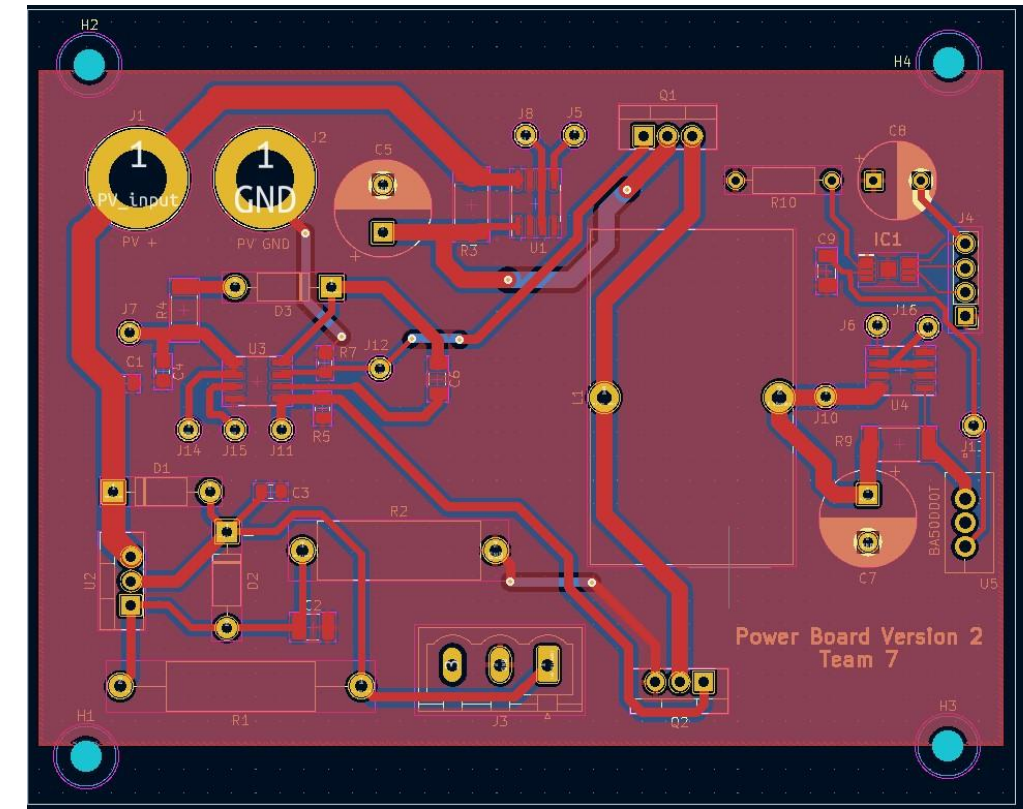

Power Board Layout

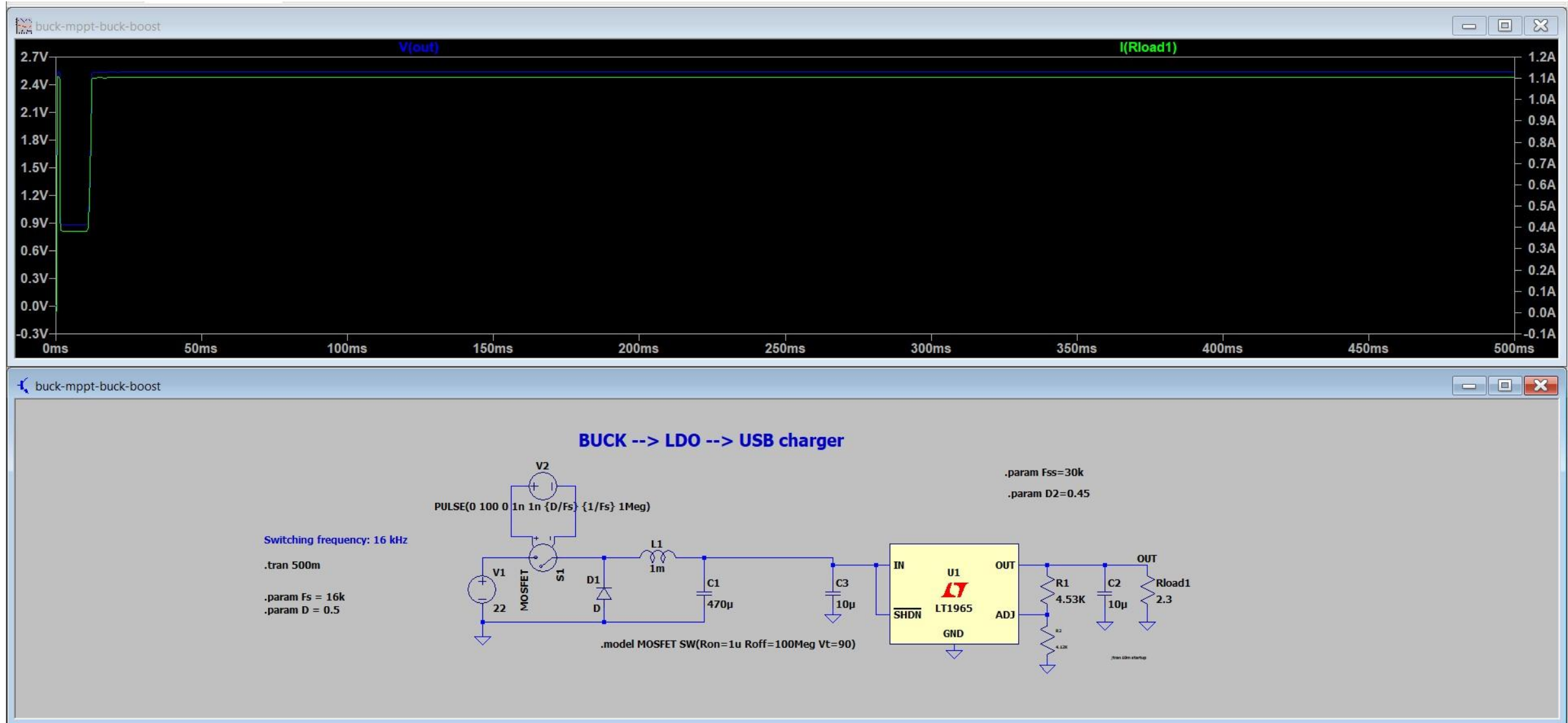
# Changes since Design Doc - Buck Converter Sizing






# Project Build and Testing




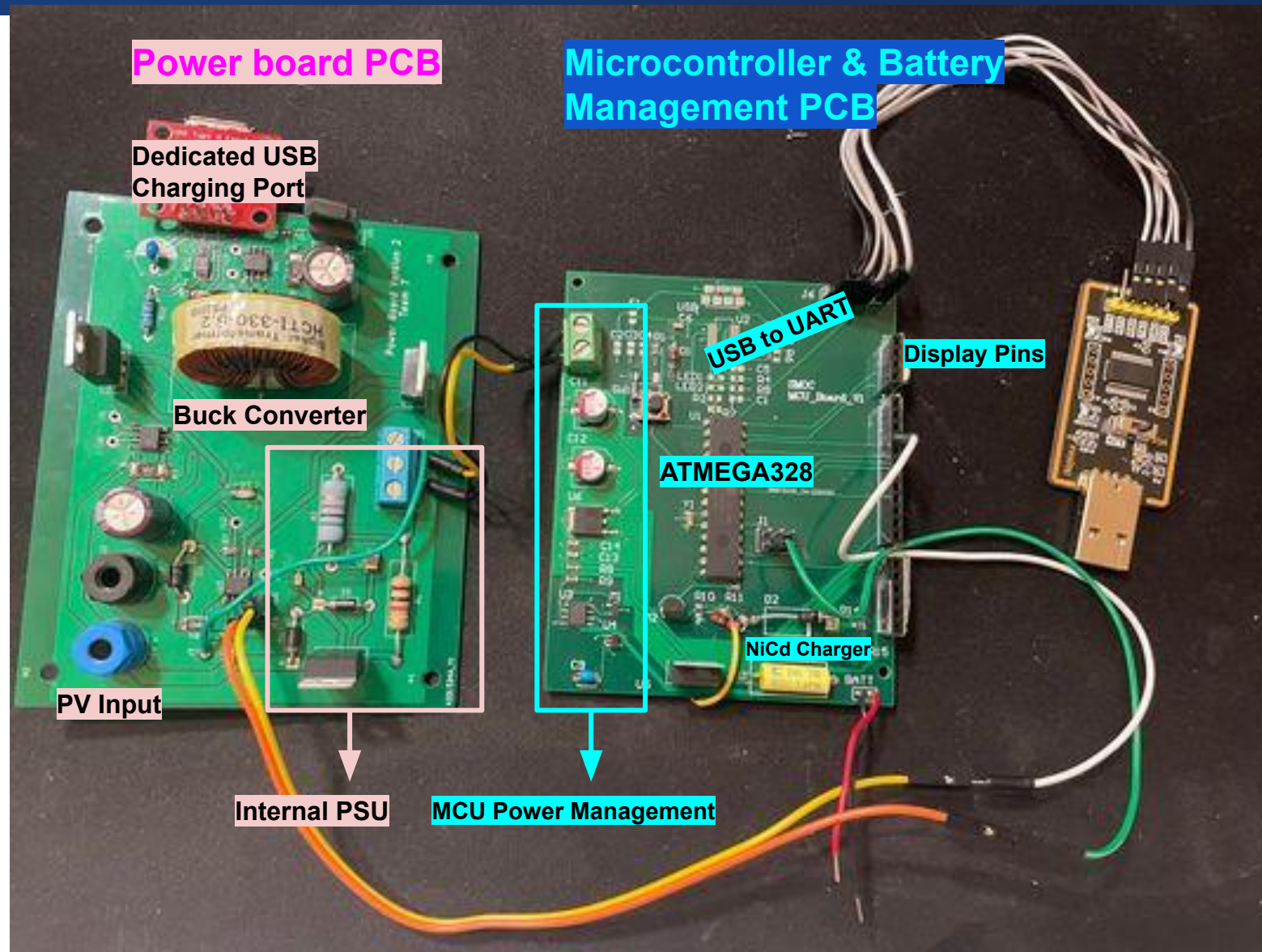

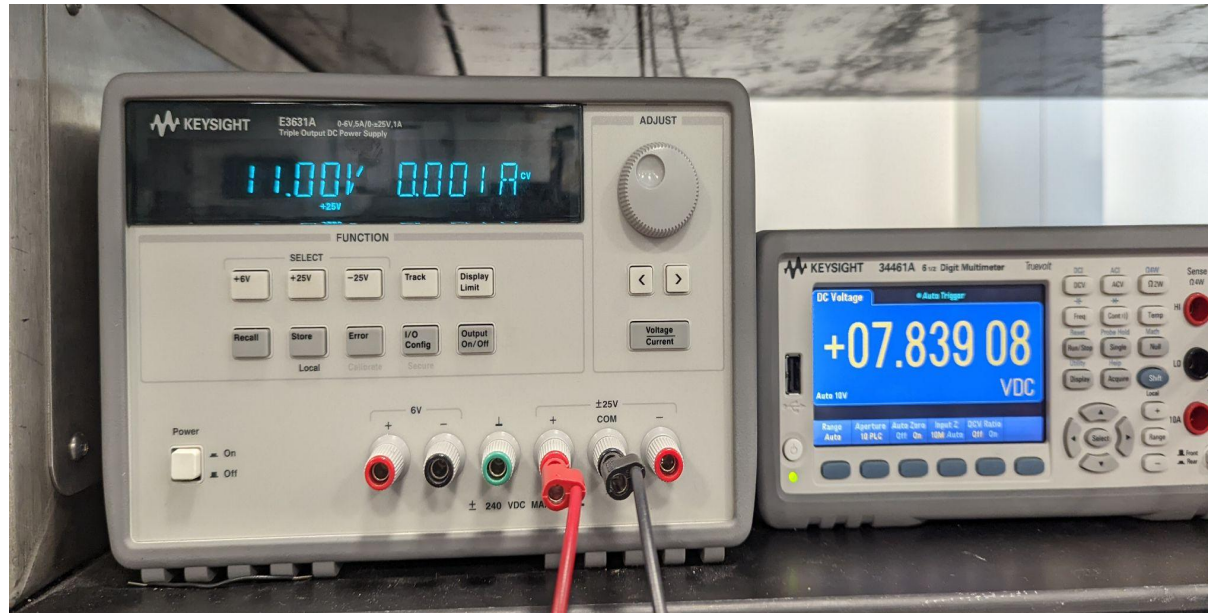Testing for internal power management and MCU board operation




Probed output for the MCU Board

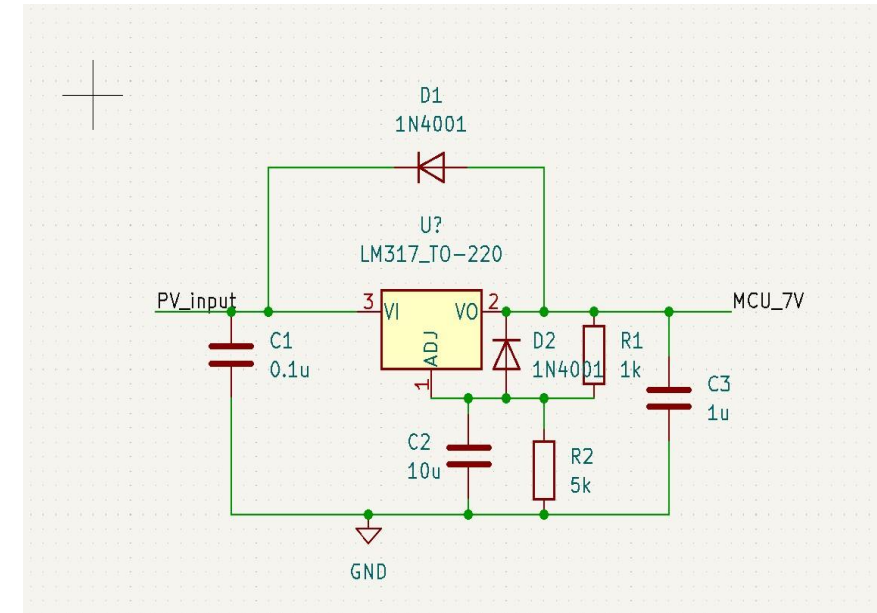


Schematic for Powering MCU

## PWM waveforms generated by MCU

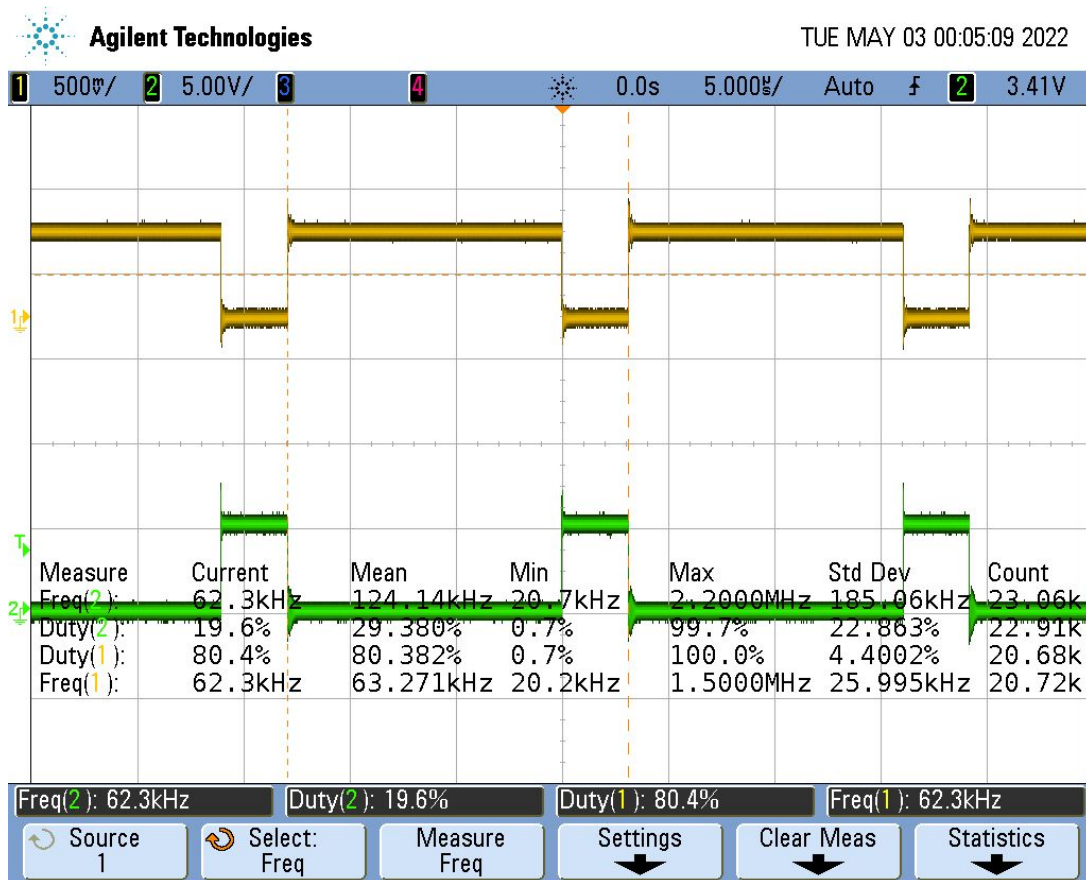

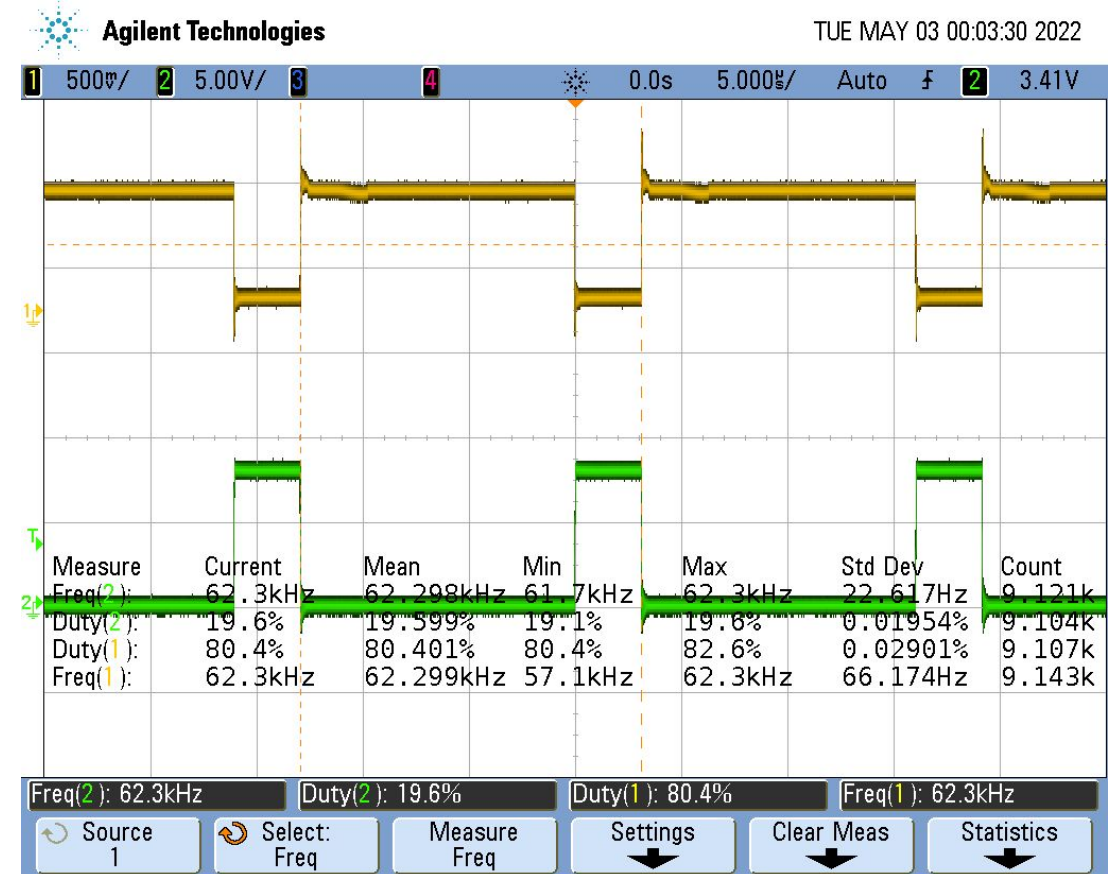Complimentary switching duty cycles from MCU




Output of the gate-drivers



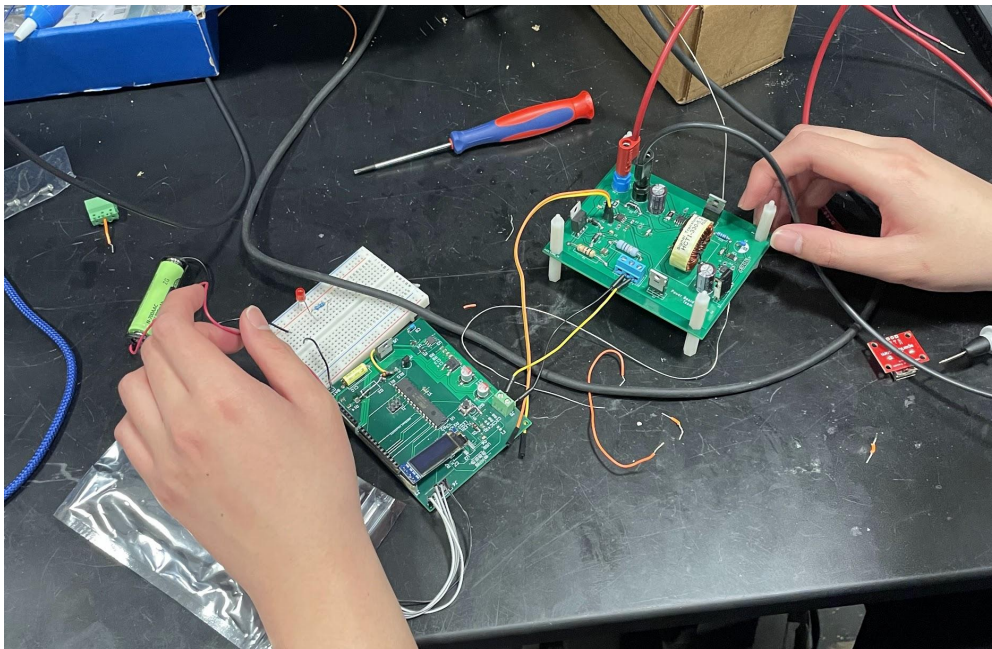
# Testing with Power Supply at Different Voltages



This test was done without the waveform generator to emulate a PV input. The MCU is providing the PWM signals to control the Buck-Converter.




Integration of both PCBs

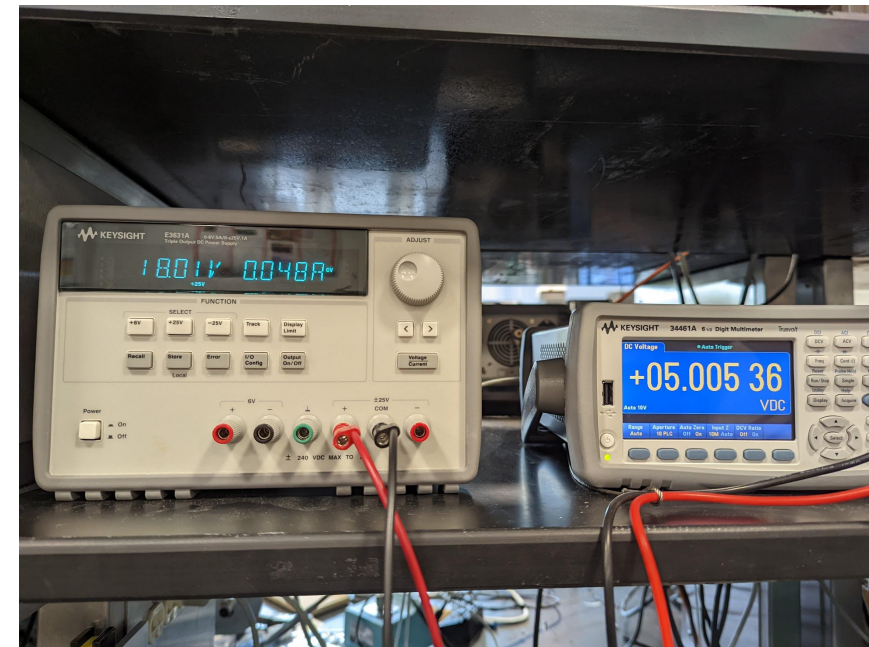


Testing USB  $V_{OUT}$  using PWM from MCU



# MCU Board Testing

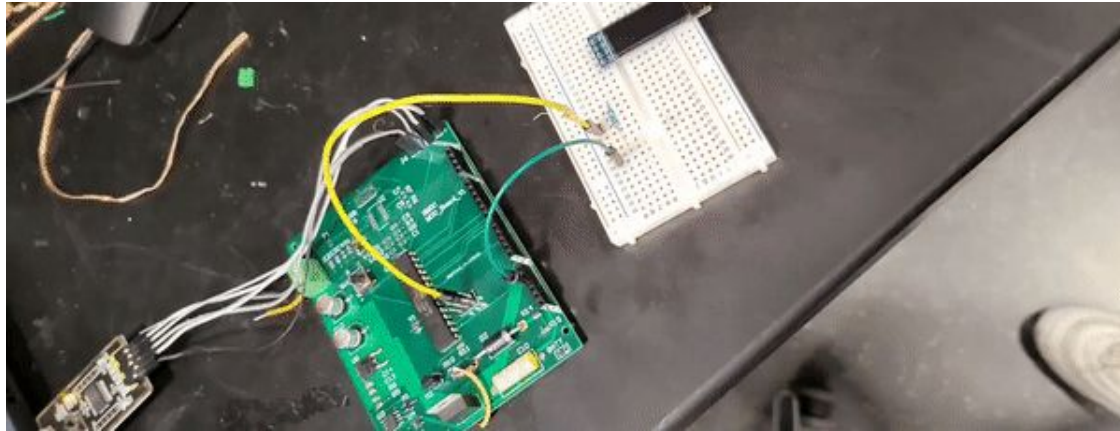

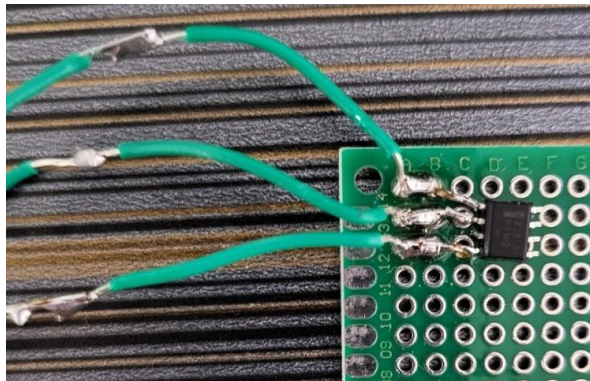
Bootloading and Programming Success of the MCU Board



MCU Board Power Logic Debugging and Testing



I2C Display Initialization

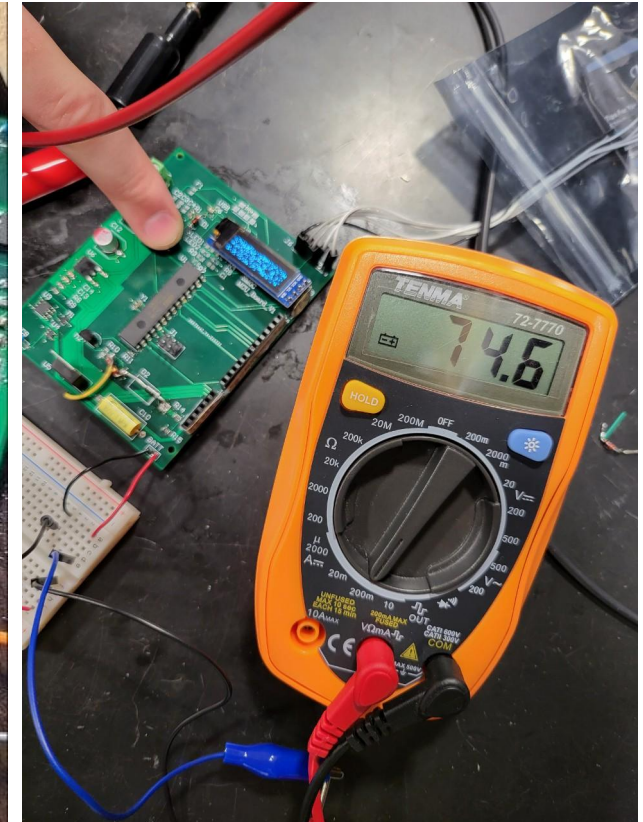

NiCd Charging Debugging

## Areas of Success

- Buck-Converter delivers 5V to a USB device
- INA240 Current Sensors to measure power
- Able to operate entirely off-grid
- USB dedicated charging port
- MCU detects voltage of NiCD batteries and provides 70mA when necessary
- LCD displays battery status and measurements for return of investment
- Functioning prototype that aggregates each subsystem into a single device








# Challenges

# USB to UART Chip Shortage



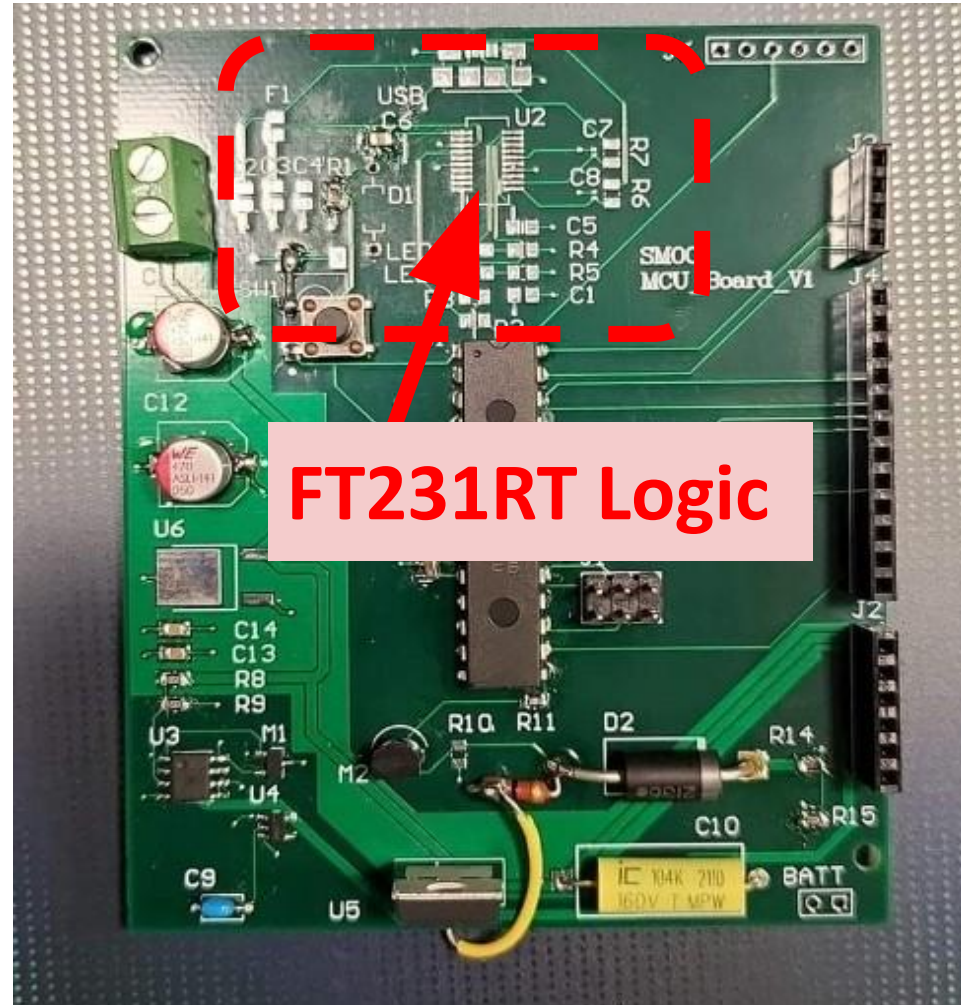
## USB Programmer Errata:

- USB to UART chips backordered
- Faulty over-the-shelf FT232 Product
- Missing convenient onboard capabilities



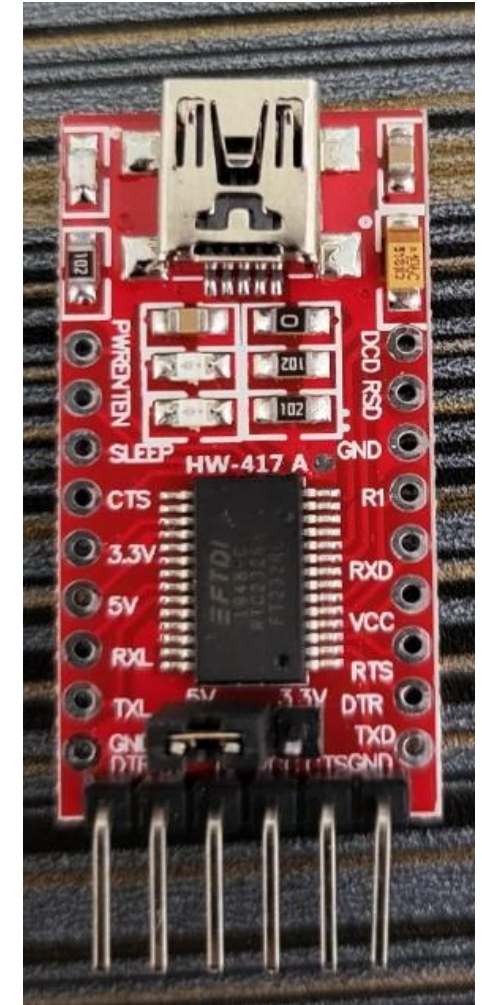
Onboard FT231RT USB to UART Programmer Logic




Faulty FT232 Chip

## Possible Sources of Error:

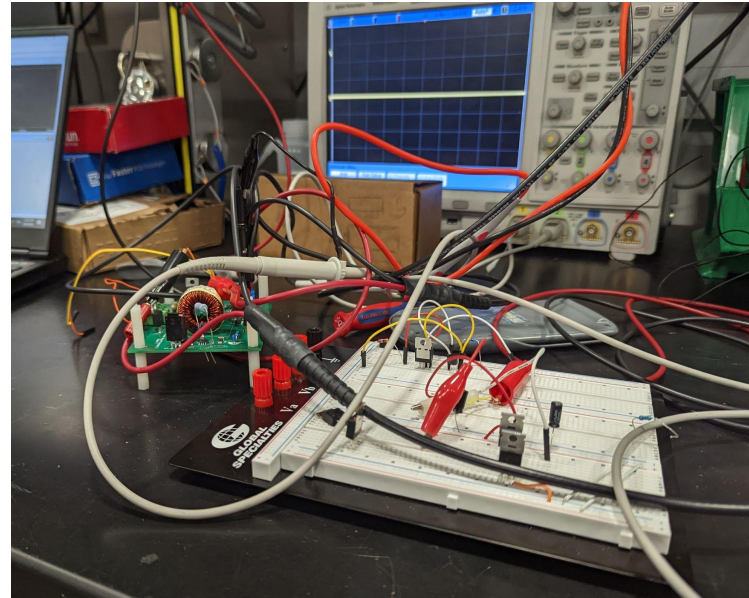1. Discontinuous Conduction Mode vs Continuous Conduction Mode
2. EMI Loop of PCB
3. ESR and ESL of Electrolytic Capacitors and Inductor
4. Errors within the bootstrap circuit



Buck converter on a breadboard

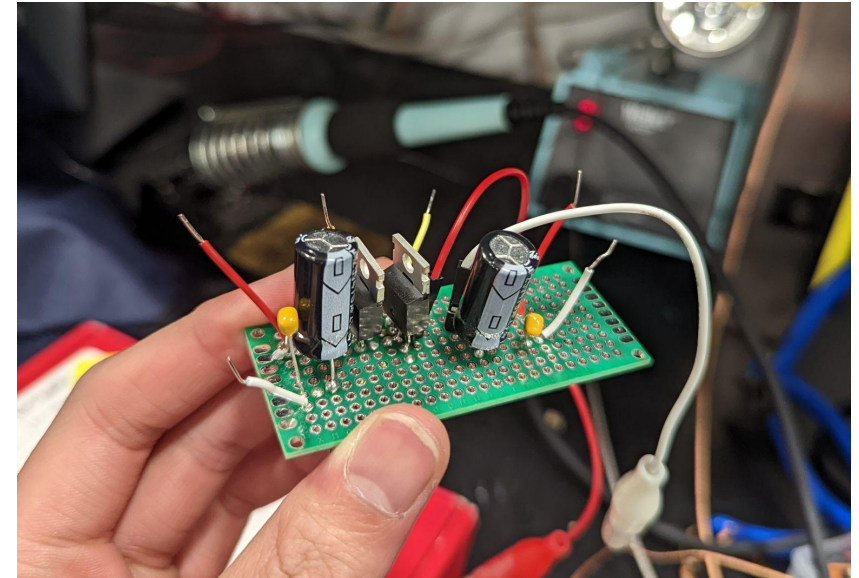


Buck converter on a perfboard

The exact cause of the buck converter not working can be attributed to these four factors



Buck Converter Non-Linearity for D=50%

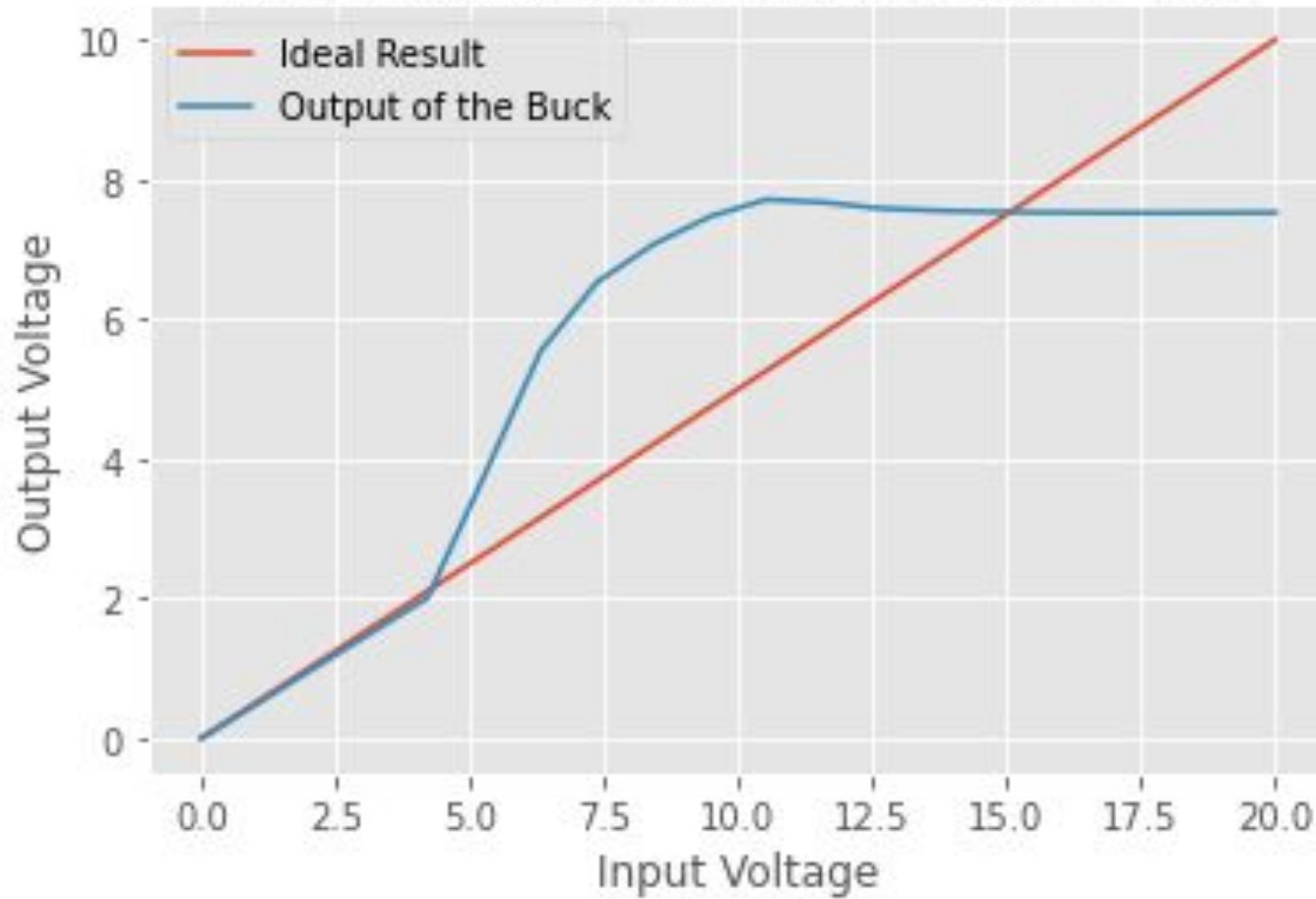



Buck Converter Gain:

$$V_{out} = DV_{in}$$


Buck converters can operate in two main modes:

- Continuous conduction mode (CCM)
- Discontinuous conduction mode (DCM)

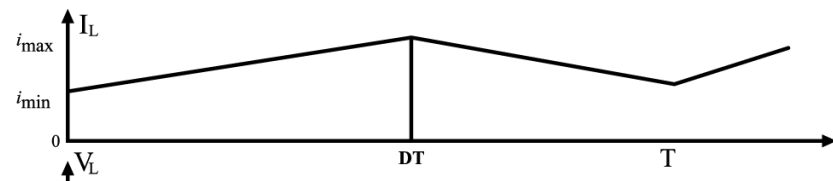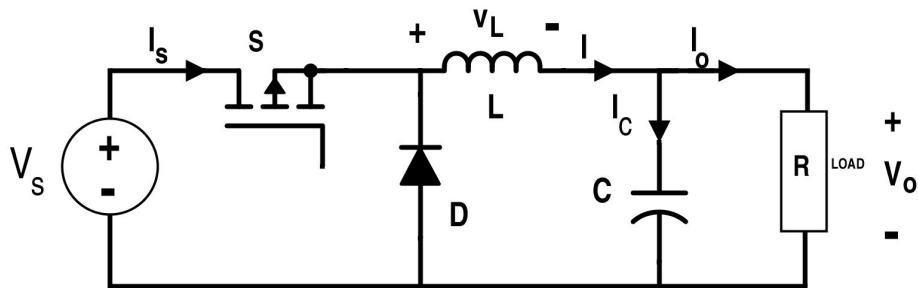If our inductors are selected at a too low of a value, the energy is not completely transferred from the inductor and thus DCM is observed.



Inductor current in CCM

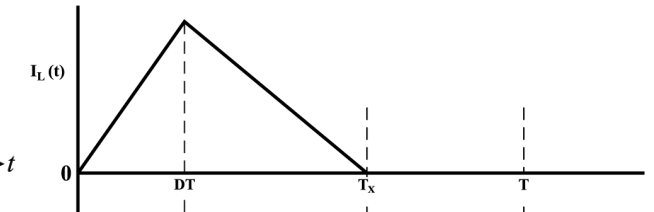

Inductor current in DCM

$$L_{CCM} = \frac{D(V_S - V_O)R}{2fV_O}$$

This affects the overall ripple voltage and DCM limits our current to low values.


Referenced from:

<https://www.allaboutcircuits.com/technical-articles/discontinuous-conduction-mode-of-simple-converters/>



# Further Work and Additional Ideas




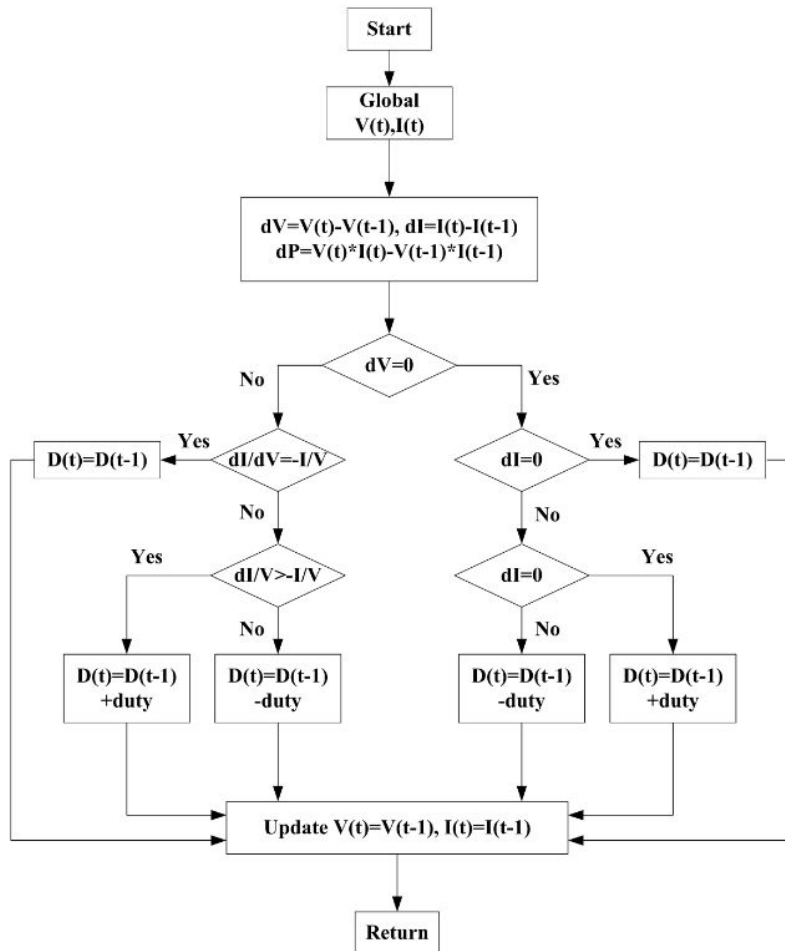

Algorithm flowchart [2]
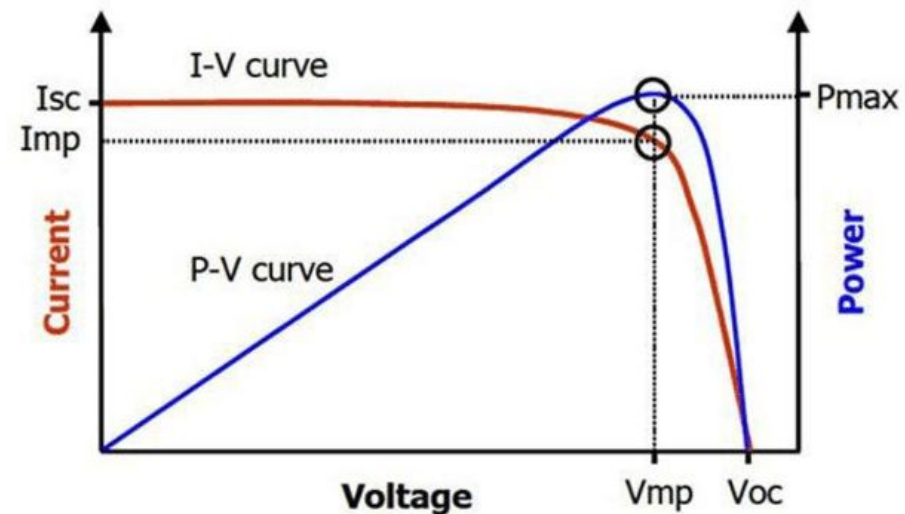
## Finish Implementation of Variable Step-size Incremental Conductance Algorithm


- This algorithm has high accuracy predicting the MPP.
- Calculates the derivative of power and adjusts duty cycle at each iteration.
- Variable step sizes leads to faster convergence.


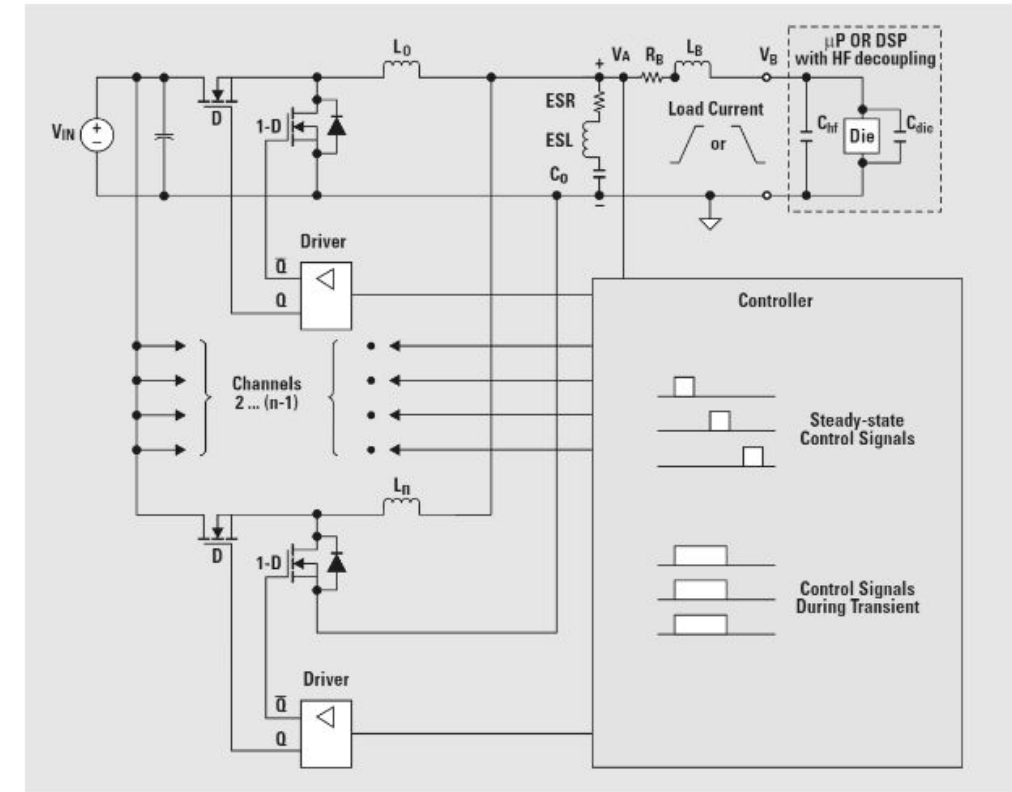
## Improving the DC-DC Converter Topology

- Synchronous Buck-Converter requires specific sizing to meet the voltage and current ripple tolerance.
- An interleaved Buck-Converter uses several stages to further limit the voltage and current ripple.
  - Requires more complex switching/control signals
  - Each stage is conducting in different intervals
- Tradeoff between efficiency and accuracy

*\*\* We could not utilize this topology with our choice of the ATMEGA328. This microcontroller cannot output more than two duty cycles that share the same clock/frequency.*



Example Schematic [3]

## Storing the Excess MPPT Power

- Implementation of additional storage units for low demand.
- Allowing for all day stable power supply.

## Control logic for supply of auxiliary power

- The additional power should be routed from auxiliary battery unit.

Current examples from industry:

- ESS - Energy Storage Systems → supplied by Huawei, Eaton, Samsung, Sungrow etc.
- Lithium Ion Batteries.







# Conclusions and Learning Points

## Takeaways from our Project

- The most significant aspect of our project was learning PCB design
- Unit testing of each circuit
- Integrating two PCBs into one device/system
- Identifying tolerances and design constraints
- Battery safety and ethics

## Final Thoughts

- Our largest challenge was finding compatible parts and navigating manufacturing delays
- Needed more time to test with the solar panel
- Successfully met most of our R&Vs





Thank you for your time, if you have any questions you can reach out to us!



Kanin Tangchartsiri  
*kanint2@illinois.edu*

<https://www.linkedin.com/in/kanintang/>



Lukas Gollings  
*lwg2@illinois.edu*

<https://www.linkedin.com/in/lukas-gollings-8b0260206/>



Wonjoon Lee  
*wonjoon2@illinois.edu*

<https://www.linkedin.com/in/wonjoon2000/>



# The Grainger College of Engineering

UNIVERSITY OF ILLINOIS URBANA-CHAMPAIGN

# References



- [1] “World Campus alerts aim to provide assurance to students during natural disaster | Penn State University,” *www.psu.edu*.  
<https://www.psu.edu/news/world-campus/story/world-campus-alerts-aim-provide-assurance-students-during-natural-disaster/> (accessed Apr. 29, 2022).
- [2] T. Instruments, “Mppt charge controller reference design for 12-v, 24-v and 48-v solar panels,” accessed: 2022-3-14.
- [3] H.-T. Yau, Q.-C. Liang, and C.-T. Hsieh, “Maximum power point tracking and optimal li-ion battery charging control for photovoltaic charging system,” *Comput. Math. Appl.*, vol. 64, no. 5, pp. 822–832, 2012.