



# Educational Wind Powered Charger

ECE 445 / Group 23

Zixi Li

Lingxiao Mou

María Carrallo

05/03/2022

# Purpose & Problems to Solve

1. **Green Energy Education.** Educate people about the importance of green energy and realize that the use green energy can be started from small steps.
2. **Scarce electricity in remote area.** Provide an alternative portable power source for cyclists interested in remote areas where electricity is scarce or absent. Provide charges to portable electronic devices such as GPS or phones.

## Design Objective

- Make a portable, inexpensive, easy-to-use bike-mounted wind turbine
- Efficient wind power harvest system from riding
- Provide charging capabilities to portable devices through a USB port.

## Uniqueness

- No commercial alternatives.
- Ideas exists, but none of them focuses on efficiency or power storage.
- Most designs are composed a simple turbine, a diode and a USB power module.

## High-Level Requirements

**Portable Blade and Rotor System:** The system is easily removable by the user with the use of common bike maintenance tools.

**The system is able to charge a phone:** The system should provide sufficient output power to a phone.

**The entire system's width must not exceed 40 cm:** We do not want our wind turbine to be too large in diameter, which might disturb view of riders.




## Main Components

The design will consist of three main components:

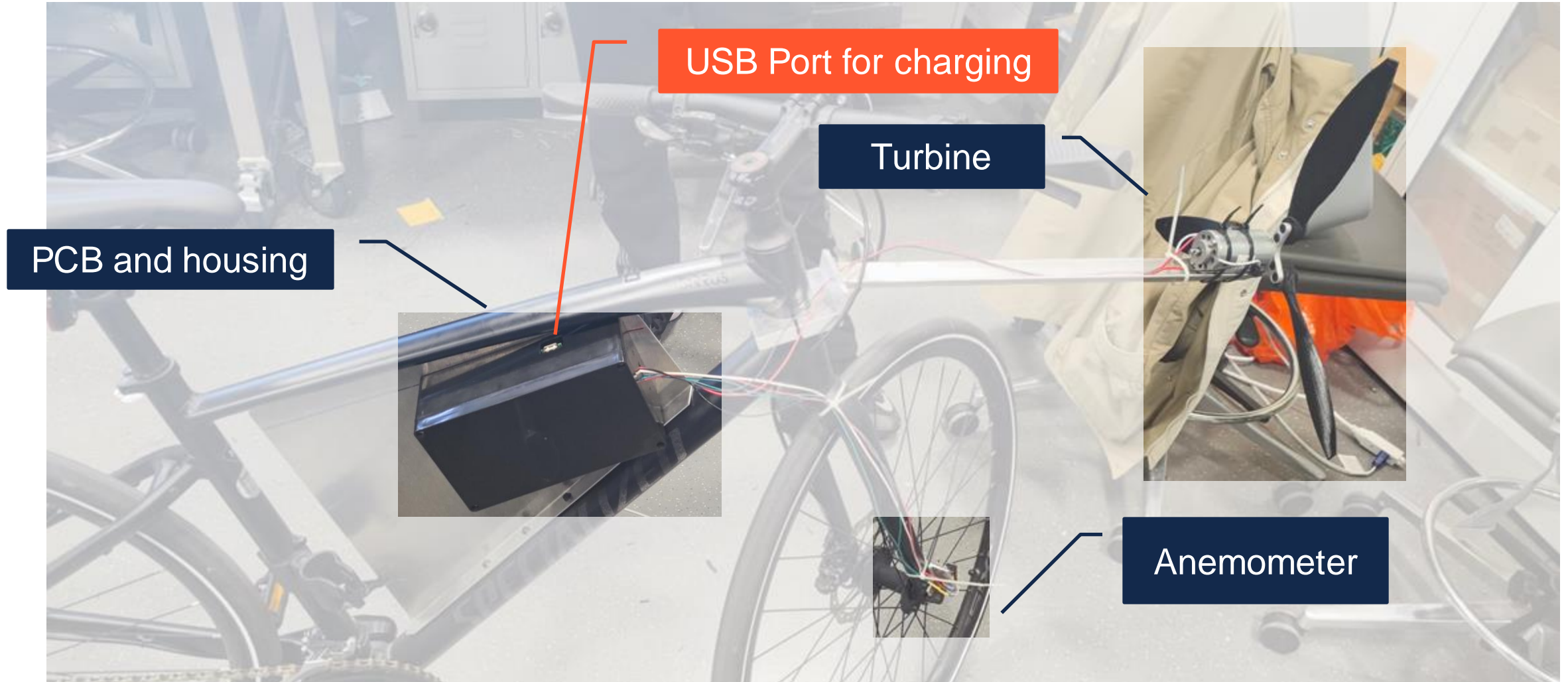
- 1. A wind turbine mounted at the front of the bike.** This is the main power input to the system. Power is harvested from the turbine and delivered to the PCB.
- 2. An anemometer mounted on the frame of the bike.** The anemometer provides information to a microcontroller, that dictates the best operating voltage of the fan and adjust the input accordingly.
- 3. PCB.** This PCB houses all the circuitry, including DC-DC converters, microcontroller and battery (shown on following slides)







<https://youtu.be/V-zmpaJNkLA>

# Design: Block Diagram

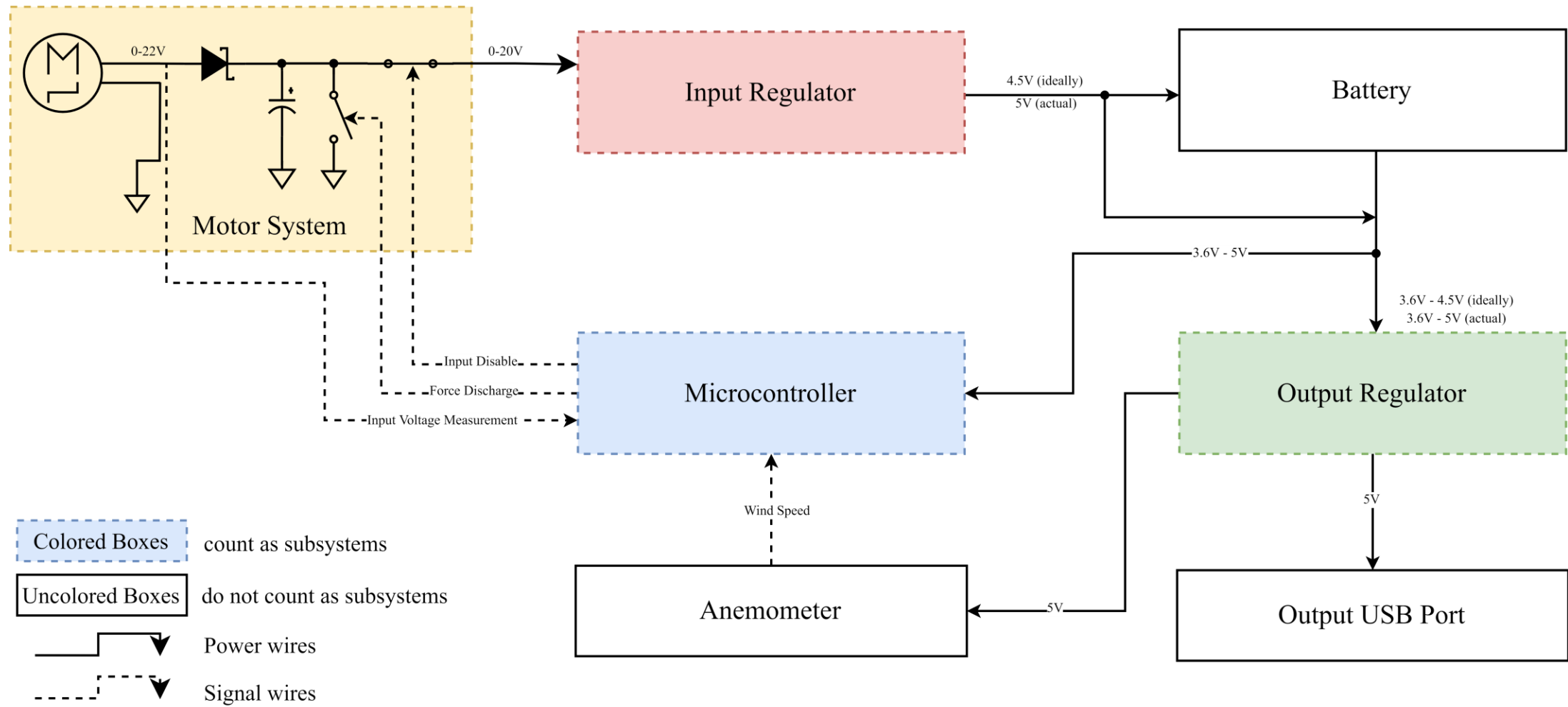



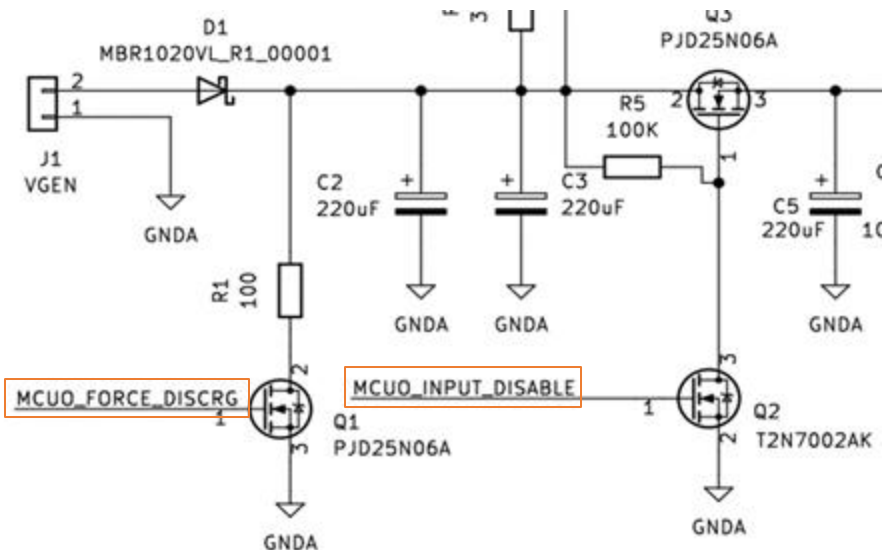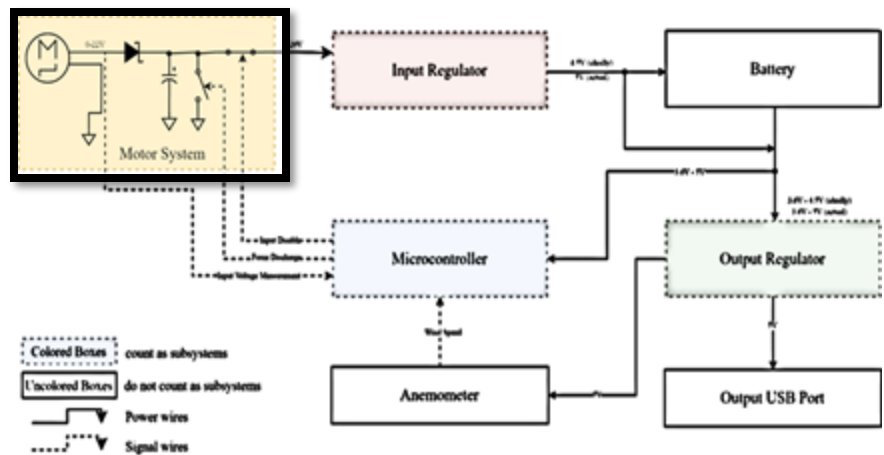

## Motor Subsystem



The motor subsystem takes the power input from the motor and buffers it, reducing voltage fluctuation and preventing damage to the circuit when motor is spinning in reverse.

It also accepts two control signals from the MCU that could:

1. Disconnect the motor from the system so no current is drawn.
2. Forcefully draw a large current from the motor and slow it down.
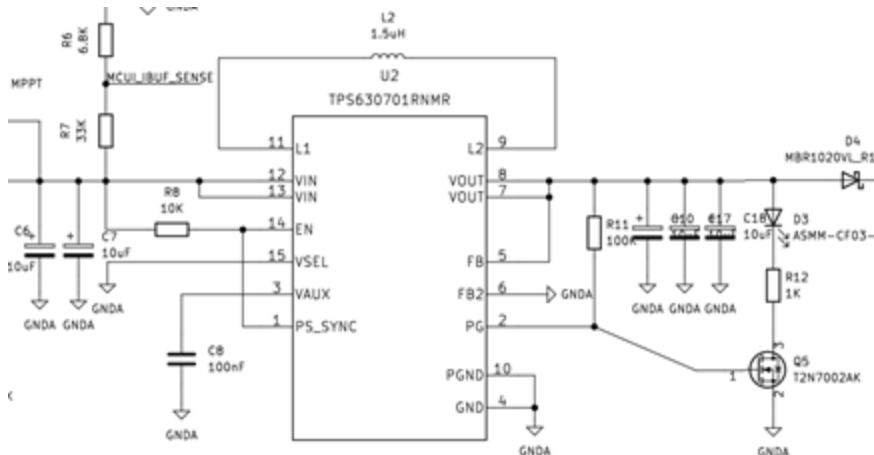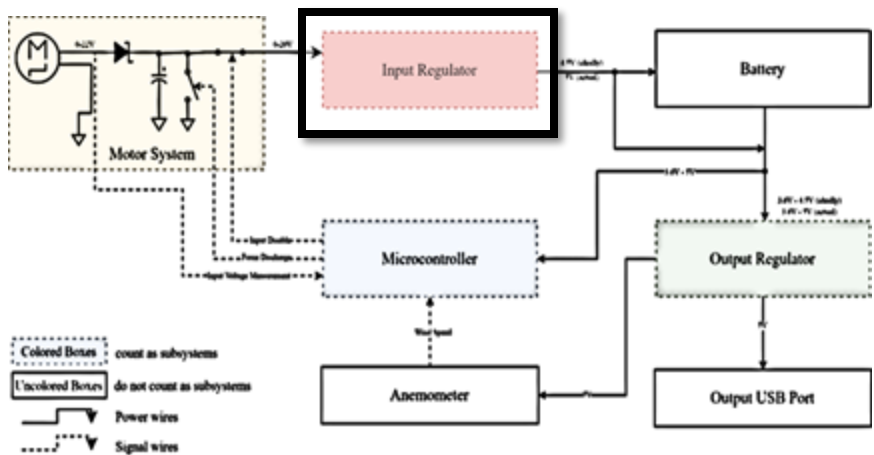
## I/O Description

It takes a fluctuating voltage around 0-20V from the motor, and outputs a less fluctuating 0-20V to the following stages.





## Input Regulator

The input regulator operates when the input voltage is greater than 2V, and outputs 5V, suitable for charging the battery.

When the output is clamped to battery voltage (3.7 – 4.2V), the regulator operates like a current source.
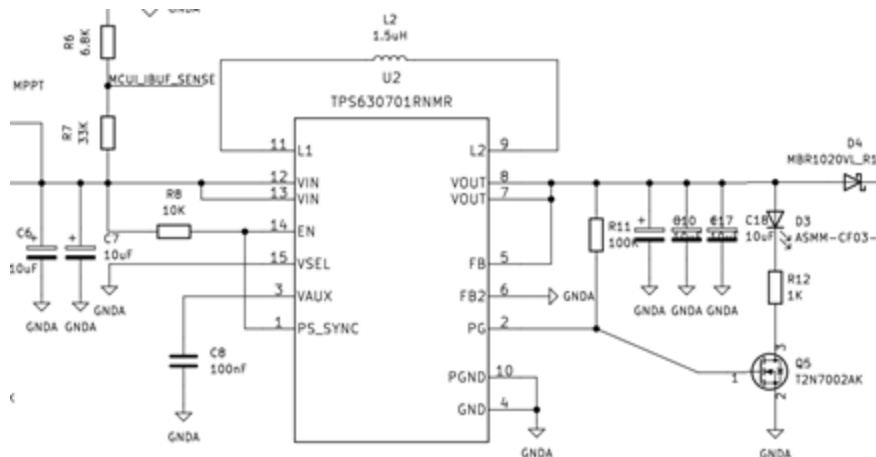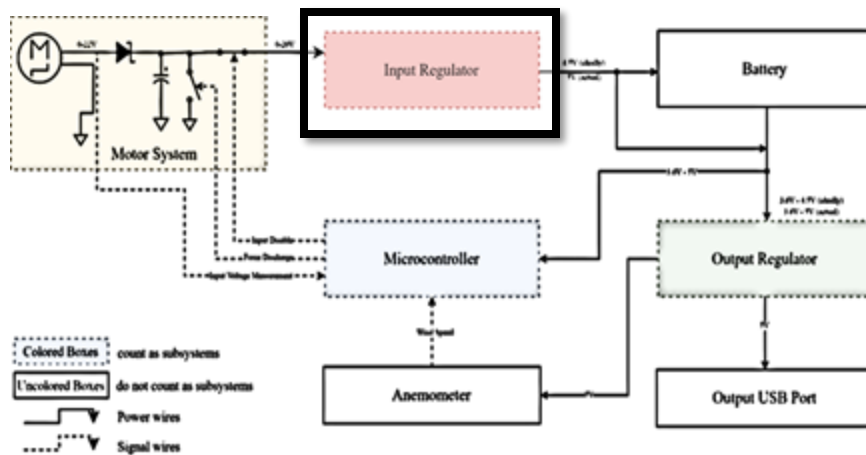
## I/O Description

The block takes an input of 0-20V and converts it into a constant 5V output.




## Difficulties of design

The input voltage range is wide, so the regulator hardware must be designed to perform both step-up and step-down conversions.

Efficiency is also important since the input power is not very high from the beginning.
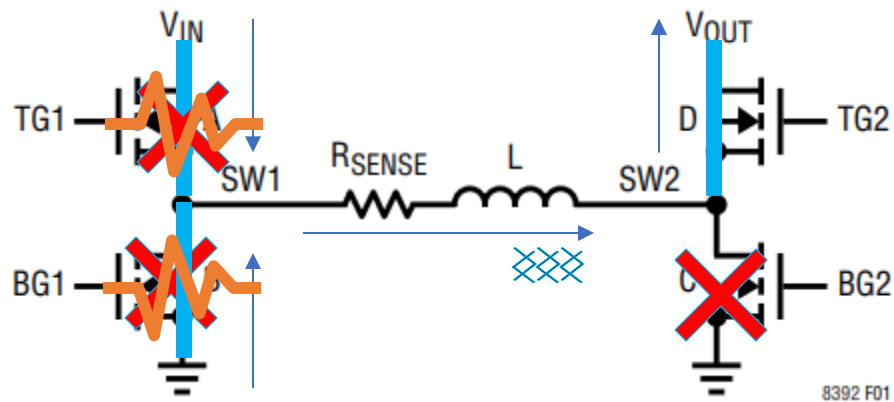
## Design Choice: Buck-Boost architecture



**Stepping down ( $V_{IN} > V_{OUT}$ )**

**Phase 1: A & D turned on,  $I_L$  increases**


**Phase 2: B & D turned on,  $I_L$  decreases**

**... and the cycle repeats.**


The duty cycle is controlled by comparators in the IC.

When output gets lower than  $V_{OUT} - V_{ripple}$ , goes into Phase 1.

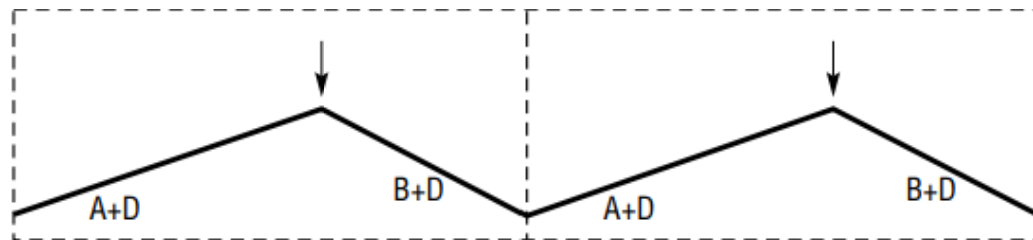When output gets higher than  $V_{OUT} + V_{ripple}$ , goes into Phase 2.



Diagrams from LT8392 datasheet

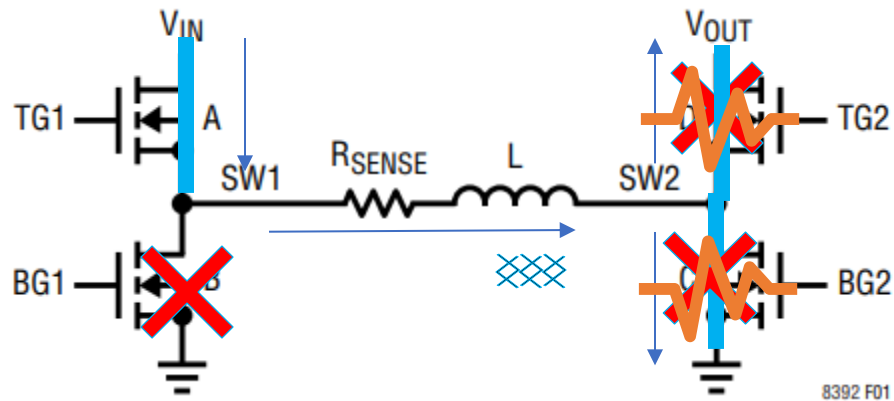


**Stepping up ( $V_{IN} < V_{OUT}$ )**

**Phase 1: A & C turned on,  $I_L$  increases**

**Phase 2: A & D turned on,  $I_L$  decreases**

**... and the cycle repeats.**

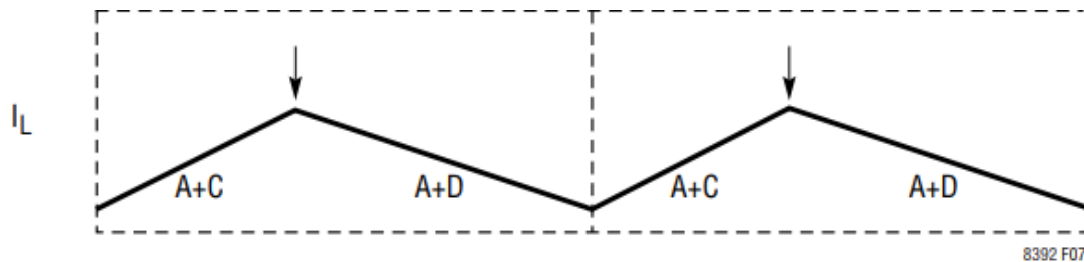


Diagrams from LT8392 datasheet

The duty cycle is controlled by comparators in the IC.


When output gets lower than  $V_{OUT} - V_{ripple}$ , goes into Phase 1.

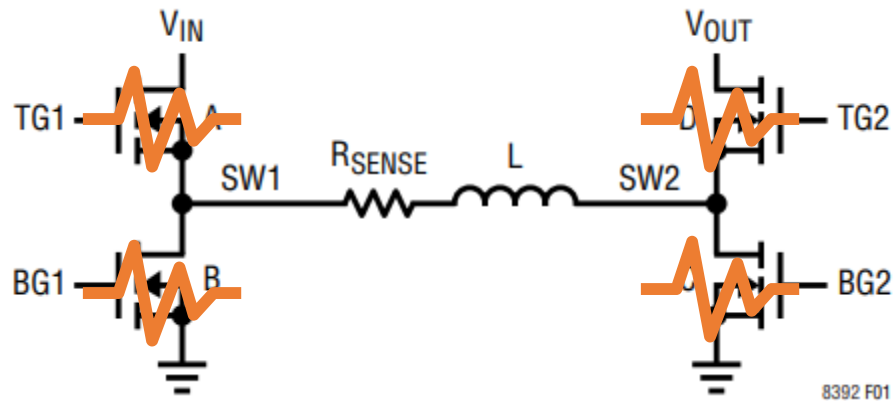When output gets higher than  $V_{OUT} + V_{ripple}$ , goes into Phase 2.



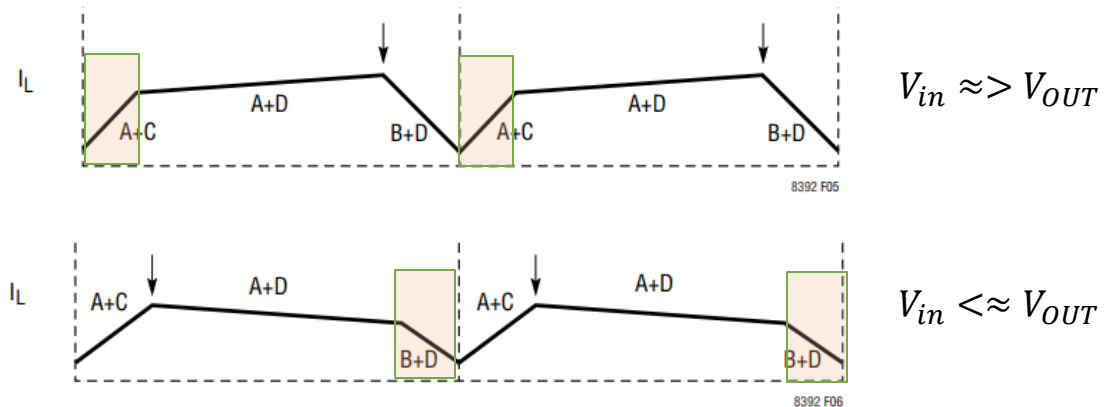
## Hybrid buck-boost ( $V_{IN} \approx V_{OUT}$ )

Depends on individual optimization, not talked about here.



Diagrams from LT8392 datasheet



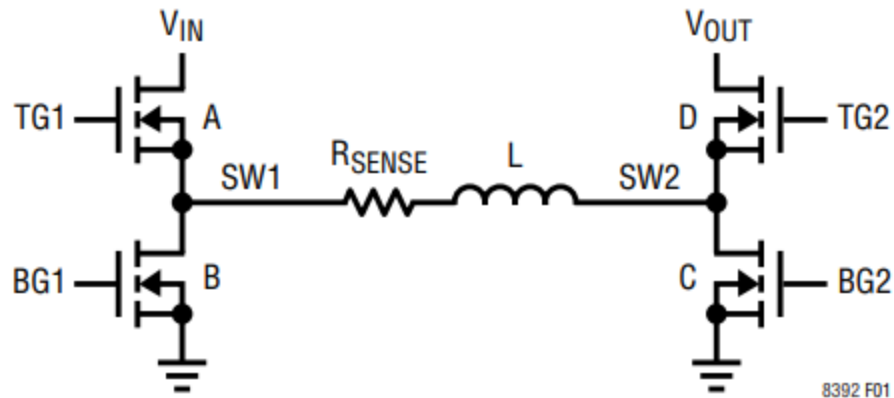

## Advantages:

- 1. Wide Input Voltage Range.** Input voltage depends on the specifications of chosen MOSFETs, and since it can either step-up or down, input voltage is less limited by output voltage.
- 2. Configurable quiescent current and high/low-power preference.** Quiescent current depends on switching frequency and MOSFET gate charge, linear to  $f_{switch} \times (\Sigma Q_c)$ . Output current depends on MOSFET  $I_{DS}$  and  $R_{DS}$ .

## Disadvantages:

- 1. Complicated Control Logic.** Four MOSFETs has to be driven, and the top gates (TG1 and TG2) has to be biased with the voltages at SW1 and SW2, requiring a charge pump to provide gate signals.
- 2. Too much hardware.** Large amount of hardware increases cost.

The diagram illustrates the internal architecture of the UCC28950 converter, enclosed in a dashed box. Key components and their connections are as follows:


- Power Stage:** A blue-outlined box at the top contains the power MOSFETs and diodes. It is connected to **VIN** and **VOUT**. The MOSFET gates are driven by the **Gate Control** block, which also receives **VIN**, **VAUX**, and **VOUT** inputs. The MOSFET sources are connected to **PGND**.
- Bias Regulator:** A block that takes **VIN** and **VOUT** as inputs and provides **VAUX** to the **Gate Control** and **Modulator** blocks.
- Current Sensor:** A block that monitors the output current and provides feedback to the **Modulator**.
- Control Loop:** The **Modulator** block receives **VAUX** and feedback from the **Current Sensor**. Its output goes to the non-inverting input (+) of the first op-amp. The inverting input (-) of the first op-amp is connected to **FB**. The output of the first op-amp drives the non-inverting input (+) of the second op-amp. The inverting input (-) of the second op-amp is connected to **FB2** and a **VREF** source. The output of the second op-amp drives the **Gate Control** block.
- Device Control:** A large block that manages the converter's operation. It receives external inputs: **PS/SYNC**, **EN**, **VSEL**, and **GND**. It provides **PG** to the **Modulator** and **Oscillator** blocks. It also interfaces with the **Temperature Protection** block.
- Other Connections:**
  - PGND** is the common ground for the power stage, feedback network, and device control.
  - The **Oscillator** block provides a timing signal to the **Modulator**.

Copyright © 2016, Texas Instruments Incorporated


We chose an IC with integrated MOSFETs. It is designed for lower powered electronics, has a low quiescent current and requires fewer external components.

This IC is also cheap.

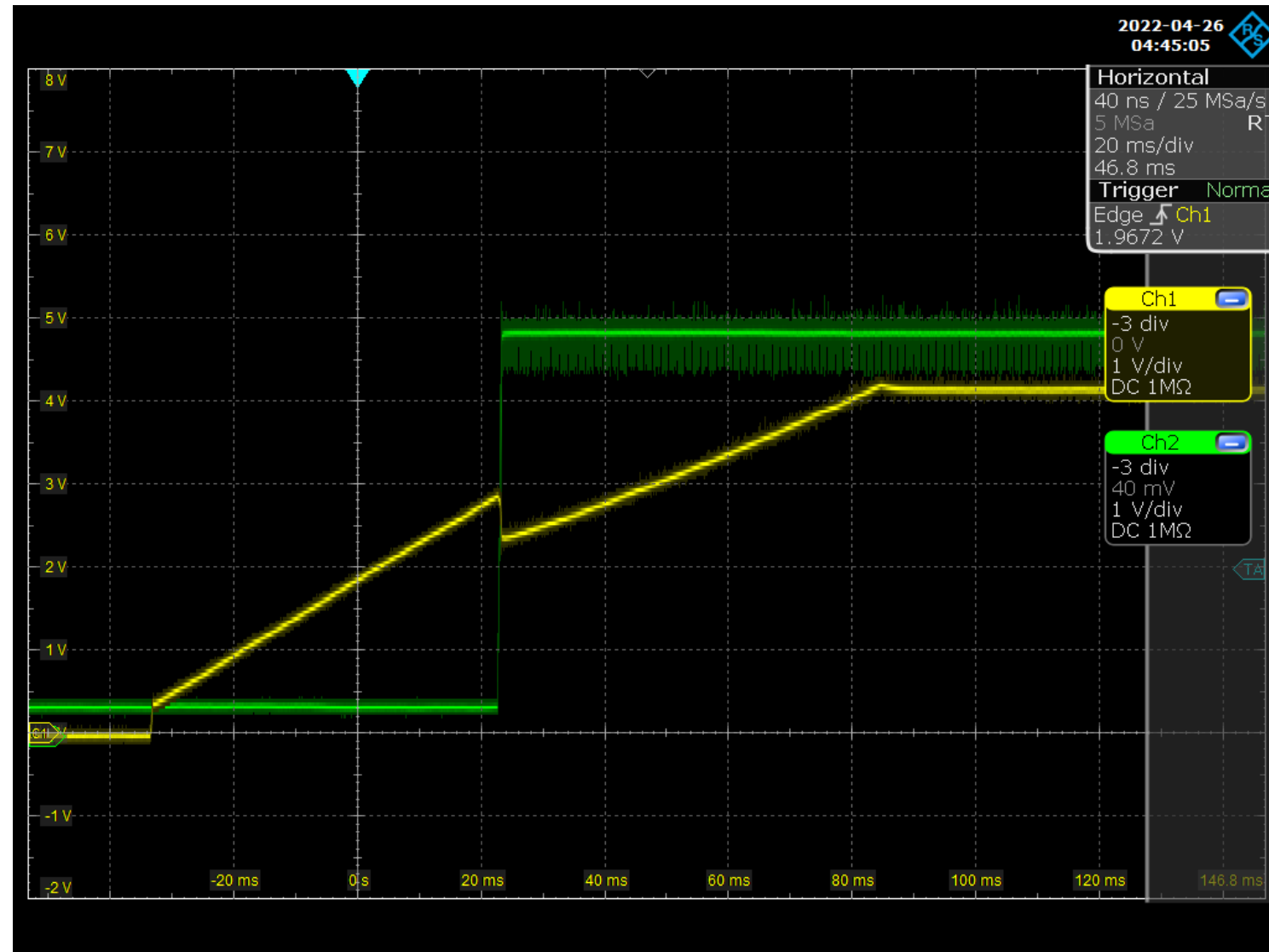
# Testing: Input Regulator – Start-up performance



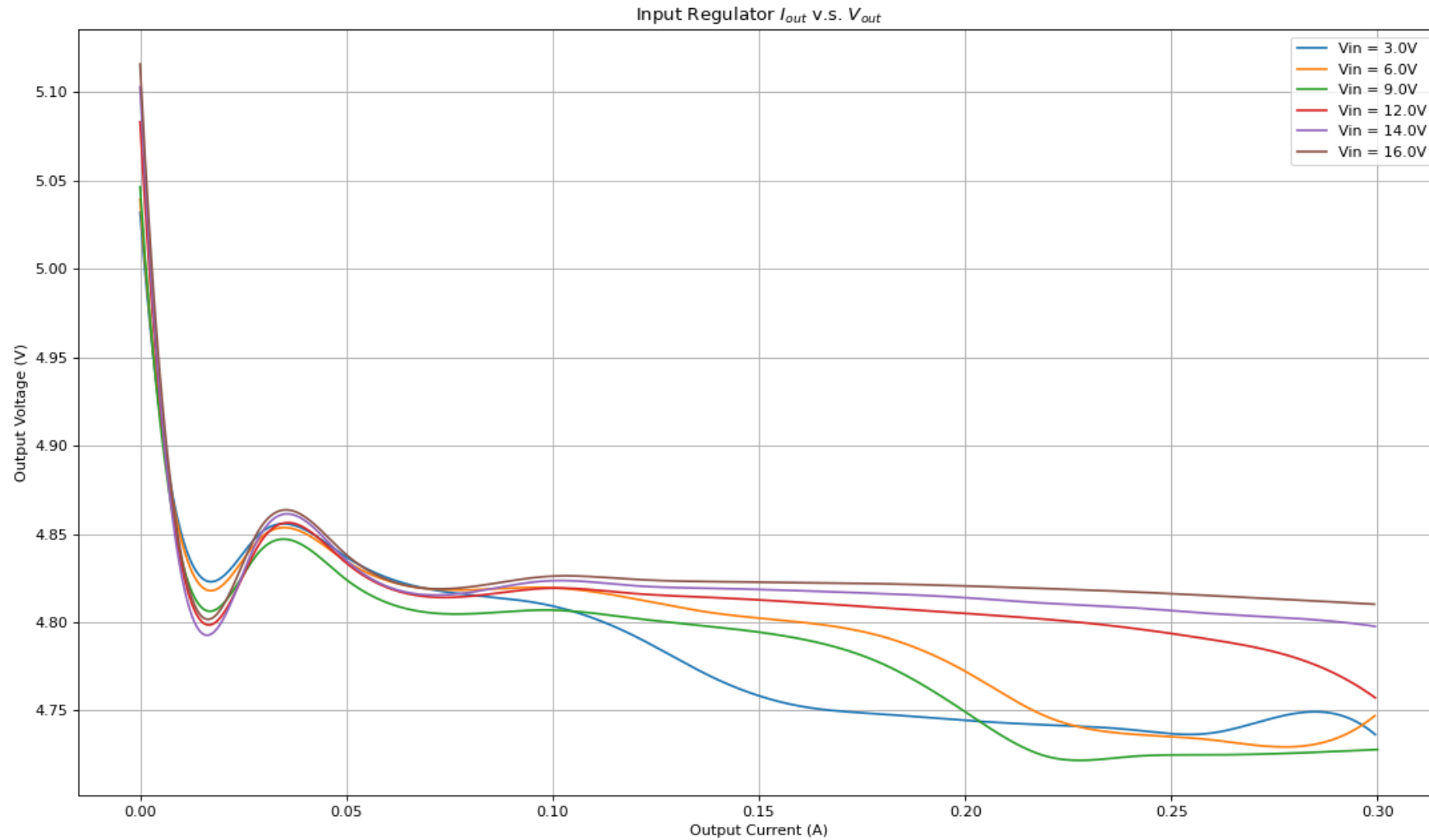
# Testing: Input Regulator – Voltage Drop




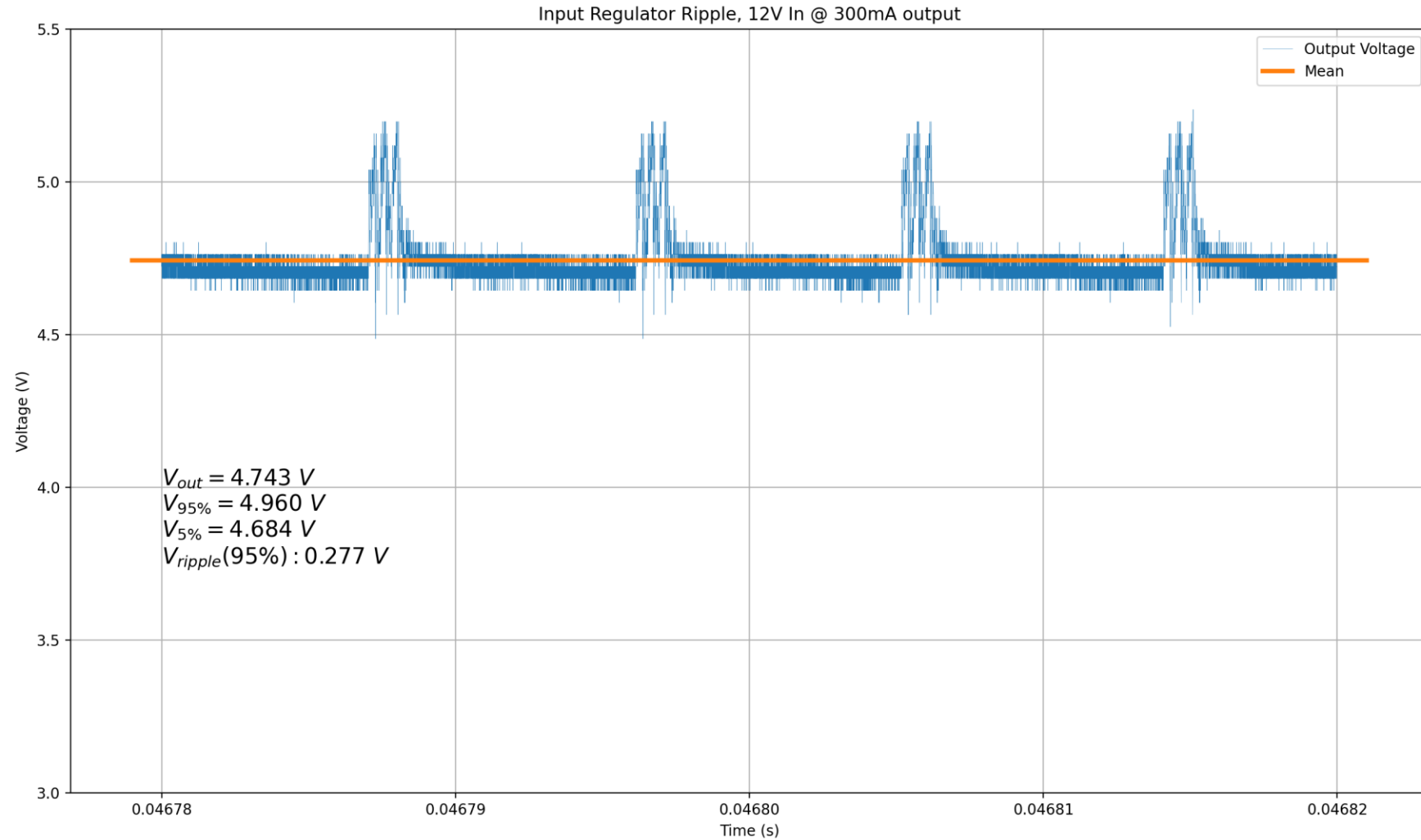
# Testing: Input Regulator – Voltage Drop


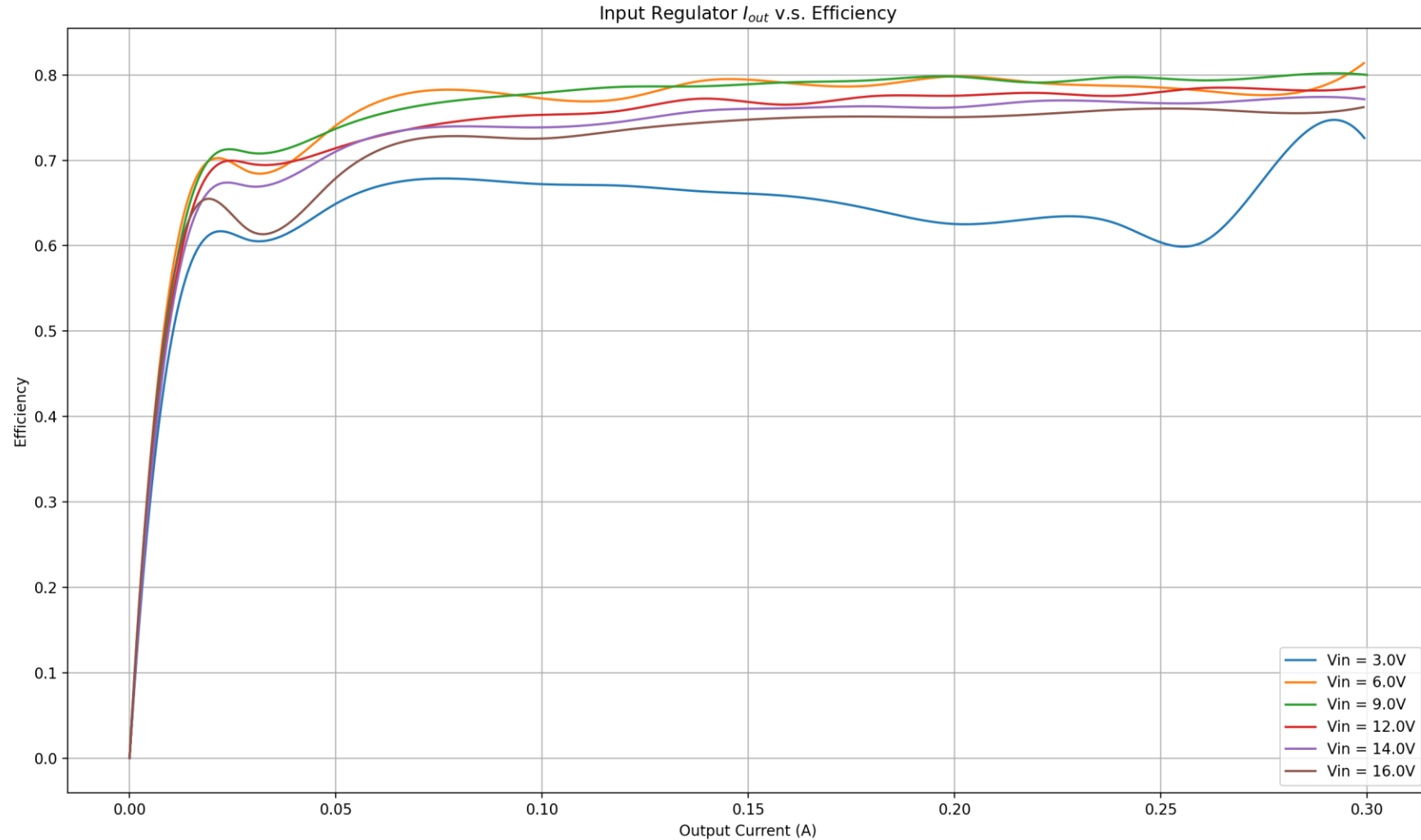
# Testing: Input Regulator – Voltage Drop





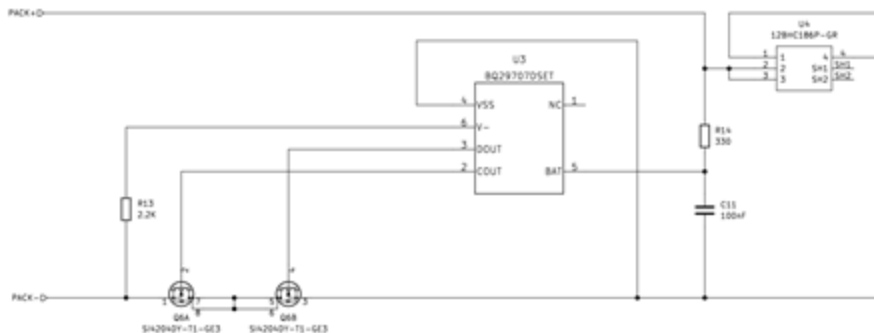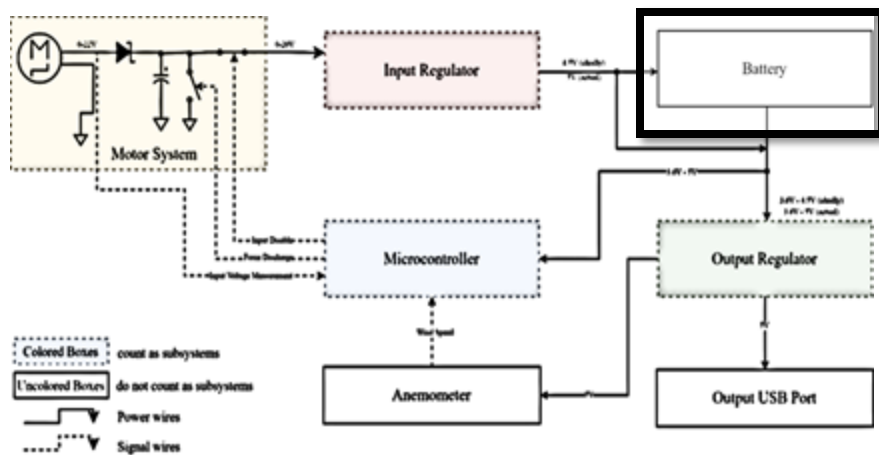


## Battery

The battery acts as a pool for the MPPT algorithm.

The MPPT algorithm will produce the maximum amount of current possible at any moment, but usual appliances is not willing to take any amount of input current, therefore not suitable for being connected directly.

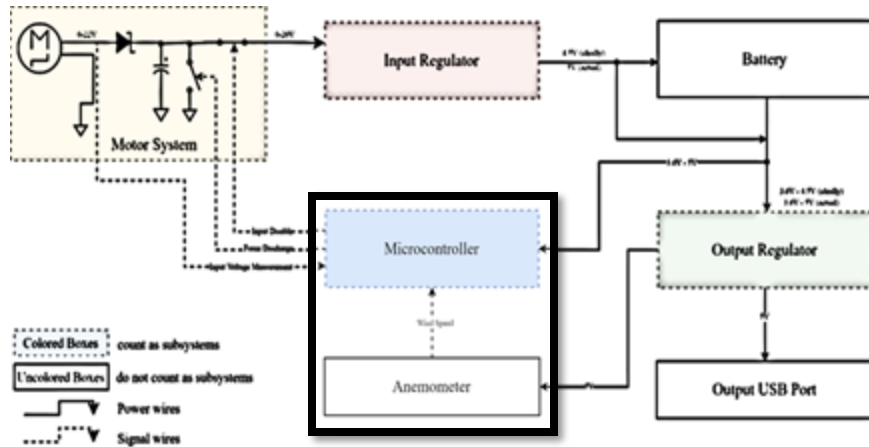A raw battery can accept charging at a wide range of current, therefore essential for MPPT operation. A protection circuit is used to prevent overcharging, undercharging or overcurrent.



## MCU & Anemometer


The microcontroller monitors the motor output voltage and regulator input voltage, as well as taking measurements from the anemometer. It runs the MPPT algorithm.

## I/O Description

Input: Anemometer signals. Input voltage sense signals.  
Output: Motor System control signals.
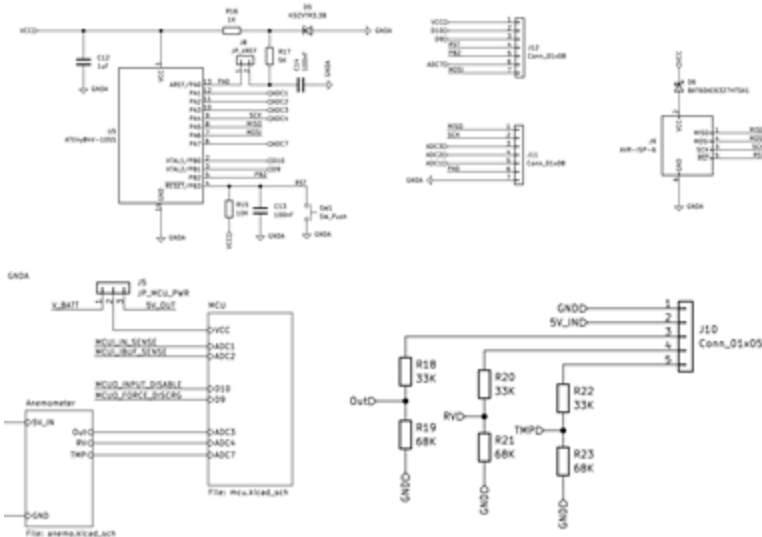
## MPPT Algorithm

Controls the motor, make it operate at the optimal spinning speed and achieve high efficiency.





## Anemometer

It is a thermal anemometer based on a traditional method for measuring wind speed called “hot-wire”.

### Hot-wire method

- Heat element to a constant temperature
- Measure the electrical power needed to maintain the temperature
- The wind speed is proportional to the heat used

### Outputs

- Out
- RV
- TMP

### Relevant data

- Zero Wind Voltage

# Maximum Power Point Tracking

It is technique used with variable power sources to maximize energy extraction as conditions vary

## Low speed

Disable the power usage to let the blades speed up

## Adequate speed

Use the MPPT to feed the system with the optimal power

## High speed


Able the discharge switch to let the system drag a lot of current to slow down the blades

# MCU Logic Testing



Anemometer		Generator		
MPH	Voltage	Voltage [V]	Current [A]	Power [W]
Speed 2 5 cm	10,2134 2,07534	9	0,017	0,153
		9,5	0,018	0,171
		10	0,0192	0,192
		10,5	0,0195	0,2
		11	0,0215	0,235
		11,5	0,0195	0,225
		12	0,0187	0,223
Speed 2 10 cm	7,7439 1,99023	12,5	0,0167	0,21
		13	0,0153	0,193
		13,5	0,0125	0,175
		9	0,0113	0,106
		9,5	0,0115	0,11
		10	0,012	0,117
		10,5	0,0102	0,108
Speed 2 15 cm	5,8437 1,7737	11	0,0179	0,175
		11,5	0,0144	0,177
		12	0,0128	0,164
		12,5	0,0119	0,144
		13	0,0101	0,128
		13,5	0,0087	0,114
		9	0,0101	0,087
Speed 2 20 cm	3,92417 1,55833	9,5	0,0095	0,087
		10	0,0086	0,085
		10,5	0,079	0,081
		11	0,0067	0,079
		11,5	0,0057	0,064
		12	0,0039	0,045
		12,5	0,0028	0,03
Speed 3 5 cm	10,835 2,11083	13	0,001	0,012
		13,5	0	0
		9	0,0124	0,105
		9,5	0,0113	0,108
		10	0,011	0,105
		10,5	0,0098	0,102
		11	0,0085	0,086
Speed 3 10 cm	11,429 2,151	11,5	0,0063	0,078
		12	0,0049	0,068
		12,5	0,0044	0,053
		13	0,0031	0,039
		13,5	0,0012	0,014
		9	0,0374	0,332
		9,5	0,0371	0,364
Speed 3 15 cm	7,485 1,99083	10	0,0301	0,263
		10,5	0,0376	0,399
		11	0,0343	0,372
		11,5	0,0331	0,378
		12	0,0317	0,369
		12,5	0,0302	0,378
		13	0,0284	0,368
Speed 3 20 cm	10,808 2,035	13,5	0,0277	0,272
		9	0,0371	0,33
		9,5	0,0355	0,338
		10	0,0379	0,371
		10,5	0,0374	0,397
		11	0,0336	0,37
		11,5	0,0339	0,367
Speed 3 25 cm	10,808 2,035	12	0,0307	0,377
		12,5	0,0303	0,371
		13	0,0266	0,357
		13,5	0,025	0,339
		9	0,0385	0,253
		9,5	0,0387	0,275
		10	0,0374	0,275
Speed 3 30 cm	10,808 2,035	10,5	0,0373	0,392
		11	0,0329	0,363
		11,5	0,0289	0,34
		12	0,0276	0,337
		12,5	0,027	0,342
		13	0,0248	0,339
		13,5	0,0225	0,315
Speed 3 35 cm	10,808 2,035	9	0,0354	0,303
		9,5	0,0339	0,326
		10	0,0335	0,33
		10,5	0,0329	0,345
		11	0,0332	0,372
		11,5	0,0309	0,355
		12	0,029	0,347
Speed 3 40 cm	10,808 2,035	12,5	0,0283	0,351
		13	0,0259	0,336
		13,5	0,0242	0,327
		9	0,0374	0,332
		9,5	0,0371	0,364
		10	0,0301	0,263
		10,5	0,0376	0,399
Speed 3 45 cm	10,808 2,035	11	0,0343	0,372
		11,5	0,0331	0,378
		12	0,0317	0,369
		12,5	0,0302	0,378
		13	0,0284	0,368
		13,5	0,0277	0,272
		9	0,0374	0,332
Speed 3 50 cm	10,808 2,035	9,5	0,0371	0,364
		10	0,0301	0,263
		10,5	0,0376	0,399
		11	0,0343	0,372
		11,5	0,0331	0,378
		12	0,0317	0,369
		12,5	0,0302	0,378
Speed 3 55 cm	10,808 2,035	13	0,0284	0,368
		13,5	0,0277	0,272
		9	0,0374	0,332
		9,5	0,0371	0,364
		10	0,0301	0,263
		10,5	0,0376	0,399
		11	0,0343	0,372
Speed 3 60 cm	10,808 2,035	11,5	0,0331	0,378
		12	0,0317	0,369
		12,5	0,0302	0,378
		13	0,0284	0,368
		13,5	0,0277	0,272
		9	0,0374	0,332
		9,5	0,0371	0,364
Speed 3 65 cm	10,808 2,035	10	0,0301	0,263
		10,5	0,0376	0,399
		11	0,0343	0,372
		11,5	0,0331	0,378
		12	0,0317	0,369
		12,5	0,0302	0,378
		13	0,0284	0,368
Speed 3 70 cm	10,808 2,035	13,5	0,0277	0,272
		9	0,0374	0,332
		9,5	0,0371	0,364
		10	0,0301	0,263
		10,5	0,0376	0,399
		11	0,0343	0,372
		11,5	0,0331	0,378
Speed 3 75 cm	10,808 2,035	12	0,0317	0,369
		12,5	0,0302	0,378
		13	0,0284	0,368
		13,5	0,0277	0,272
		9	0,0374	0,332
		9,5	0,0371	0,364
		10	0,0301	0,263
Speed 3 80 cm	10,808 2,035	10,5	0,0376	0,399
		11	0,0343	0,372
		11,5	0,0331	0,378
		12	0,0317	0,369
		12,5	0,0302	0,378
		13	0,0284	0,368
		13,5	0,0277	0,272
Speed 3 85 cm	10,808 2,035	9	0,0374	0,332
		9,5	0,0371	0,364
		10	0,0301	0,263
		10,5	0,0376	0,399
		11	0,0343	0,372
		11,5	0,0331	0,378
		12	0,0317	0,369
Speed 3 90 cm	10,808 2,035	12,5	0,0302	0,378
		13	0,0284	0,368
		13,5	0,0277	0,272
		9	0,0374	0,332
		9,5	0,0371	0,364
		10	0,0301	0,263
		10,5	0,0376	0,399
Speed 3 95 cm	10,808 2,035	11	0,0343	0,372
		11,5	0,0331	0,378
		12	0,0317	0,369
		12,5	0,0302	0,378
		13	0,0284	0,368
		13,5	0,0277	0,272
		9	0,0374	0,332
Speed 3 100 cm	10,808 2,035	9,5	0,0371	0,364
		10	0,0301	0,263
		10,5	0,0376	0,399
		11	0,0343	0,372
		11,5	0,0331	0,378
		12	0,0317	0,369
		12,5	0,0302	0,378
Speed 3 105 cm	10,808 2,035	13	0,0284	0,368
		13,5	0,0277	0,272
		9	0,0374	0,332
		9,5	0,0371	0,364
		10	0,0301	0,263
		10,5	0,0376	0,399
		11	0,0343	0,372
Speed 3 110 cm	10,808 2,035	11,5	0,0331	0,378
		12	0,0317	0,369
		12,5	0,0302	0,378
		13	0,0284	0,368
		13,5	0,0277	0,272
		9	0,0374	0,332
		9,5	0,0371	0,364
Speed 3 115 cm	10,808 2,035	10	0,0301	0,263
		10,5	0,0376	0,399
		11	0,0343	0,372
		11,5	0,0331	0,378
		12	0,0317	0,369
		12,5	0,0302	0,378
		13	0,0284	0,368
Speed 3 120 cm	10,808 2,035	13,5	0,0277	0,272
		9	0,0374	0,332
		9,5	0,0371	0,364
		10	0,0301	0,263
		10,5	0,0376	0,399
		11	0,0343	0,372
		11,5	0,0331	0,378
Speed 3 125 cm	10,808 2,035	12	0,0317	0,369
		12,5	0,0302	0,378
		13	0,0284	0,368
		13,5	0,0277	0,272
		9	0,0374	0,332
		9,5	0,0371	0,364
		10	0,0301	0,263
Speed 3 130 cm	10,808 2,035	10,5	0,0376	0,399
		11	0,0343	0,372
		11,5	0,0331	0,378
		12	0,0317	0,369
		12,5	0,0302	0,378
		13	0,0284	0,368
		13,5	0,0277	0,272
Speed 3 135 cm	10,808 2,035	9	0,0374	0,332
		9,5	0,0371	0,364
		10	0,0301	0,263
		10,5	0,0376	0,399
		11	0,0343	0,372
		11,5	0,0331	0,378
		12	0,0317	0,369
Speed 3 140 cm	10,808 2,035	12,5	0,0302	0,378
		13	0,0284	0,368

```
// MCU Logic
if (orig_volt >= 18)
{
    digitalWrite(MCUO_FORCE_DISCRG, HIGH);
    digitalWrite(MCU_IN_DISABLE_PIN, LOW);
#ifdef DEBUG
    mySerial.println("C-1");
#endif
}
else
{
    if (orig_IBUF_volt > orig_volt)
    {
#ifdef DEBUG
        mySerial.println("C-2");
#endif
        digitalWrite(MCUO_FORCE_DISCRG, LOW);
        digitalWrite(MCU_IN_DISABLE_PIN, LOW);
    }
    else
    {
        if (orig_volt > best_voltage)
        {
#ifdef DEBUG
            mySerial.println("C-3");
#endif
            digitalWrite(MCUO_FORCE_DISCRG, LOW);
            digitalWrite(MCU_IN_DISABLE_PIN, LOW);
        }
        else
        {
#ifdef DEBUG
            mySerial.println("C-4");
#endif
            digitalWrite(MCUO_FORCE_DISCRG, LOW);
            digitalWrite(MCU_IN_DISABLE_PIN, HIGH);
        }
    }
}
}
```

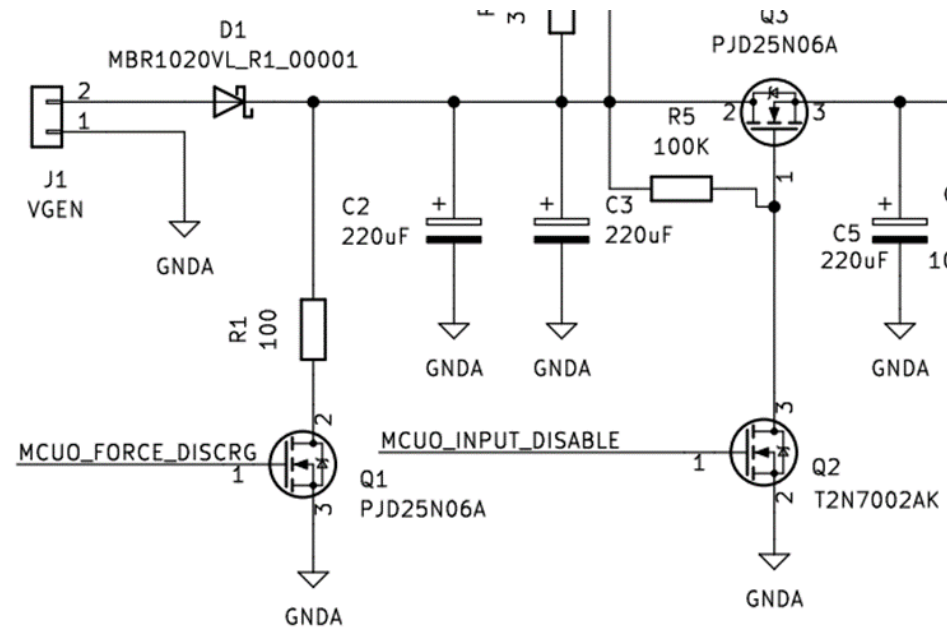





# Technical Details: MPPT – Simulations



Simulated Operation, MPPT Enabled

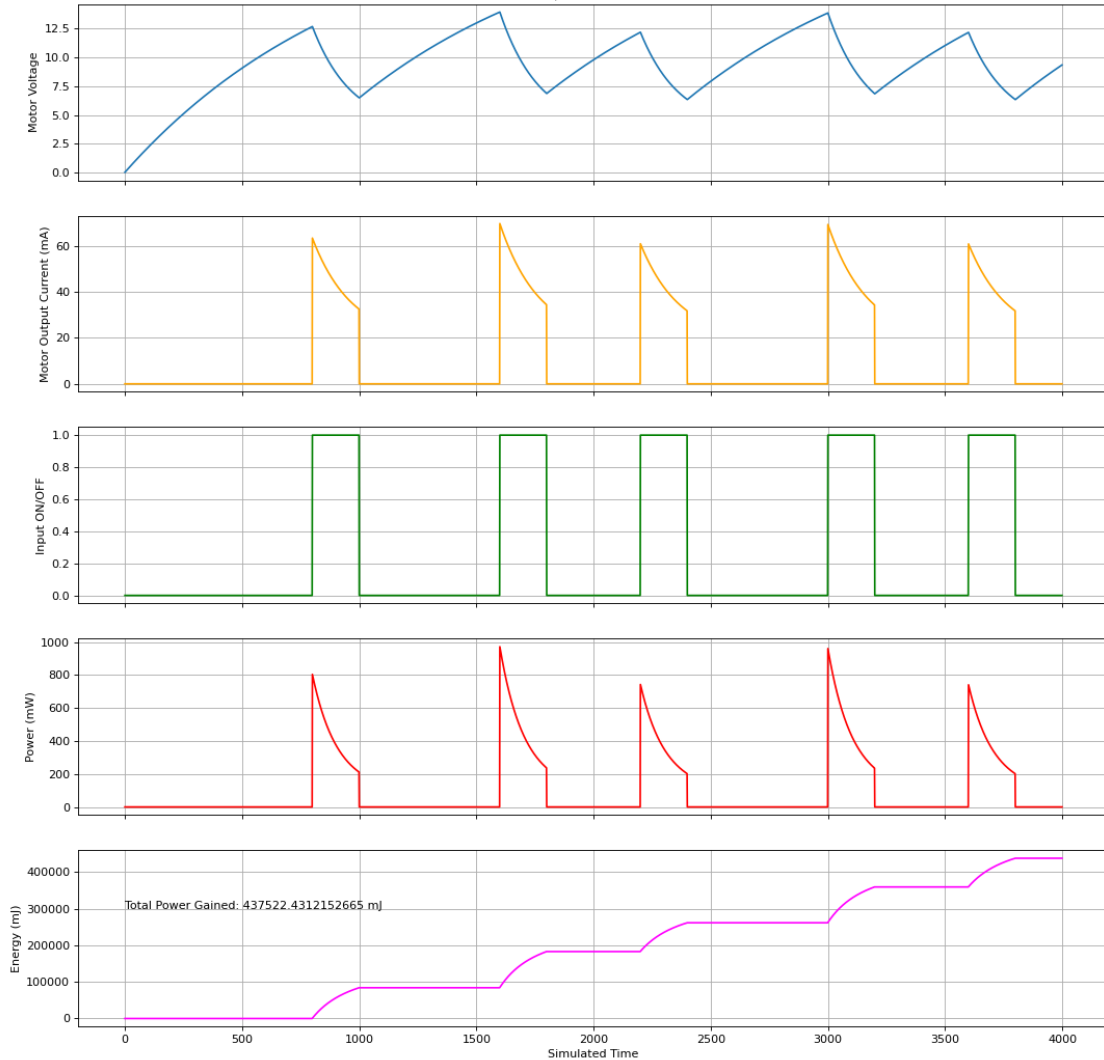

Simulated Operation, MPPT Disabled

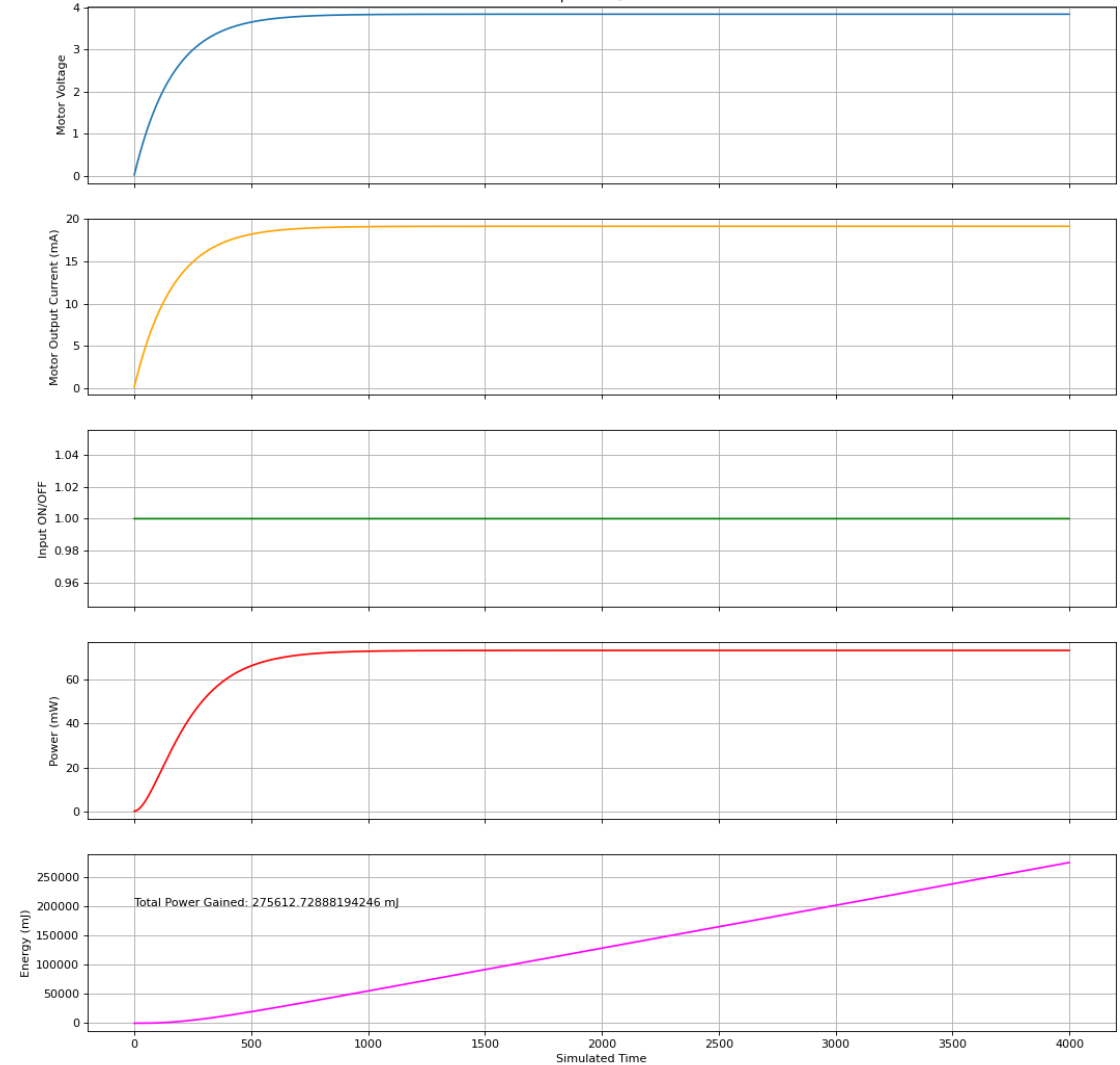




## Power consumption

**Expected input power: 10 Watts**

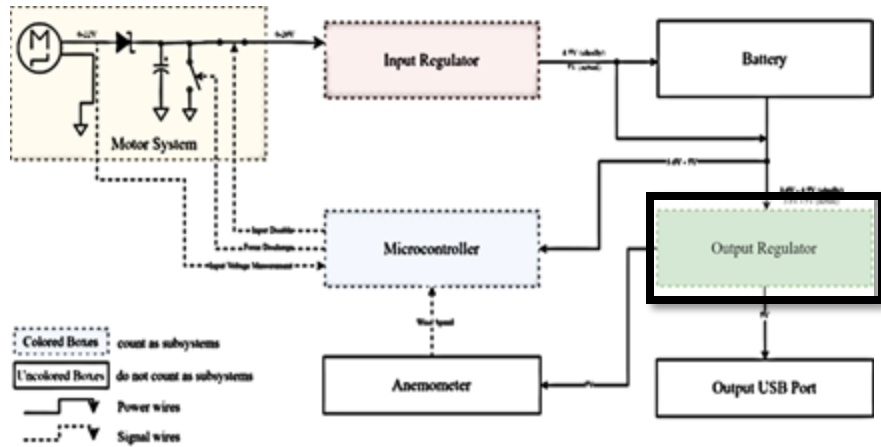**Real input power: 1 Watt**

- Solution 1: Eliminate the anemometer and use a constant value of best\_voltage of 12 V
- Find an anemometer that consumes less power, such as spinning-speed based anemometer or pitot tubes.
- Find a generator that provides a higher input power



## Output Regulator


The output regulator takes an input voltage from either the battery or the input regulator and converts it to 5V for the USB port. The output voltage must meet USB specification, between 4.75 – 5.25V

Used the same IC as the input regulator to save design effort.


## I/O Description

Input: 3.7-5.0V (In most cases 3.7 – 4.2V)


Output: 5V (tolerance: 5%)

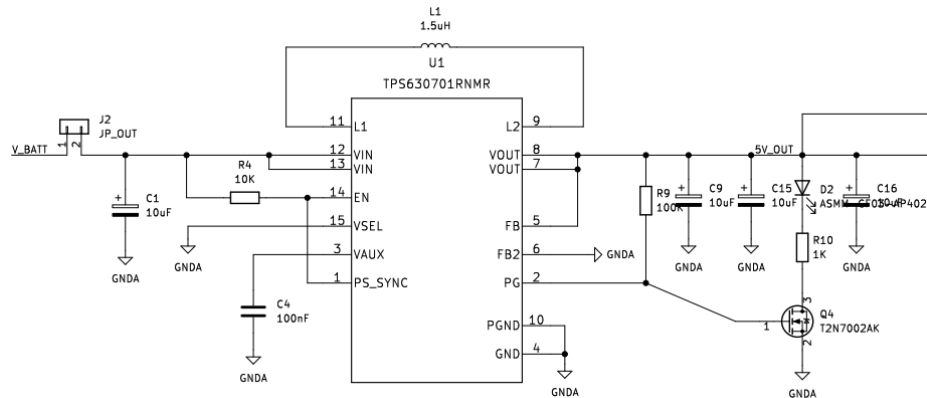

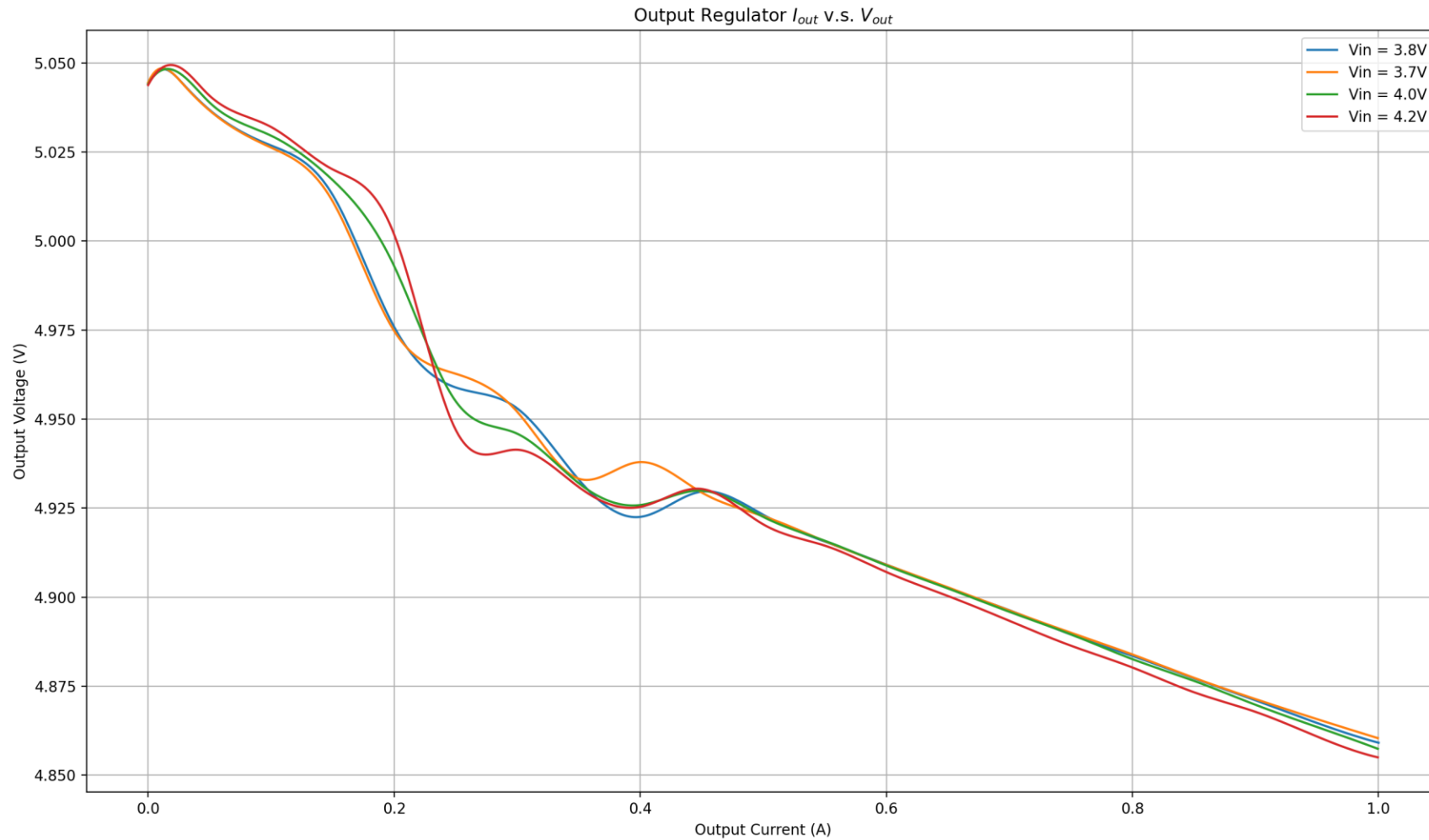
# Testing: Output Regulator – Voltage Drop


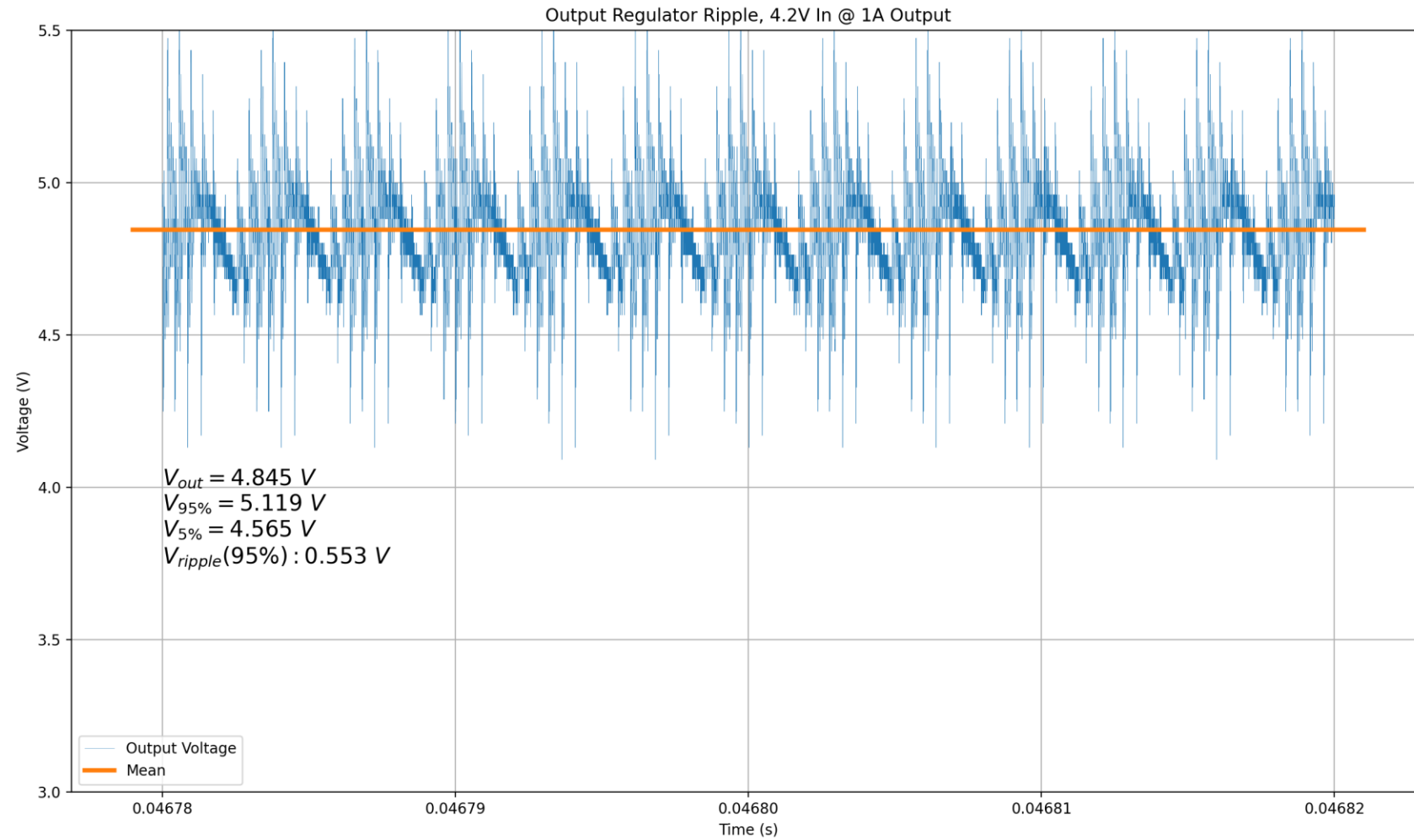
# Testing: Output Regulator – Voltage Drop



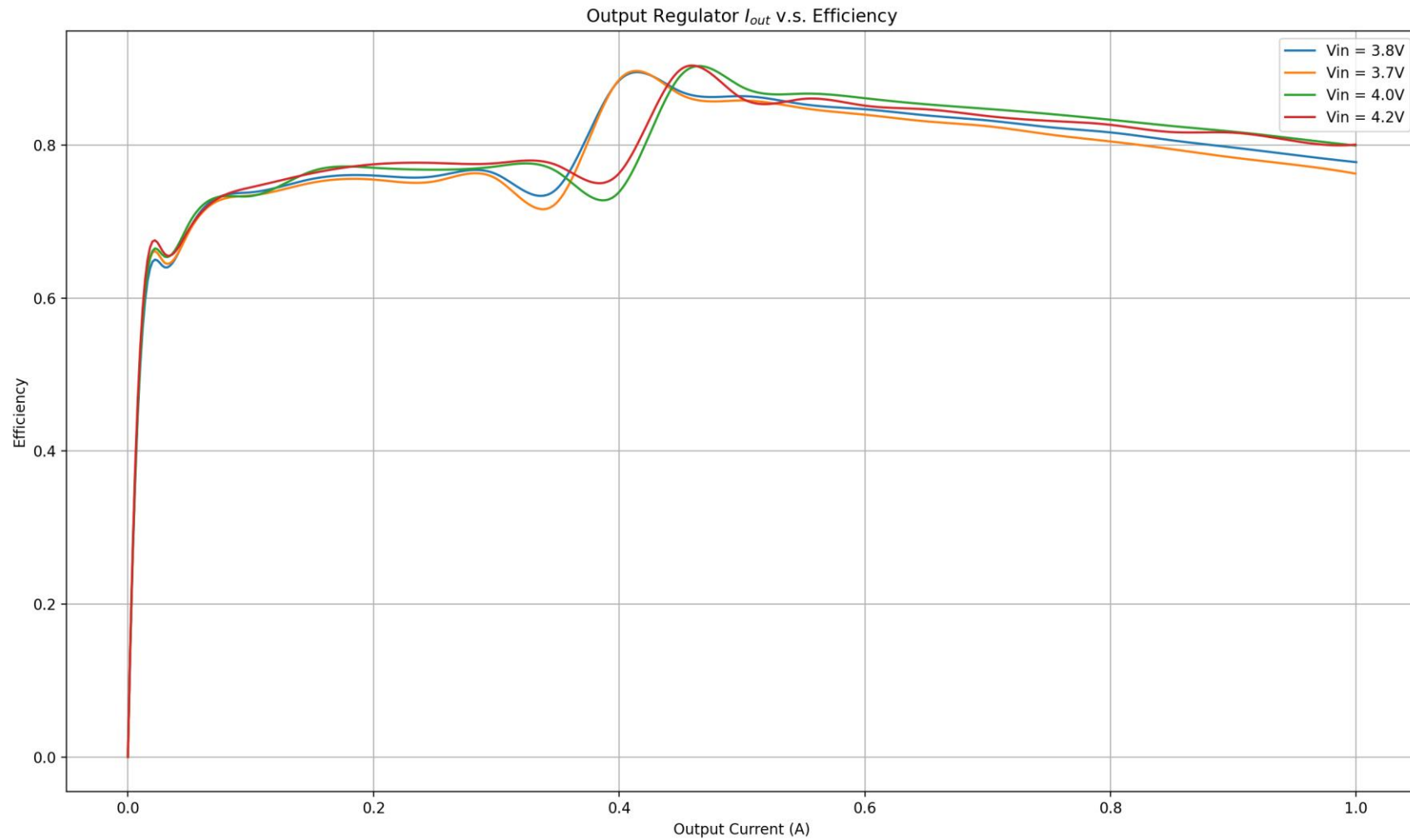
# Testing: Output Regulator – Voltage Drop



# Setbacks and challenges: Design: Version 1 & 2



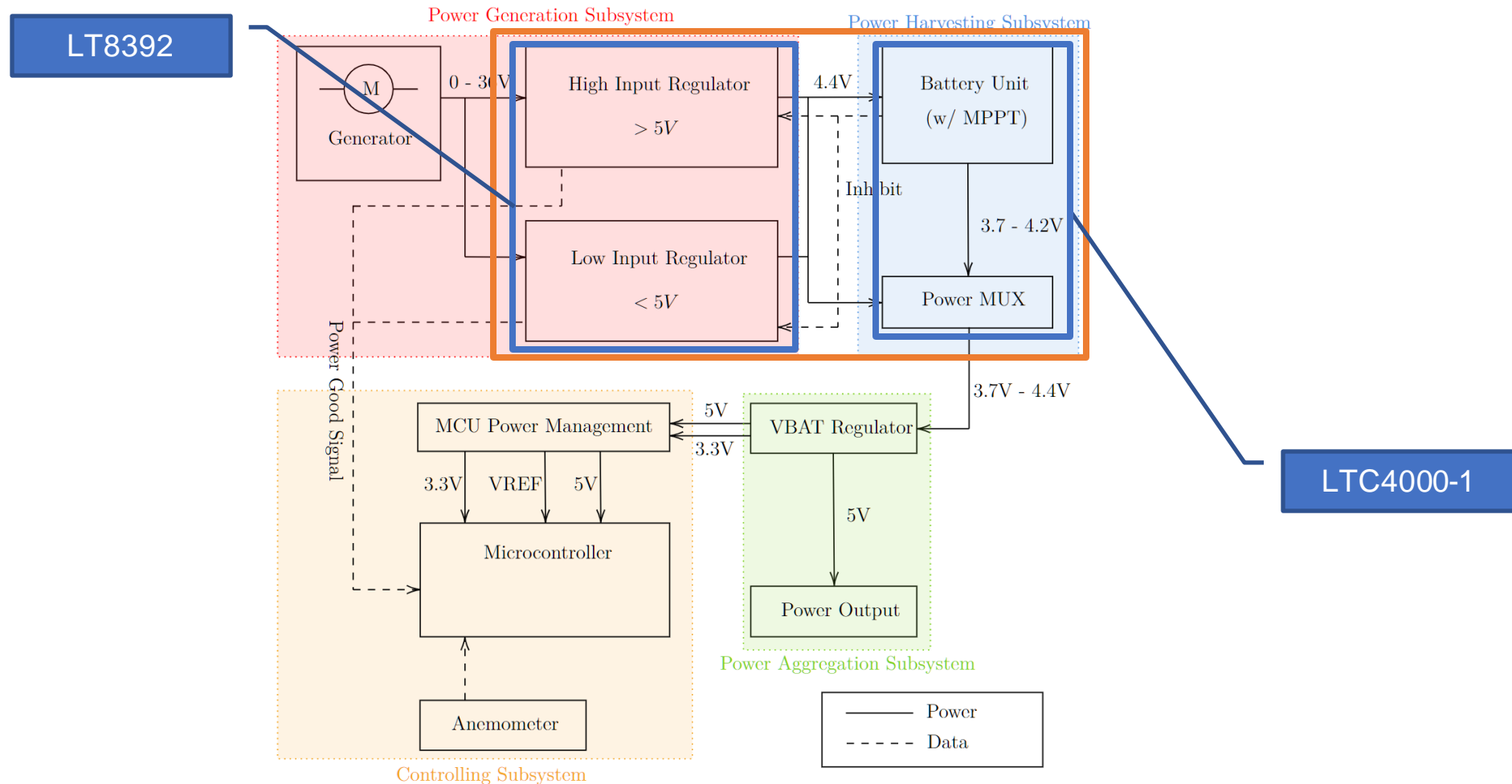
1. The first and second version PCBs was ambitious and complicated, they did not work, and it is hard to diagnose what happened.



# Setbacks and challenges: Design: Version 1 & 2



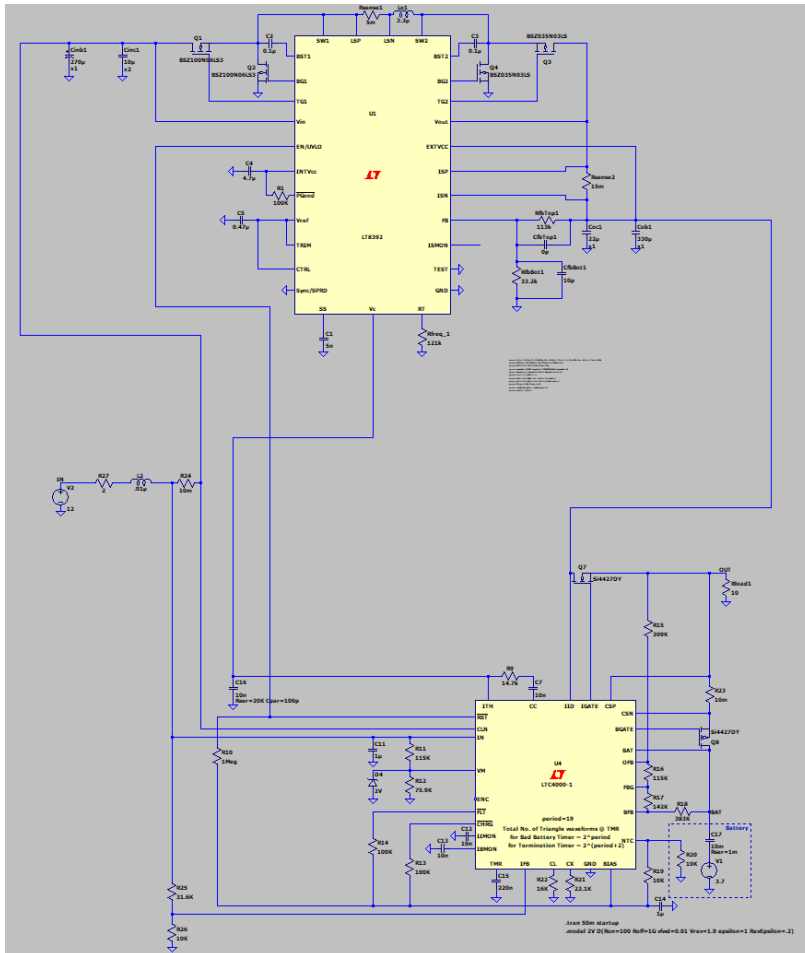1. The first and second version PCBs was ambitious and complicated, they did not work, and it is hard to diagnose what happened.



## Version 1 & 2 PCB


### Top: DC/DC Converter

This is also a Buck-Boost architecture converter, MOSFETs are external. It has a Inhibit pin for controlling output current.
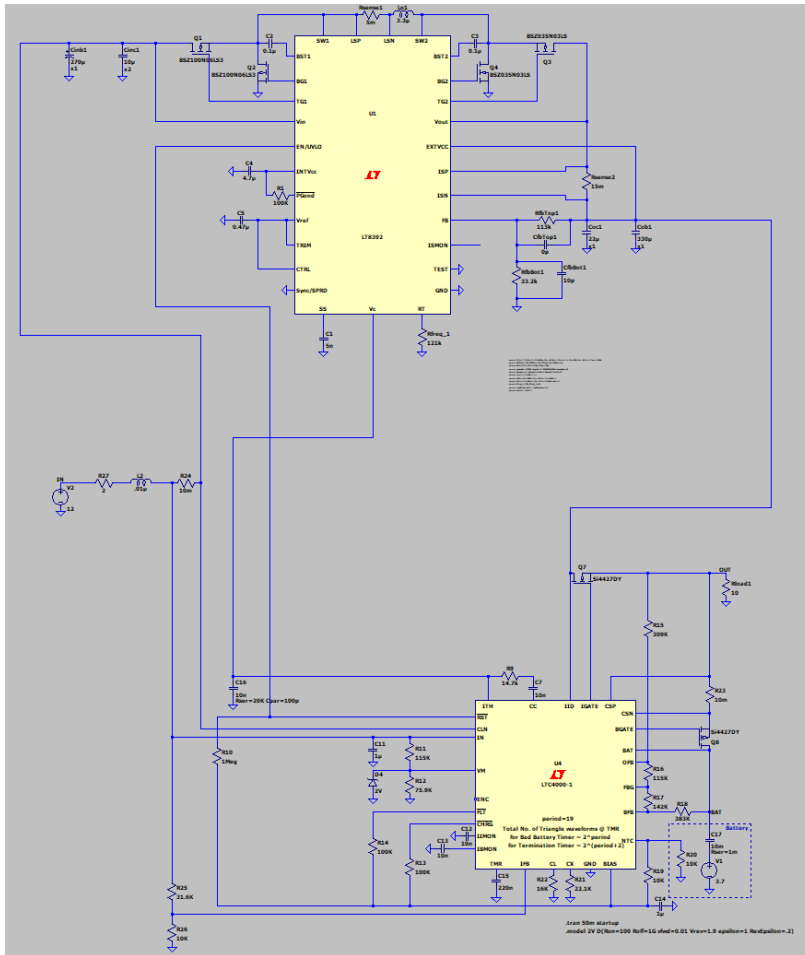
### Bottom: MPPT & Battery Management IC

This IC measures input voltage, compares it with a set optimal voltage(provided by the MCU & Anemometer or transistor), and pulls the inhibit pin to control output current.





## Version 1 & 2 PCB

### Advantage:

Fine-grained control over input voltage and current, responds to fluctuations in input instantly, instead of a simple digital ON/OFF.

### Disadvantage:

1. The two subsystems cannot work without each other.

The management IC provided lots of signals to the controller IC. The ITH pin lacks specification to simulate with instruments.


2. Not designed for low-power operation.

The DC/DC converter is designed for systems up to 300W. Expected our system to work at 10W. We chose smaller MOSFETs to suit our use case, but the IC itself contains too much internal logic.


3. Requires complicated PCB design

The DC/DC IC provided guidelines for PCB design but no example layouts. A similar IC from Texas Instruments gave out a 6-layer PCB layout recommendation.
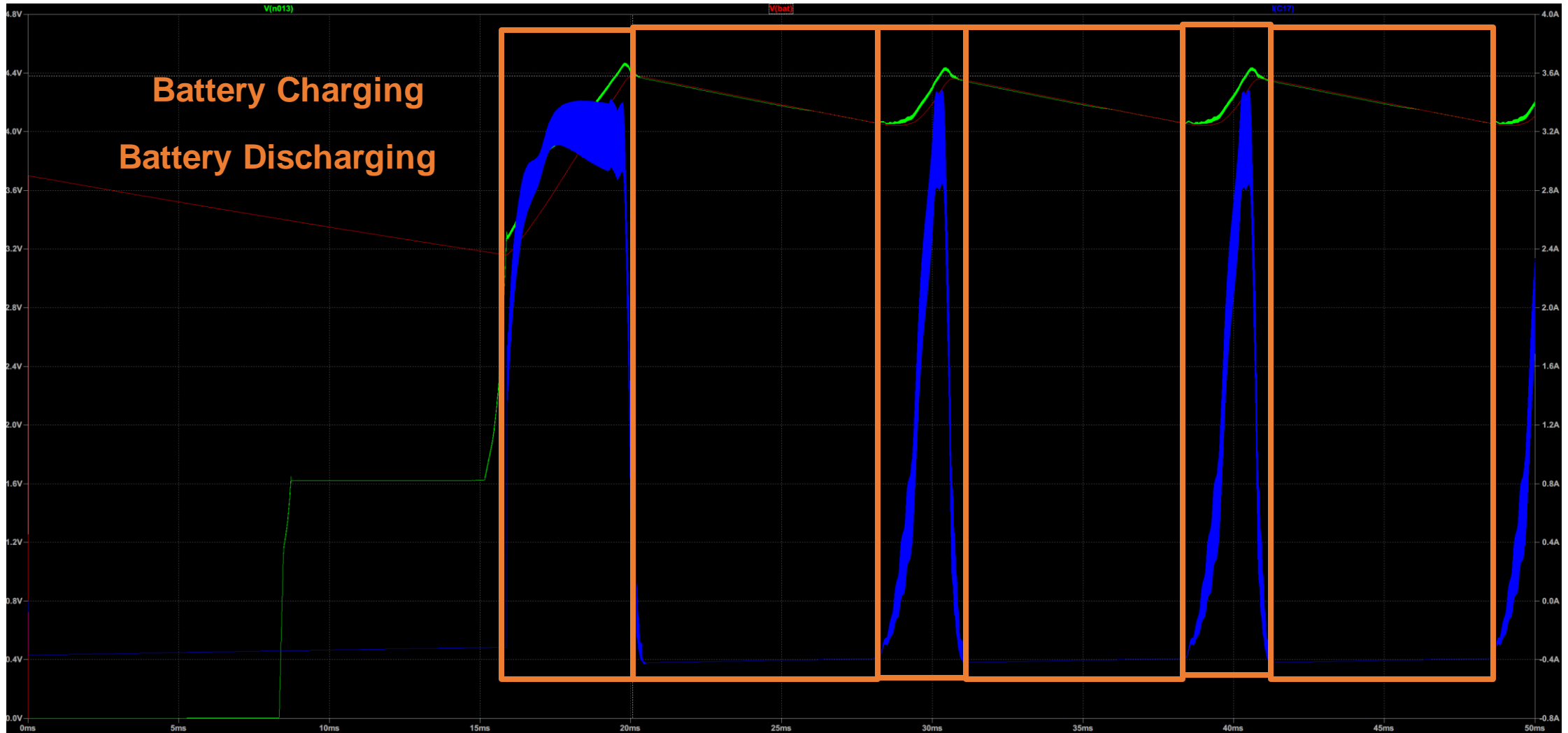
# Setbacks and challenges: Simulation: Version 1&2


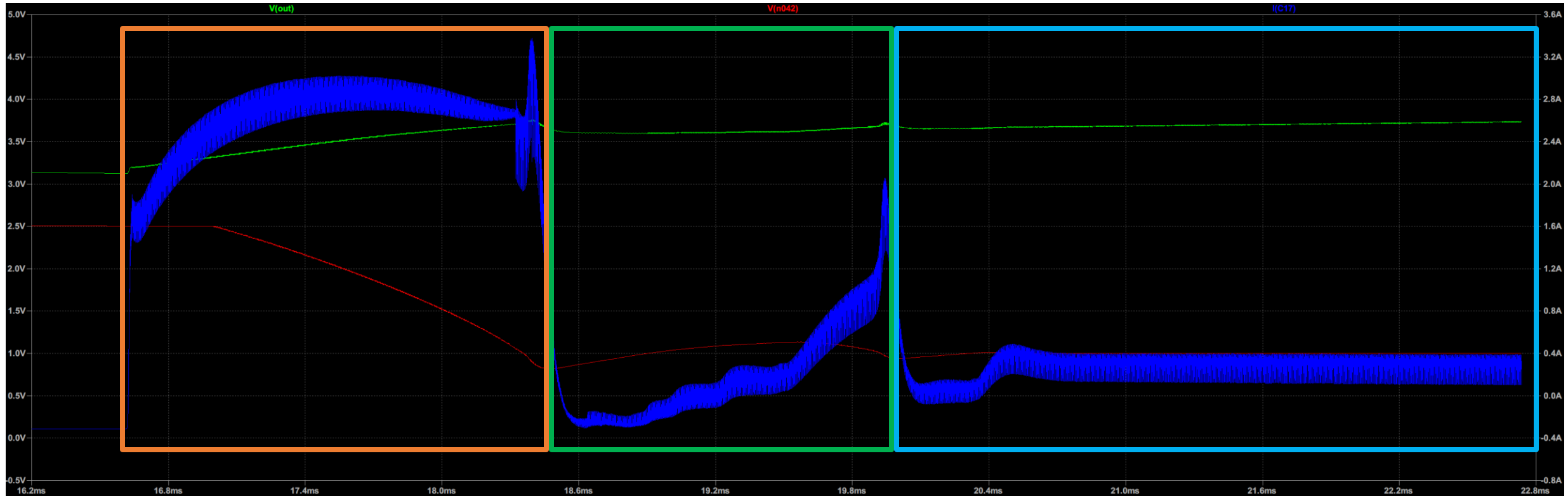
# Setbacks and challenges: Simulation: Version 1&2







Drawing too much current  
Input Voltage Drops

Current reduced  
Input voltage rises back

Current stabilized  
Optimal point reached
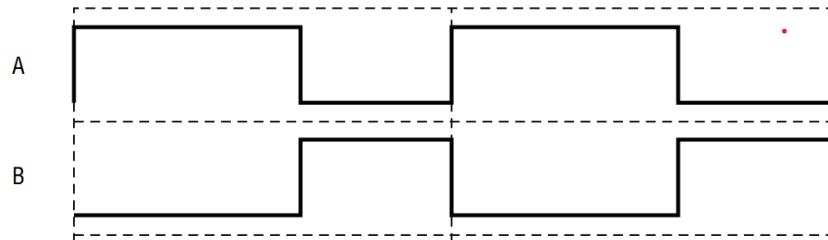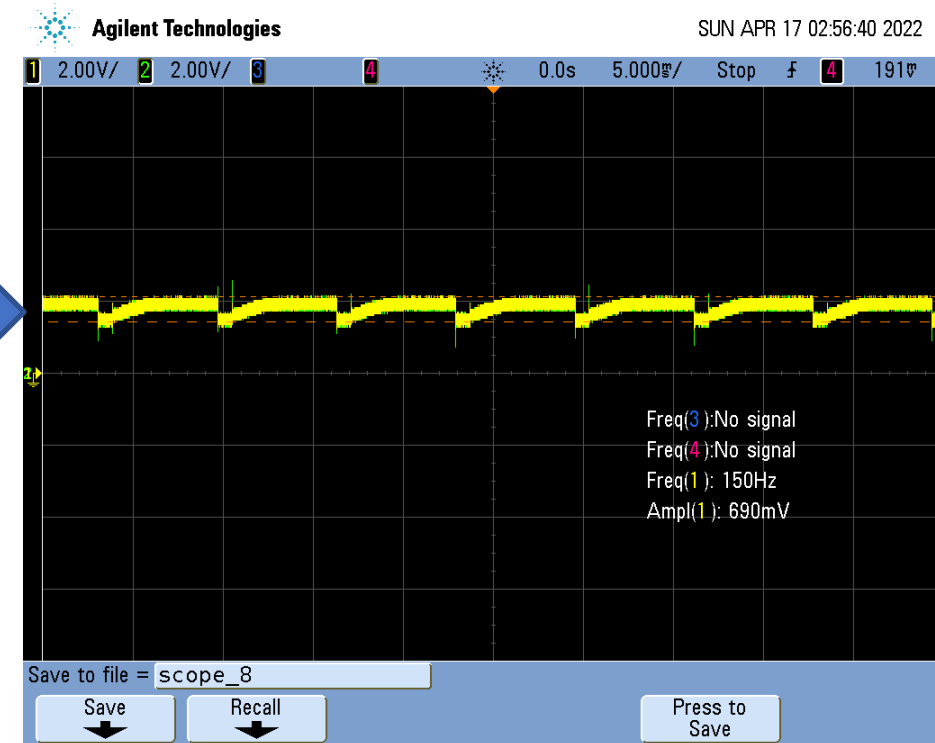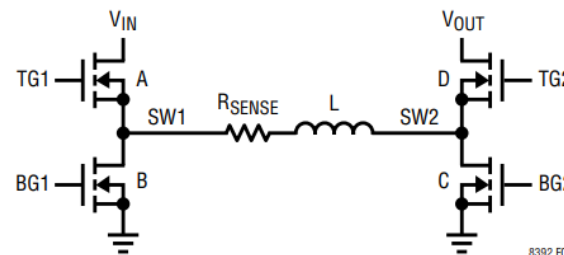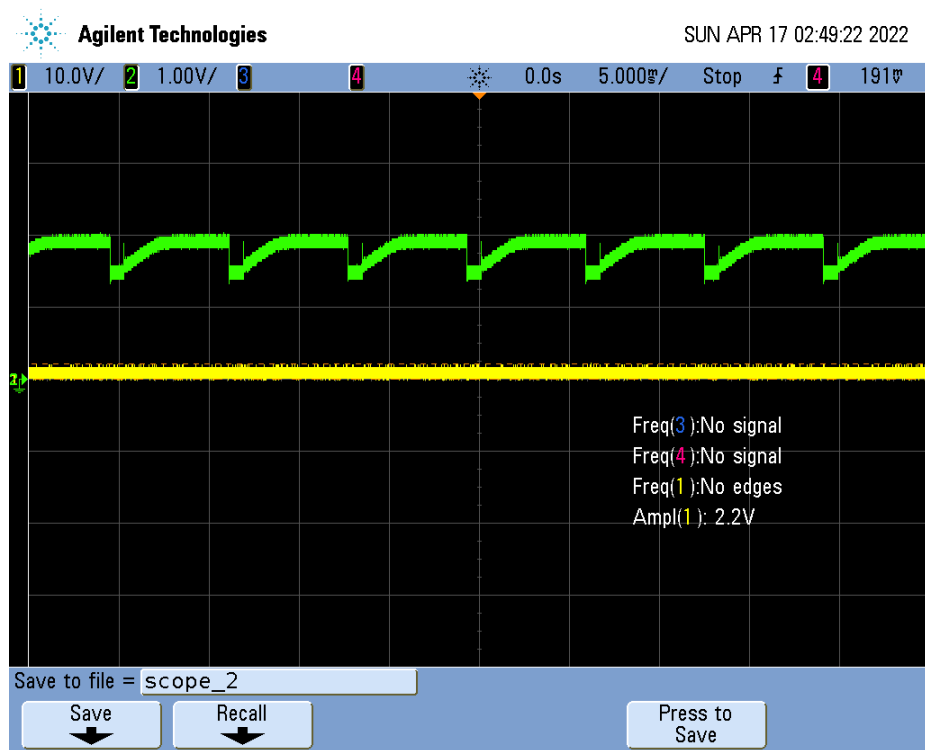
# Setbacks and challenges: Measurements: Version 1&2




Expected A&B

## Conclusion:

MOSFETs A & B are both turned off.  
No such status exists in buck-boost architecture  
or LT8392's datasheet.


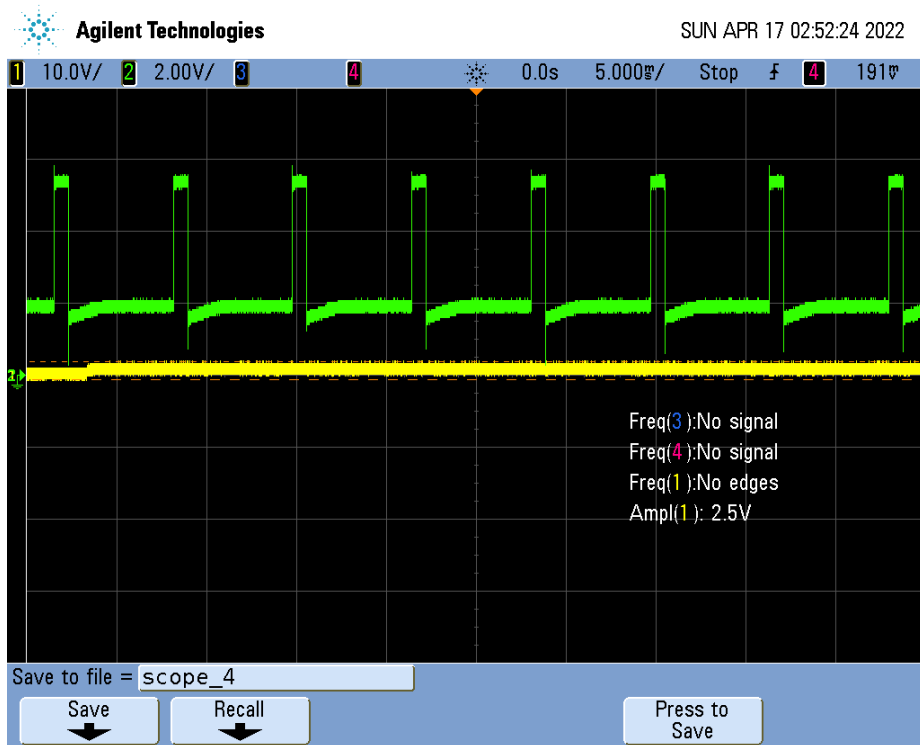
# Setbacks and challenges: Measurements: Version 1&2



Measured TG2 (D + SW2)

Measured SW2

Measured BG2 (C)

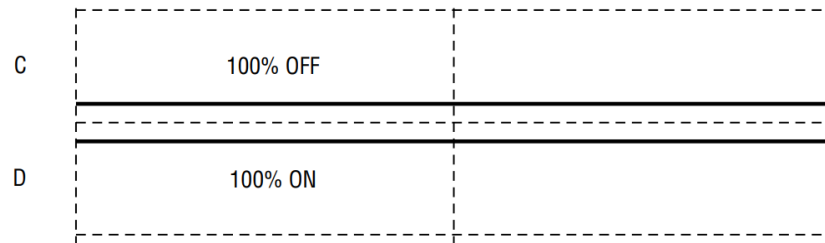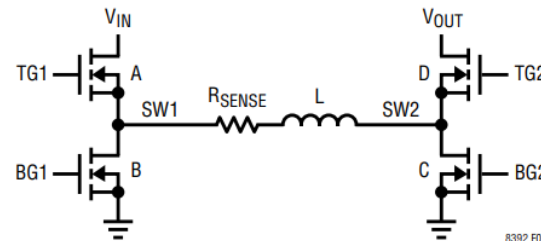


**Conclusion:**

MOSFET D is switched at around 15%

MOSFET C is off

Expected C&D (Either)

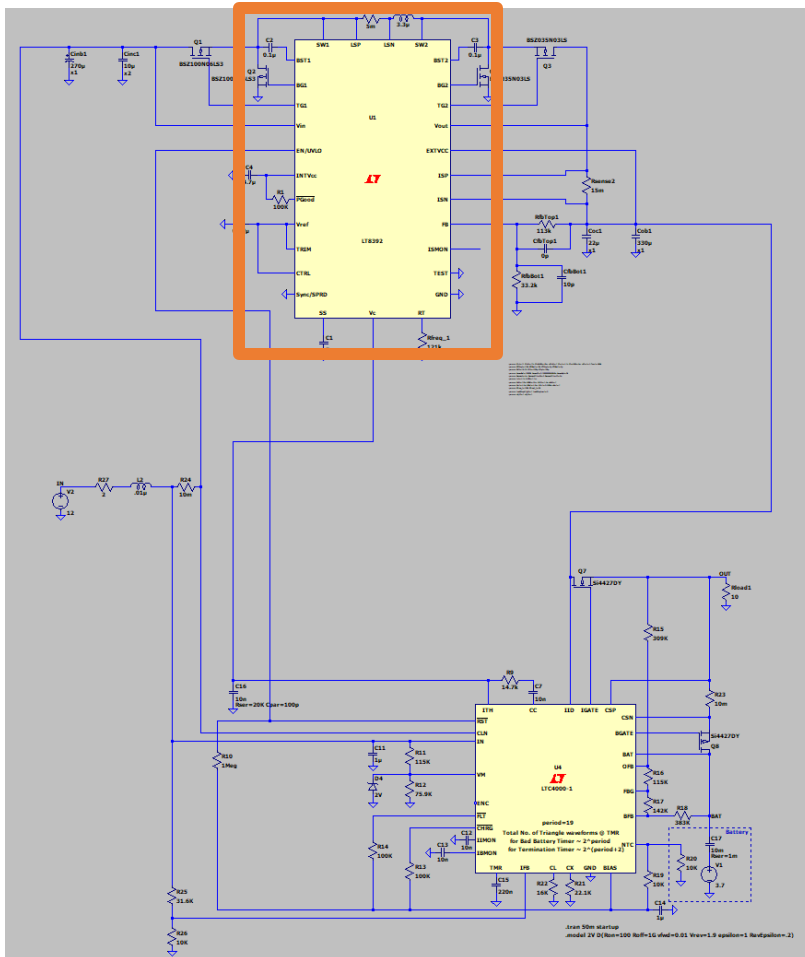No such status exists in buck-boost architecture or LT8392's datasheet



## Conclusion

The IC is not providing correct signals for buck-boost operation.

1. **Soldering temperature?** We used lead-free Sn99/Cu0.7/Ag0.3 solder, which has a higher melting temperature than normal Sn63/Pb37 solder.

- The IC we use, *Analog Devices LT8392* is RoHS (lead-free), but did not say explicitly in the datasheet that it is compatible with higher temperatures for lead-free soldering
- A similar IC from Texas Instruments, *LM34936-Q1* has almost same functionality and same packaging. In the datasheet it explicitly said it is compatible with lead-free processes.

2. **PCB Design?** We followed all PCB design guidelines in *LT8392's* datasheet, but an example design from *LM34936-Q1's* application note showed a 6-layer PCB design.

Following the guidelines from the IEEE Code of Ethics, we are willing to develop this project to hold paramount the safety, health and welfare of the public (IEEE Code of Ethics, 2015).

We have made sure that:

- The mechanism is safe to attach to a bicycle.
- Avoid any possible accidents due to a piece of our project falling off.
- The system will not distract the cyclists' view.
- The system does not expose the user to harmful chemicals

1. Use more efficient anemometers to assist with MPPT.
2. Investigate on more efficient blades or motors in achieving the optimal theoretical power.
3. Tweak the MPPT algorithm, take DC/DC converter efficiency into account.





# **The Grainger College of Engineering**

UNIVERSITY OF ILLINOIS URBANA-CHAMPAIGN