

---

# LED Swim Pacer

**ECE 445 Design review**

Spring 2012

TA: Ryan May

Jonathan Lee, Yi-Liang Chen

---

# Table of Contents

## I. Introduction

1. Title.....	3
1.1 Motivation.....	3
2. Objectives.....	3
2.1 Functions.....	3
2.2 Benefits.....	3
2.3 Features.....	3

## II. Detailed electrical design

1. Block Diagram.....	4
2. Figures and Schematics.....	5

## III. User Interface

1. LCD Display .....	10
2. LCD Flow Chart .....	11
3. LCD microcontroller flow chart .....	12
4. Main microcontroller flow chart .....	13

## IV. Circuit operation and specifications

1. Wire resistance .....	14
2. Power battery .....	14

## V. Performance Requirements

1. Testing & Verification.....	15
--------------------------------	----

## VI. Cost and Schedule

1. Schedule.....	17
2. Cost Analysis.....	18

## VII. Ethical Issues

1. Ethics.....	19
----------------	----

# I. Introduction

## 1. Title

### LED Swim Pacer

This project is proposed by Coach Howard. He wants a swim pacer unit as a training tool to help improve the performance of his swimmers. This variable speed sequential LED pacer will help pace swimmers to swim at a faster speed, helping them improve their speed and consistency.

## 1.1 Motivation

A swimming pacer helps swimmers improve their swim time. With a strip of LED underwater, the swimmer can easily see and follow the LED light. The swimmer could also increase the speed of the LED to improve his or her performance.

## 2. Objectives

The goal of this project is to design and build a swim pacer using a strip of LED. It will be 25 meters in length so it will fit most of the swimming pools. There will be a main controller controlling seven bidirectional shift registers. Each of the shift register will be connected to 8 LEDs. The controller will send signal and clock data to the shift registers which will turn on or off the LEDs. The controller will have pre-programmed modes which can be changed easily from the control box. This pacer is only meant for one swimmer, doesn't support multiple swimmers.

## 2.1 Functions

- LED lights to pace swimmers
- Simple user interface, easy to operate
- Different colored LED to warn swimmers that end of pool is close
- Simple to deploy

## 2.2 Benefits


- Allows swimmer to pace and improve himself
- Allows swim coach to interact with swimmers

## 2.3 Features


- Strip of green LEDs with a 50cm separation between each LEDs
- Two ends of the strip will have red LEDs to alert the swimmer
- Beginning of LED programmed to be faster as the lap begins
- Waterproof LED strip and control box
- Batteries last at least 4 hours
- Timing increments at 0.5sec
- Maximum of 40 seconds and minimum of 10 seconds

# II. Detailed electrical design


## 1. Block Diagram

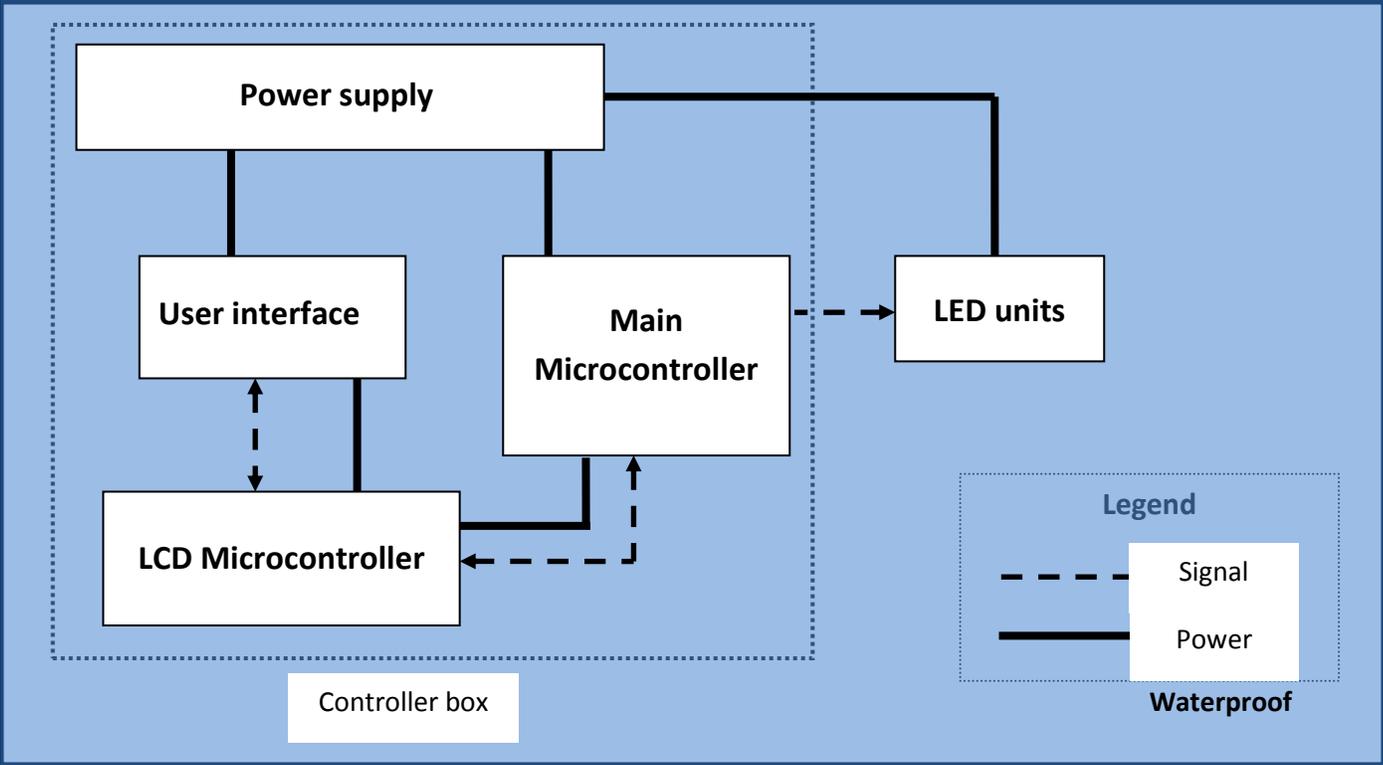

## 2. Figures and Schematics

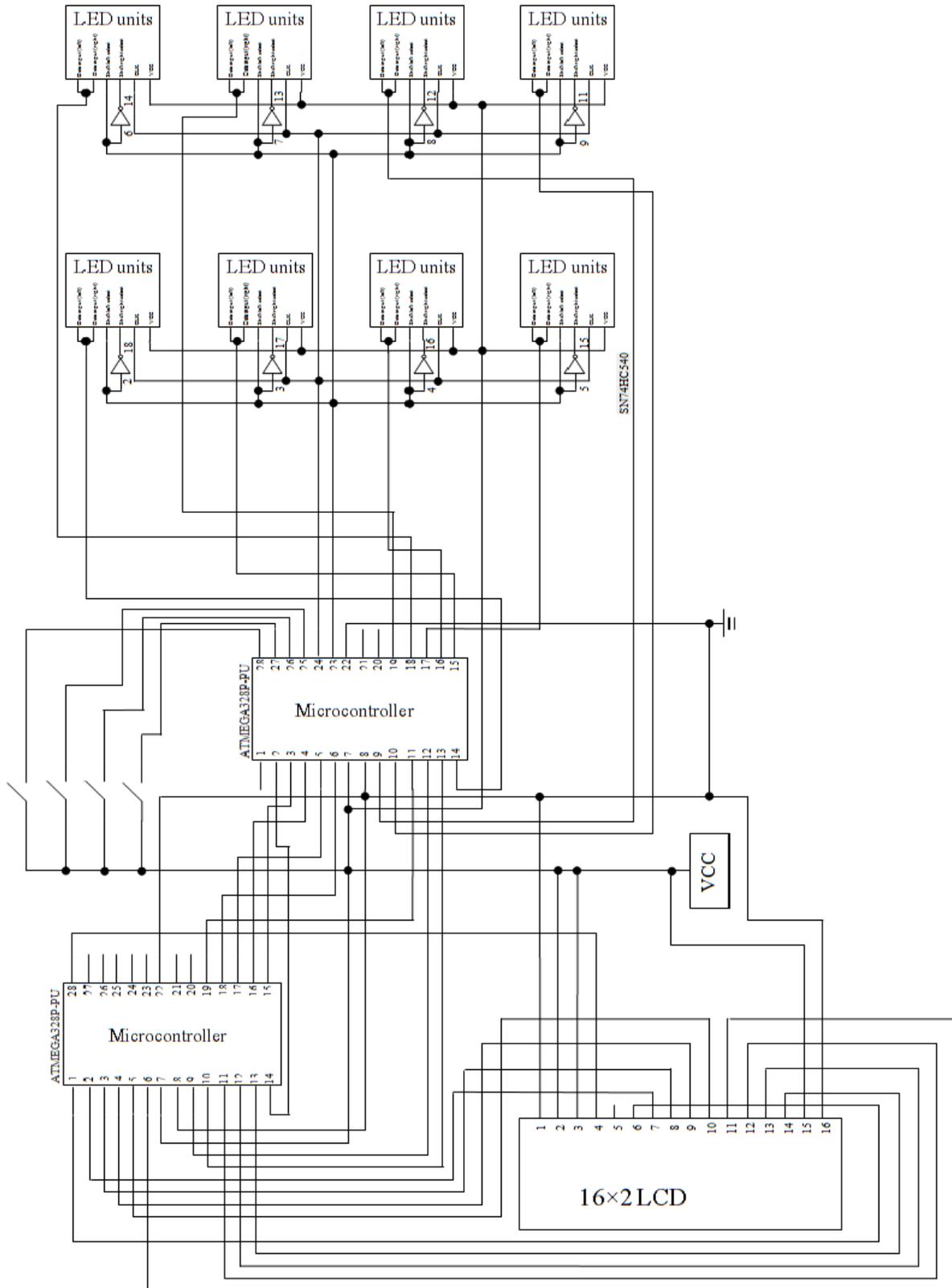

## LED unit

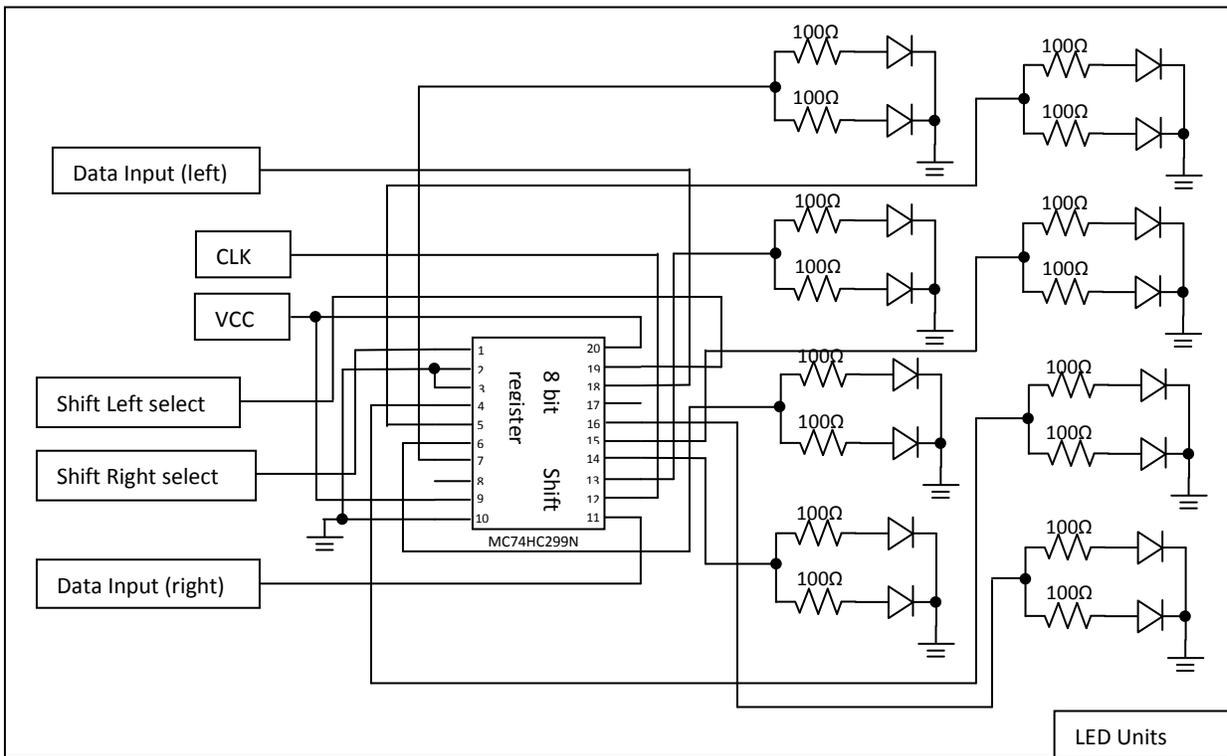


## 8-bit shift register

Pin NO	Symbol	Function
1	S1	Mode select
2	OE1	Output enable
3	OE2	Output enable
4	P <sub>G</sub> /Q <sub>G</sub>	Parallel data port outputs
5	P <sub>E</sub> /G <sub>E</sub>	Parallel data port outputs
6	P <sub>C</sub> /G <sub>C</sub>	Parallel data port outputs
7	P <sub>A</sub> /G <sub>A</sub>	Parallel data port outputs
8	Q <sub>A</sub> '	Serial data outputs
9	Reset	Reset
10	GND	Ground
11	S <sub>A</sub>	Shift right select
12	CLK	Clock
13	P <sub>B</sub> /G <sub>B</sub>	Parallel data port outputs
14	P <sub>D</sub> /G <sub>D</sub>	Parallel data port outputs
15	P <sub>F</sub> /G <sub>F</sub>	Parallel data port outputs
16	P <sub>H</sub> /G <sub>H</sub>	Parallel data port outputs
17	Q <sub>H</sub> '	Serial data outputs
18	S <sub>H</sub>	Shift left select
19	S2	Mode select
20	VCC	+5V

The LED unit contains one 8-bit bidirectional shift register (MC74HC299N) and 8 sets of parallel LED bulb, and each LED is connected with a 100Ω resistor. The shift register gets input data, shift left/right select, and clock signals from main microcontroller. The shift register will shift the input data to left or right according to the select signal input, and the shift speed is determine by the slow clock we created in microcontroller.


### 16 × 2 LCD Display

Pin NO	Symbol	Function
1	V <sub>DD</sub>	+5V
2	V <sub>SS</sub>	Ground
3	RS	Register select
4	NC	No connection
5	E	Read/write enable
6	R/W	Read/write
7	DB1	Data bit
8	DB0	Data bit
9	DB3	Data bit
10	DB2	Data bit
11	DB5	Data bit
12	DB4	Data bit
13	DB7	Data bit
14	DB6	Data bit
15	CLED	LED C(+)
16	ALED	LED A(+)
17	S1	Switch 1
18	BLED	LED B(+)
19	S3	Switch 3
20	S2	Switch 2
21	S4	Switch 4
22	NC	No connection
23	V <sub>SS</sub>	Ground
24	V <sub>DD</sub>	+5V

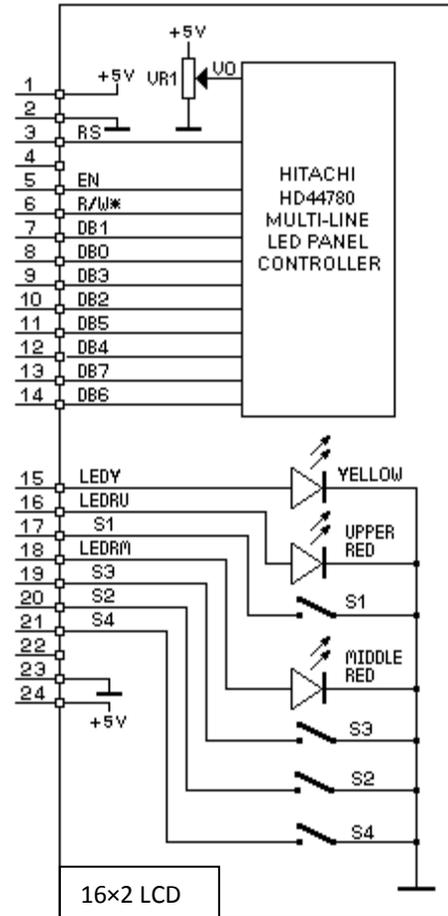

16 × 2 LCD display will display the message that we pre-program in the LCD microcontroller, and interact with user input signal. User can change menu, select mode, and set up time by using the buttons. The buttons are connected with the LCD microcontroller, once it receives the signal, it will change the display on the LCD.

## Microcontrollers

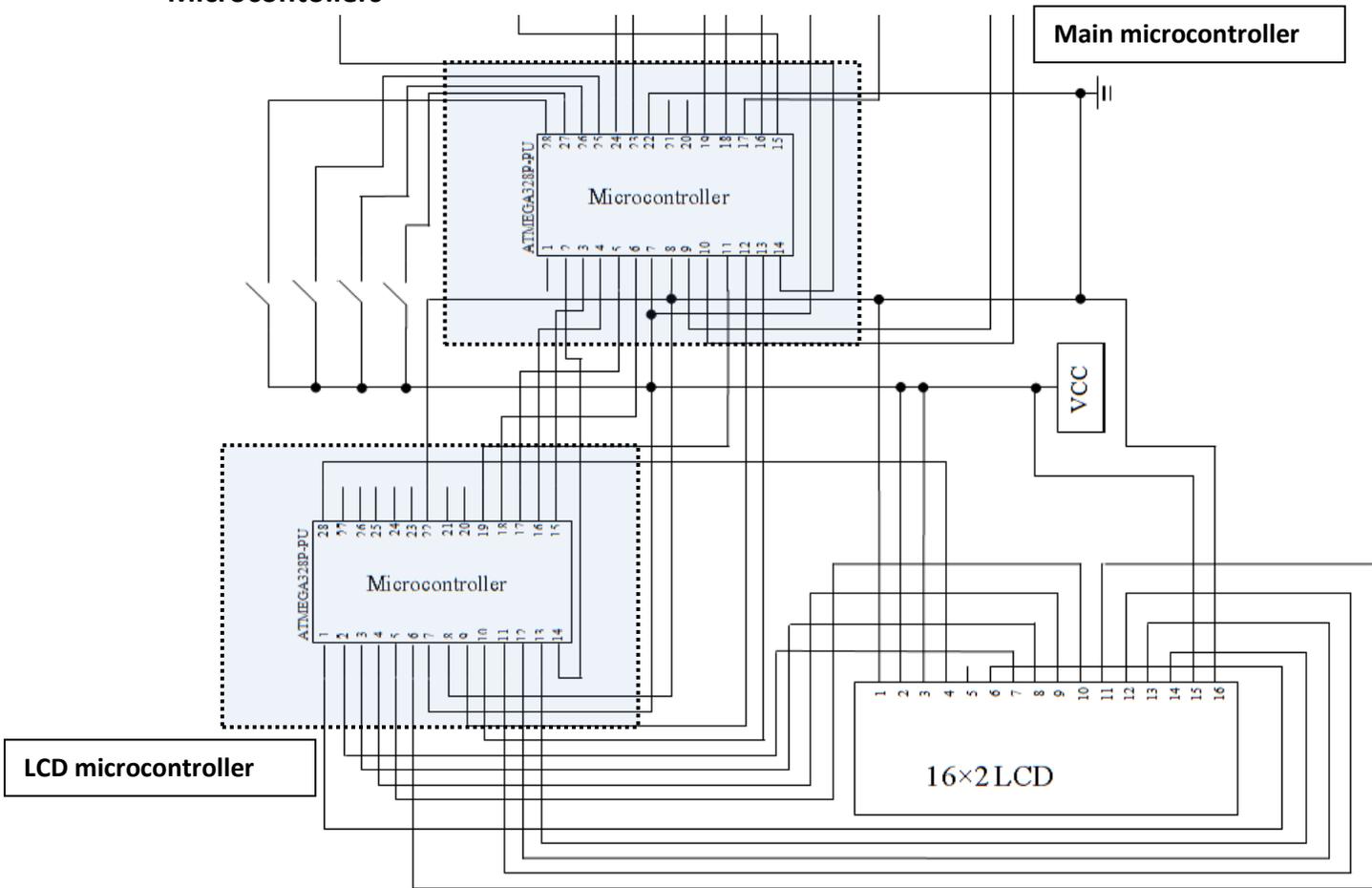

Pin NO	Symbol	Function
1	PC6	Port C I/O port
2	PD0	Port D I/O port
3	PD1	Port D I/O port
4	PD2	Port D I/O port
5	PD3	Port D I/O port
6	PD4	Port D I/O port
7	VCC	Digital supply voltage
8	GND	Ground
9	PB6	Port B I/O port
10	PB7	Port B I/O port
11	PD5	Port D I/O port
12	PD6	Port D I/O port
13	PD7	Port D I/O port
14	PB0	Port B I/O port
15	PB1	Port B I/O port

16	PB2	Port B I/O port
17	PB3	Port B I/O port
18	PB4	Port B I/O port
19	PB5	Port B I/O port
20	AVCC	AVCC is the supply voltage pin for the A/D Converter
21	AREF	AREF is the analog reference pin for the A/D Converter
22	GND	Ground
23	PC0	Port C I/O port
24	PC1	Port C I/O port
25	PC2	Port C I/O port
26	PC3	Port C I/O port
27	PC4	Port C I/O port
28	PC5	Port C I/O port

### **Main microcontroller**

Main microcontroller will receive data from LCD microcontroller for speed data from the user inputs. It will process the data and calculate the clock cycle. Then it will send out individual data input, universal clock and left/right shift select to the 7 LED units. Any adjustment from the user will be updated to the main microcontroller which will alter the speed accordingly.

### **LCD microcontroller**


The LCD microcontroller will receive user inputs from the buttons and update the menu. After the users selected the speed they wanted, the microcontroller will send this information to the main microcontroller. Any adjustment from the user will be send to the main microcontroller.

### **Batteries**

We will be using 8 AA alkaline batteries with a total of 24watts-hour. This will be used to power the main microcontroller and LED unit. The LCD microcontroller and LCD will get their power from the main microcontroller.


### III. User Interface

#### 1. LCD Display

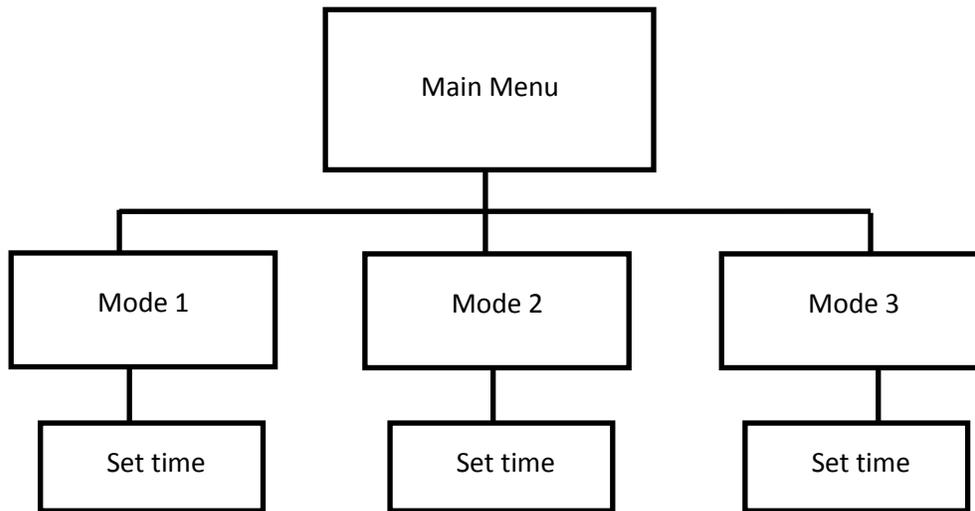


The user interface will have 4 buttons and a LCD to display the menu. In this menu, the users can choose from 3 different modes. The first mode will require the user input the time for one 25m lap. The lap speed will be consistent throughout. The second mode gives the users an option for setting two different speeds. Therefore the user can set a faster pace for the first half and a slower pace for the second half of the lap. The third mode gives the swimmers three different speeds to set. The options are a fast, slow, fast speed, etc.


## 2. LCD Flow Chart

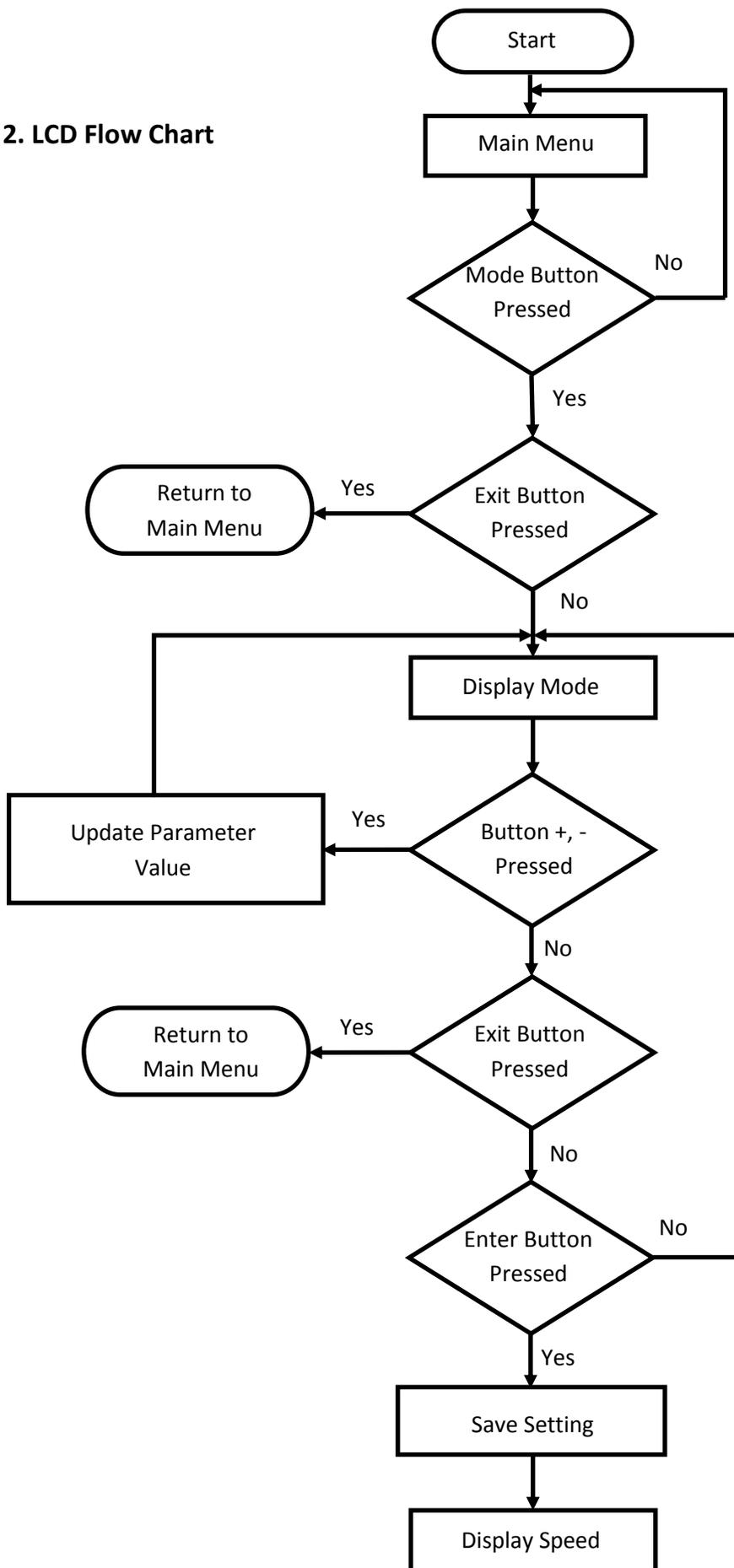

### 3. LCD microcontroller flow chart

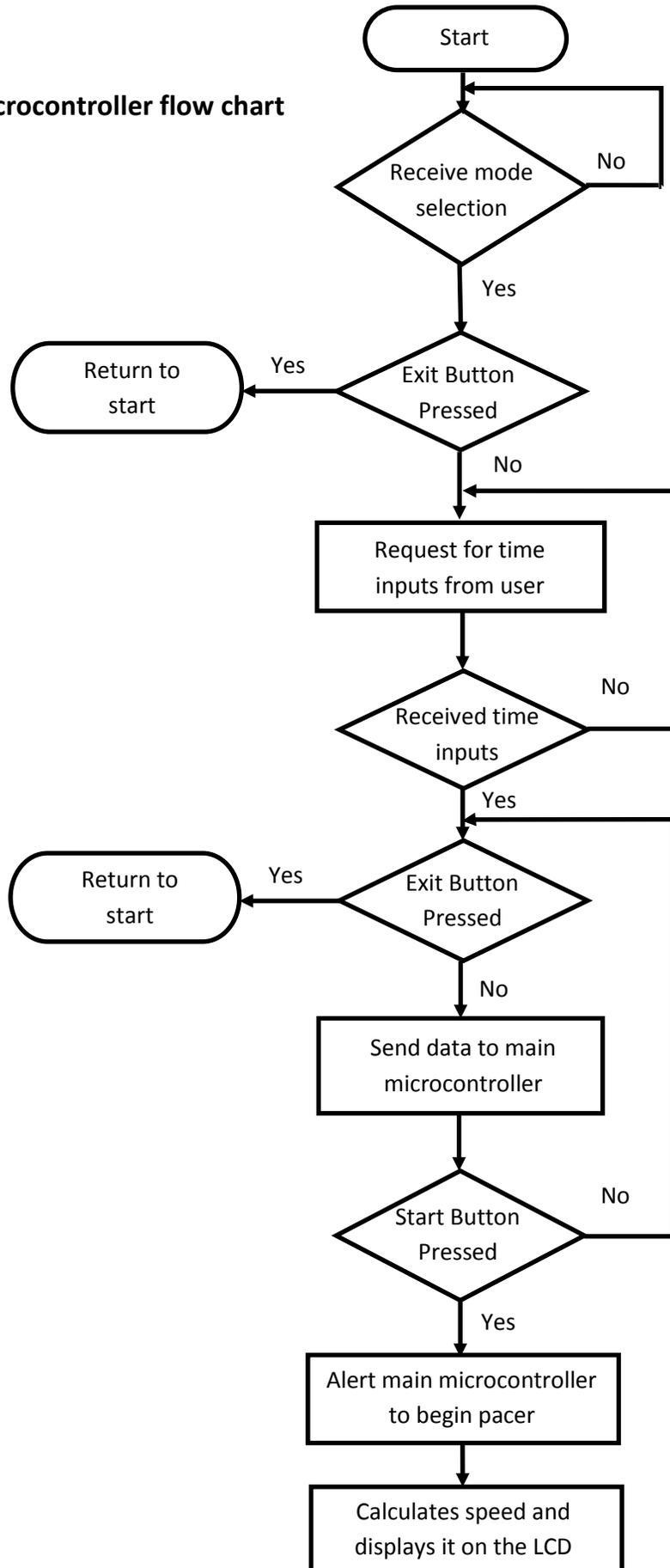

#### 4. Main microcontroller flow chart

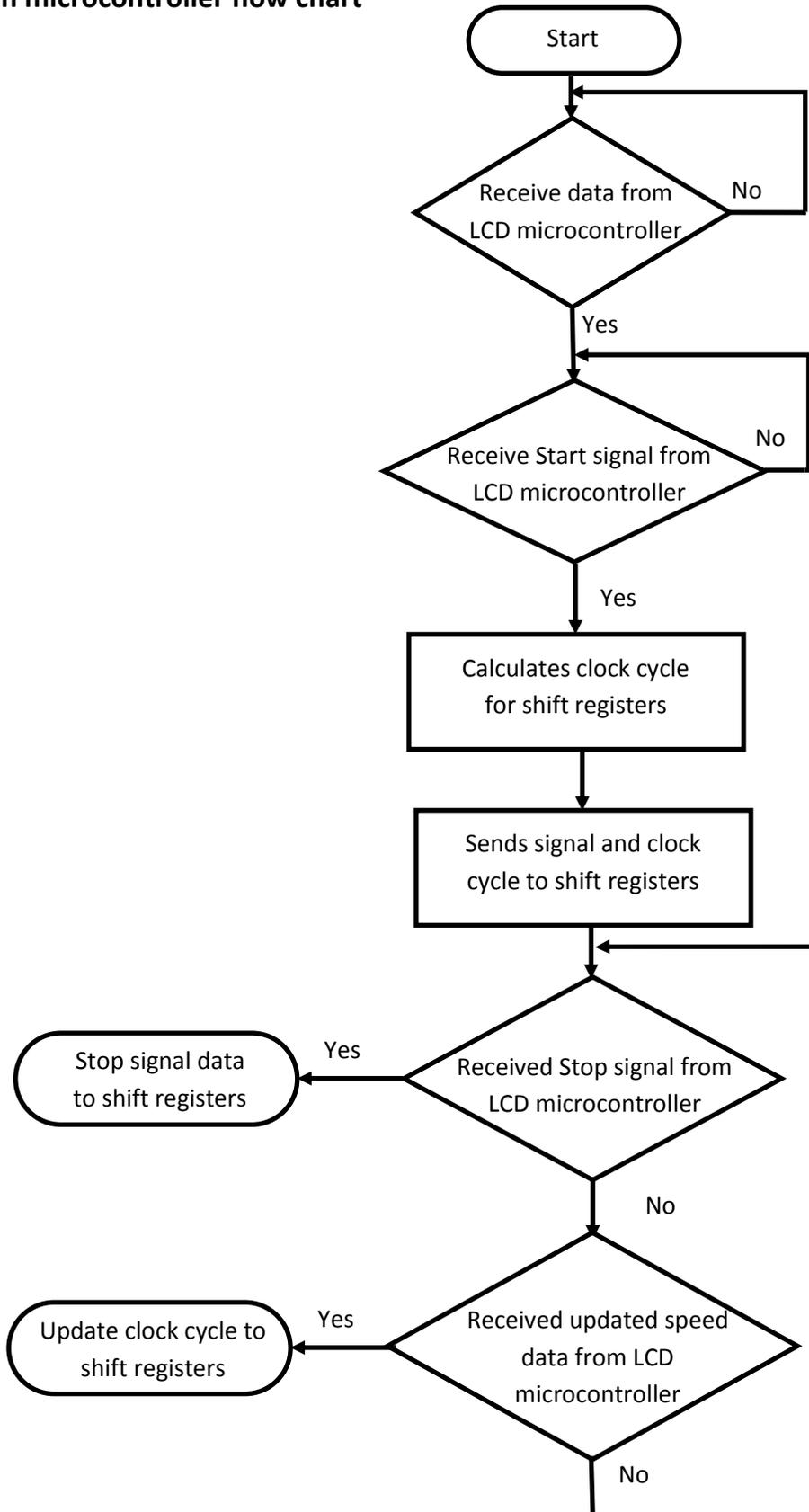

## IV. Circuit operation and specifications

### 1. Wire resistance

Since this led pacer will be 25 meters in length, wire resistance will be an issue in this pacer. The shift registers will be connected to the main microcontroller through 9 wires. The furthest shift register will be 24 meters away from the main microcontroller. We will need to calculate the resistance and check if the power and signal is enough to ensure that all the shift registers are functioning correctly

$$R = \rho \frac{\ell}{A}$$

Resistivity of 22 gauges wire: 0.01614 ohm per foot

Diameter: 0.64516mm

Area: 3.6167E-7 m<sup>2</sup>

Length: 79.74 feet (24m)

R= 0.01614\*78.74 feet =1.271 ohms

Wire Resistance= 1.271 ohms

Since the wire resistance is just 1.271 ohms, it won't affect the functionality of the bidirectional shift register. The operating voltage range of the shift register is 2 to 6volts and it has an input current of 20mA. Therefore the wire resistance isn't going to affect the shift register.

### 2. Power battery

We need the battery to power the swim pacer for at least 4 hours continuously. Since we are not using an AC input from a power plug for safety reasons, we will need batteries to power the device.

Each of the LED has a rating of 0.03amps with 2.27V. The power dissipation is 0.068watts. Not all of the 100 LEDs are powered at once; only 2 of them are lit at one time. Therefore the LEDs will use 0.1362watts.

The two microcontrollers each uses roughly 0.042amps at 5v with nothing connected to it. Therefore they add up to around 0.42watts. The LCD has a rating of 0.3amps with 5v, which is 1.5watts. The seven shift registers are rated at 0.75watts each which has a totals of 5.25 watts. However only one led will be lit up when the shift register is running. Using a digital multimeter, the each shift register uses 5v with 0.05 amps, which uses 0.25. The total of seven shift register will use 1.75 watts

0.05

The 8 AA alkaline batteries will have roughly 1.5V each but since each battery is different; we will use 1.2V each for the battery which has a rating of 2amp-hour. Thus the batteries will add up to 24 watt-hour

Modules	Power usage (watts)
LED	0.1362 watts
Microcontrollers	0.42 watts
Shift registers	1.75 watts
LCD	1.5 watts
<b>Total</b>	<b>3.8062 watts</b>

$$24\text{watt-hour} / 3.8062 \text{ watts} = \underline{6.31 \text{ hours}}$$

With our design, the battery is able to last more than 6 hours of continuous usage. This is more than enough for a swim session and the users can use rechargeable batteries so that they could save money on batteries and be more environmental.

## V. Performance Requirements

The LED swim pacer consists of five modules: LCD, Main microcontroller, LCD microcontroller, shift register and the LEDs. We will use digital multimeter, lab equipment and test breadboard to simulate and test our circuit.

Since the LED strip will be 25meters long, we will test the LED on a breadboard to simulate its functionality. The shift registers will be tested to make sure the data and clock cycle from the main microcontroller is computed correctly. We will also make sure that the battery power will be enough to power the unit.

### 1. Testing & Verification

Requirement	Verification
1. LCD display information and interact with user inputs correctly	a. Powered by the microcontroller, LCD will be tested by receiving a test data from the LCD

<ul style="list-style-type: none"> <li>a. Display main menu when the power is turned on and the mode it's in</li> <li>b. Print and retrieve data</li> <li>c. Transmit data to main microcontroller</li> </ul>	<p>microcontroller to confirm that it's displaying the information correctly</p> <ul style="list-style-type: none"> <li>b. A test data will be sent from the user input which can be displayed on the Arduino serial monitor to confirm accurate information is received.</li> <li>c. A test data from the user input will be transmitted to the main microcontroller and these data will be displayed on the Arduino serial monitor to inspect the correctness of the data</li> </ul>
<p>2. Main Microcontroller should be able to receive mode and speed data from LCD microcontroller and decode and calculate clock cycle for the LED</p> <ul style="list-style-type: none"> <li>a. Receive data and decode it</li> <li>b. Transmit data to shift registers</li> </ul>	<ul style="list-style-type: none"> <li>a. A test data will be sent from the LCD microcontroller to the main controller. The data can be displayed on the Arduino serial monitor to ensure that correct data is received and correct calculations are computed.</li> <li>b. The microcontroller then transmit the clock cycle which can be displayed on the Arduino serial monitor to confirm that it has the correct data</li> </ul>
<p>4. LED unit should accurately light up when it receives a high signal from the shift registers</p> <ul style="list-style-type: none"> <li>a. Turn on and off accordingly</li> </ul>	<ul style="list-style-type: none"> <li>a. The LED and the shift register will be tested on a breadboard to confirm that it can be turned on and off correctly from the signal of the shift registers.</li> </ul>
<p>5. The LED strip will have a minimum time of 10 seconds and maximum time of 40 seconds</p>	<p>The LED will be tested both on the breadboard and actual finished product with a stop watch to make sure that it does indeed comply with the minimum of 10 sec and maximum of 40 sec accurately to the 100ms. This test is only for one way (25meters)</p>
<p>6. Power Supply</p> <ul style="list-style-type: none"> <li>a. Supply +5V to the microcontrollers</li> </ul>	<ul style="list-style-type: none"> <li>a. The power supply will be tested with a multimeter to ensure that it can power the two microcontrollers and all seven of the shift registers. It should measure 5v for a pass and if it's less than 2v or more than 7v, then the test will fail</li> </ul>

## VI. Cost and Schedule

### 1. Schedule

Week	Task	Member
1/16-1/30	Brain storming for idea Get RFA approved Start working on proposal	Jonathan Lee
	Start working on proposal	Yi-Liang Chen
2/6	Finish proposal	Jonathan Lee
	Search parts	Yi-Liang Chen
2/13	Detail electrical design schematics Research microcontroller implementation	Yi-Liang Chen
	Sign up for Design review Verification and tolerance analysis	Jonathan Lee
2/20	Complete flow charts and calculations Design review	Yi-Liang Chen
	Simulation, block diagram Design review	Jonathan Lee
2/27	Begin implementing microcontroller	Yi-Liang Chen
	Order parts Implement LCD and user input	Jonathan Lee
3/5	Microcontroller programming	Yi-Liang Chen
	LCD microcontroller programming	Jonathan Lee
3/12	Prototype of LED strip on breadboard	Yi-Liang Chen
	Implement and build LED strip	Jonathan Lee
3/19	<b>Spring Break</b>	Jonathan Lee, Yi-Liang Chen
3/26	Sign Up for Mock Presentation Program microcontroller	Yi-Liang Chen
	Test LED strip	Jonathan Lee
4/2	Assemble the product	Yi-Liang Chen
	Waterproof test	Jonathan Lee
4/9	Testing and Debugging	Yi-Liang Chen
	Verification of specifications, tolerance analysis	Jonathan Lee
4/16	Sign up for Demo and Presentation Finish Testing and Debugging	Yi-Liang Chen
	Work on final paper	Jonathan Lee
4/23	Demo and Presentation	Yi-Liang Chen

	Revise Final Report	Jonathan Lee
4/30	Finish final report	Yi-Liang Chen
	Presentation	Jonathan Lee

## 2. Parts list

Name	Hourly Rate (\$/hr)	Total Hours to complete (hrs)	Total= Hourly Rate*2.5*hours to complete
Jonathan Lee	\$32/hr	150 hrs	\$12,000
Yi-Liang Chen	\$32/hr	150 hrs	\$12,000
Total			\$24,000

Part Name	Part Number	Cost (\$)/unit	Quantity	Total (\$)
16x2 LCD display with 4 push buttons	HD44780	\$13.95	1	\$13.95
LED (Green)	LTL-4238	\$0.28	60	\$16.80
LED (Red)	LTL-307EE	\$0.28	40	\$11.20
Wire(100 inches) 22gauge	-	\$14.20	6	\$85.20
Energizer alkaline Battery AA	-	\$1.57	8	\$12.56
Resister ¼ watt 100ohm	-	\$0.02	100	\$2.00
Clear PVC Tubing (3/4 inch) 25 meters	-	\$30	1	\$30.00
Clear Silicone Sealant	-	\$6.95	1	\$6.95
Black Acrylic Sheet 24"x 24" x 3/16"	-	\$31.85	1	\$31.85
8-CH inverter	SN74LS540N	\$0.65	1	\$0.65
Arduino UNO board	ATmega328P-PU	\$29.95	2	\$59.90
Bidirectional Shift register	MC74HC299N	\$1.50	7	\$10.50
Total				\$281.56

Section	Total
Labor	\$24,000
Parts	\$281.56
Grand Total	\$24,281.56

## VII. Ethical issues

The safety of the users is very important and we don't believe the project have any ethical issues conflicting with the IEEE ethic code. IEEE Code of Ethics issue #9 states, "to avoid injuring others, their property, reputation, or employment by false or malicious action". Since the product will be submerged underwater, there might be a chance of causing electric shock to users. Therefore the product will be sealed tight and waterproofed. The main controller will also be waterproofed even though it will be on the ground most of the time. The power is supplied by batteries, not AC line input therefore it will reduce the potential danger of electric shock.