

1D LiDAR TOF Rangefinder

ECE 445: Senior Design

Chee Loh, Ping-Wen Wang, Xingliang Wu


Team 28

April 27, 2012

Introduction

- Objective:
 - Create a system that can measure the distance and speed of an object
- Applications
 - Object Detection on Cars
 - Speed Detection
 - Terrain Mapping

System Overview

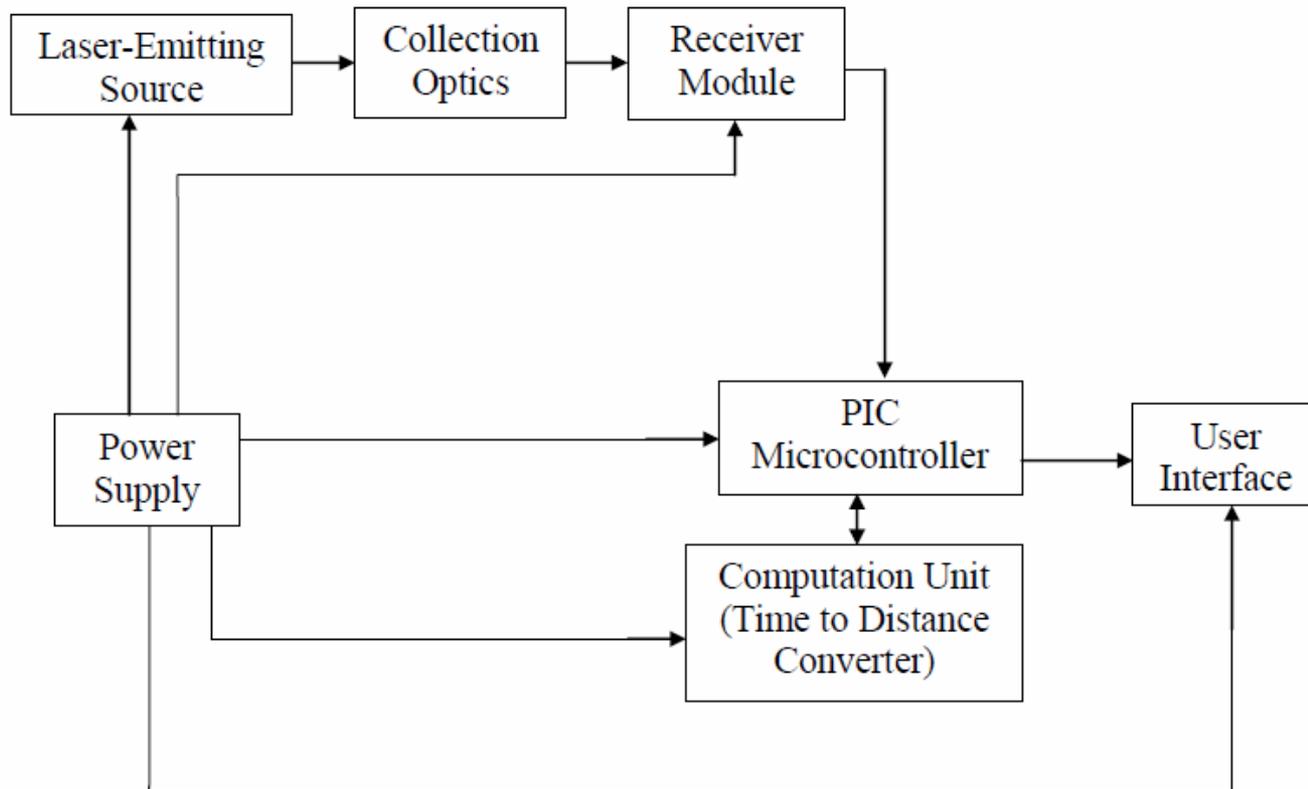


Original Design

- **Single, Avalanche Photodiode Receiver**
 - Costly
 - Requires high reverse bias voltage
 - Requires temperature control circuitry
- **Transimpedance Amplifier**
 - Amplifies both signal and unwanted noise
- **Bare Laser Diode**
 - Does not provide enough reception light
 - Cannot be mounted easily


Final Design

- **Dual, Monolithic Photodiode Receiver**
 - Inexpensive
 - Has built in transimpedance amplifier that can be adjusted
- **Differential Amplifier**
 - Subtract out environmental light from signal
- **Collimated Laser Diode Module**
 - Provides focused, current limited laser signal
 - Large module can be mounted more easily

Main Board Layout

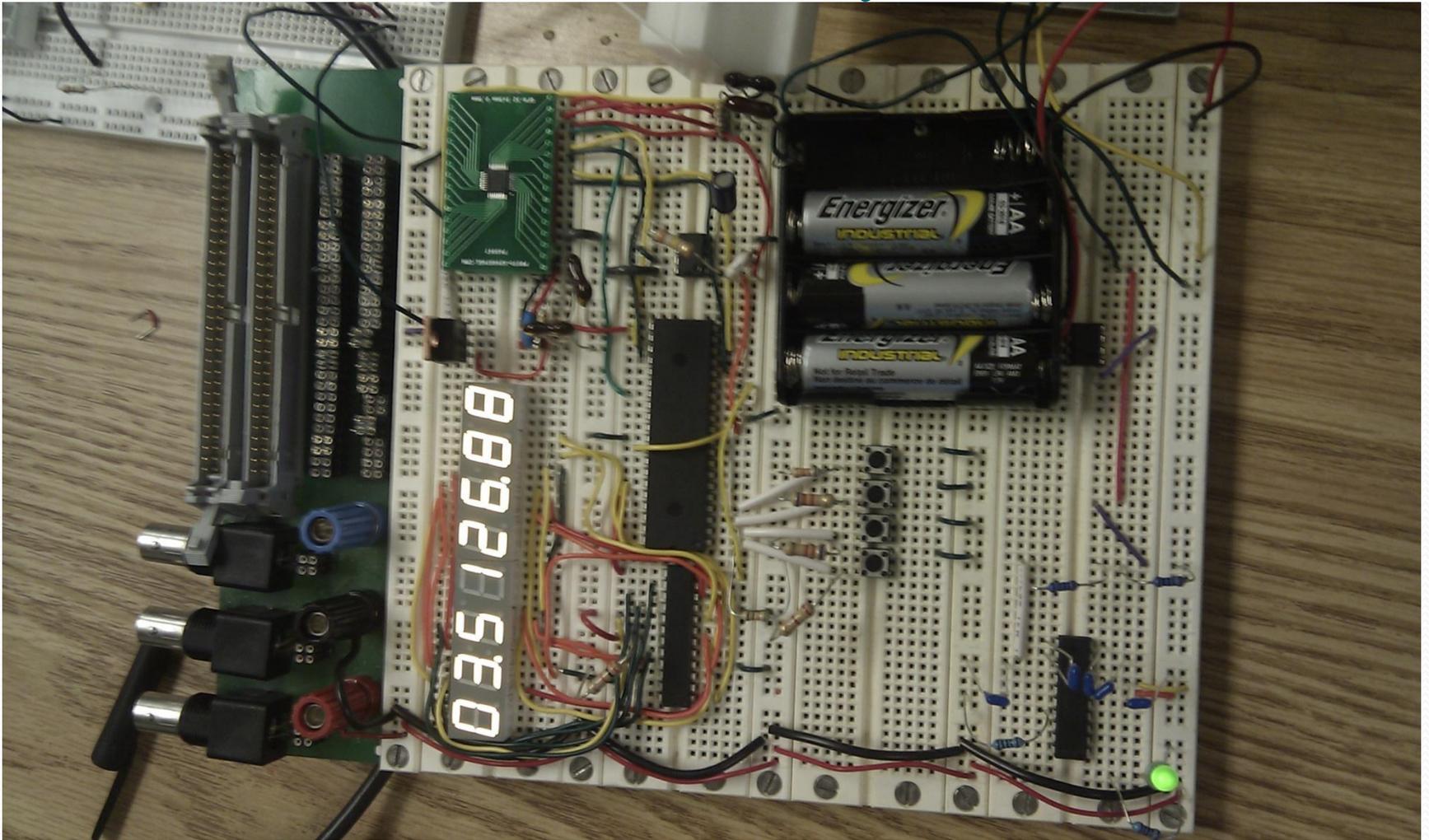

Transmission/Receiving Unit


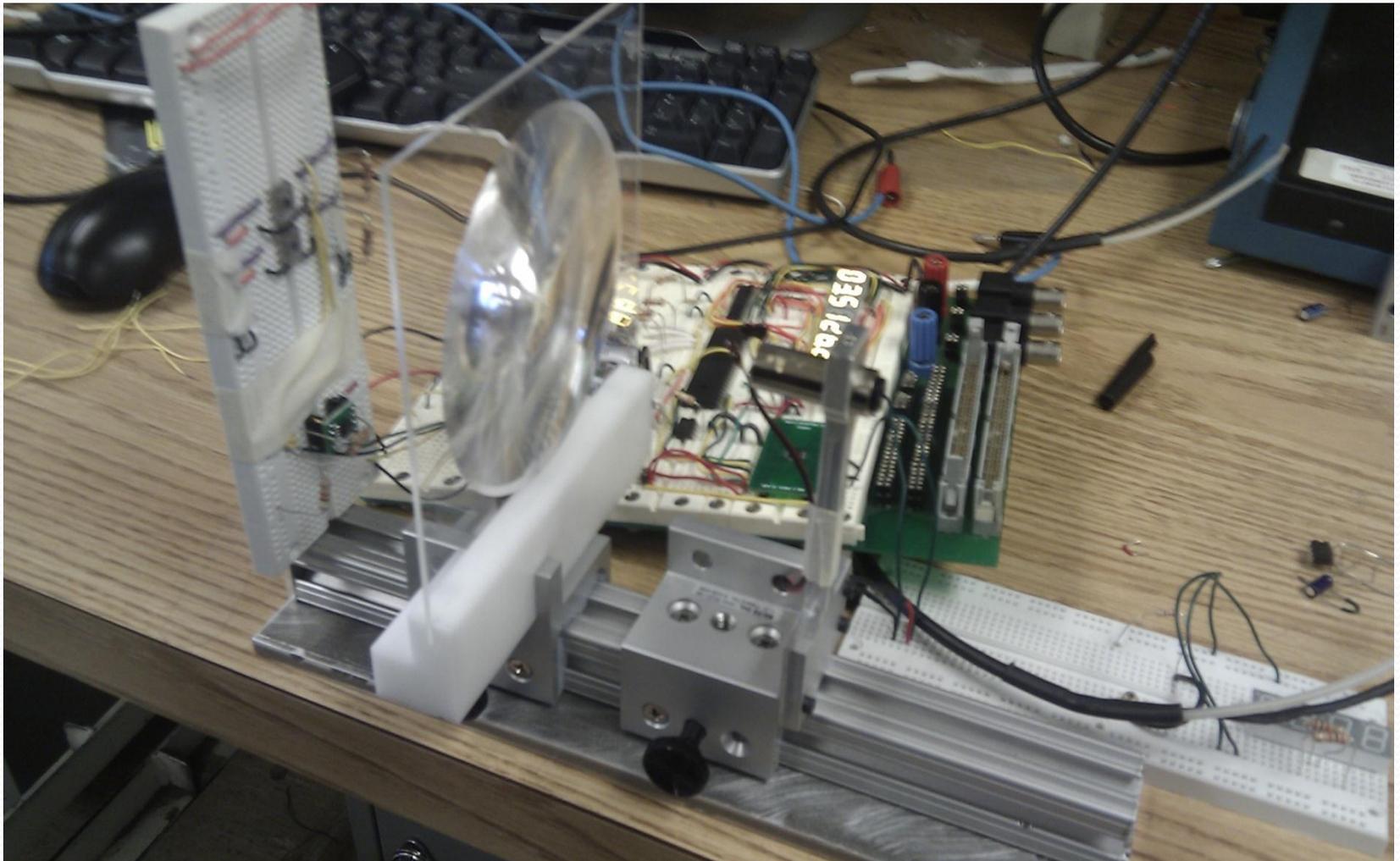


System Overview



- Hardware Components
 - Power Supply, Laser Driver, Transmission/Receiving Unit, Computation and Control Unit(PIC), User Interface, TDC Chip
- Software Components
 - PIC Control and Communication

Power Supply

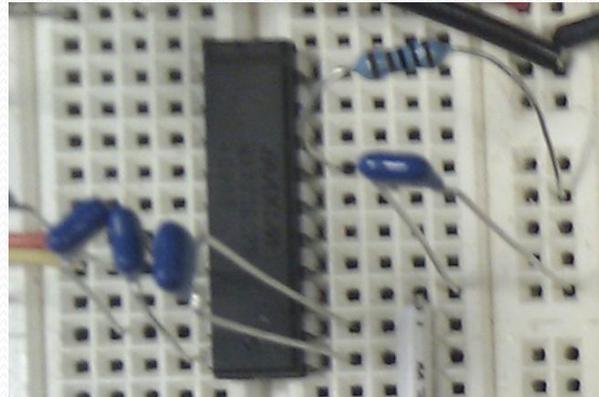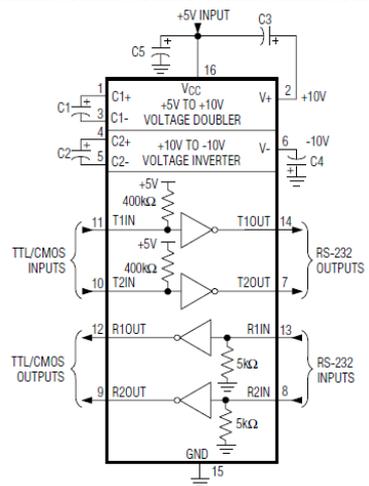- Provides 4.5 V to the system through AAA batteries
- Batteries used not only for portability but for cleaner power source than typical wall outlet
- Includes DC-DC converter(MAX232) for ± 9 V which are used to supply operational amplifiers





Supply Testing

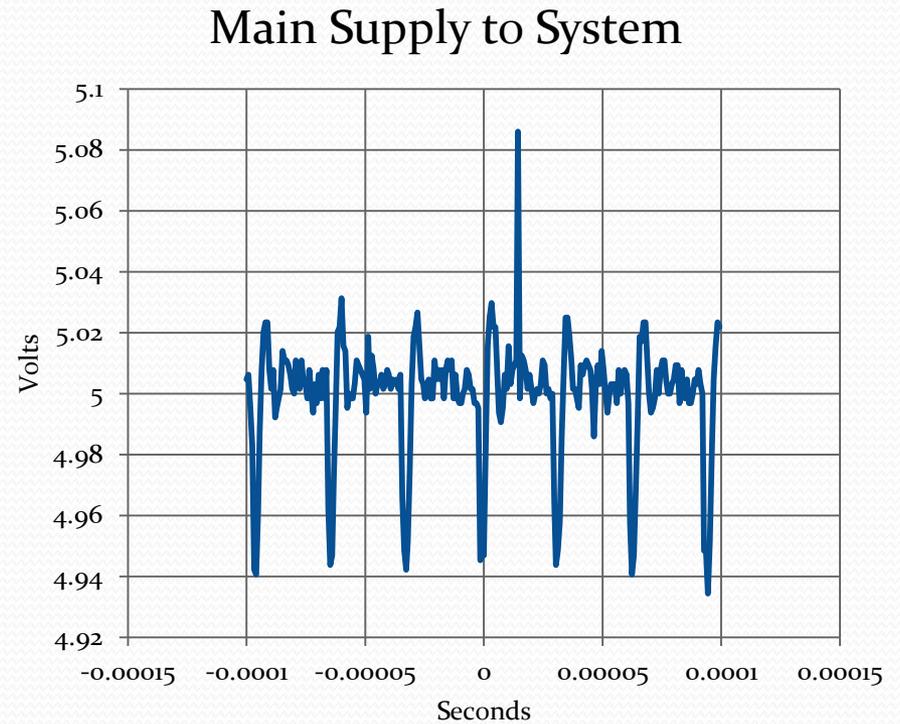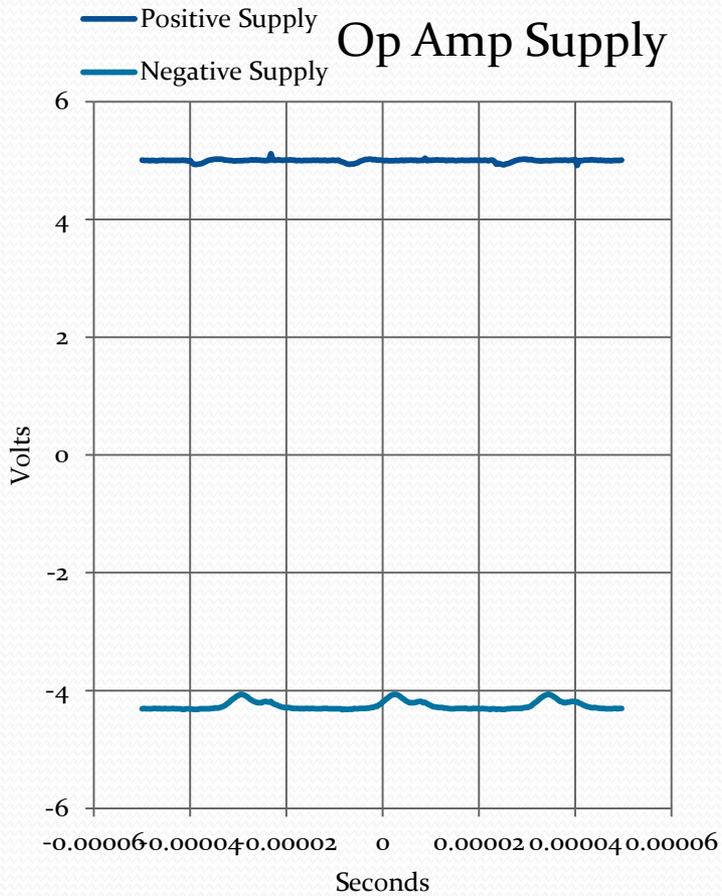


Power Supply

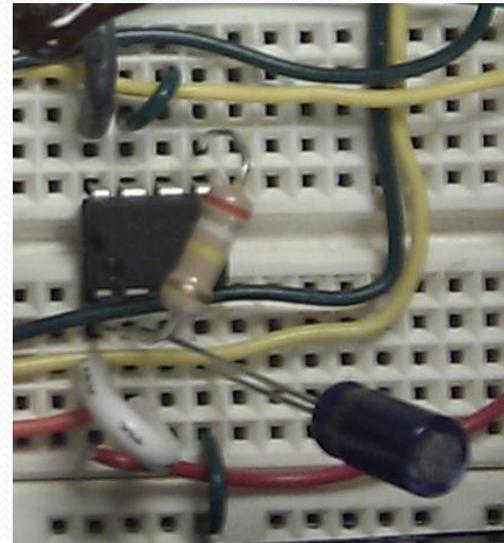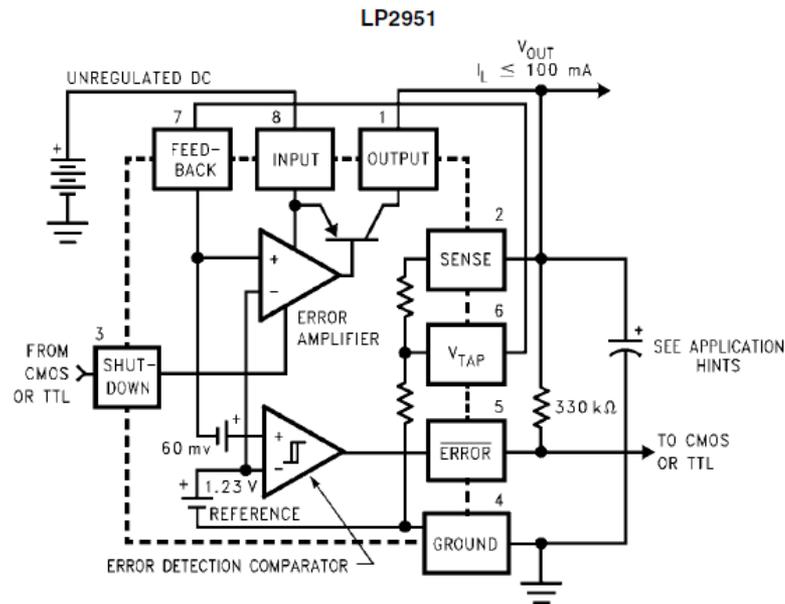- 3.3 V voltage regulator is also necessary to supply the TDC chip safely




Voltage Regulator Verification

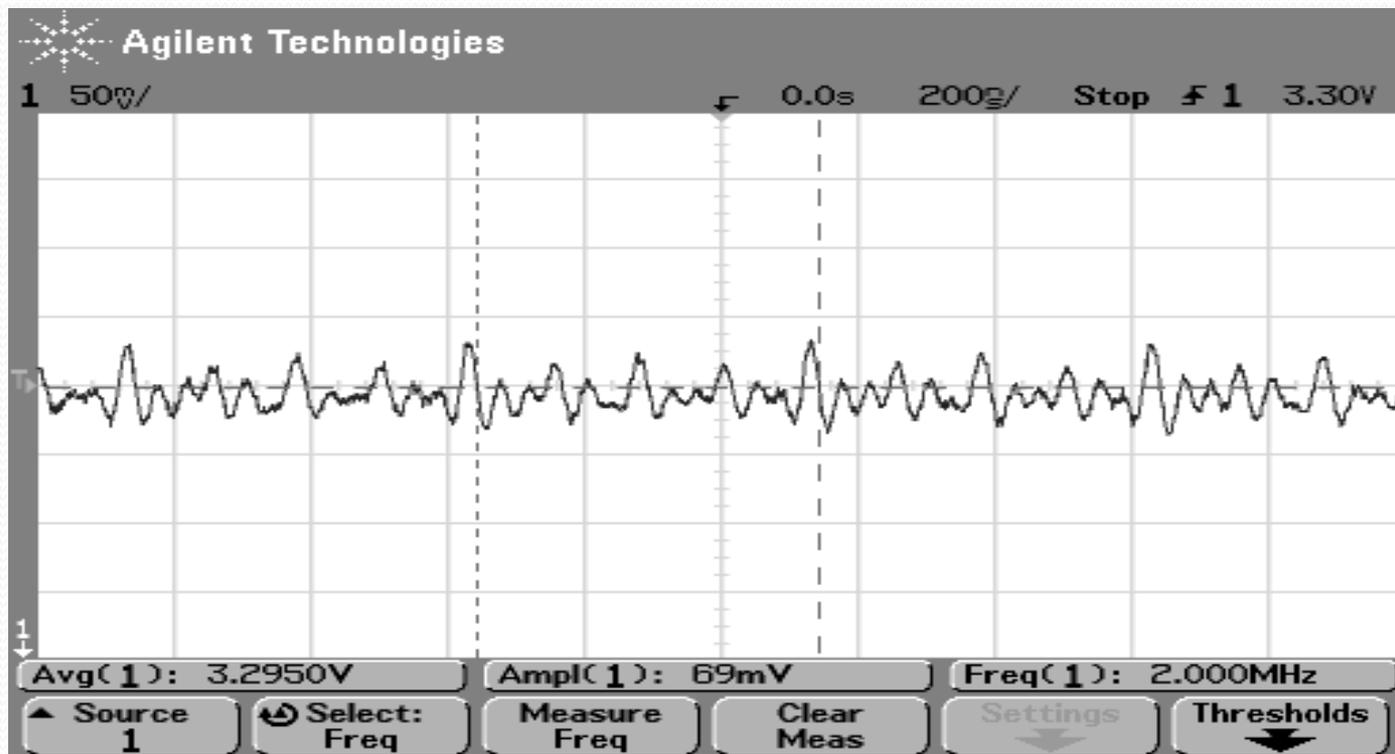- Average Voltage Level: 3.295 V
- Ripple: 69 mV
- Frequency: 2 MHz




Laser Driver

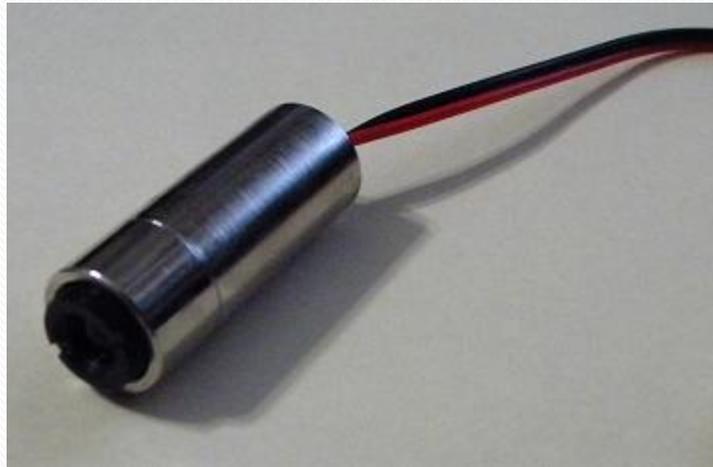- A 650 nm, 5 mW laser module is used to send measurement signals
- The module houses an internal current limiting circuit to protect the laser diode when driven




Laser Driver

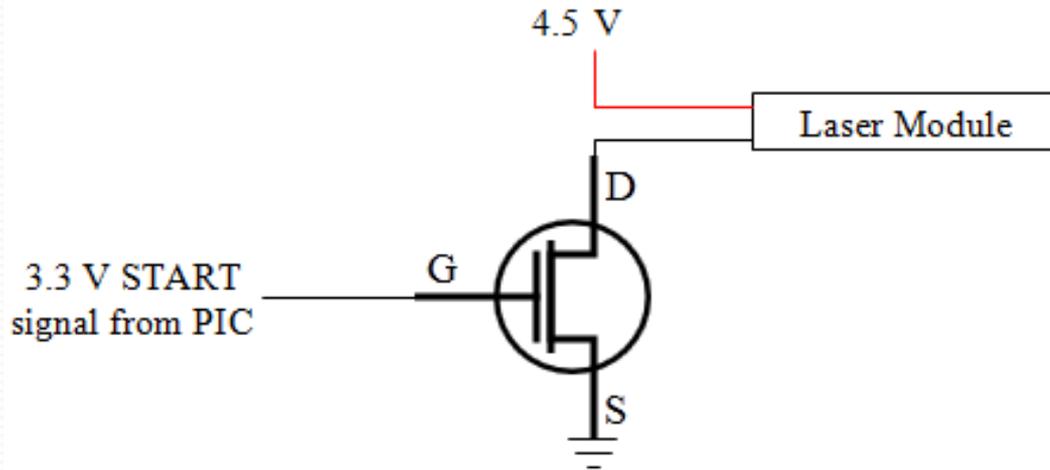- In order to supply the 4.5 V needed to source the module, the PIC's start signal is sent to a simple NMOS(MTP10N10EL) switch that is connected to 4.5 V dc





Laser Pulse Verification

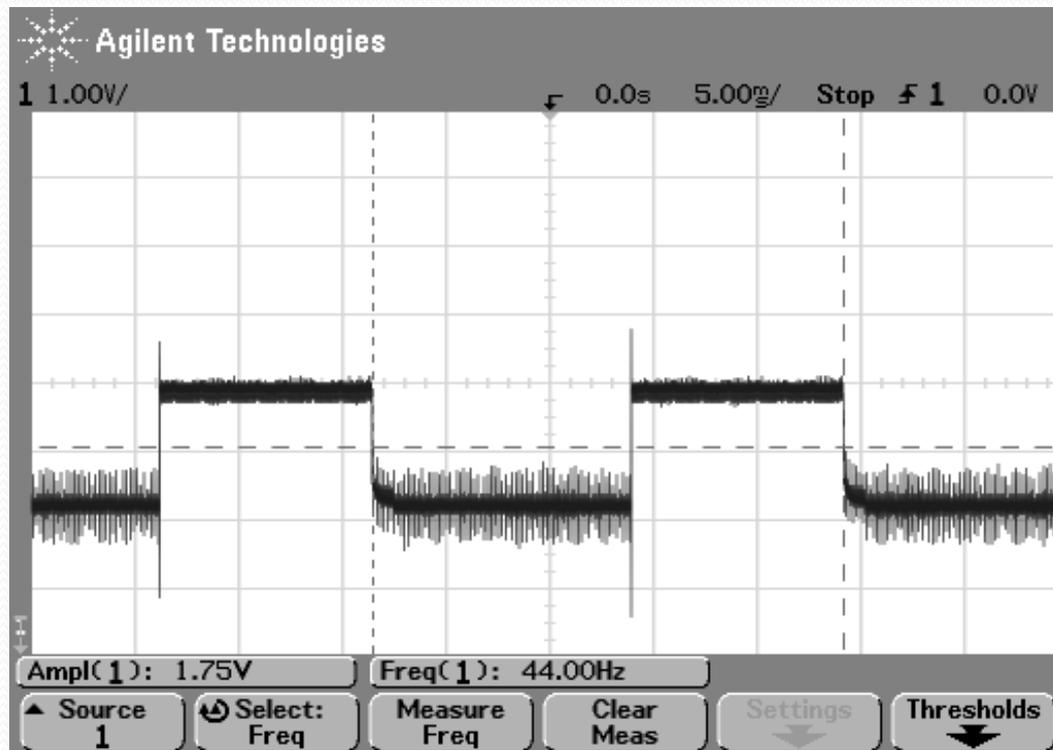- Total Measuring Time of ≈ 22.284 ms
- Results in Laser Frequency ≈ 44.875 Hz




Signal Transmission/Reception

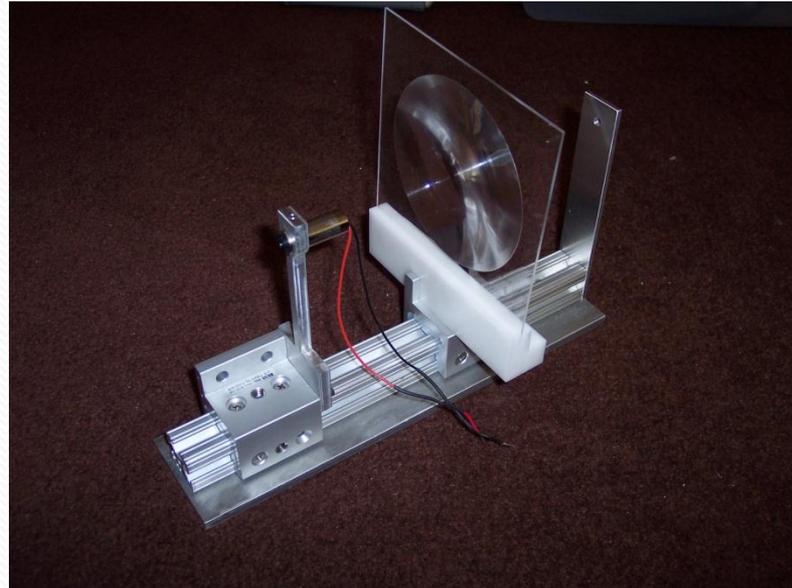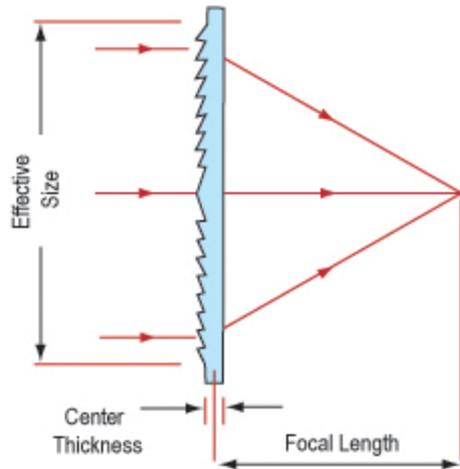- Original proposal: use simple laser diode
- However, the need for a collimated laser beam called for a laser module
- Fresnel lens implemented to collect return signal



Signal Transmission/Reception

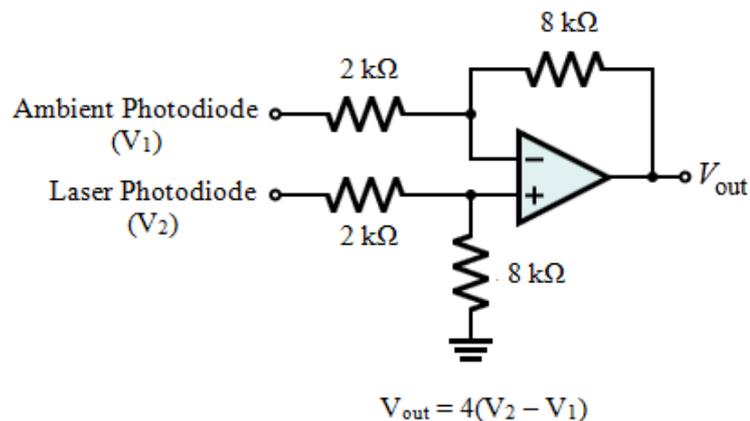- Photodiode Receiver
 - Switched from APD to regular photodiode in order to eliminate need for high reverse bias
- Differential amplifier implemented to take voltage difference from reception photodiode and ambient light photodiode





Receiver Response

Maximum Distances for Objects of Varying Reflectivity

- Presence of noise is due to divergence of received signal across both photodiodes

Reflective Metal: 5.5 m

Cardboard : 1.3 m

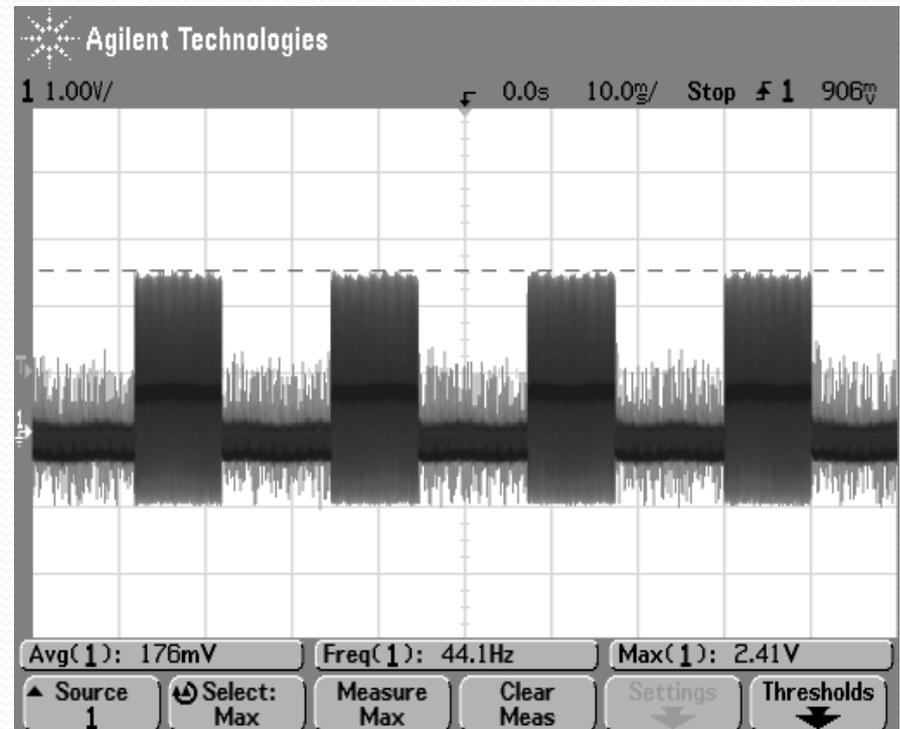
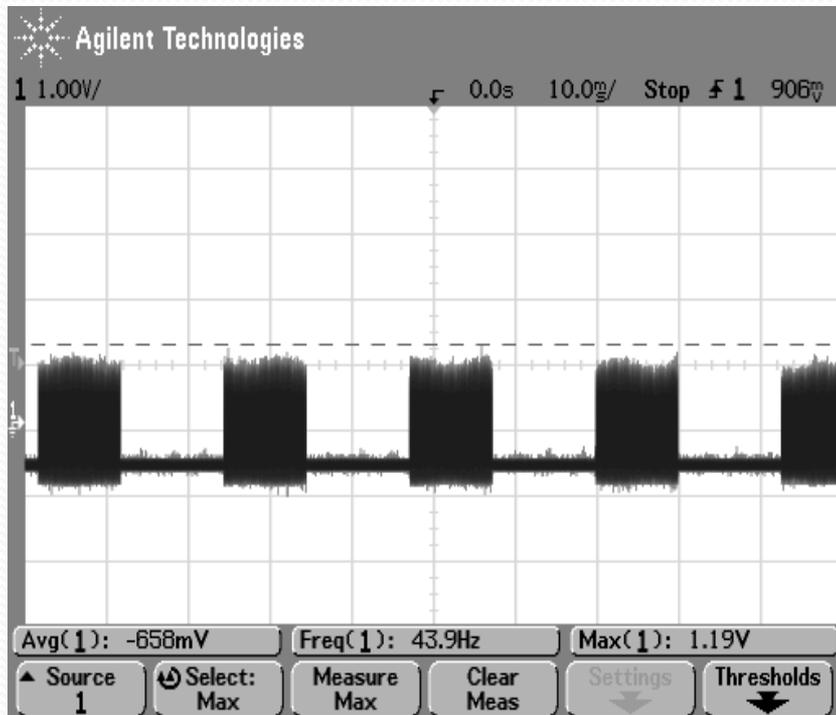


Receiver Response

Maximum Distances for Objects of Varying Reflectivity


Plastic Bottle: 0.7 m

Human Hand : 0.87 m

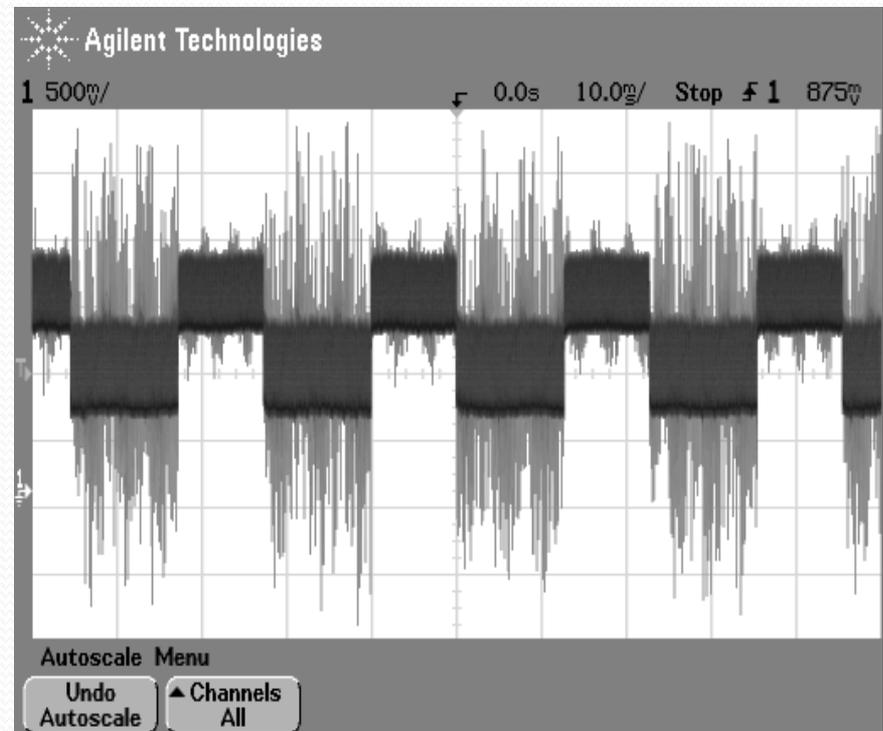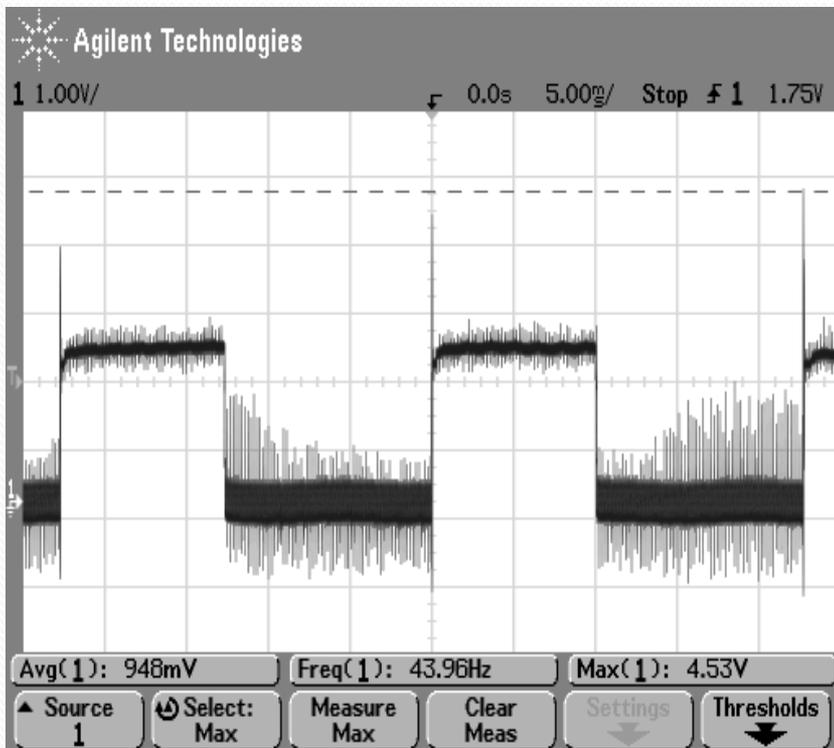


Control and Display

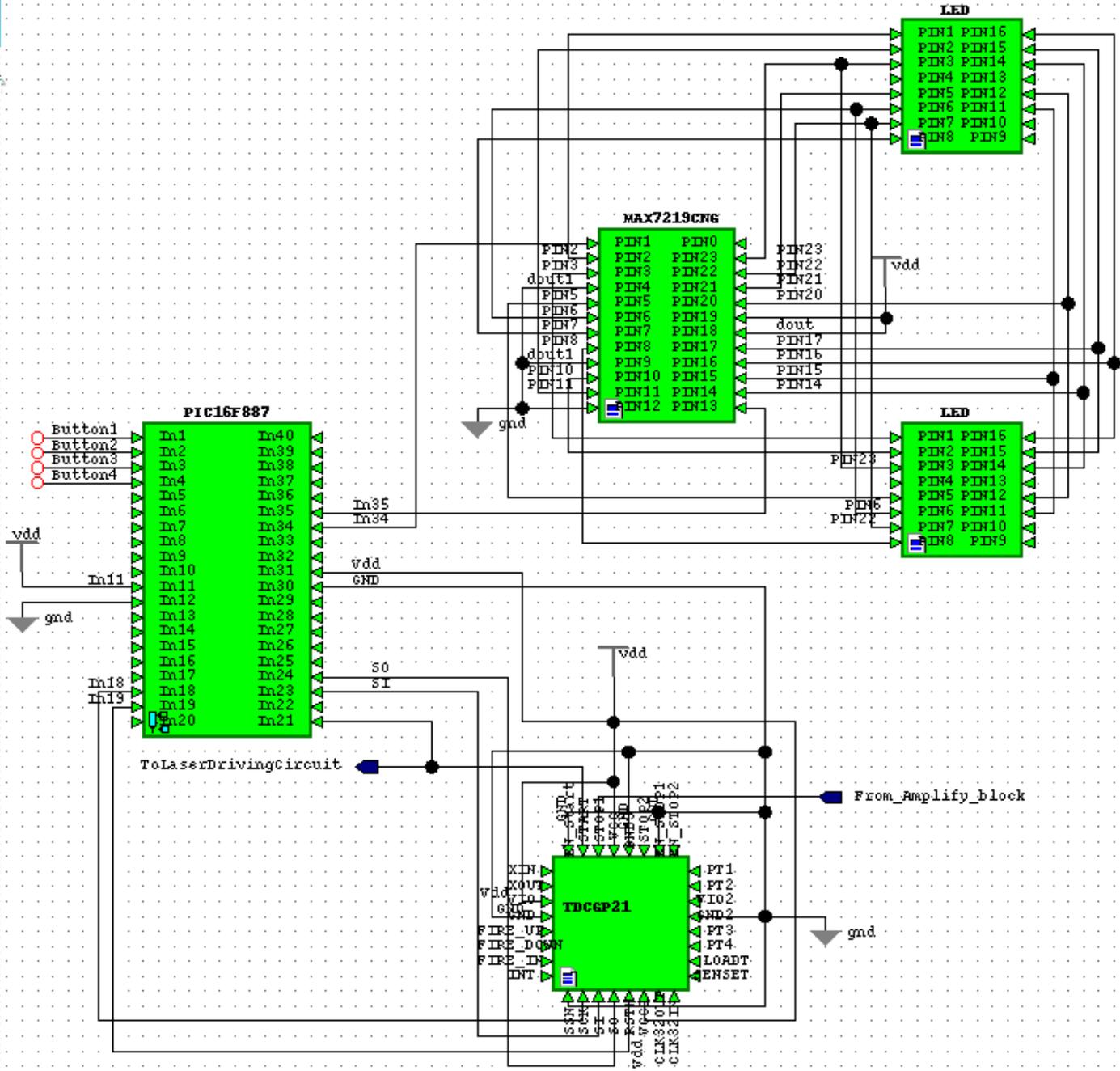- PIC16F887 provides the main control of our system
- PIC communicates with TDC chip when reading measurements as well as displays results on 7-segment display
- PIC also sends the start signal to the laser module to begin pulses
- A user interface provides: system reset and individual measurements



Control and Display



User Interface

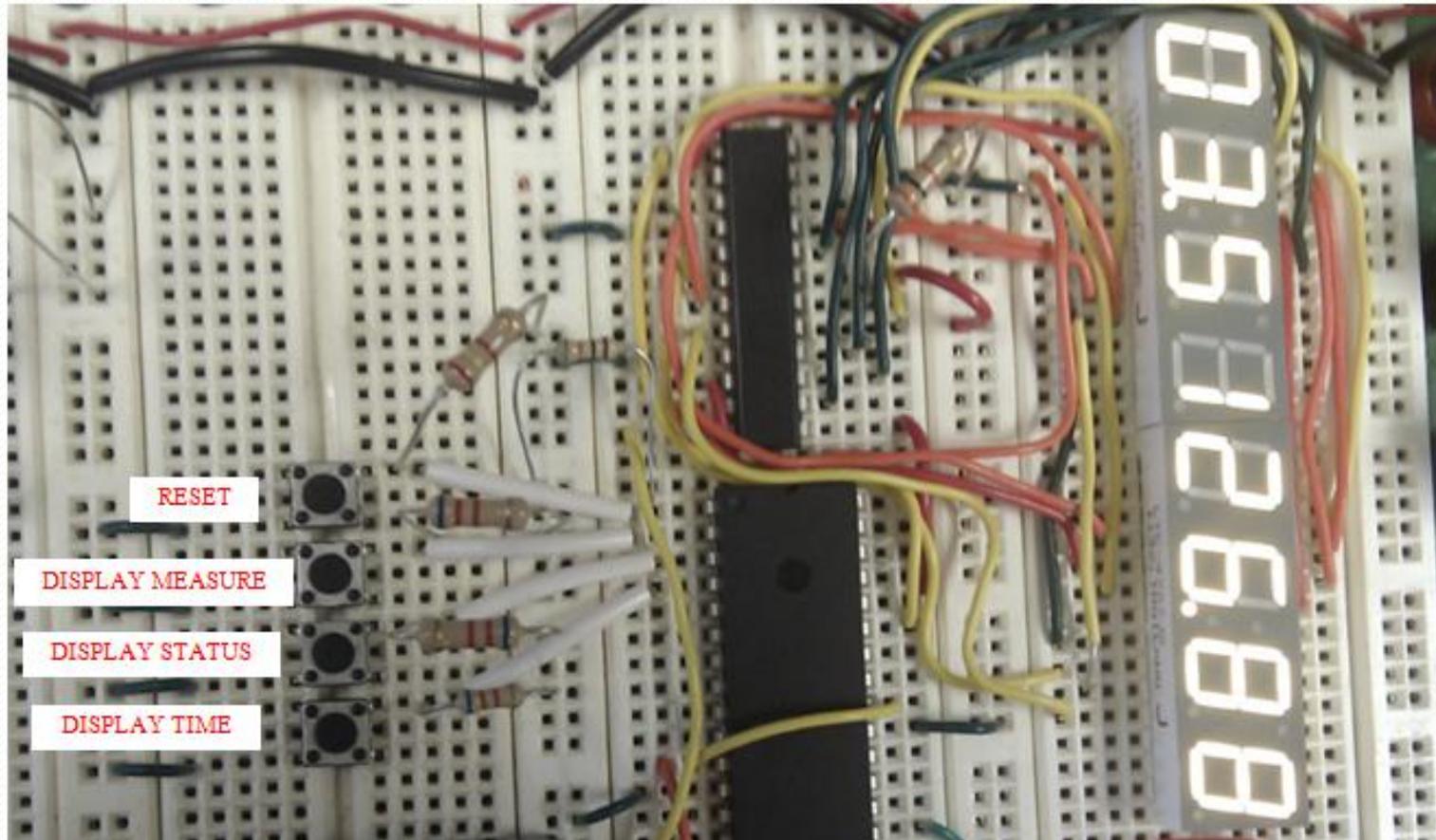

Time-of-Flight Measurement


- The TDC chip represents the most critical computation in our design
- Uses an internal capacitor in order to measure the time of flight of the laser pulse
 - Stop signal triggers a measurement of the voltage on the capacitor, leading to a time measurement
- Very accurate external oscillators(32.768 kHz and 4 MHz) are required for clocking and proper initialization

TDC Layout

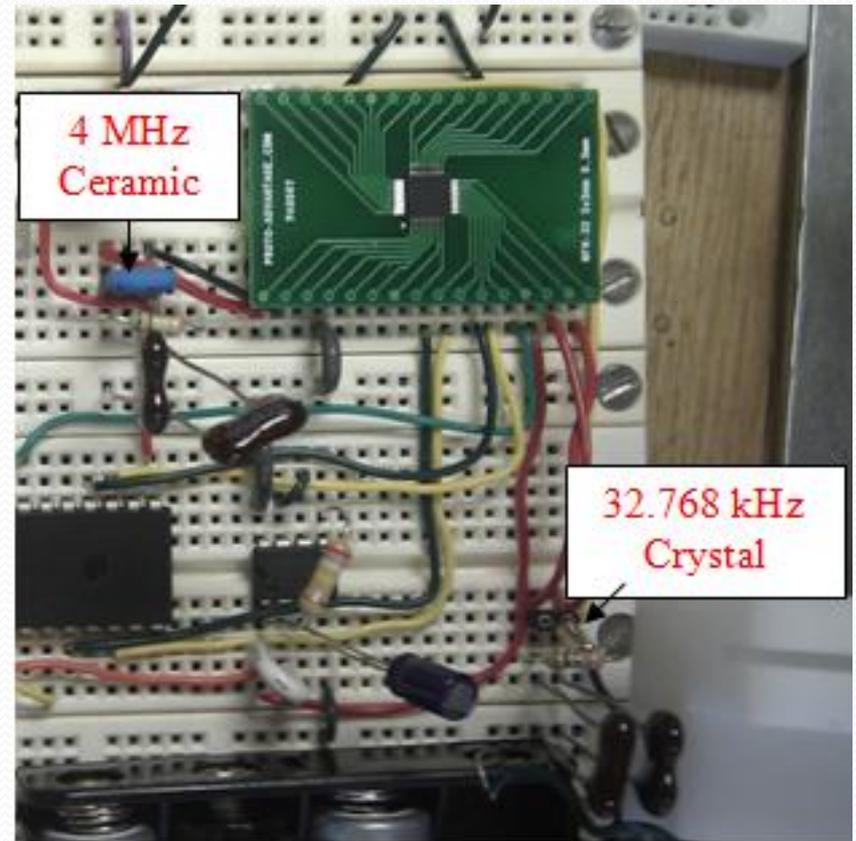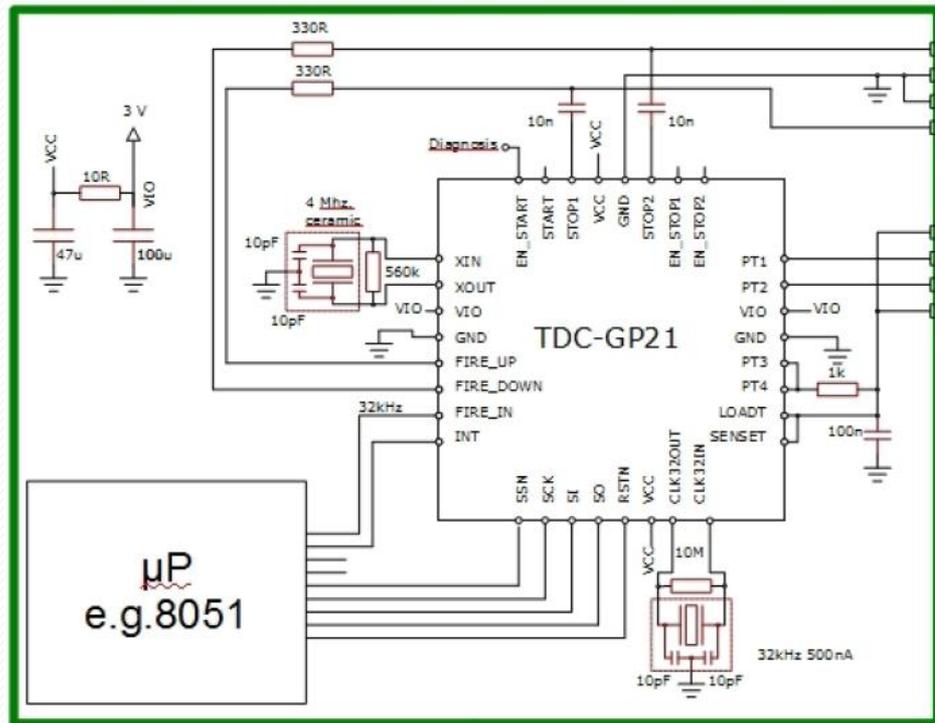


Measurement Results


Delay from NMOS Switch

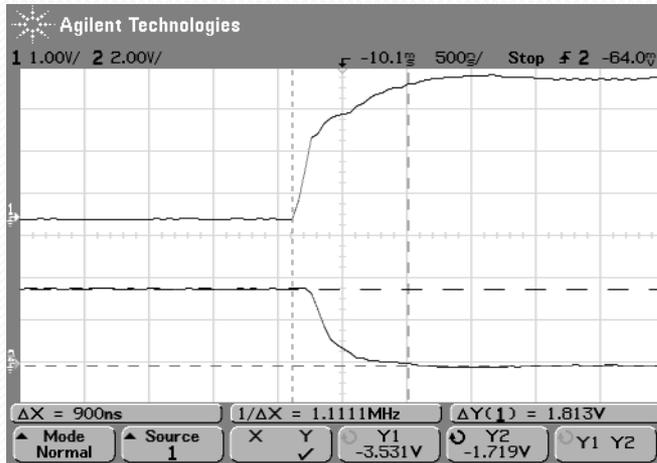


Delay from Laser through photodiode

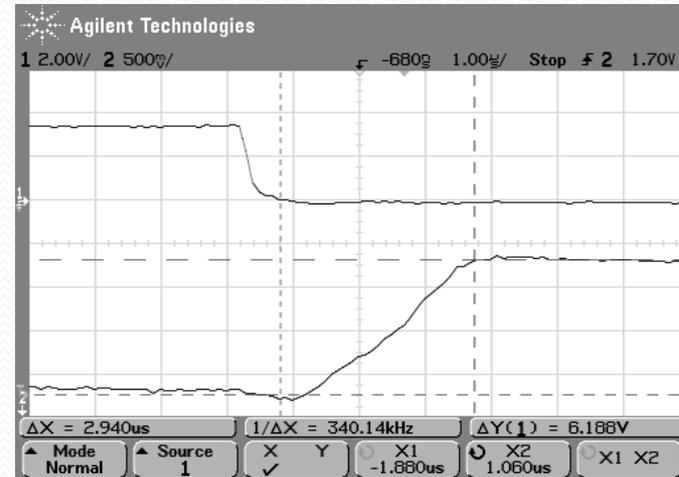

Delay from Differential Amplifier

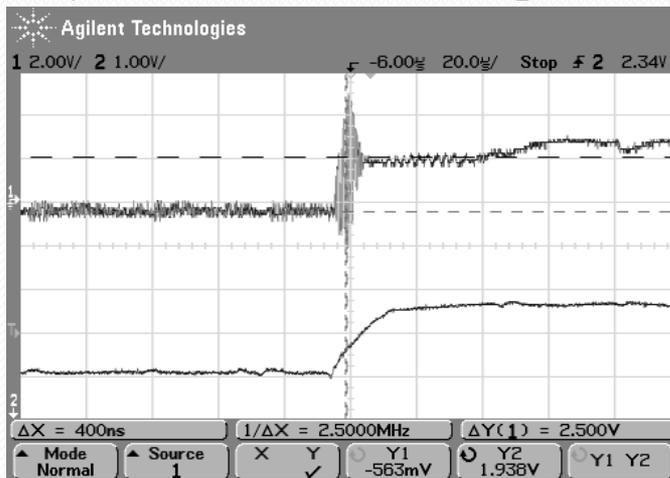

Total Delay from Start to Stop Signal

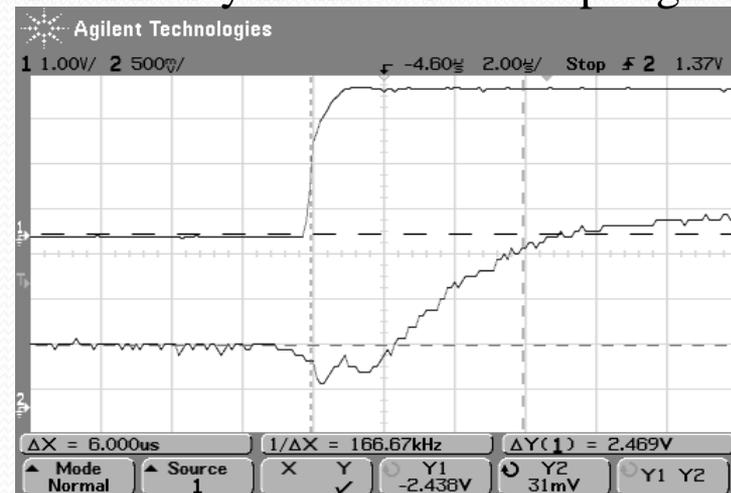

Measurement Results

Distance	Test 1	Test 2	Test 3	Test 4	Test 5	Test 6	Test 7	Test 8	Test 9	Test 10	Test 11	Test 12	1200 Point Average
1	3.02	2.85	1.35	3.97	5.25	1.29	2.94	3.13	2.07	1.02	1.1	1.43	2.942
2	2.21	0.78	0.82	1.44	1.48	2.04	0.85	2.74	1.68	0.78	1.59	1.61	1.802
3	1.35	1.79	1.37	1.17	3.7	0.2	1.75	2.06	3.61	3.73	1.17	1.73	2.363

- Clearly, inconsistencies in measurements lead to inaccurate results that need to be improved...

Successes

- Successful communication with TDC
- Successful transmission and reception of laser signal
- Successful calculation algorithms, user interface, and display

Challenges

- Initial communication with TDC chip
- Maintaining sensitivity as well as responsiveness on photodiodes
- Slow component response times lead to inaccurate and inconsistent results

Suggestions for Future Work

- Improve response times on remaining components
- Upgrade to TDC-GPX for improved resolution
- Upgrade to APD for improved distance and response time
- Implement circuitry on PCB in order to isolate components and minimize parasitic capacitances, further minimizing inconsistencies

Special Thanks

- Generous Funding
 - Professor Carney
- Machine Shop
 - Scott McDonald
- Parts Shop
 - Skot Wiedmann
 - Mark Smart
 - Wally Smith
- TA and Lab Assistance
 - Mustafa Mir
 - Alex Suchko



Questions?

Thank You!

Works Cited

1. <http://datasheets.maxim-ic.com/en/ds/MAX220-MAX249.pdf>
2. <http://www.ti.com/lit/ds/symlink/lp2950-n.pdf>
3. <http://www.aixiz.com/store/images/1230.jpg>
4. <http://www.edmundoptics.com/products/displayproduct.cfm?productid=2040>
5. http://www.acam.de/uploads/media/DB_GP21_en_04.pdf