



ECE 445 – Senior Design

Multi-Source, High-Power Converter

Spring, 2012


Viktor Terziysky
Eric Kapinus

Introduction

- Idea:
 - Convert standard AC voltages (Europe and U.S.) back and forth
 - Convert running car battery DC voltage to either AC standard
- Motivation:
 - Bridge gap between international AC voltages
 - Power critical items from running car battery during power outage
 - Supply high power to power tools or communication devices if car breaks down on the road

Overview

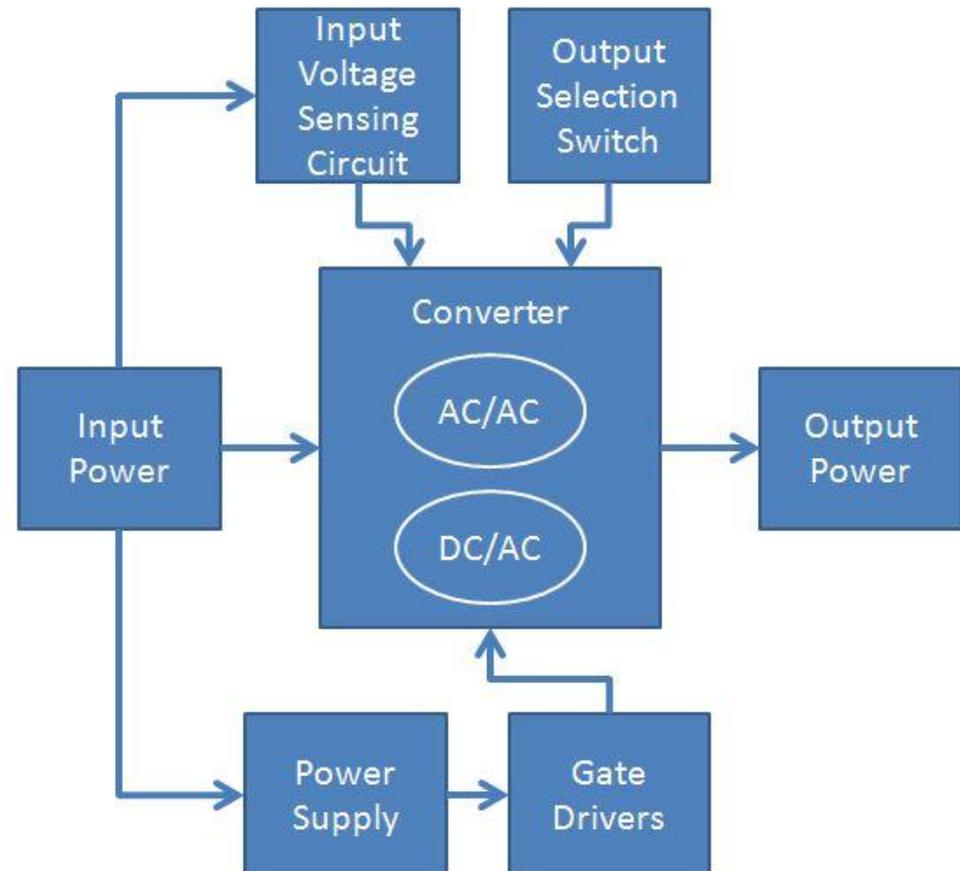- Inputs:
 - 115Vac/60Hz
 - 230Vac/50Hz
 - 14Vdc
- Outputs:
 - 115Vac/60Hz
 - 230Vac/50Hz
- Maximum Power:
 - 1,000 W for DC-AC
 - 650 W for AC-AC




AC/AC Circuit: General Topology




- AC input voltage is fed into 1:2 or 2:1 transformer
- AC signal is then rectified using a full wave diode bridge and a filtering capacitor
- Rectified DC voltage is then switched at the appropriate frequency (60Hz or 50Hz) using a MOSFET bridge
- A VSI wave is received at the output


AC/AC Converter: Initial Design

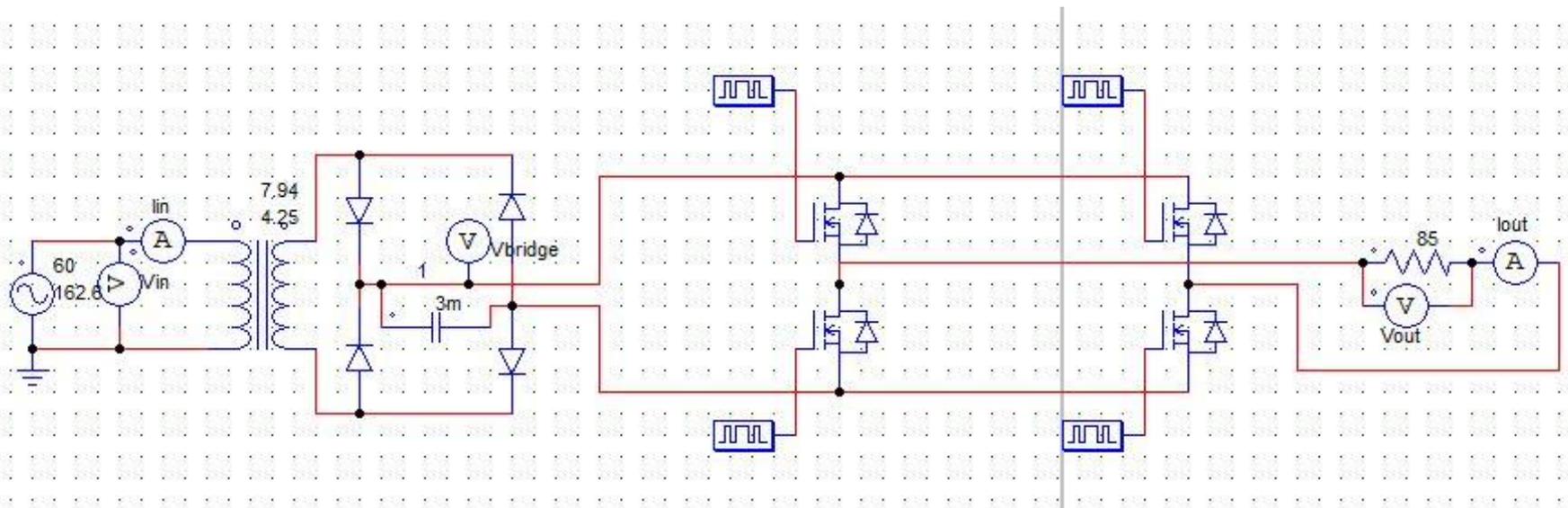

AC/AC Converter: Actual Implementation


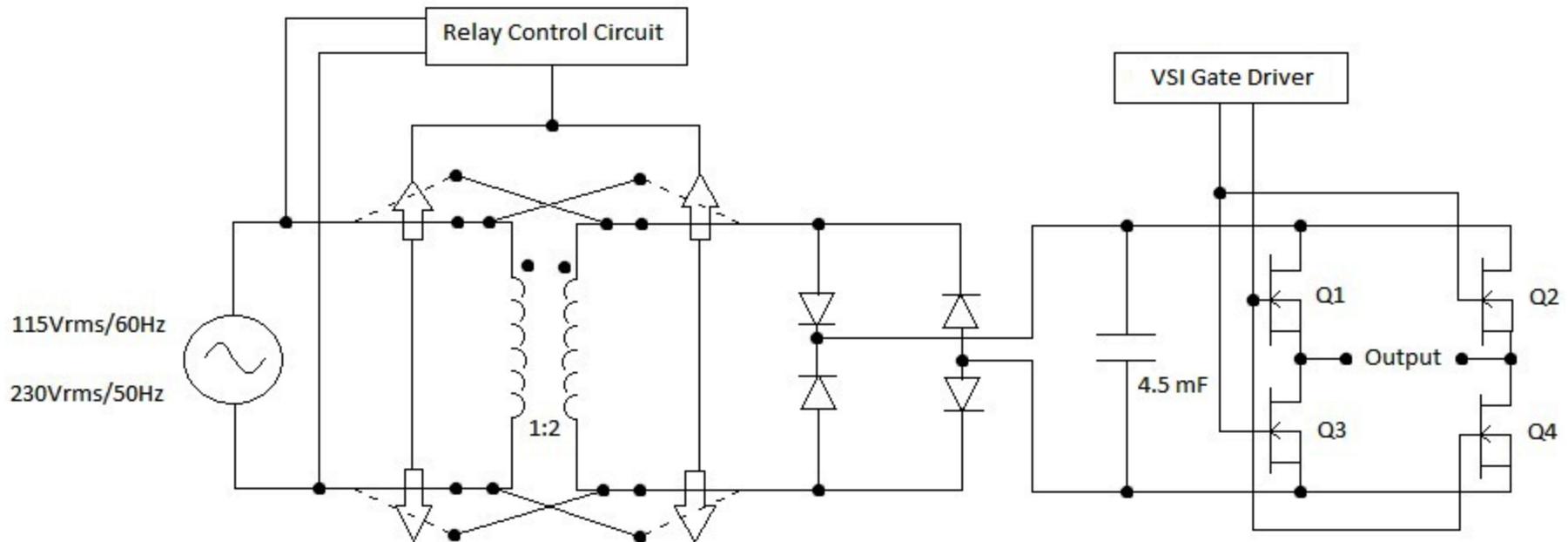


Automatic Step-up/Step-down Selection

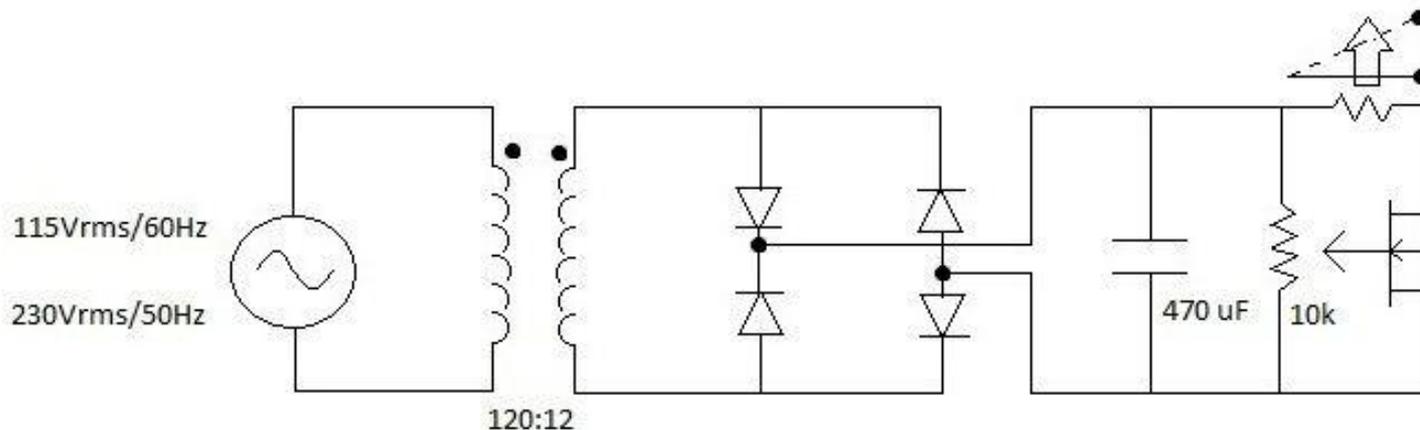


- Uses small transformer to step down the input voltage
- Diode bridge and filter capacitor rectify input voltage to 12Vdc/24Vdc
- Potentiometer creates a voltage divider
- 115V input $\rightarrow V_{gate} < V_{threshold} \rightarrow$ Relay stays in initial position
- 230V input $\rightarrow V_{gate} > V_{threshold} \rightarrow$ Relay switches to second position


VSI Circuit and Waveforms

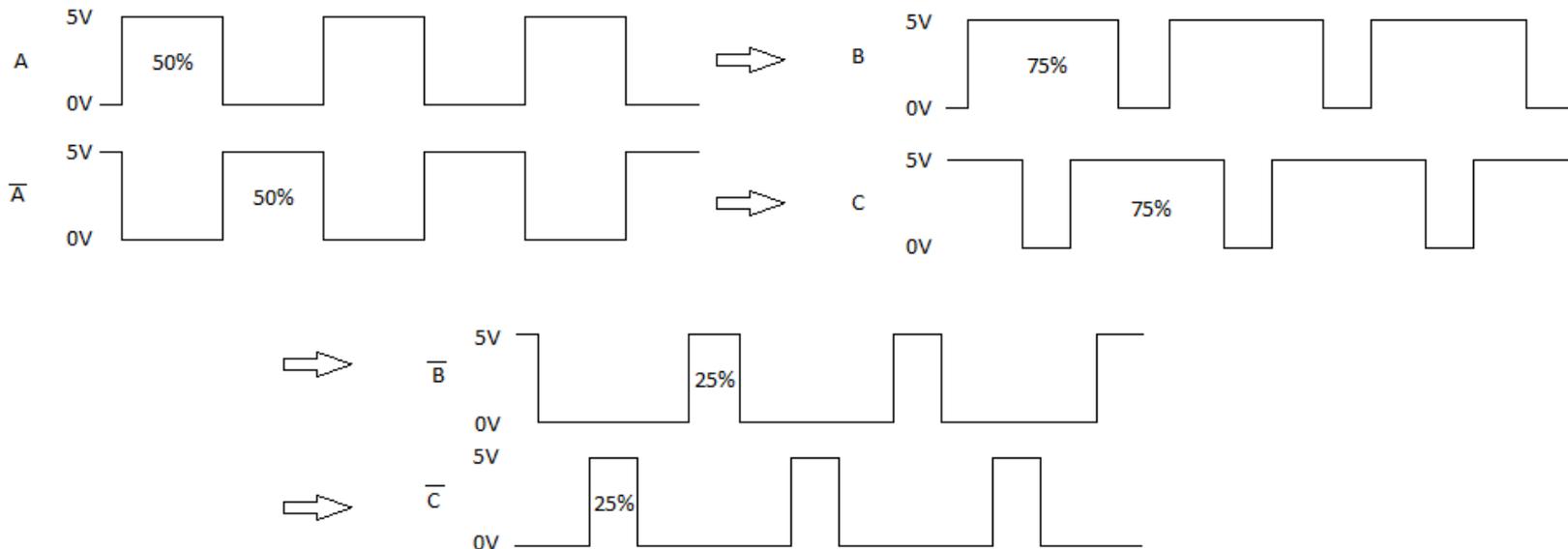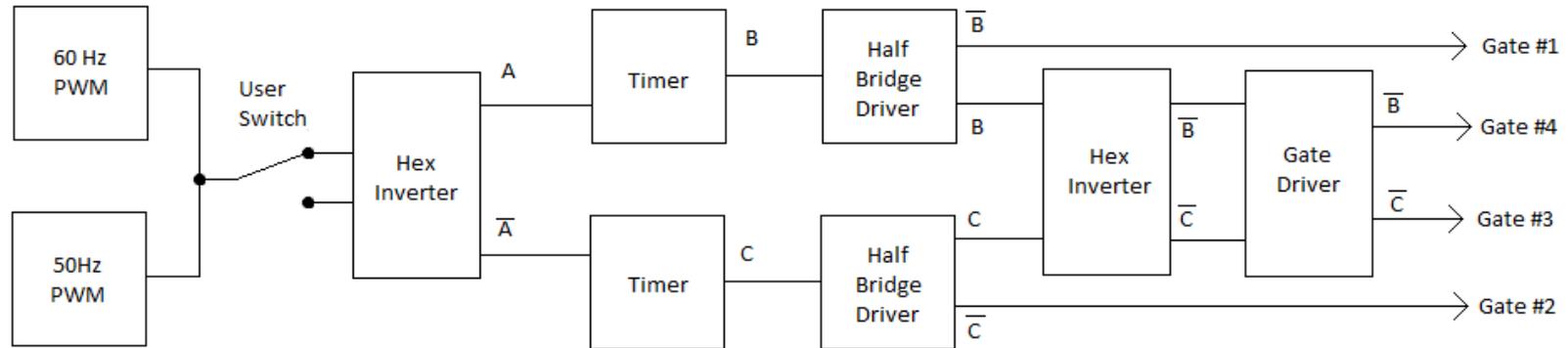



The Importance of a VSI Waveform

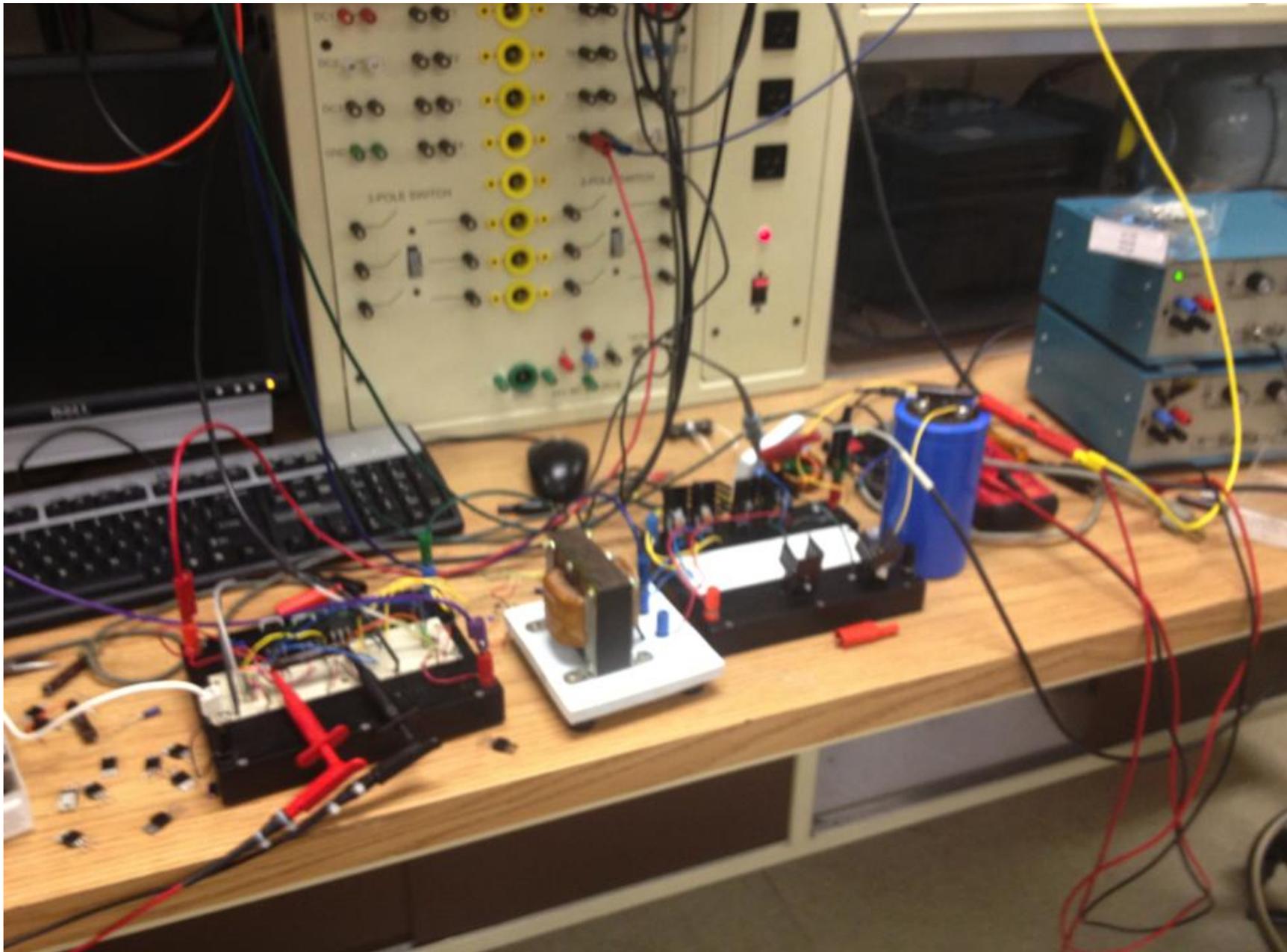
- Rectifier and filter capacitor create a DC voltage based on peak value of AC waveform
- $115V_{rms} = 163V_{peak} \rightarrow 163V_{dc}$
- $230V_{rms} = 325V_{peak} \rightarrow 325V_{dc}$
- If switching had 50% duty ratio, outputs would be 163Vrms and 325Vrms
- To achieve outputs of 115Vrms and 230Vrms, dead time between switches must be introduced
- Switching signals need 25% duty ratio



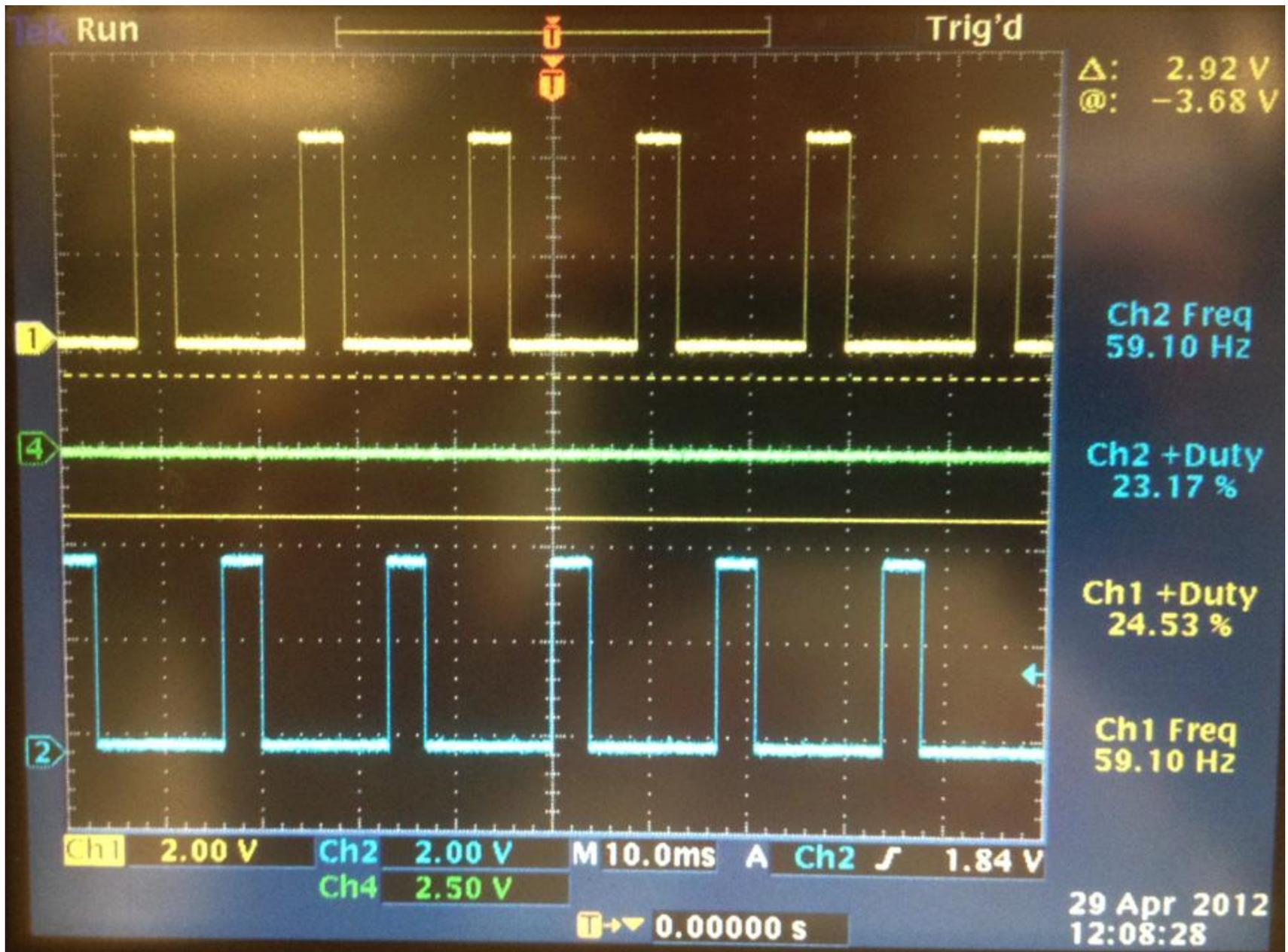


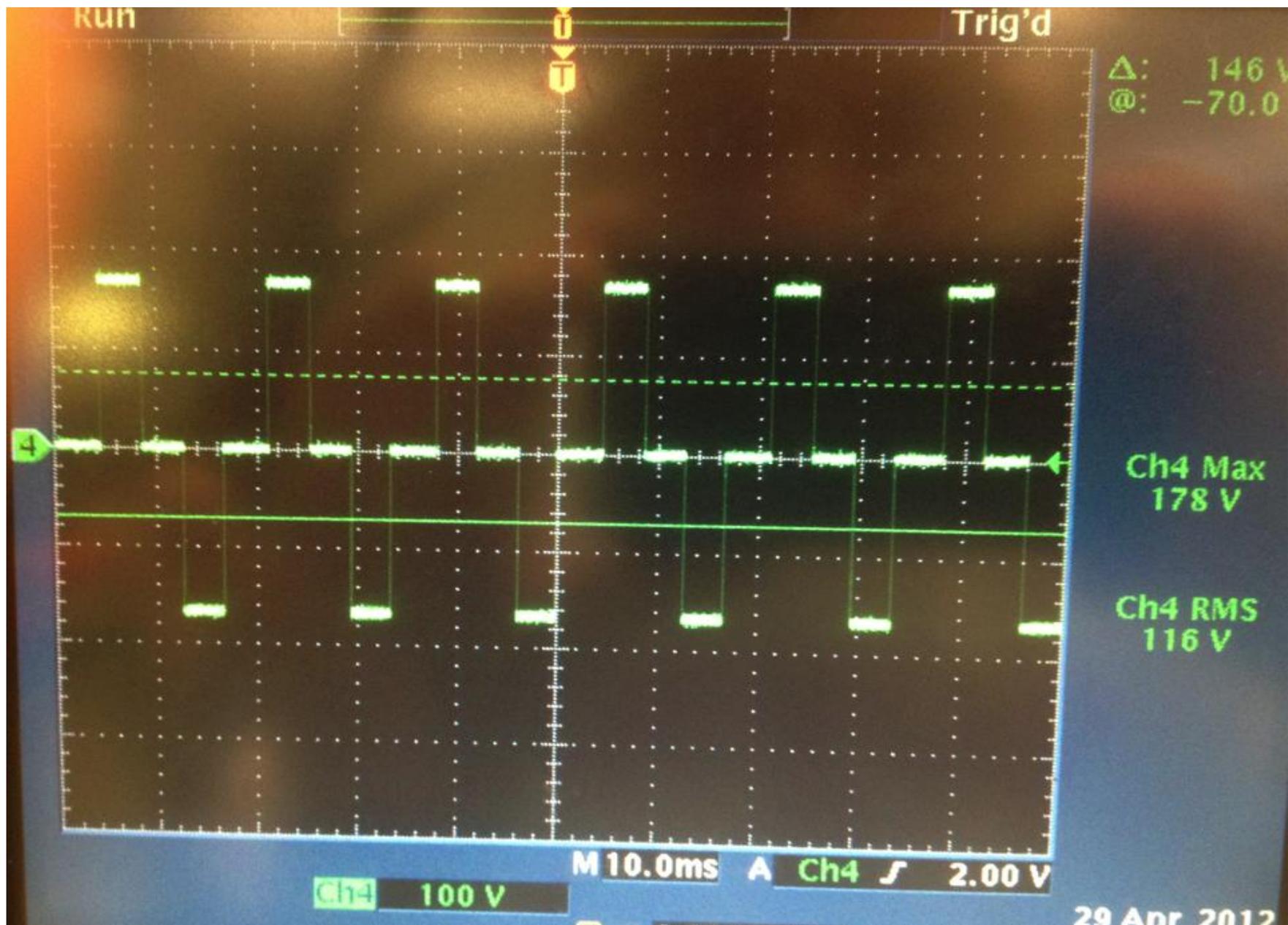

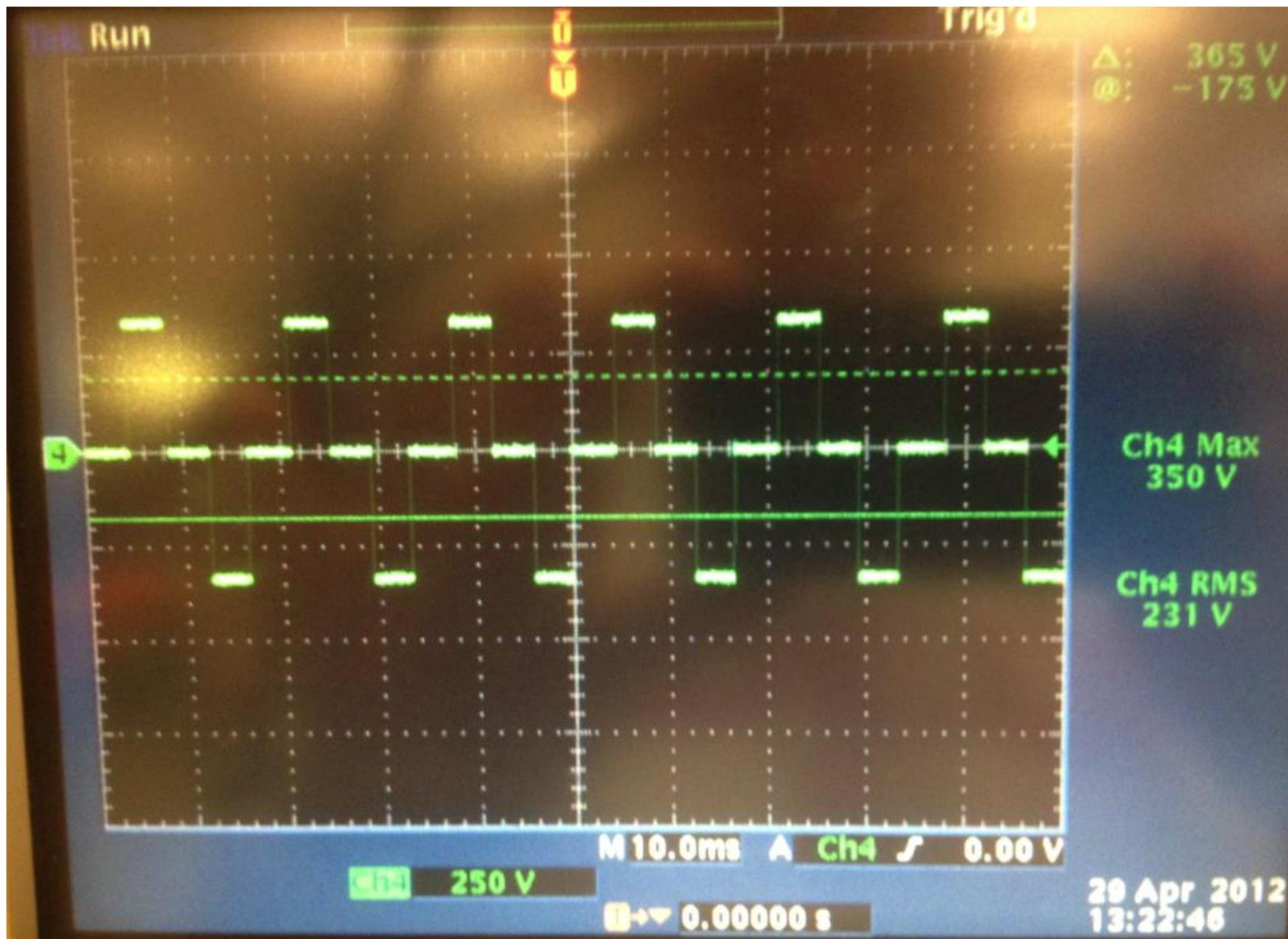


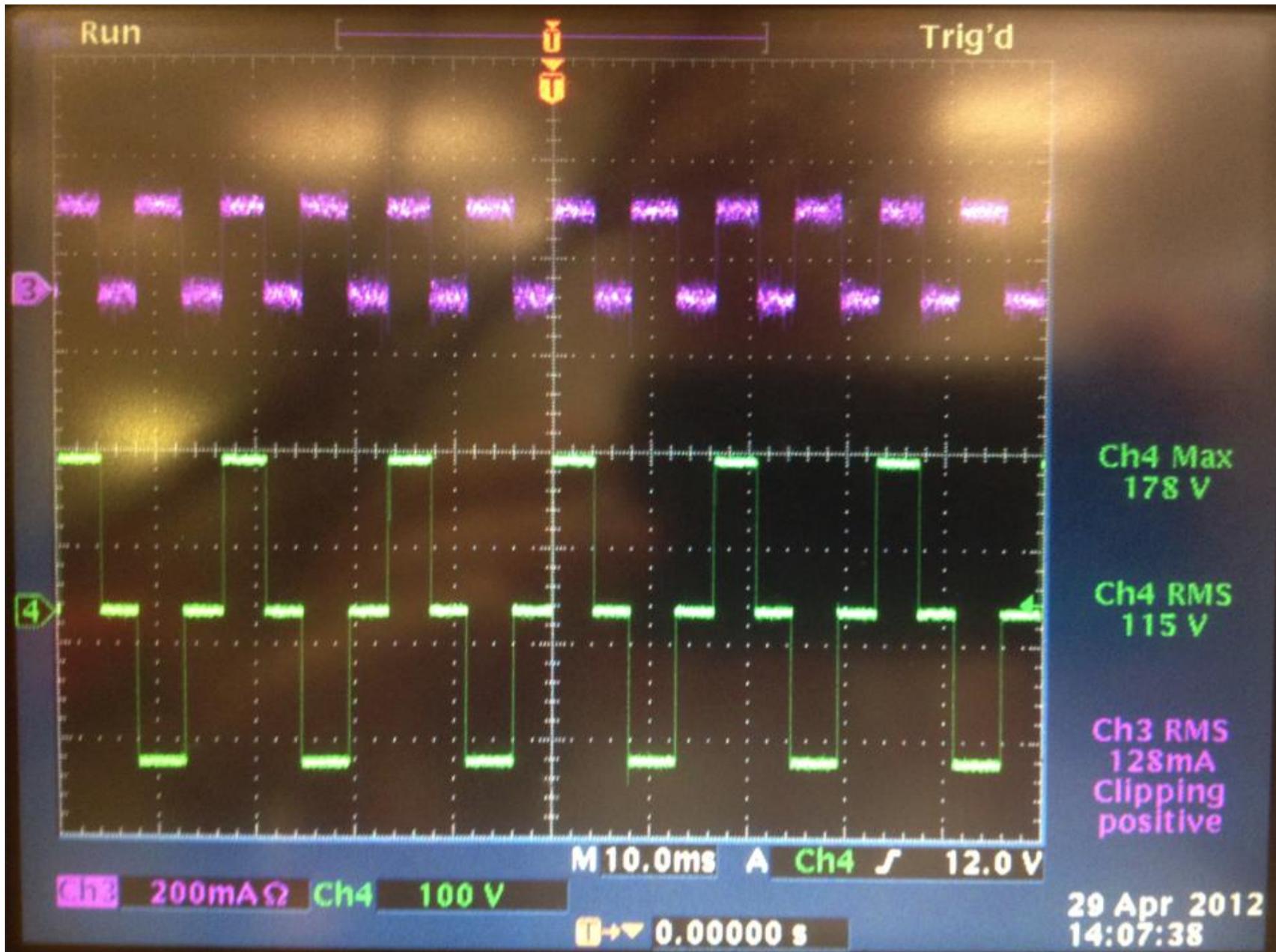

Rectifier Efficiency

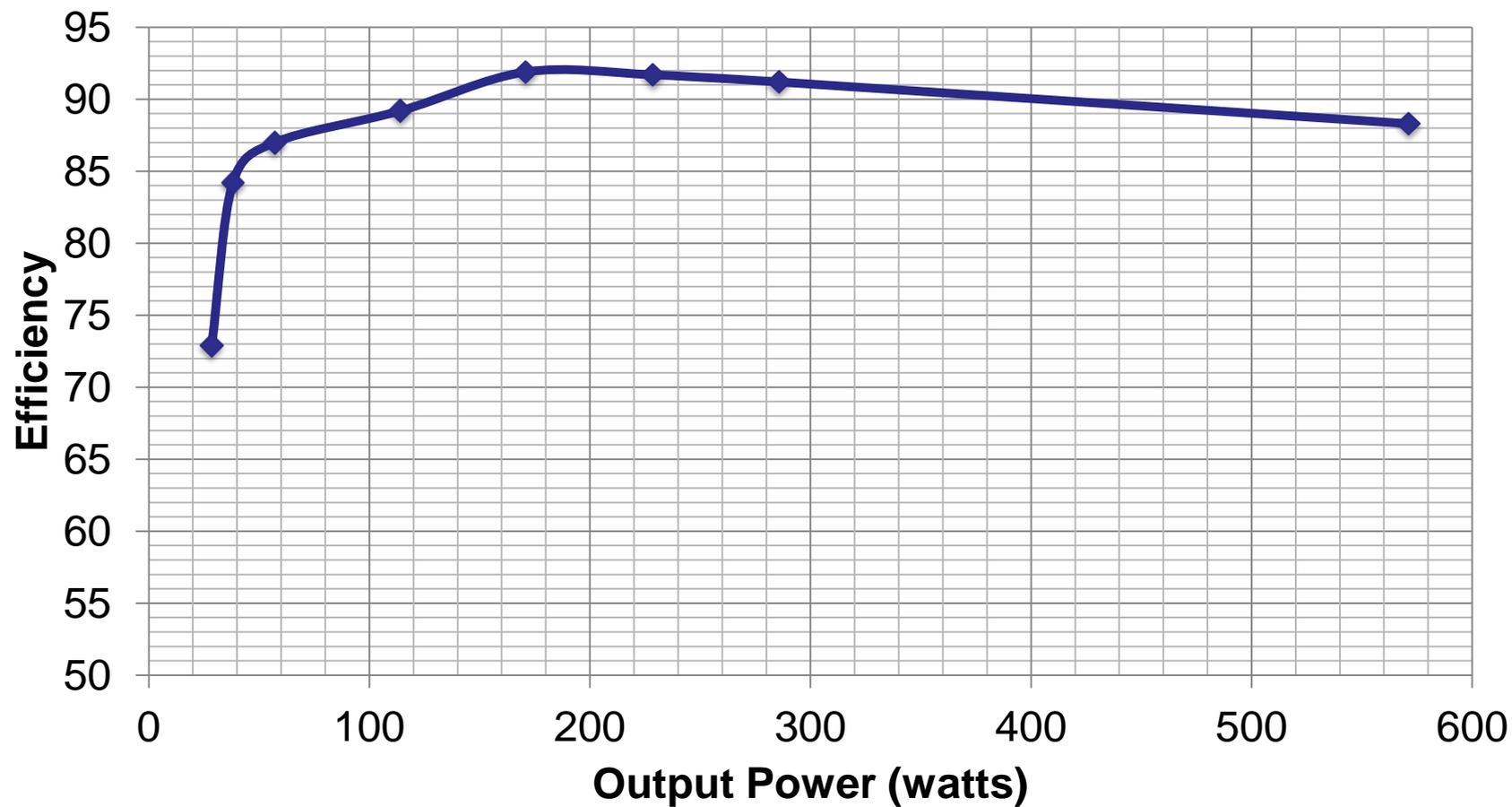

MOSFET Bridge Efficiency

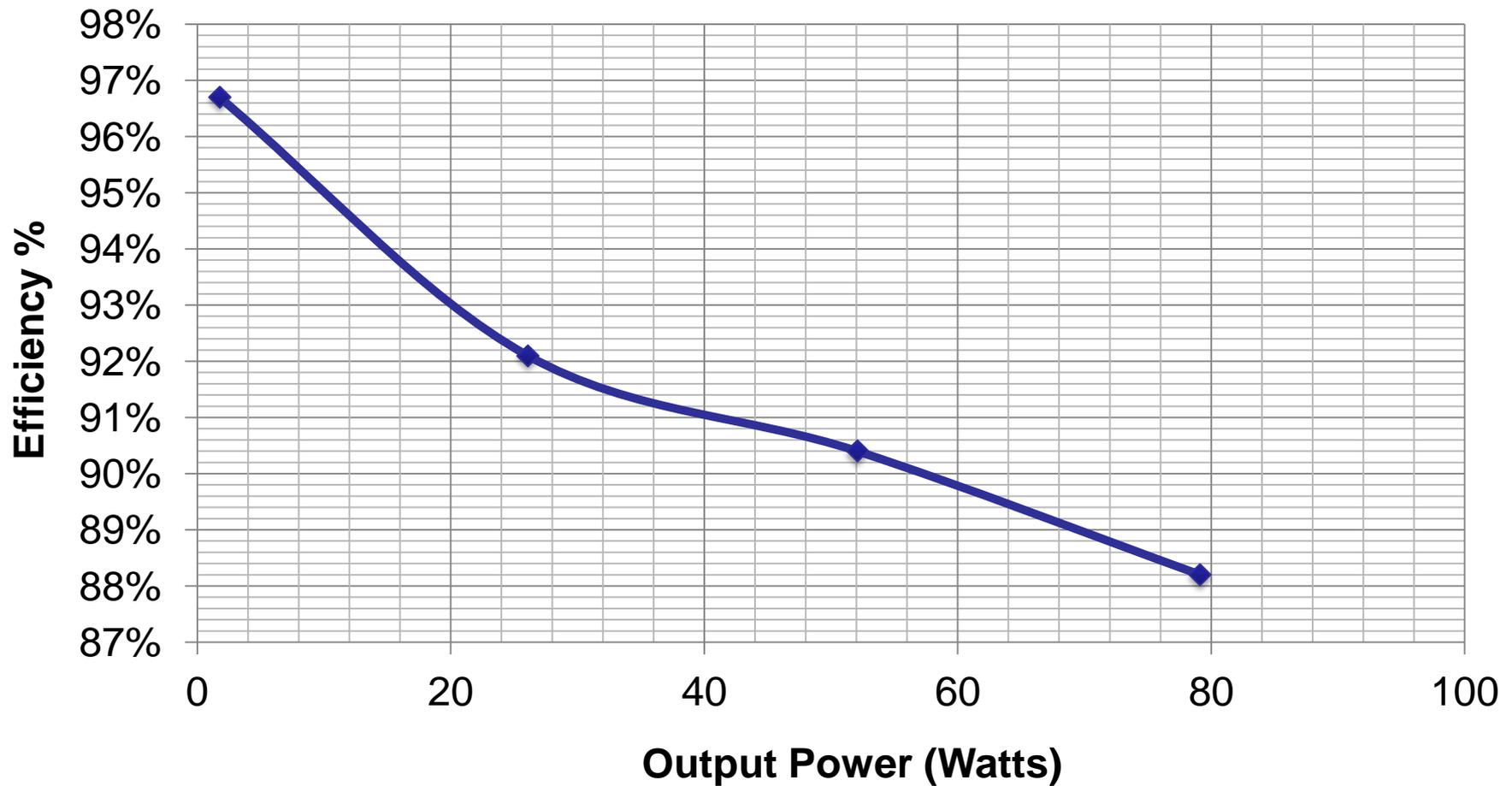

Overall Efficiency


- Initial targeted efficiency = 80% (Proposal)
- Targeted efficiency after simulations = 70% (Design Review)
- Rectifier efficiency = 72.9%-91.9%
- H-bridge efficiency = 88.2%-96.7%
- Overall efficiency = 64.3%-88.9%

DC/AC Circuit: General Topology




- DC input voltage is fed into 1st stage of DC-DC boost converter and is stepped up to 4x
- DC signal is then channeled through 2nd stage DC-DC boost converter and is stepped up to the appropriate amount (115V or 230V)
- The signal is then switched at the appropriate frequency (60Hz or 50Hz) using the same MOSFET bridge as the AC/AC circuit
- A square wave is received at the output


DC/AC Converter: Initial Design

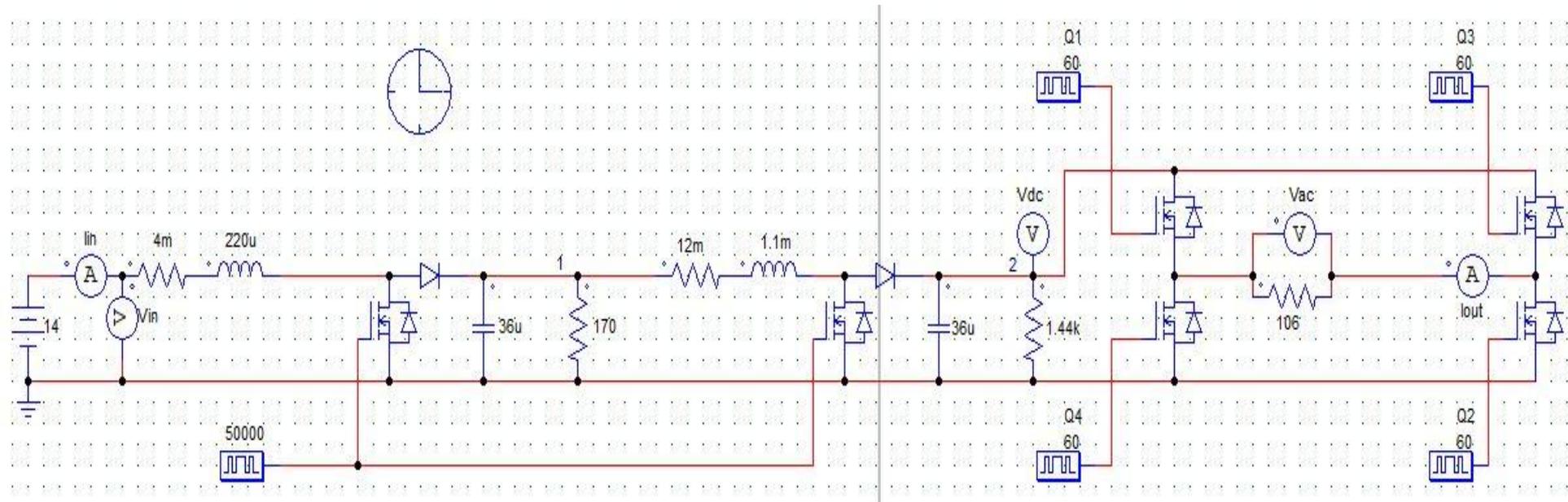

DC/AC Converter: Actual Implementation

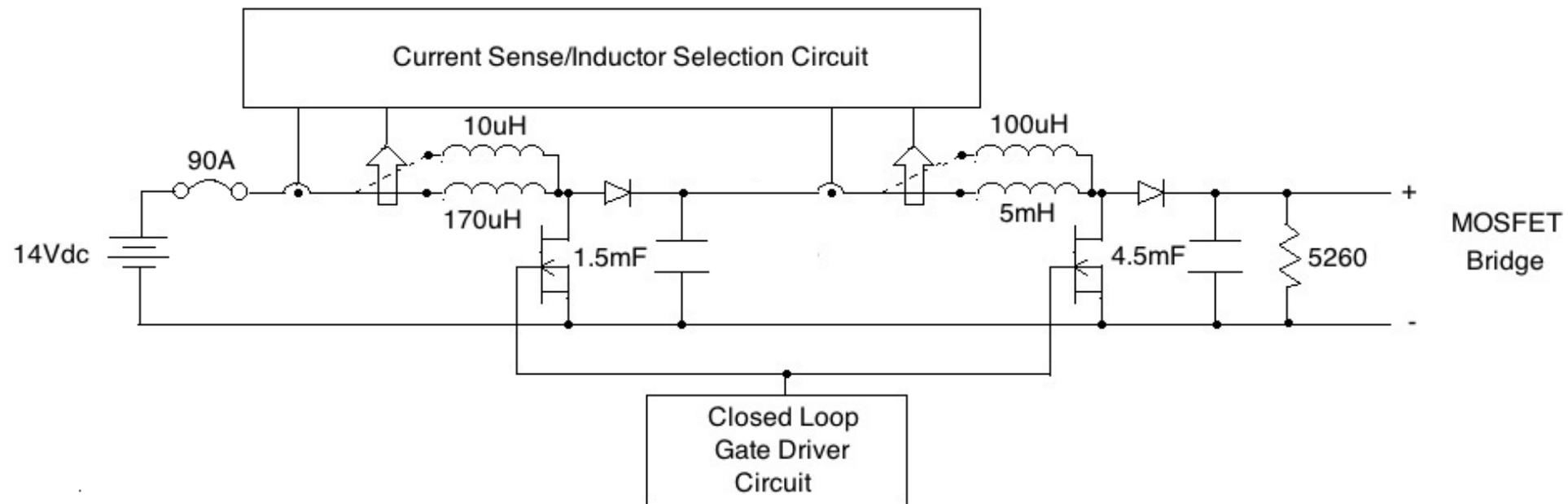


Current Sensing Circuit

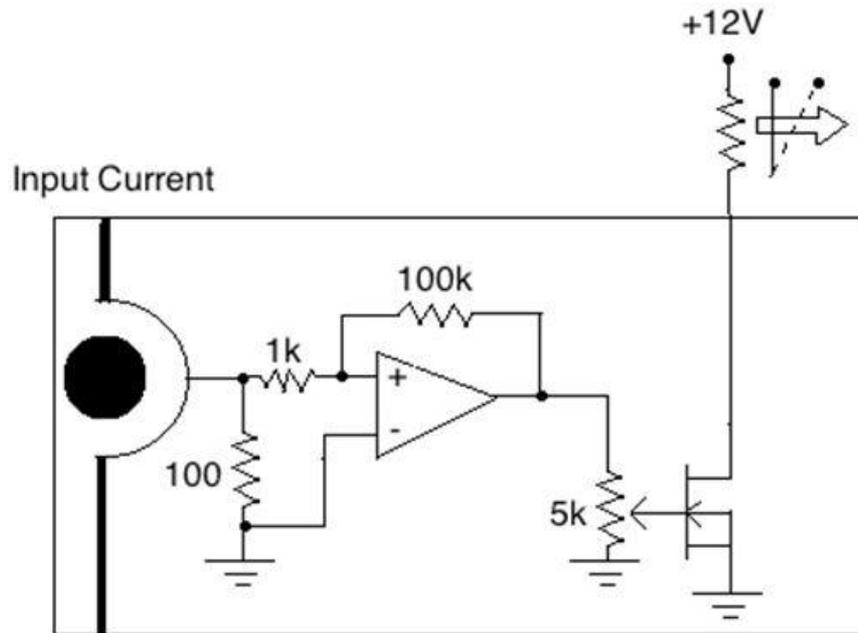



- Hall effect sensor creates an output voltage based on input current
- Non-inverting amplifier increases sensitivity
- Output voltage of amplifier controls gate voltage of N-channel MOSFET
- SPDT relay switches when sensed current is high enough


Snubber Circuit

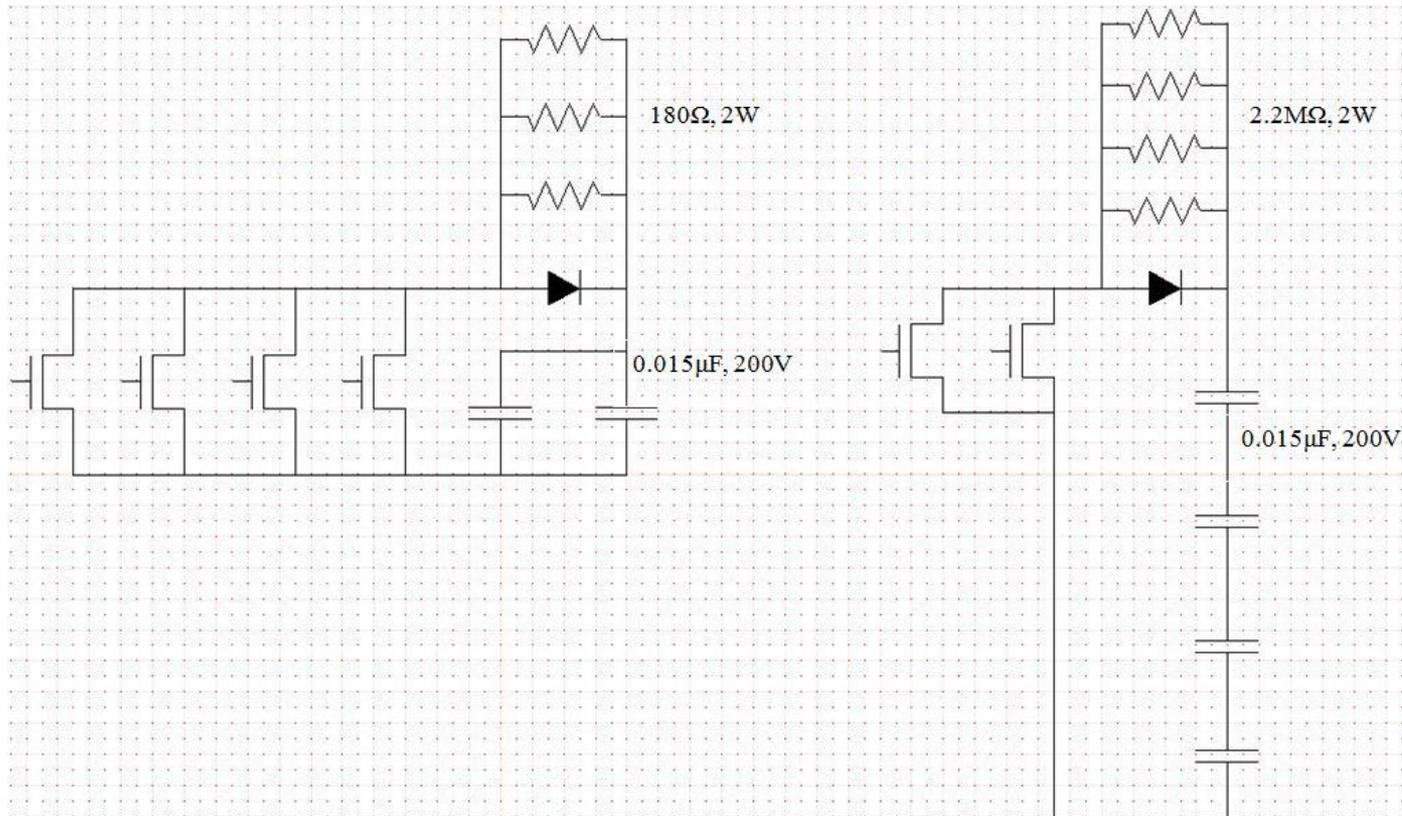

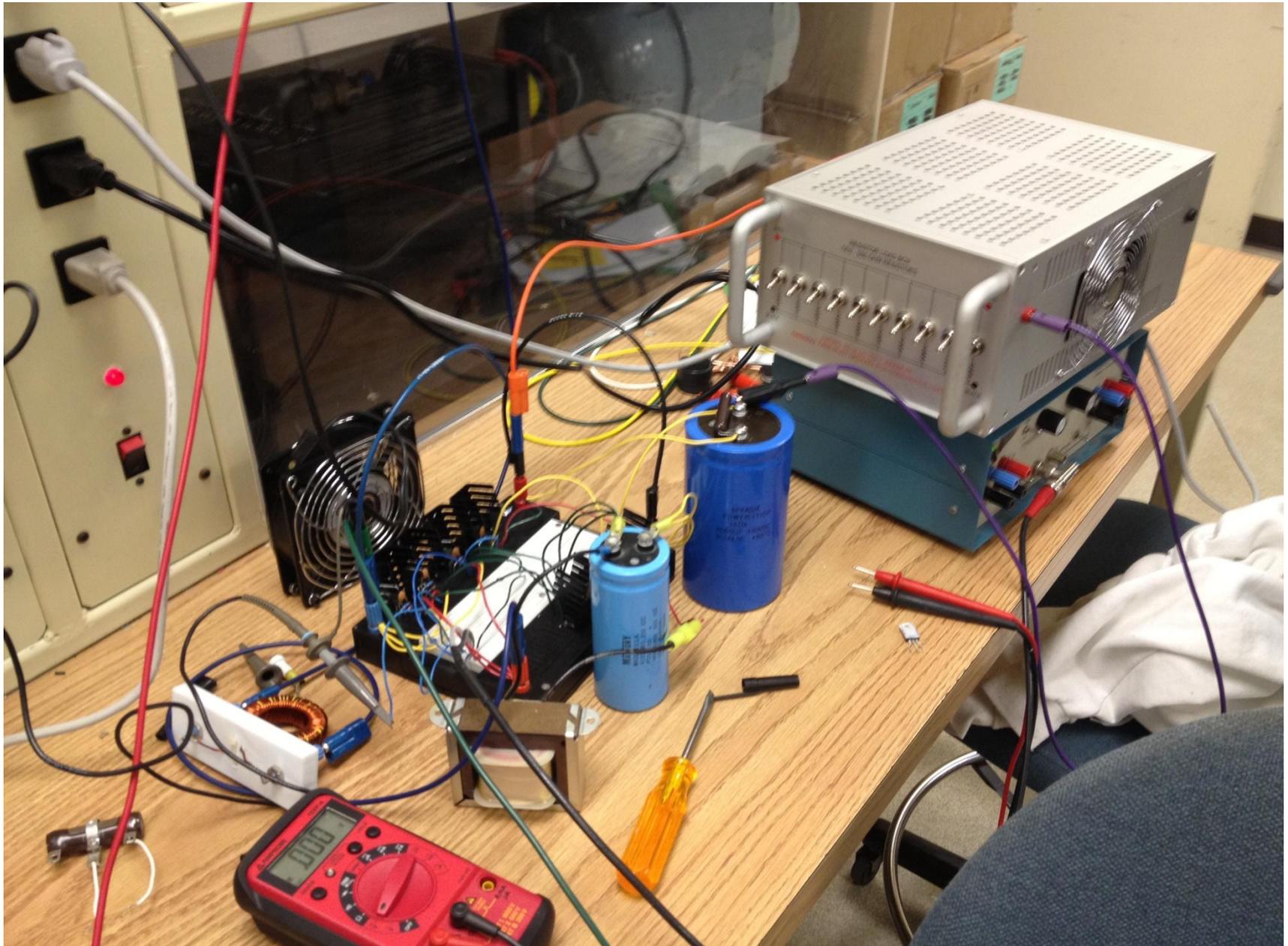
- To dissipate power when switches are off
- To reduce switching losses at high frequencies (50kHz)




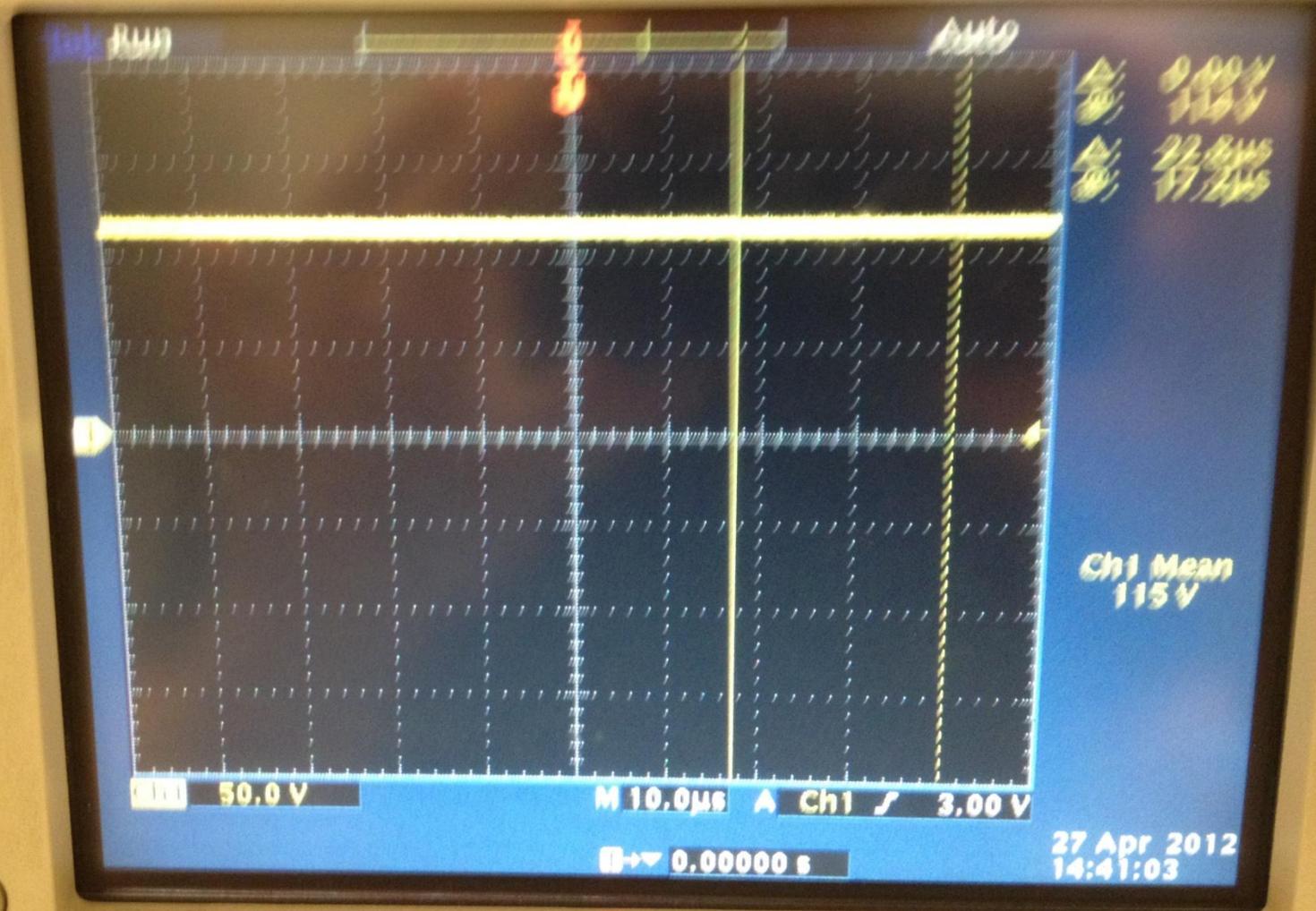

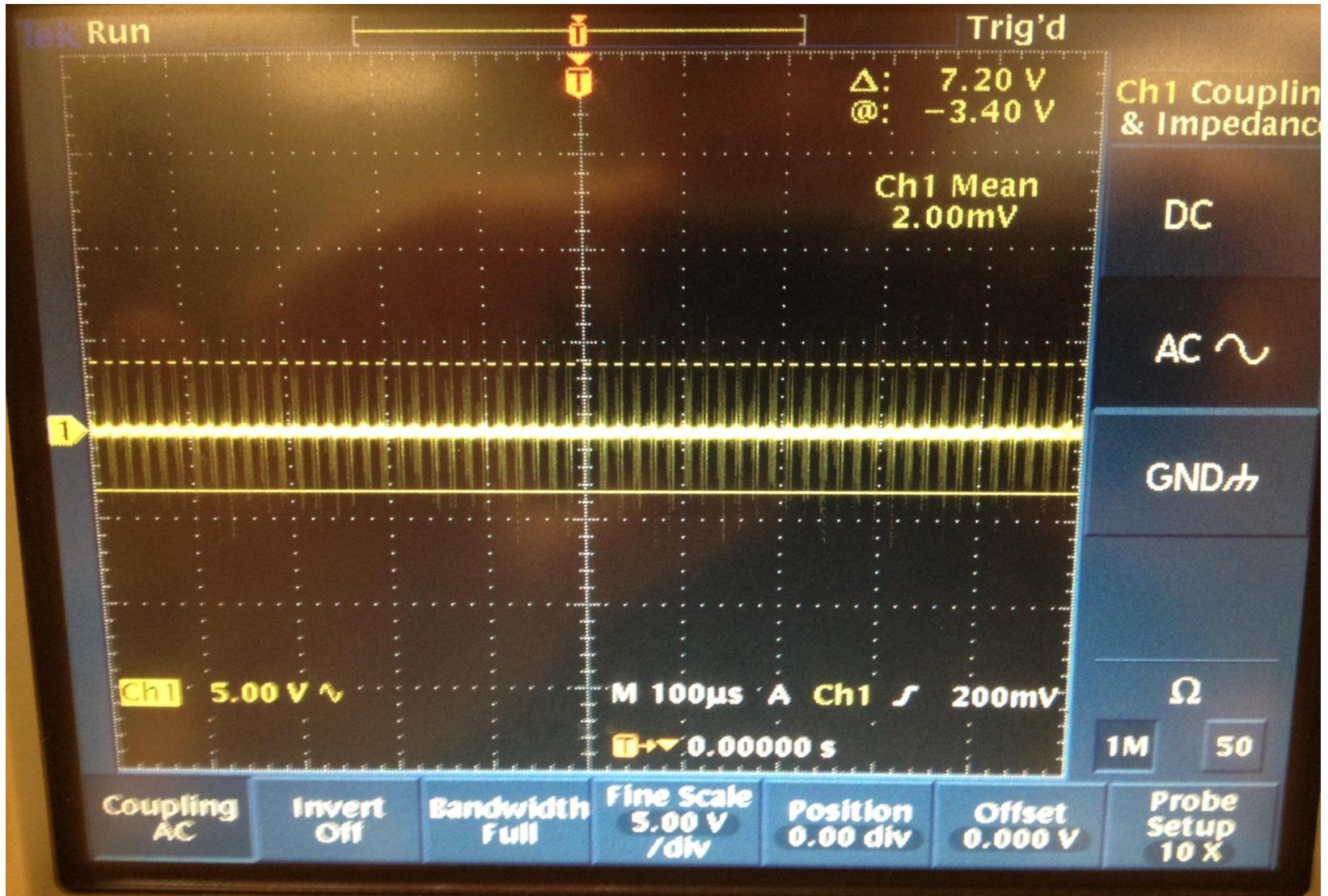

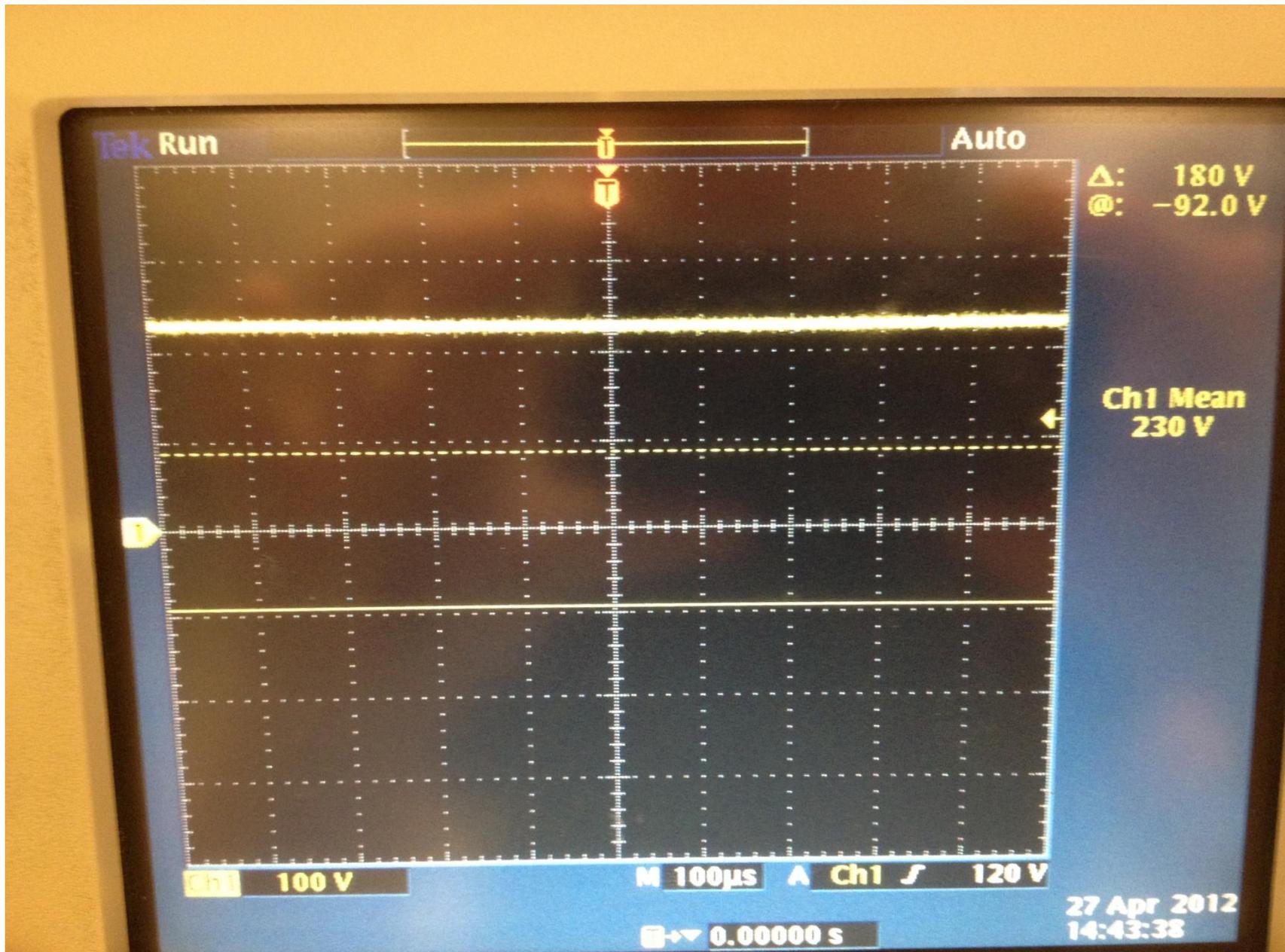115V ripple measurement = 7.2Vpp = ± 3.1%



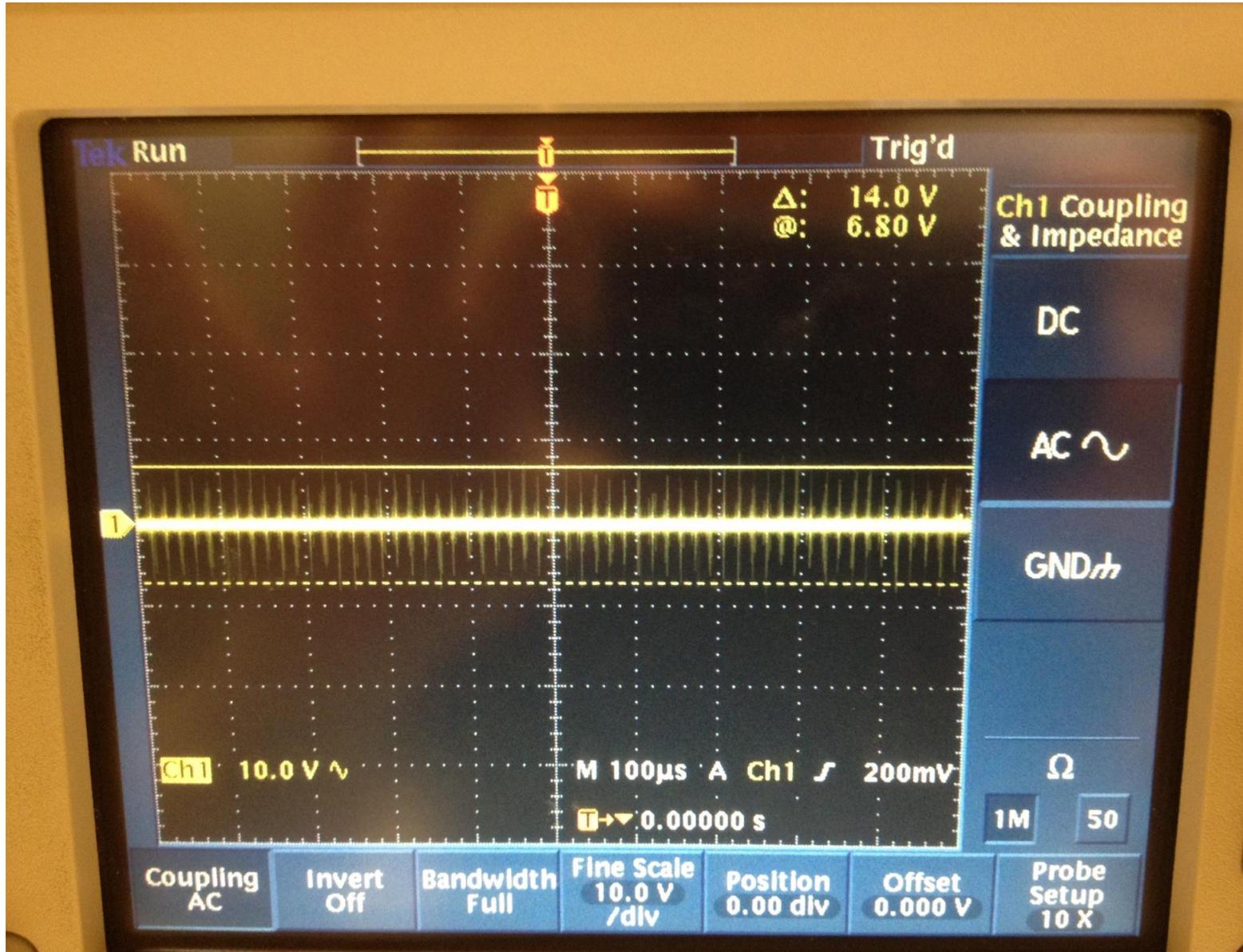


230V ripple measurement = 14Vpp = $\pm 3.0\%$

DC/AC Converter Efficiency



Overall Physical Circuit Layout

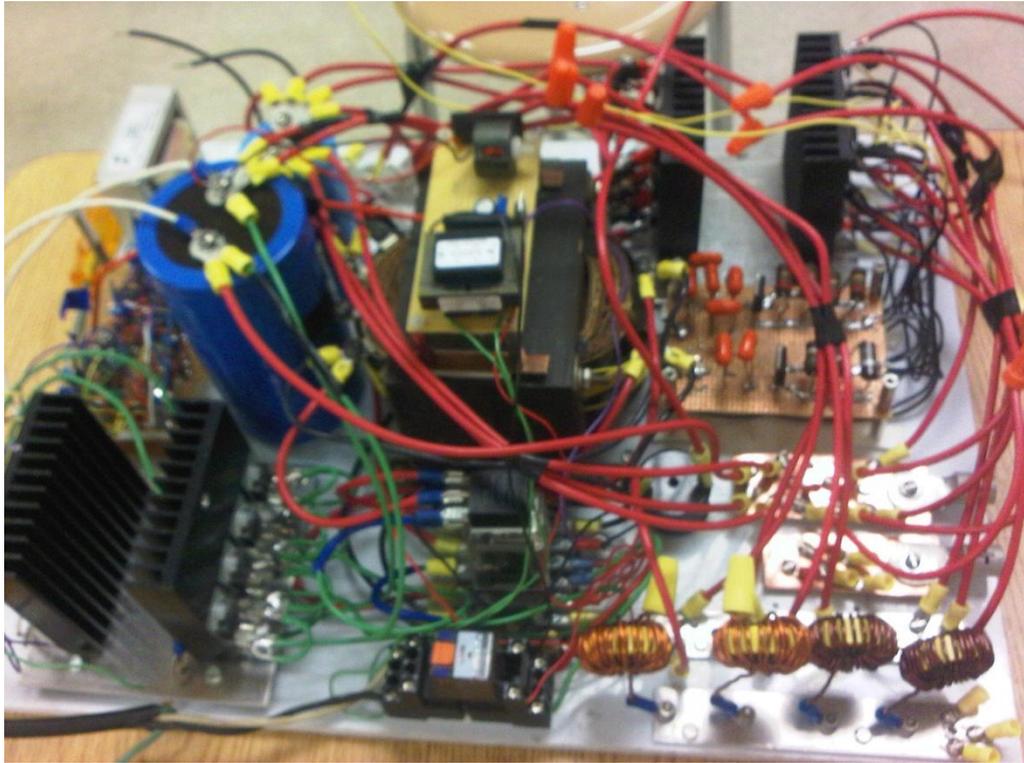

Challenges

AC/AC Design

- Needed to build a VSI waveform circuit (instead of original 50% DR)
- Power supply of 12Vdc for digital components
- High-side and low-side gate drivers
- No mains ground (isolated)

DC/AC Design

- Boost converter voltage regulation
- In depth magnetics design
- PWM reliability
- High input current ($\sim 90\text{A}$)


Reasons For Failure

- Hard Start – voltage and current immediately seen by MOSFETs
- Power Resistors – Wire wound and can act like inductor causing initial current spike
- PWM signal oscillation – Witnessed in video, dangerous to MOSFETs, causes quick changes in inductor current
- Rapid inductor current variation causes voltage spikes
- Analog circuits cause cascading problems

Recommendations

- Use a 3-stage boost converter instead of a 2-stage
- Implement slow start circuits
- Micro controller for PWM signal and closed loop control
- Use a center tap transformer circuit (shown on next slide) instead of a boost converter
- Use high power MOSFETs instead of parallel combination
- Micro controller for VSI waveform
- Opto-coupler to isolate digital components from power components
- Create a pure sine wave output

Inverter Design II

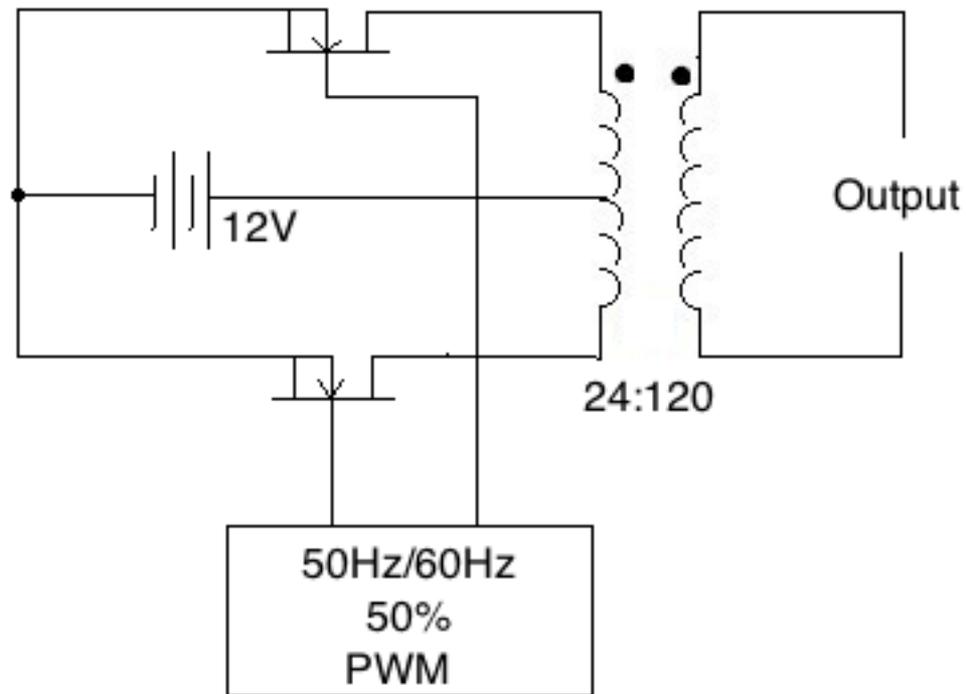

Special Thanks To

Kevin Colravy

Prof. Krein

Prof. Carney

Ryan May

ECE Machine Shop

ECE Parts Shop



Thank You

Questions?