

# LOST

## Lost Object Search Technology

...

By Brittany Joy, Cecil Macgregor, and Adithya Sairam  
Group #22

# Introduction



- LOST can be used by everyone to find their objects
  - Target market
- Tile's Phone app does not work for blind people
- Deaf people are unable to hear Tile's ringing
- >3.4 million (3%) of Americans ages 40 years and older are either visually or audibly impaired

# Objective


- Users can easily track down lost objects
- Handheld receiver that connects to one of three transmitters
- Selected transmitter broadcasts to the receiver in the 915 MHz industrial, scientific, and medical (ISM) radio band
- Receiver evaluates signal strength
  - Gives tactile, audio, and visual feedback guide user to transmitter

# Block Diagram


## Transmitter (one of three)

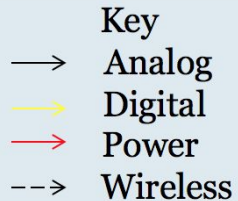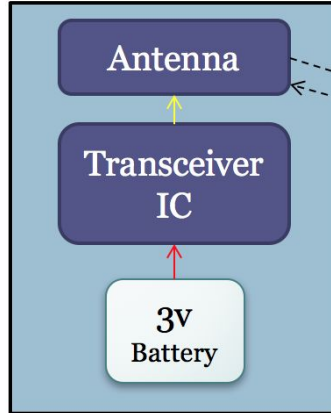

## Receiver Unit

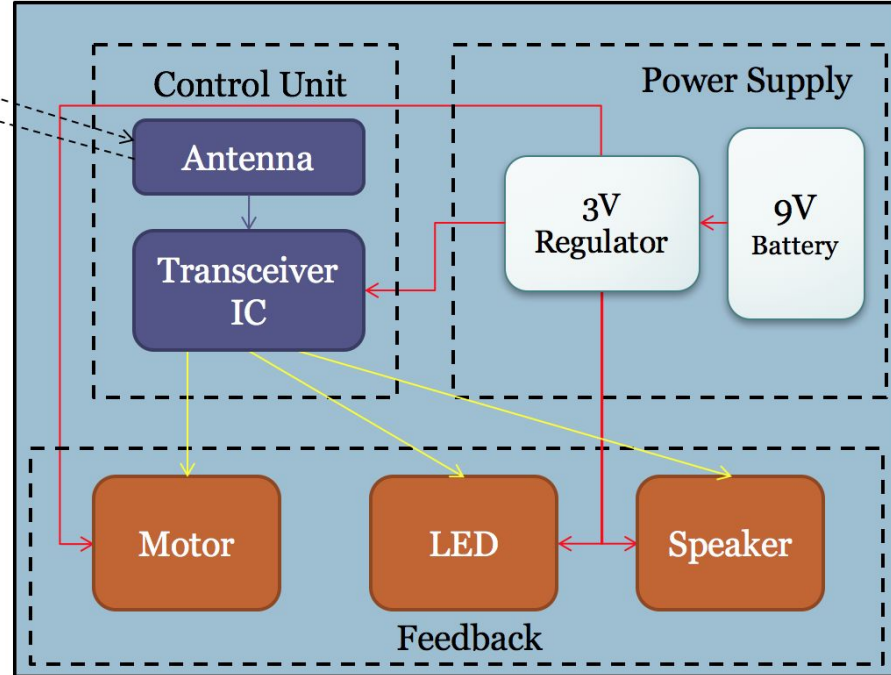


# Final System

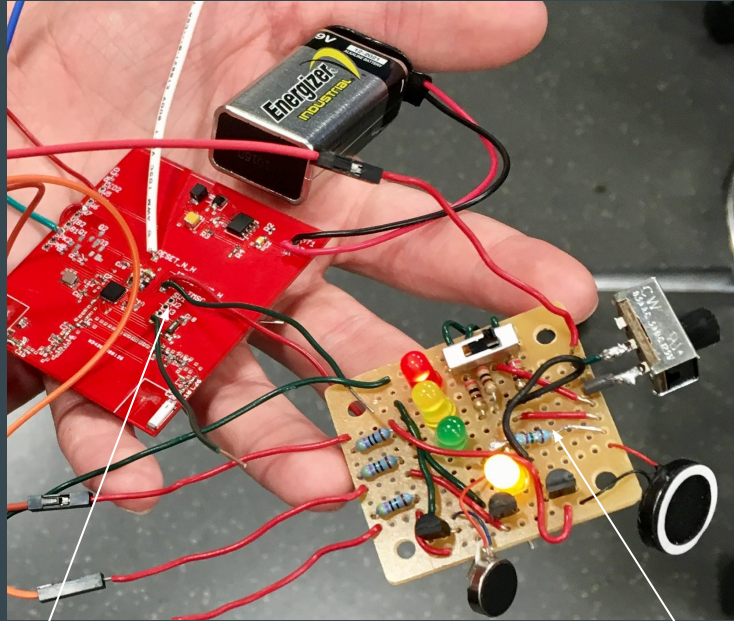Receiver  
PCB

## Receiver Unit

## Feedback Module

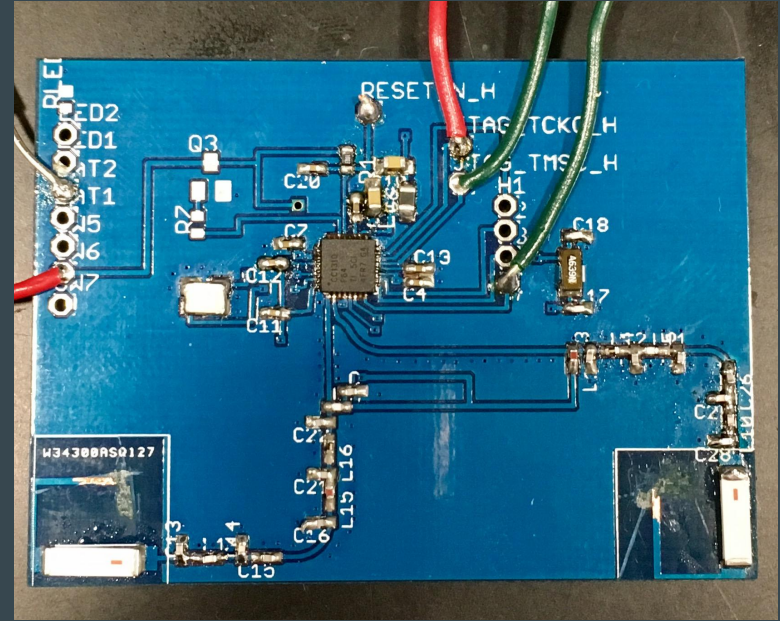

# Transmitter

# Hardware

...


# Antenna (Transmitters and Receiver)

## Requirements:

- Antenna must be able to receive and transmit at 902, 915, 927 MHz
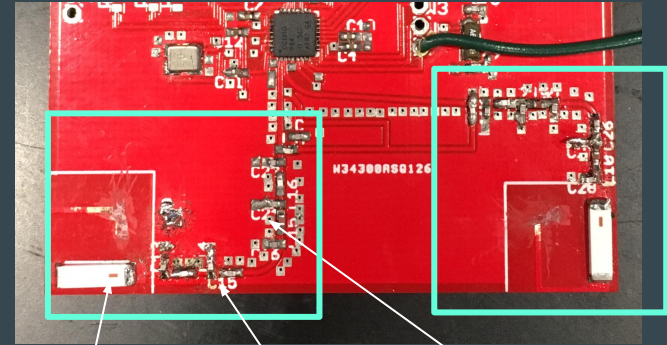
## Design:



- Selected chip antenna (size)
- Antenna diversity - two antennas
- Tune resonance of antenna
- Impedance match antenna - two networks




Antenna      Matching network 1      Matching network 2



# Antenna Tuning - Resonance (Setup)

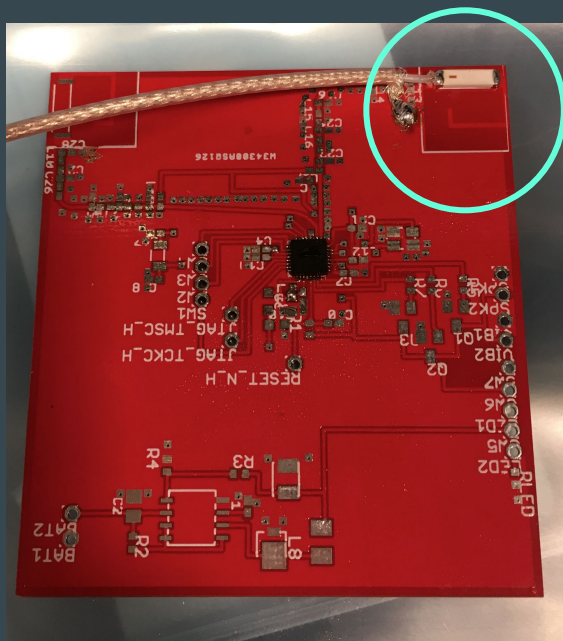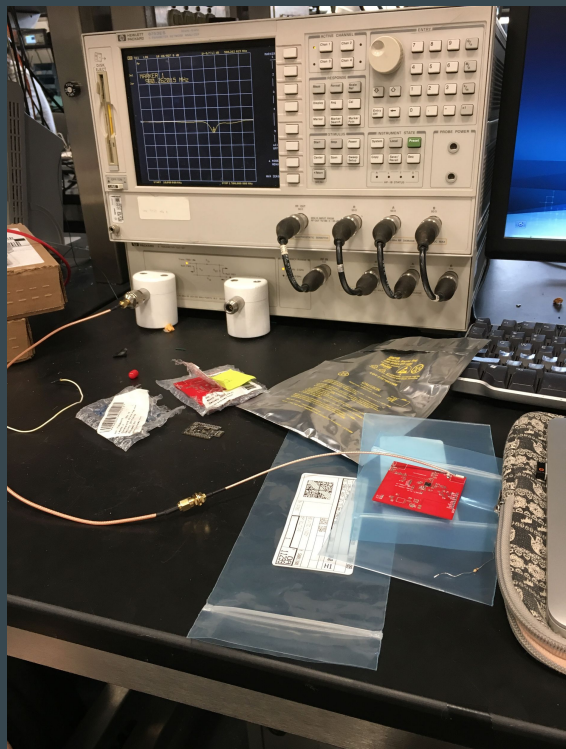


Before

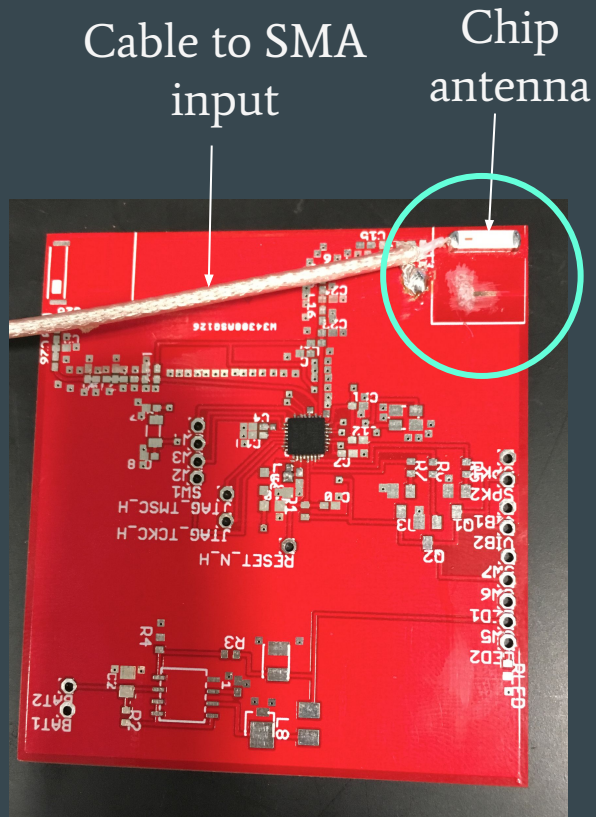


After



# Antenna Tuning - Resonance (Data)

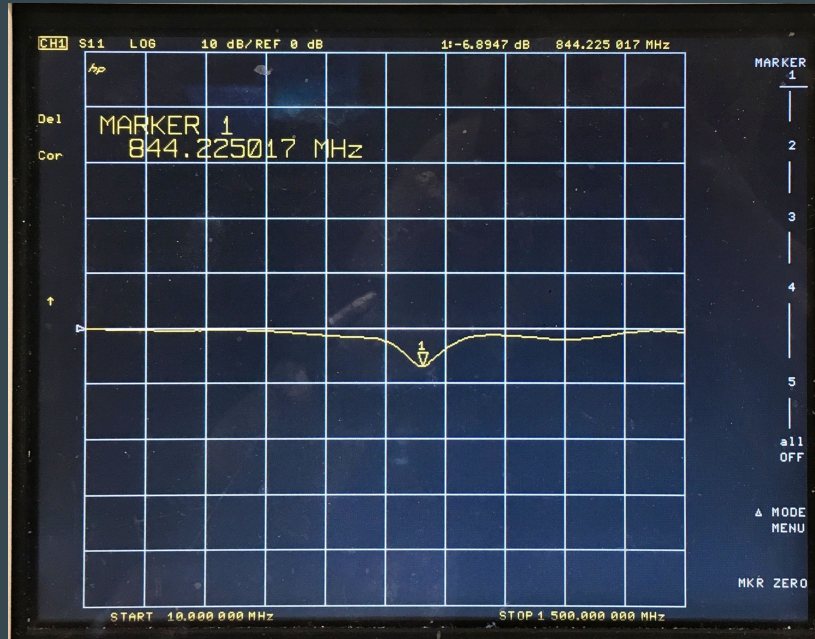

Before (844 MHz) (-6.9 dB)

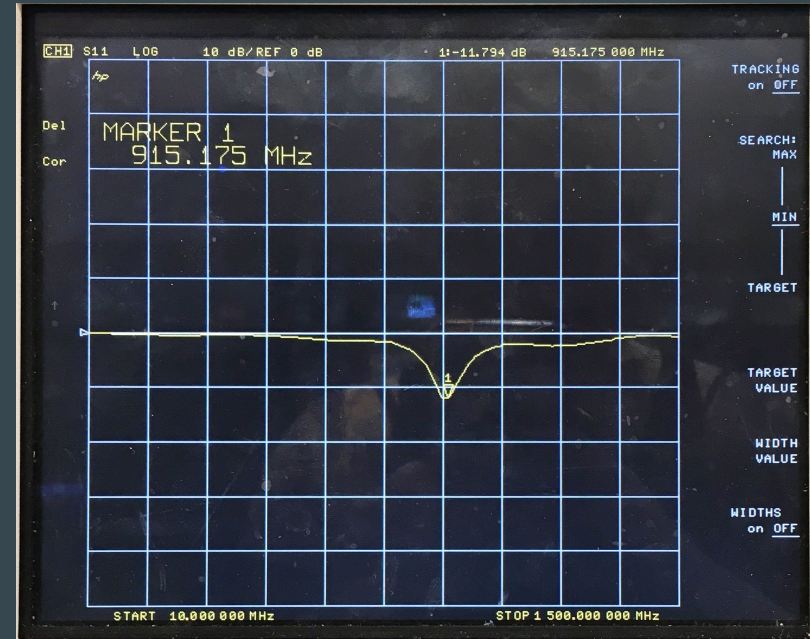

After (915 MHz) (-11.8 dB)

# Antenna Tuning- Impedance Matching




S11 Before

No matching network (1) implemented

$$Z = 28.6 - j17.7 \text{ ohms}$$

Mismatch Factor: .881

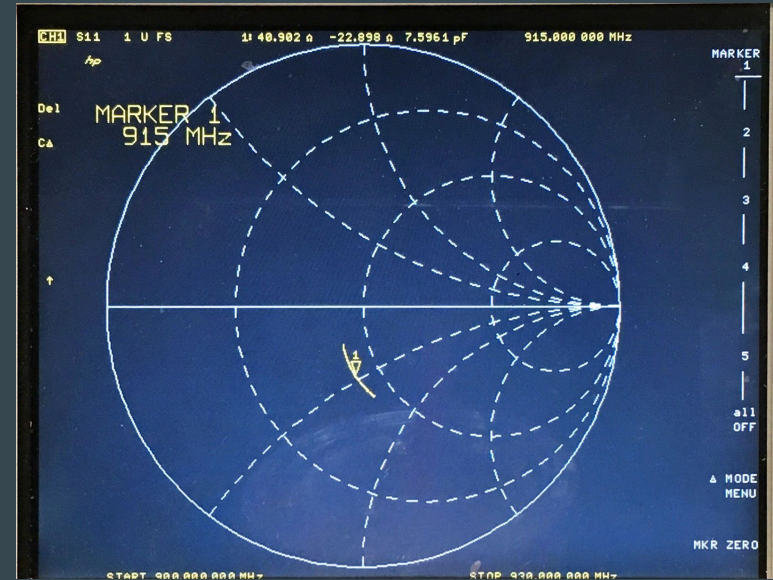

S11 After

Matching network (1) implemented

$$Z = 40.9 - j22.9 \text{ ohms}$$


Mismatch Factor: .930





# Requirements for Transceiver IC

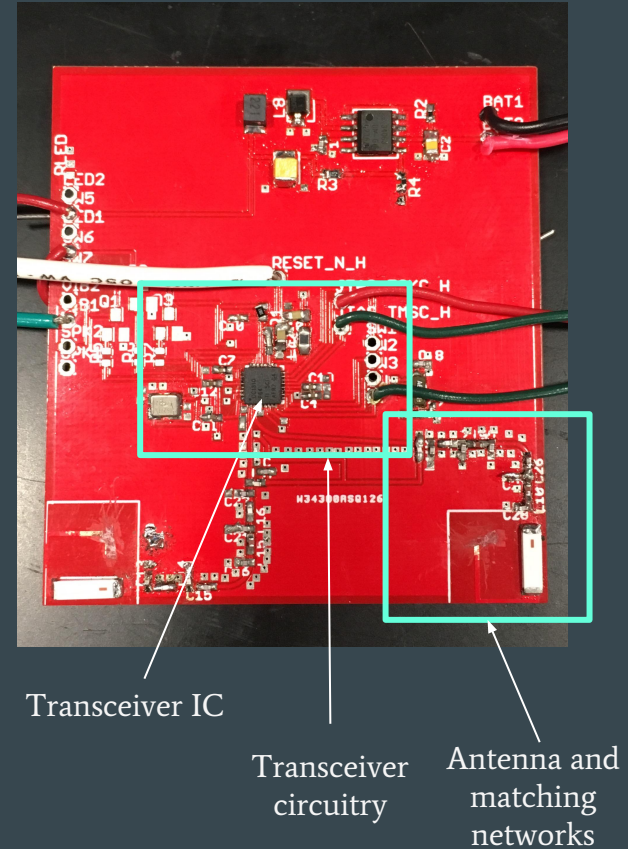1. Receive signals over the 915 MHz ISM band.
2. Transmit signals over the 915 MHz ISM band at selected frequencies (below) within the band (max bandwidth 2 MHz).
  - a. 903 MHz
  - b. 915 MHz
  - c. 927 MHz
3. In listen mode, the transceiver module consumes  $\leq 0.5\text{mA}$  on average
4. During transmission, it will consume  $< 15\text{ mA}$ .



# Transceiver IC (Transmitters and Receiver)

- TI CC1310 SimpleLINK Ultra-Low-Power Sub-1 GHz Wireless MCU
- Low-power RF Transceiver and ARM Cortex-M3 processor with 16kB of RAM
- 10 GPIO (General Purpose Input/Output) pins
  - Both digital and analog inputs available
  - Necessary to work with RSSI Signal and Feedback module


# Power Supply - Buck Converter

## Requirements:

- Step down 9V to ~3V
  - Provide enough power to turn on receiver (dev board)
  - Power the feedback module

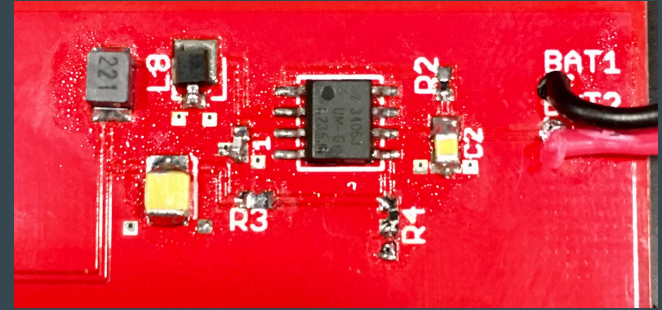
## Design:

- Buck converter vs linear regulator - efficiency
- Output voltage - two resistors



Buck Converter circuit  
mounted on Receiver PCB

# Buck Converter Schematic

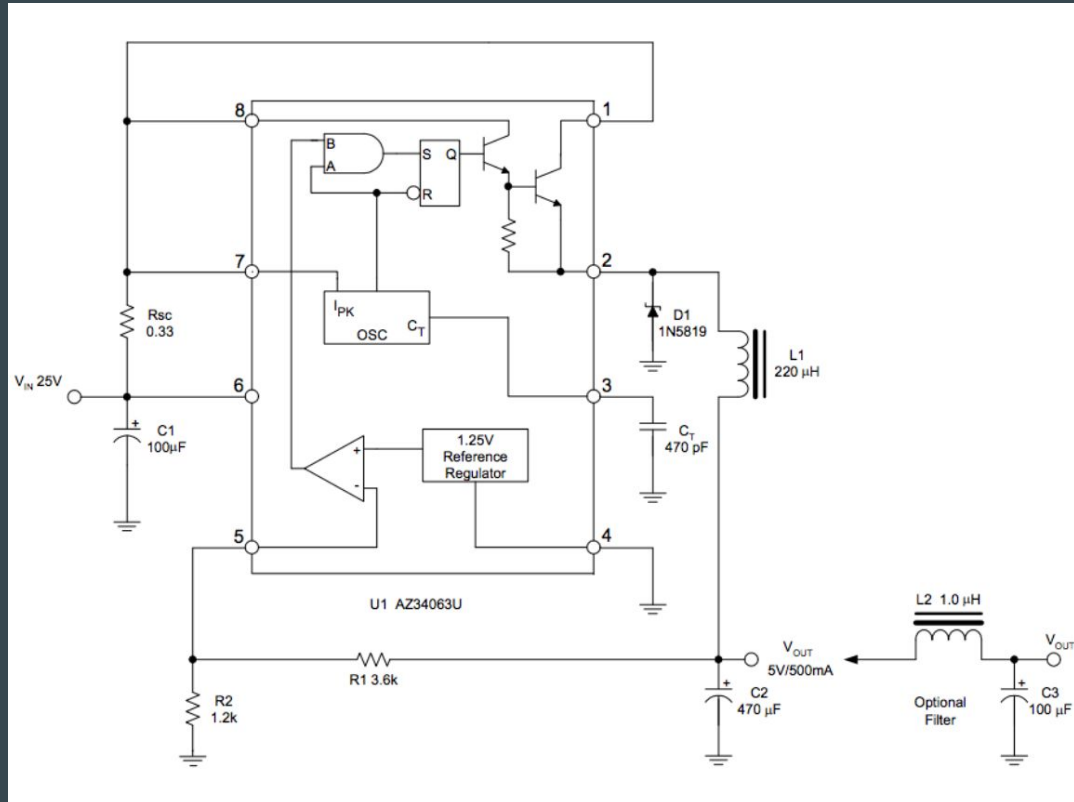

Design Equations:

$$V_{PIN5} = V_{OUT} \left( \frac{R2}{R1 + R2} \right) = 1.25 (V)$$

$$V_{OUT} = 1.25 \left( \frac{R1 + R2}{R2} \right) (V)$$

Values Chosen:

$$R1 = 2.32k$$

$$R2 = 1.2k$$

$$V_{out} (calc) = 3.7 V$$

$$V_{out} (meas) = 3.5 V$$




# Feedback Module

## Requirements:


- Motor, LED, speaker controlled by GPIO pins and driver circuit with 3.5V supply (output from buck converter)
- Components should draw less than 22 mA
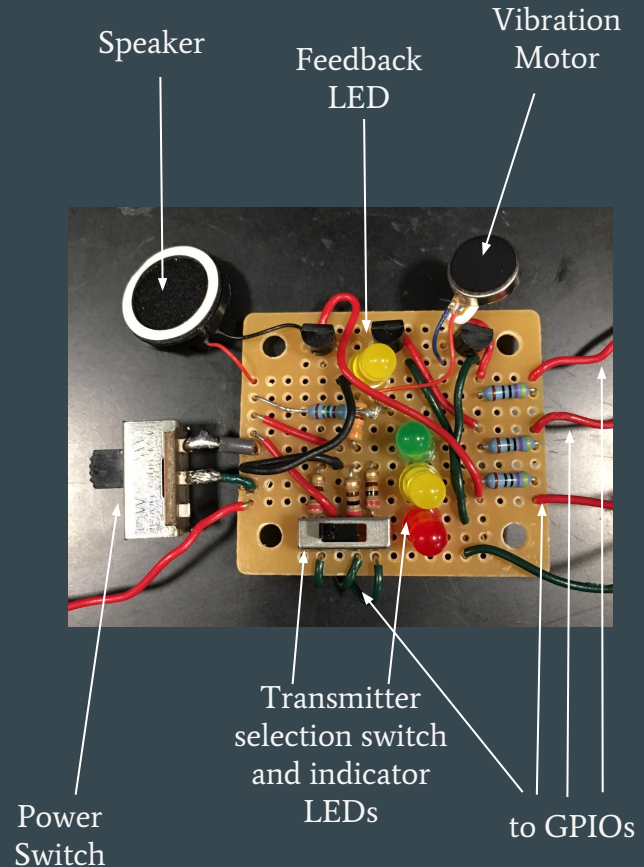
## Design:

- Open-collector configuration - driver
- Circuit incorrect on PCB
  - Final module on perf board
- Components - cost, size, power consumption



# Feedback Module Schematic

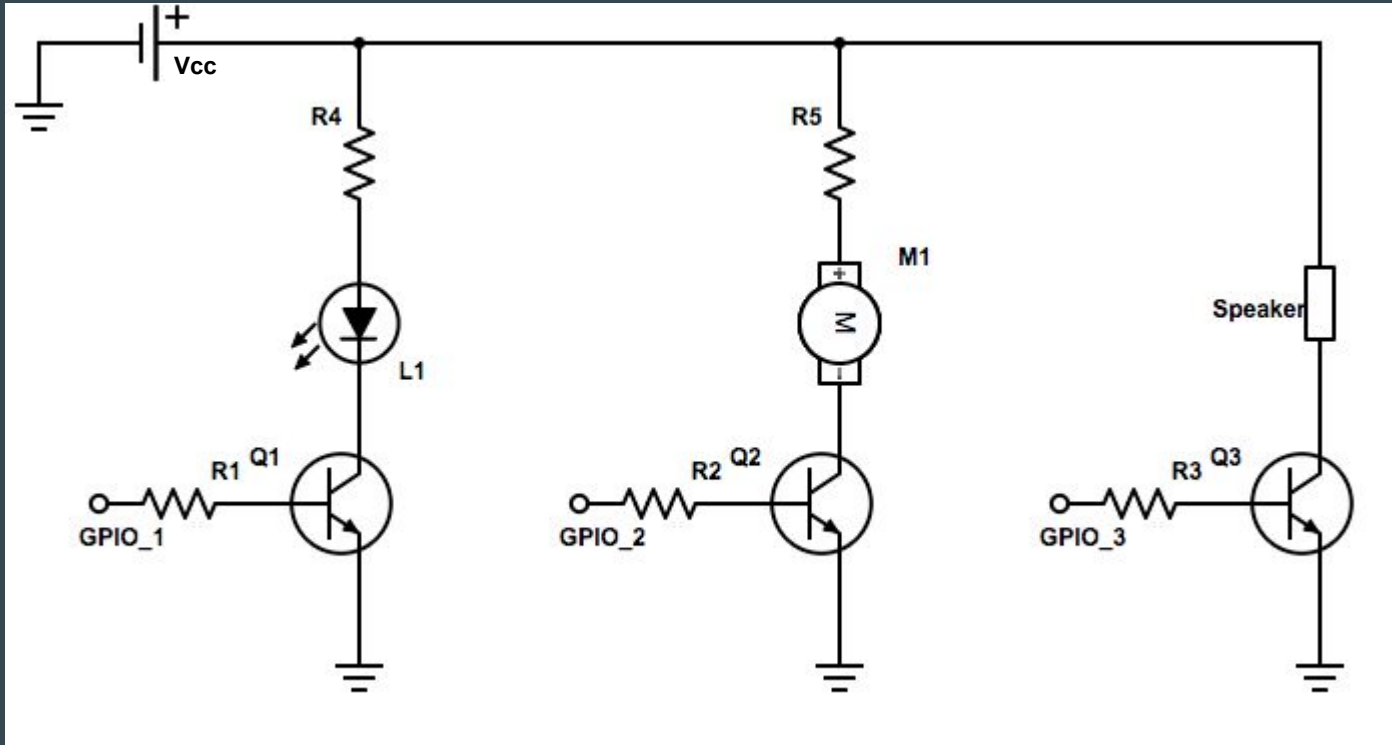

$V_{cc} = 3.5V$   
 $R1 = 470 \text{ ohms}$   
 $R2 = 470 \text{ ohms}$   
 $R3 = 470 \text{ ohms}$   
 $R4 = 47 \text{ ohms}$   
 $R5 = 47 \text{ ohms}$


# Software

...

# RSSI

- Foundation of signal strength calculations that goes into feedback module
- Transmit and receive RF signal between two transceivers and access RSSI in dBm
  - Translate RSSI value into a frequency that varies proportionally with distance

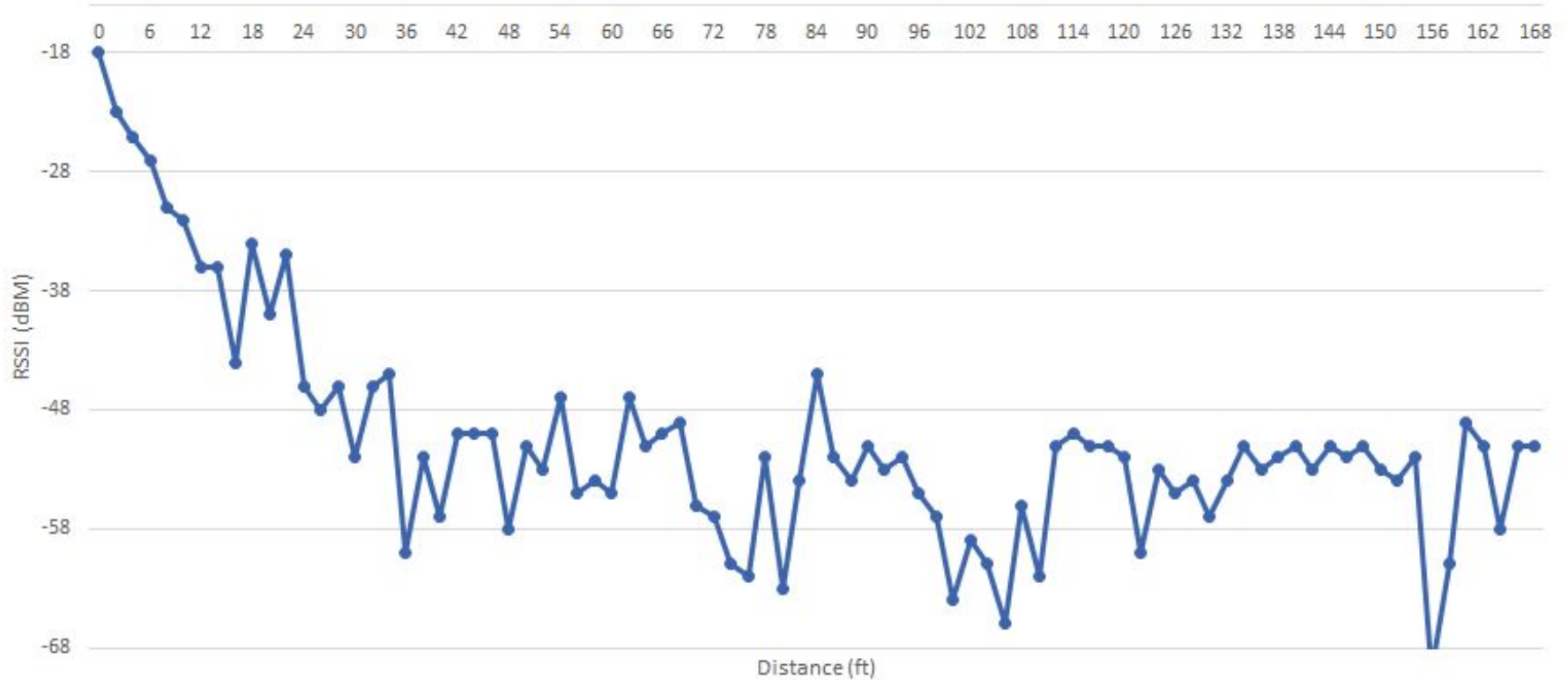
# Distance vs Received Signal Strength Indicator (RSSI)



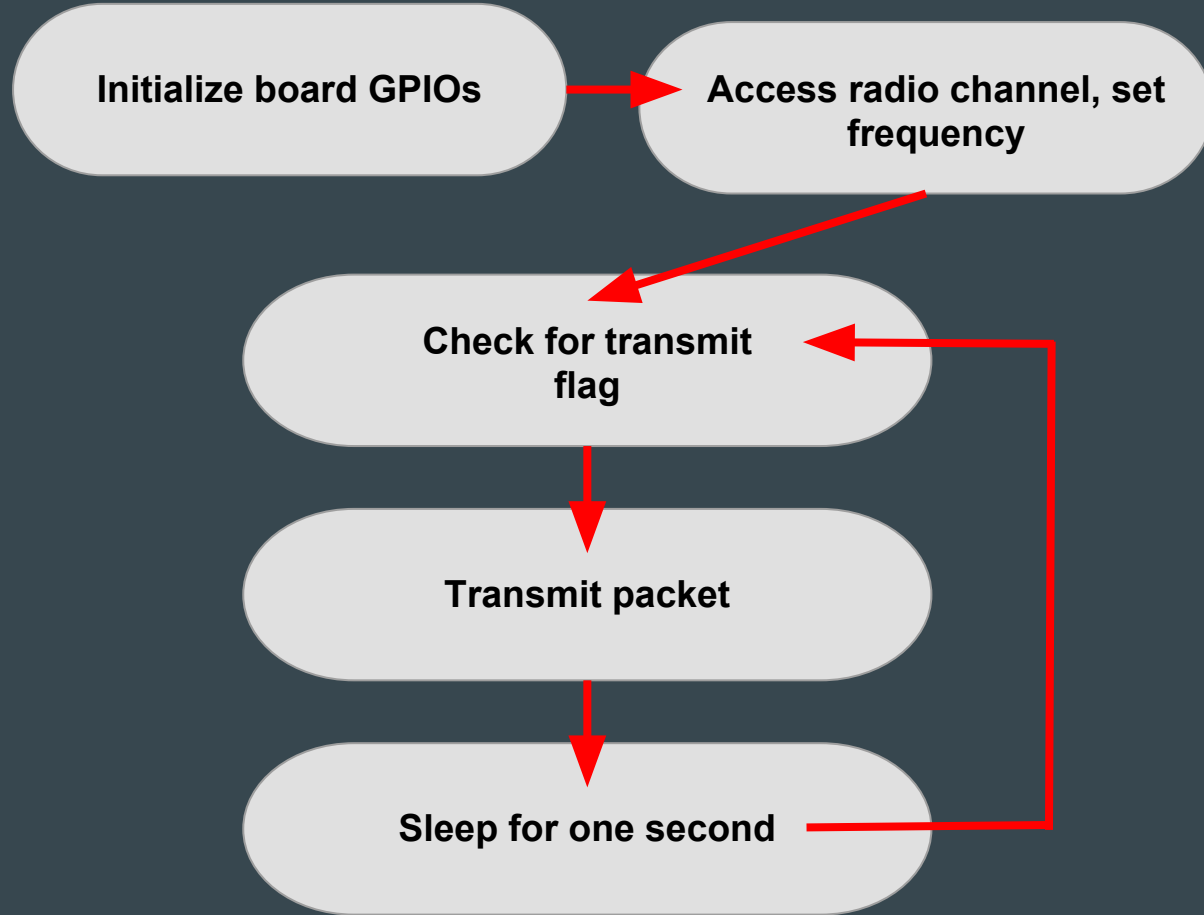
# Transmitter Code Flow

**Button One:  
Set transmit flag**

**Button Two:  
Deactivate transmit  
flag**



# Receiver Code Flow

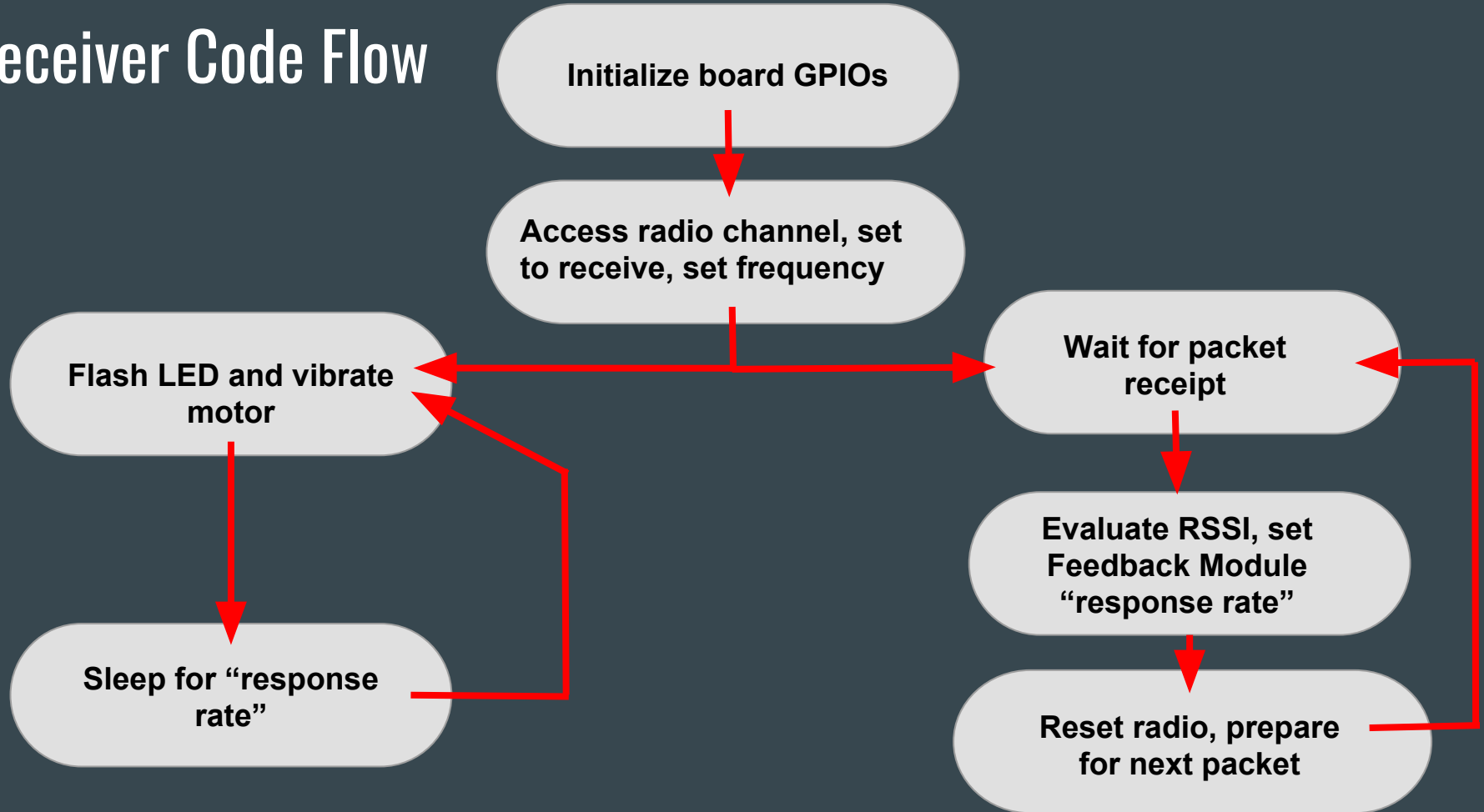



# CC1310 Troubleshooting

- Configuration files
  - Pin mapping
- JTAG connections
  - Visible communication
- Memory map
- CC1310 clock frequency

# Future Development and Conclusion


- Successfully implemented all modules required using dev board
  - Microcontroller on PCB failed
- Microcontroller with better documentation
  - Arduino Micro
- Move feedback module onto PCB
- House entire project in small, portable case

# Credits

- Michael Goldstein
- Professor Michael Oelze
- Daniel Gardner

**Thank You**
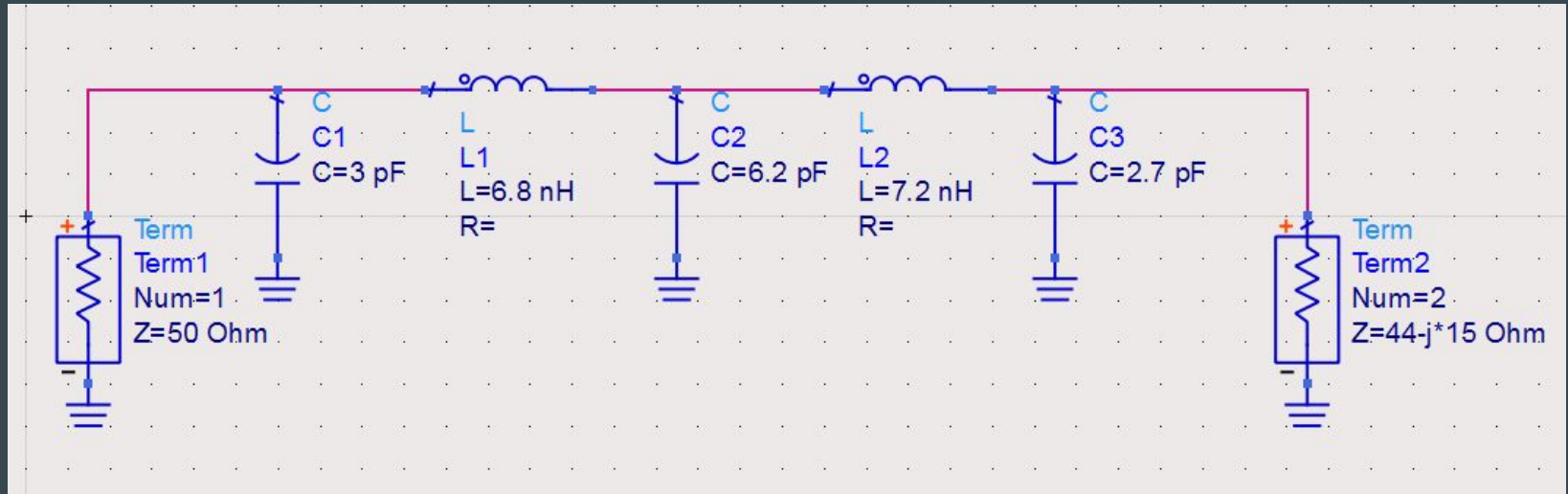
# Appendix - Matching Network 2 Schematic



Optimal impedance seen from the RF pins into the balun and filter and antenna is  $44 + j15\text{ ohms}$  - conjugate match