



Power Electronics

Day 5 – Dc-dc Converters; Classical Rectifiers


P. T. Krein

Department of Electrical and Computer Engineering
University of Illinois at Urbana-Champaign



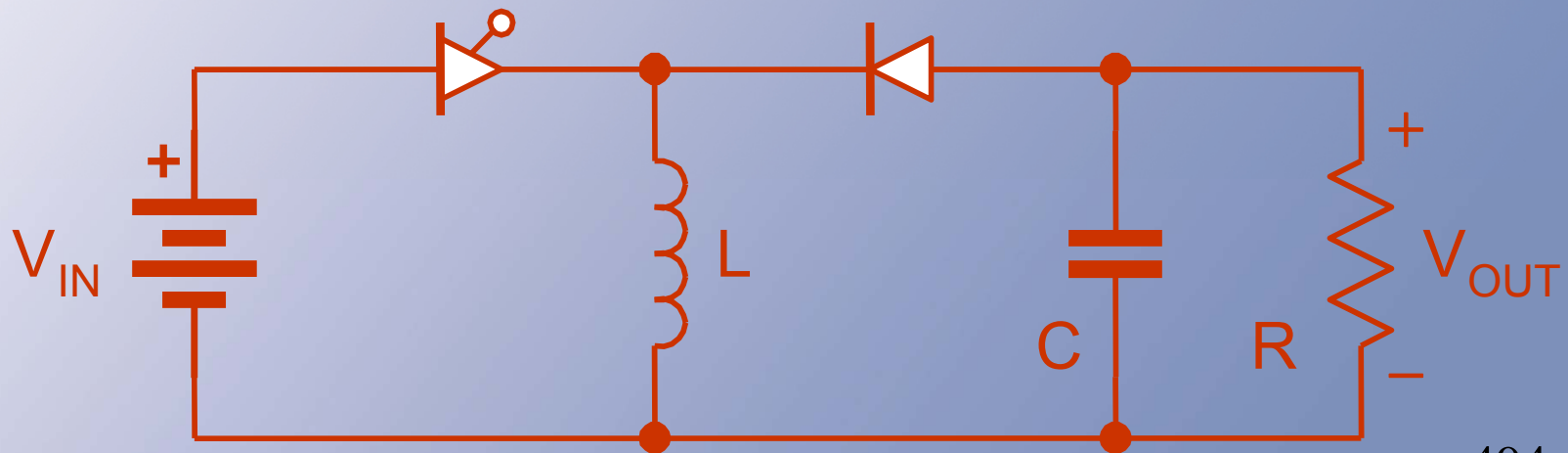Example

- Input: +5 V to +15 V
- Output: -12 V \pm 0.5%
- Power: 10 W to 20 W
- Switching: 100 kHz
- Find a circuit, and then L, C, and duty ratios to meet these needs.





Duty Ratios

- The converter gives $V_{\text{out}} = -D_1 V_{\text{in}} / (1 - D_1)$, when V_{out} is defined as on this drawing.
- With +5 V in and -12 V out,
 $12 \text{ V} = D_1 (5 \text{ V}) / (1 - D_1)$.
- The solutions: $D_1 = 12/17$, $D_2 = 5/17$.
- With +15 V in and -12 V out,
 $(12 \text{ V}) = D_1 (15 \text{ V}) / (1 - D_1)$.
- The solutions: $D_1 = 12/27 = 4/9$,
 $D_2 = 15/27 = 5/9$. They add to 1.





Currents

- To meet the need, D_1 must be adjustable from $4/9$ to $12/17$, or 0.444 to 0.706 .
- At 10 W , the average output current is $(10\text{ W})/(12\text{ V})= 0.833\text{ A}$.
- The input current depends on duty.
- Let us allow $\pm 5\%$ inductor current ripple (somewhat arbitrary).



Inductor Current

- Since $I_{\text{out}} = D_2 I_L$, the inductor current is I_{out}/D_2 . For 10 W to 20 W, the output is 0.833 A to 1.67 A
- D_2 ranges from 5/17 to 5/9, so I_s could be as high as $1.67/(5/17) = 5.67$ A. It could be as low as $0.833/(5/9) = 1.5$ A.



Inductor Value

- The $\pm 5\%$ current variation limit is most restrictive with the lighter load (10 W).
- When switch #2 is on, the inductor sees -12 V, and its current falls.
- $12 \text{ V} = v_L = L \, di/dt = L \, \Delta i/\Delta t$.
The time is $D_2 T$, with $T = 10 \text{ us}$.
- We want $(12 \text{ V})(D_2 T)/L = \Delta i$,
and $\Delta i < (0.1)(0.833)/D_2$.





The Current Change


- This reduces to $L > 144 D_2^2 T$.
- We need it to work for **all allowed duty values**. Highest is 5/9.
- A 0.444 mH inductor should meet the requirements over the entire range.



Capacitor Value

- Output capacitor must carry the load current when switch #2 is off.
- Consider this interval:
 $i_C = I_{out}$ when #2 is off, and
 $i_C = C \, dv/dt$
 $= C \, \Delta v/\Delta t$ ← since i_C is constant during the interval when #2 is off

Capacitor Value

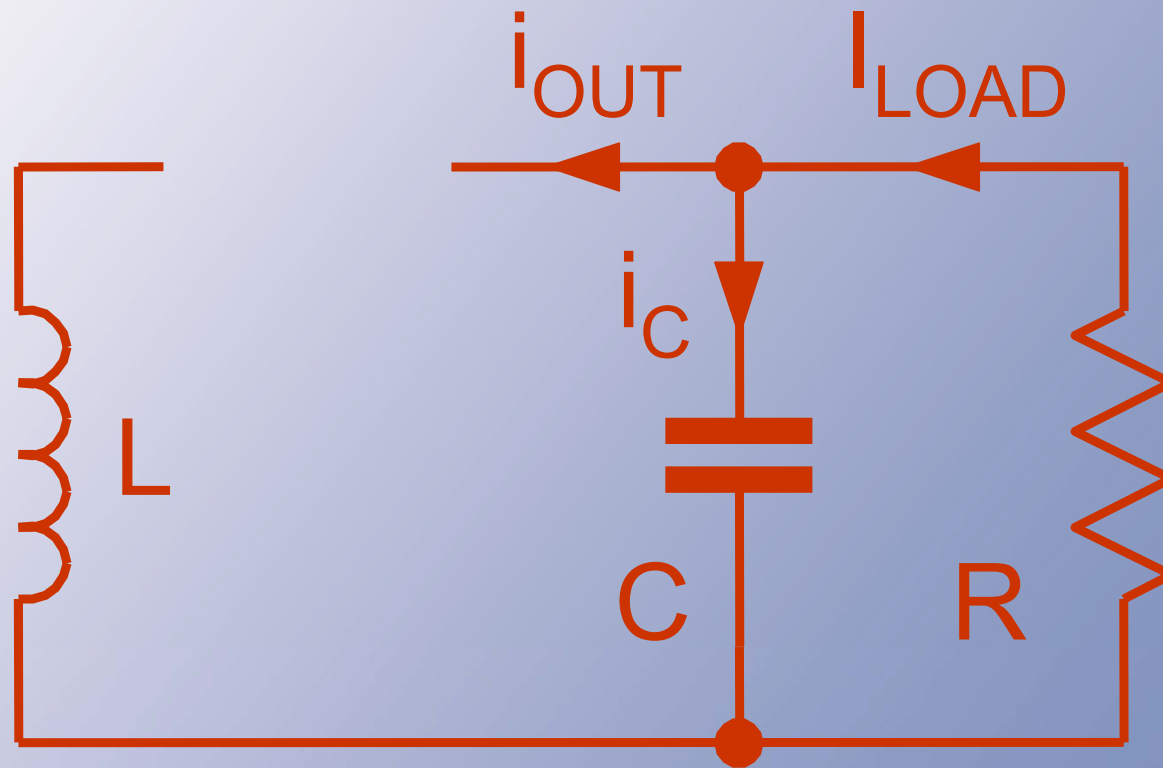



Capacitor

- The time when #2 is off is the same as the time with #1 on, $\Delta t = D_1 T$.
- The allowed variation of voltage is $\pm 0.5\%$ of 12 V, so the total changes should not exceed 1% of 12 V peak-to-peak.





Capacitor

- Therefore, $I_{\text{out}} \Delta t / C = \Delta v < 0.12 \text{ V}$.
- This requires $C > I_{\text{out}} D_1 T / (0.12 \text{ V})$
- The capacitor must work for any allowed values, so we need the highest value of the right side.
- This occurs at the highest load current and highest D_1 value.





Final Result

- Then $C > (1.67 \text{ A})(12/17)(10 \text{ us}) / (0.12 \text{ V})$, $C > 98.0 \text{ } \mu\text{F}$.
- In conclusion, we could use a 0.5 mH inductor, a 100 μF capacitor, and would have a duty ratio range of $0.444 < D_1 < 0.706$ for this 100 kHz frequency selection.







More Indirect Converters

- We could use a boost as the input to a buck.
- This again ought to allow any level of output.
- Will there be a polarity change?


Boost-Buck Development

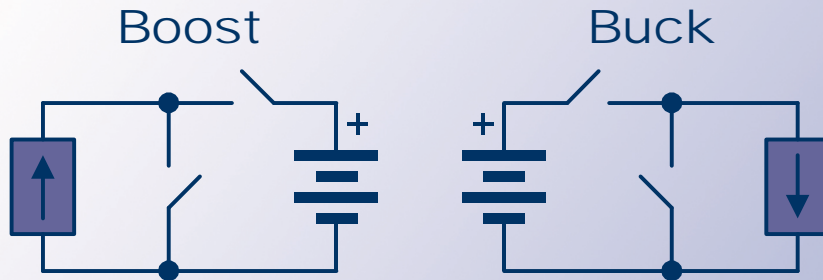

a) Boost and Buck.

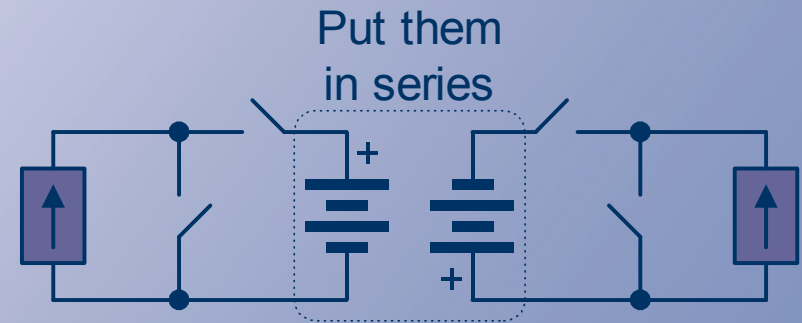

b) Buck upside down.

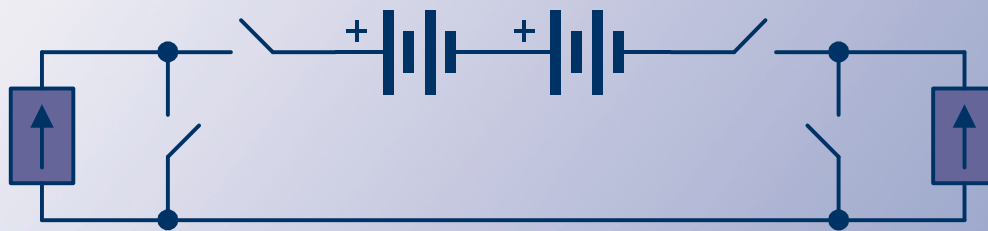

c) Voltages in series.



d) Remove redundancy.






Final Simplification

- The switch in series with the voltage source is not necessary for KCL.
- Try removing it.
- The voltage source is a transfer source.

Boost-Buck Converter

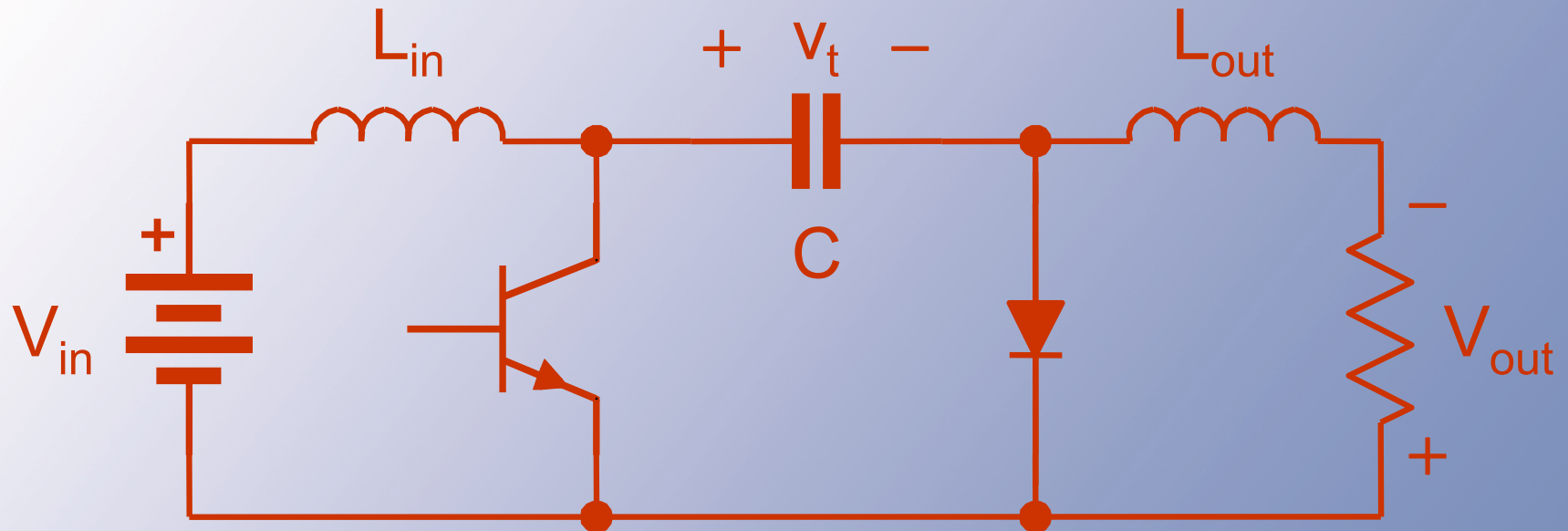

- Left switch is FCFB.
- Right switch is FCRB.



Relationships

- To meet KVL and KCL, $q_1 + q_2 = 1$.
- There are really two matrices now. Let us consider the transfer source.
- Transfer current is subject to control.
- Transfer current $i_t = q_2 I_{in} - q_1 I_{out}$.
- Transfer source power is
 $i_t V_s = q_2 I_{in} V_s - q_1 I_{out} V_s$ ← Want 0 average!






Relationships

- This can be done if $D_2 I_{in} = D_1 I_{out}$.
- Since $D_1 + D_2 = 1$, we have
$$D_1 I_{out} = (1 - D_1) I_{in}.$$
- This becomes $V_{out} = D_1 V_{in} / (1 - D_1)$, based on conservation of energy.
- The polarity reversal comes from the cascade process.



Relationships

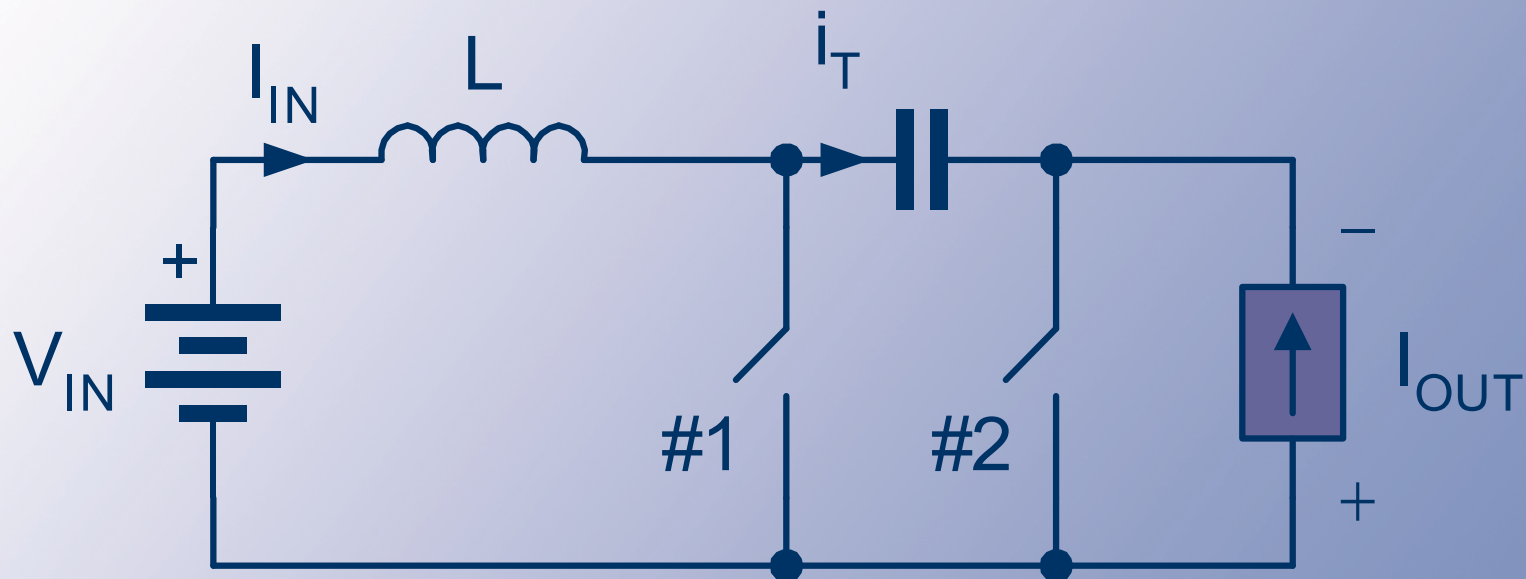

$$D_1 I_{out} = (1 - D_1) I_{in}$$

$$D_1 V_{in} = (1 - D_1) V_{out} \quad (\text{Same as for the buck - boost})$$

Relationships

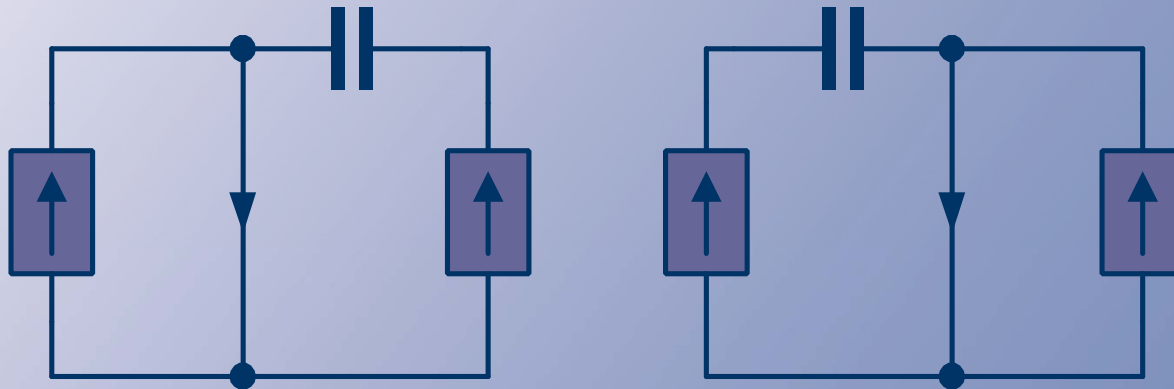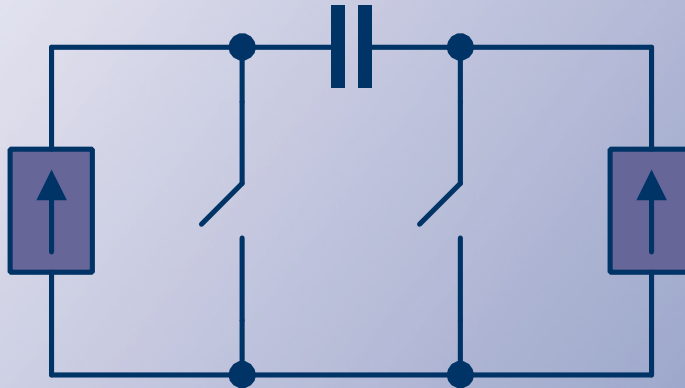


The switches must carry both I_{in} and I_{out} .



Boost-Buck

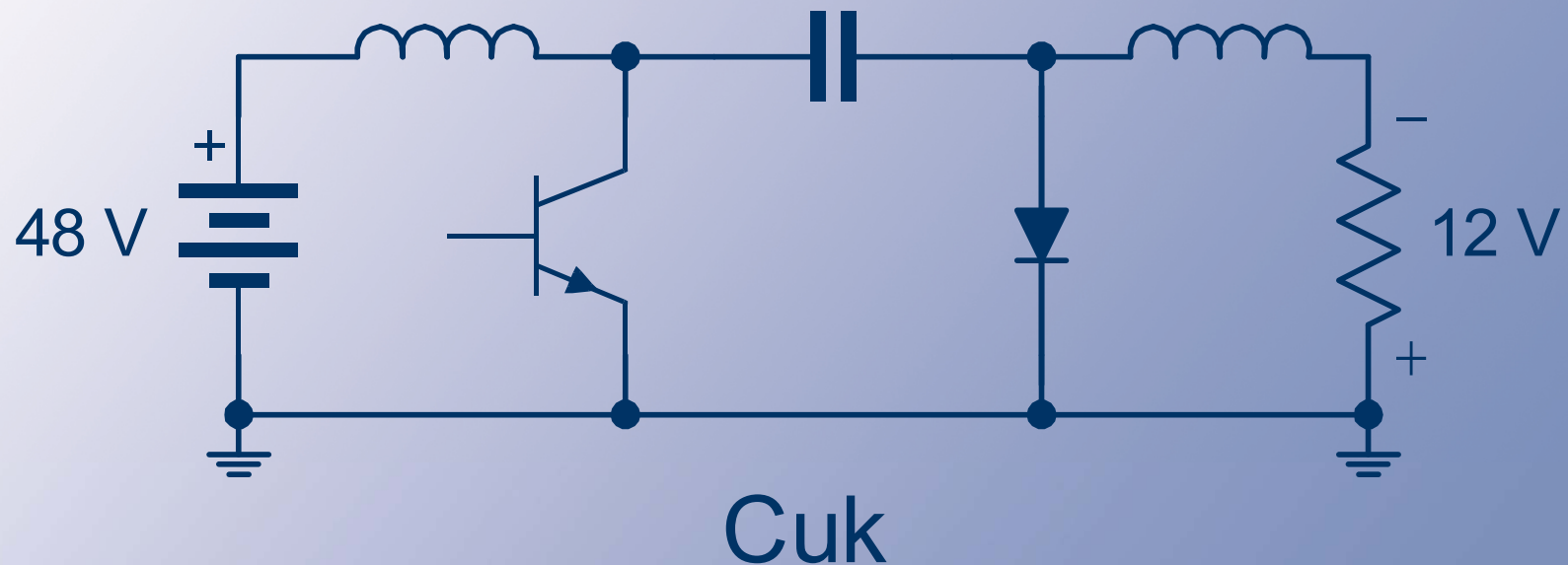The circuit is often called the “Cuk” converter, after the original patent holder (now expired).





Relationships

- The boost-buck (Cuk) also has a polarity reversal, and generally produces the same relationships as the buck-boost .
- Each switch must carry $I_{in} + I_{out}$ and must block $V_s = V_{in} + V_{out}$.
- Transfer source: a capacitor.





What About Voltages?

- The input voltage: $v_{in} = q_2 V_s$,
- The output voltage in a negative direction : $v_{out} = q_1 V_s$,
- Average input: $V_{in} = D_2 V_s$,
- Average output: $V_{out} = D_1 V_s$.
- Add to get
$$V_{in} + V_{out} = (D_1 + D_2)V_s$$
$$= V_s.$$



Example

- Input: $+15\text{ V}$
- Output: $-15\text{ V} \pm 1\%$
- Power: 15 W
- Switching: 150 kHz
- We need to find L , C , and duty ratios to meet these needs.





Duty Ratios

- The converter gives $V_{\text{out}} = -D_1 V_{\text{in}} / (1 - D_1)$.
- With +15 V in and -15 V out,
 $(15 \text{ V}) = D_1 (15 \text{ V}) / (1 - D_1)$.
- The solutions: $D_1 = 1/2$, $D_2 = 1/2$
- At 15 W, the average output current is 1 A. So is the average input current.
- The output inductor is allowed $\pm 1\%$ current ripple to enforce the target output voltage variation.



Inductor Current

- When the diode is on, the output inductor sees $15 \text{ V} = L \text{ di/dt}$.
- The duration of the diode-on interval is $D_2 T = 3.33 \text{ us}$.
- Simplify to $15 \text{ V} = L \Delta i / \Delta t$, with $\Delta t = D_2 T$, and $\Delta i < (0.02) \times (1 \text{ A})$.
- Therefore, $L > (15 \text{ V})(3.33 \text{ us}) / (0.02 \text{ A})$.
 $L > 2.5 \text{ mH}$ (output inductor).



Transfer Capacitor

- Rather arbitrarily, allow $\pm 10\%$ variation in transfer voltage.
- The average voltage is $V_{in} + V_{out} = 30 \text{ V}$.
Allowed variation: 6 V (a total of 20%).
- With switch #2 on, $i_C = I_{in}$

$$= 1 \text{ A.}$$

$$i_C = C \, dv/dt$$
$$= C \, \Delta v / \Delta t,$$

$$\Delta t = 3.33 \text{ us.}$$





Capacitor Result

With $\Delta v < 6 \text{ V}$,

$$C > (1 \text{ A})(3.33 \text{ us})/(6 \text{ V}),$$

$$C > 0.56 \text{ uF}.$$

The transfer capacitor in this converter typically carries substantial ripple current.





Polarity Issue

- We have any allowed output value -- except that the values are negative.
- This is not always convenient.
- Options: Cascade some more, e.g., boost-buck-boost.
- Other option: check inductor.






Coupled Inductors

- The buck-boost converter uses a transfer inductor.
- The energy is stored in a magnetic field, with $W_L = 1/2 Li^2$.
- The inductor is built as a coil on a magnetic core.




Coupled Inductors

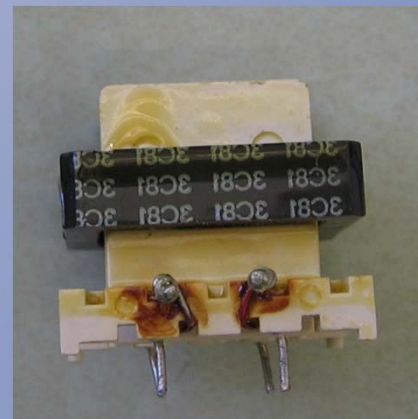- What if we use two (or more) core windings? Then the stored energy is a sum for individual windings:
- $W_L = \sum \frac{1}{2} Li^2$.
- We could have $i = 0$ in one winding -- if another carries current.



Buck-Boost, Coupled L

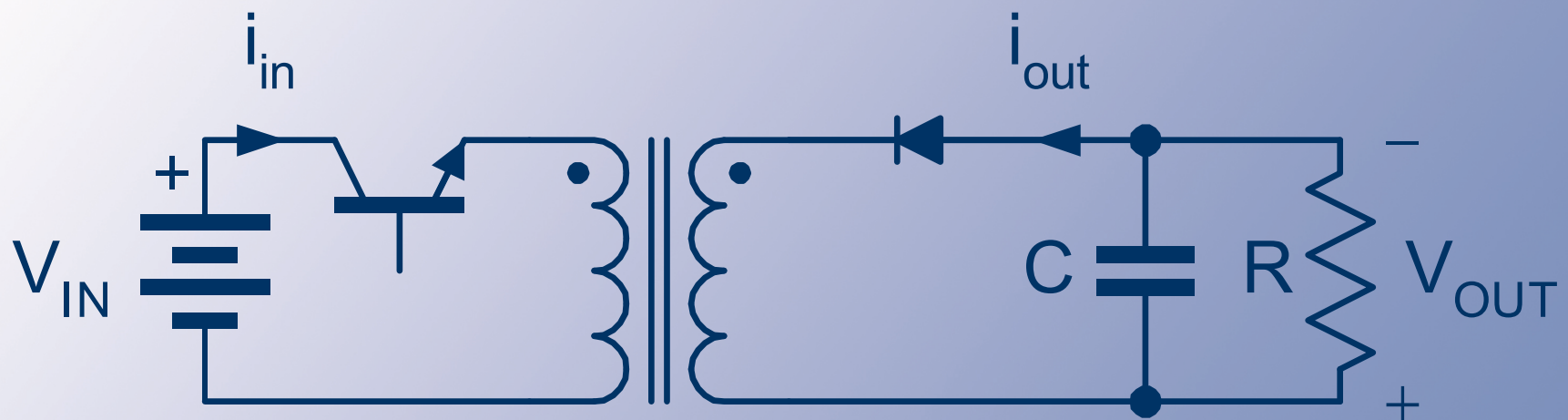


- When switch #1 turns off, the other coil provides a current path.
- We meet KCL, based on magnetics.



What About This?

- This converter (which is still a buck-boost, really) adds isolation.
- We can connect the output in either polarity!
- The result allows either polarity, and also any output.
- This is called a *flyback* converter.

Flyback Converter

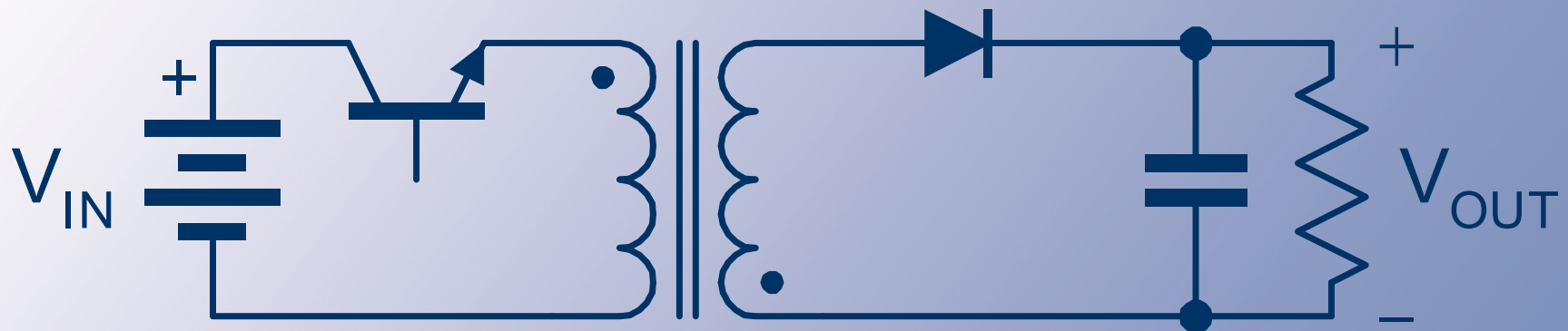

The basis for most switching power supplies up to about 100 W.



Flyback Converter

- We also have the option of providing a turns ratio.
- This is very helpful when high conversion ratios are desired.
- The flyback converter is a “true” dc transformer.





Analysis

- What if there is a turns ratio?
 - We know how to analyze it at 1:1, since that is a buck-boost circuit.
 - Do a conversion to get 1:1, then analyze.
- Example: 200 V to 5 V. If we use a 200:5 turns ratio, $D = 1/2$.






Analysis

- Why? The 200 V input to a 200-turn winding is equivalent to a 5 V input on a 5-turn winding.
- In general, V/N is a constant, so a simple ratio can give an equivalent.
- The inductance depends on N^2 .

Boost Alternative

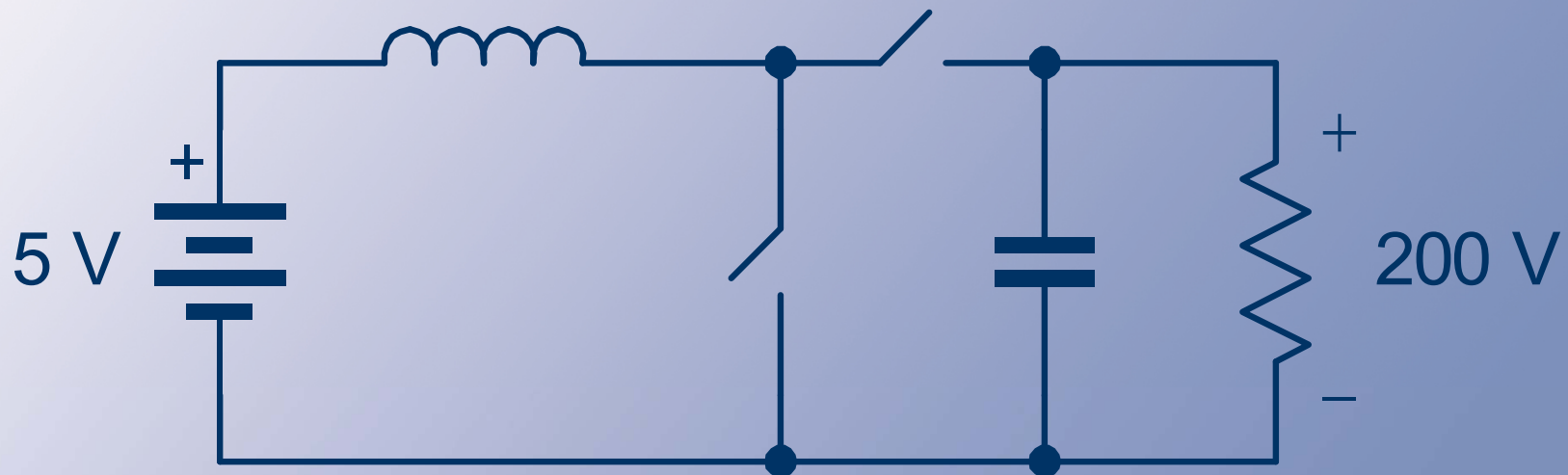
If V_{in} is very different from V_{out} , one of the switches needs to be on for a very short time. Time errors will be more important.



$$D_1 = \frac{39}{40}$$

Flyback Converter

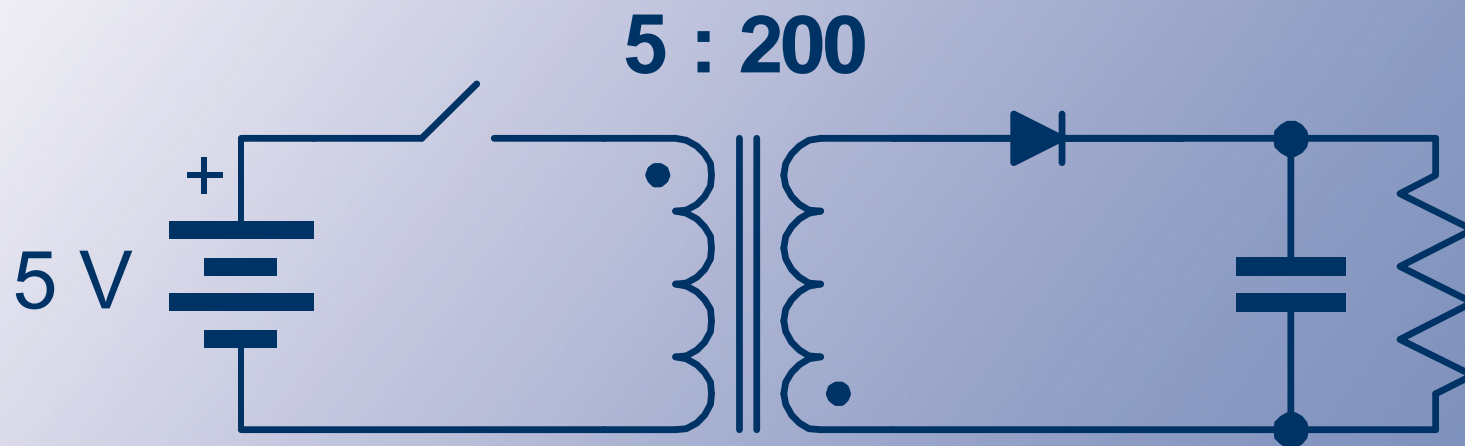
More practical: Take advantage of the turns ratio of the transformer.





$D_1 = \frac{1}{2}$ Much easier to achieve,
and not so sensitive.

Flyback Converter: Equivalent Buck-Boost Converter

5 : 200

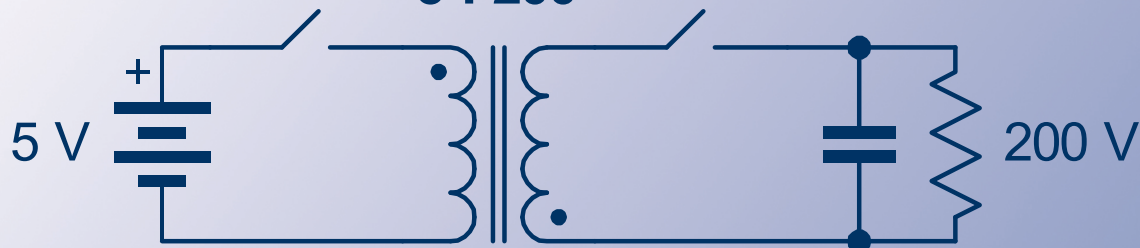

200 : 200

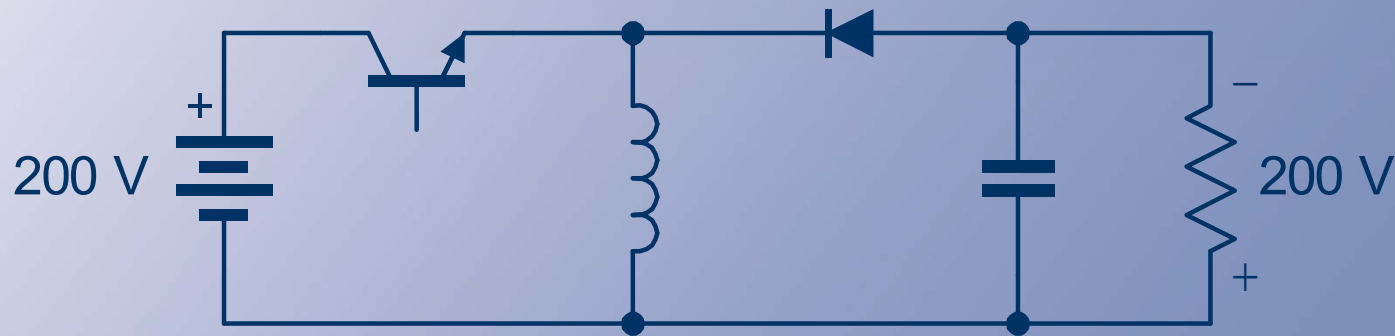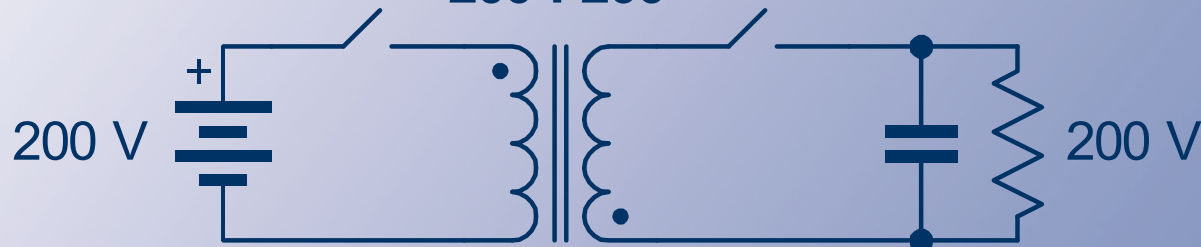



A Pointer

- It is usually helpful to have a duty ratio D_1 in the 0.3 to 0.5 range.
- We often select a turns ratio for a target duty ratio of about 40%.






Example

- 200 V to 5 V converter, 50 W, 100 kHz switching. Want $\pm 1\%$.
- Let us select a turns ratio of 200:5.
Then a +5 V to -5 V, 50 W, buck-boost converter can be the basis for design.



Example

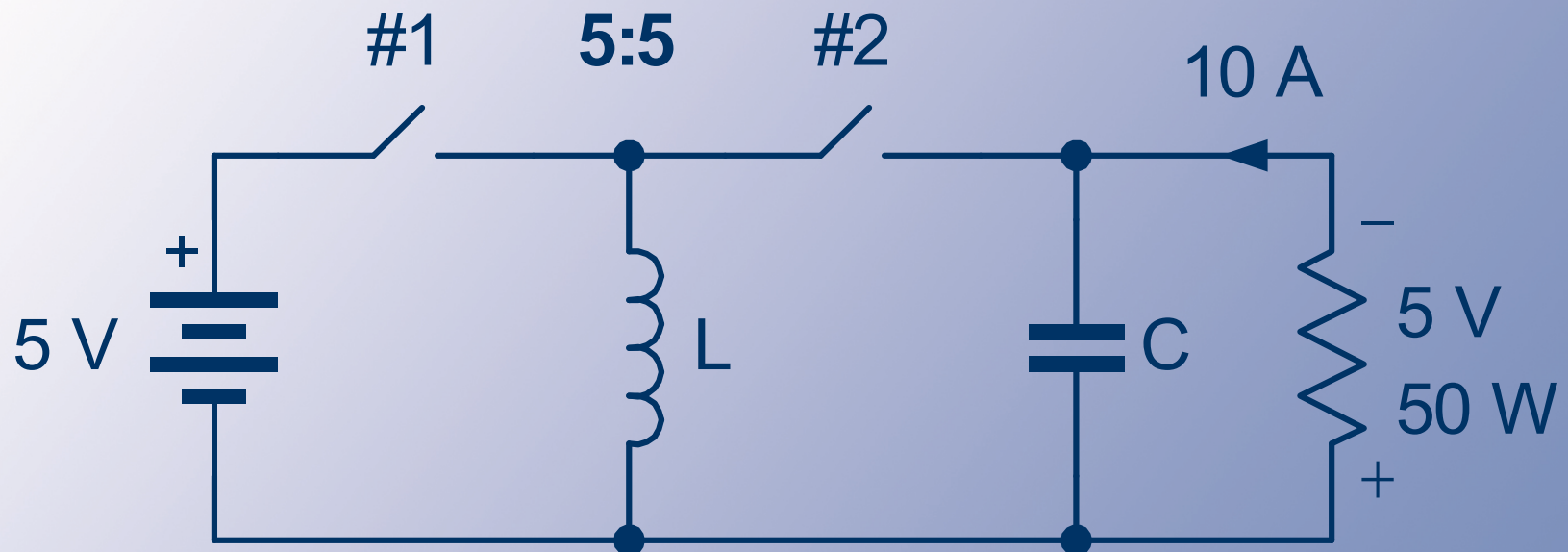

$$D_1 = D_2 = \frac{1}{2}$$



Example

- The duty ratio is 50%. The average output current is 10 A. The inductor current must be $(10\text{A})/D_2 = 20\text{ A}$.
- The capacitor carries 10 A when the diode is off, and $i_C = C\text{ } dv/dt$.
- For $\Delta t = 5\mu\text{s}$, $C > 500\text{ }\mu\text{F}$.





Inductor Value

- Consider a $\pm 5\%$ current ripple (but what does this mean in a flyback?).
- The inductor sees 5 V when the diode is on, $5 \text{ V} = L \Delta i / (5 \text{ us})$.
- With $\Delta i < 2 \text{ A}$, $L > 12.5 \text{ uH}$.






The Flyback

- For the flyback, the coupled inductor should measure $12.5 \mu\text{H}$ from the 5 V side, and that coil will carry 20 A when on.
- On the other side, at $200:5$ ratio, there are 40 times as many turns.



The Flyback

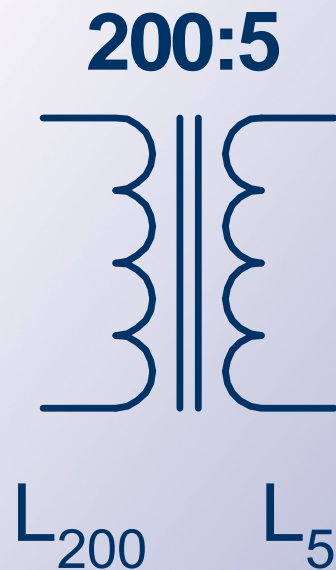

$$\frac{L_{200}}{L_5} = \left(\frac{200}{5} \right)^2 = 1600$$



The Flyback

- The inductance measured at the input is 1600 times higher, or 20 mH.
- The input coil carries $(20 \text{ A})/40 = 1/2 \text{ A}$.
- The input switch must carry $1/2 \text{ A}$ and block 400 V (why?)
- The output switch must carry 20A and block 10 V.
- It is not the inductor current that stays nearly constant, but rather the magnetic flux.





Major Indirect Converters

- Buck-boost
- Boost-buck (Ćuk)
- SEPIC (single-ended primary inductor converter) = boost-buck-boost
- Zeta = buck-boost-buck
- These are all “two switch” converters
- There are a few others.
- Some “four switch” versions exist, but are less common.






Ratios

- SEPIC and Zeta same ratio as buck-boost and boost-buck, $V_{out}/V_{in} = D_1/D_2$, *except:*
- No polarity reversal.
- Others: boost-buck-boost-buck... buck-boost-buck-boost...
- Two switch versions just add more filter elements.
- Notice: current-voltage-current...



Isolation needs

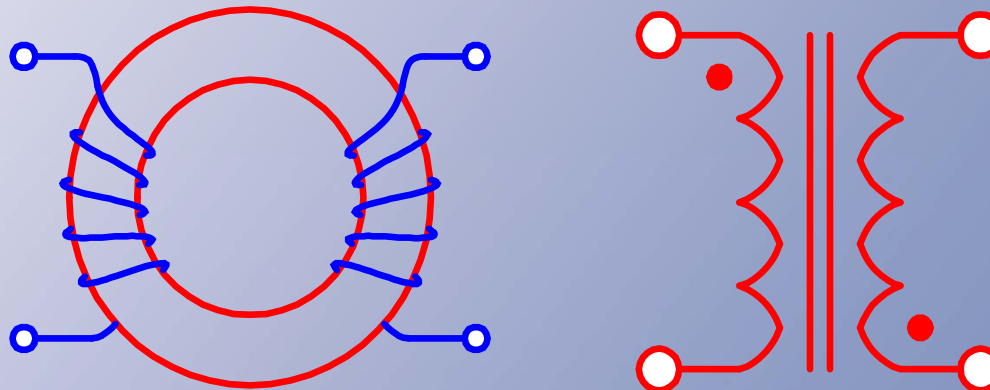- The flyback circuit (derived from buck-boost) uses a “coupled inductor” for isolation.
- This part is **not the same** as a magnetic transformer. It stores energy.



Isolation needs

- A true transformer has

$$p_{in} = p_{out}$$

$$i_{out}/i_{in} = 1/a$$

$$v_{out}/v_{in} = a$$

isolation

- We want a dc transformer. A flyback does this, up to ~100 W.




Magnetic Transformers

- Can we insert a magnetic transformer into a converter?
- To answer this, we need to consider ac issues in a magnetic transformer.
- In a true transformer, voltages and currents are related by a ratio.
- We cannot turn one winding “off” and then draw current from another.



Magnetic Transformers

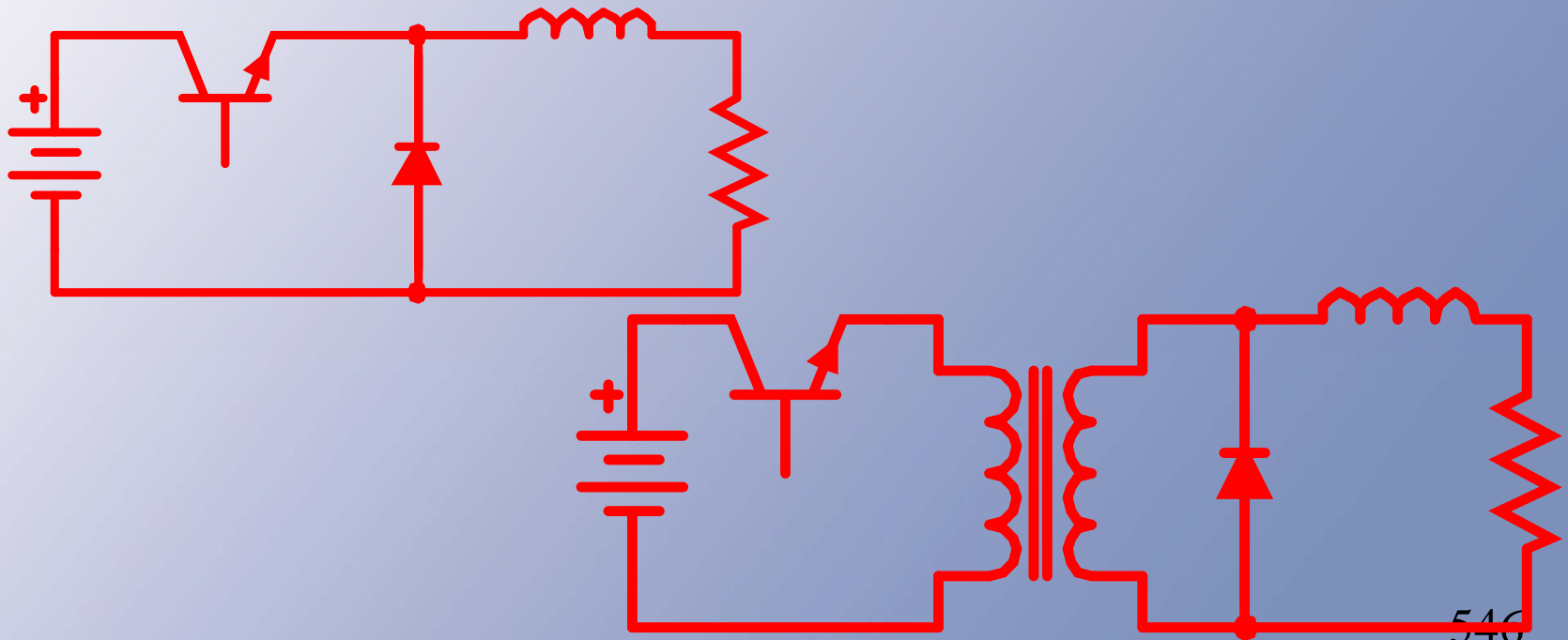- Example: insert a magnetic transformer into a buck converter.
- No. This is a KCL problem.





Magnetic Transformers

- We need to analyze this to understand:
 - Distinctions between coupled inductors and magnetic transformers
 - How and when a magnetic transformer can be used in a dc-dc converter.



Real Transformers

$\lambda \rightarrow$ magnetic flux linkage


$\lambda_1 = N_1 \phi \rightarrow$ magnetic flux linkage

$\lambda_2 = N_2 \phi$

Faraday's Law:

$$v_1 = d\lambda_1/dt$$

$$v_2 = d\lambda_2/dt$$

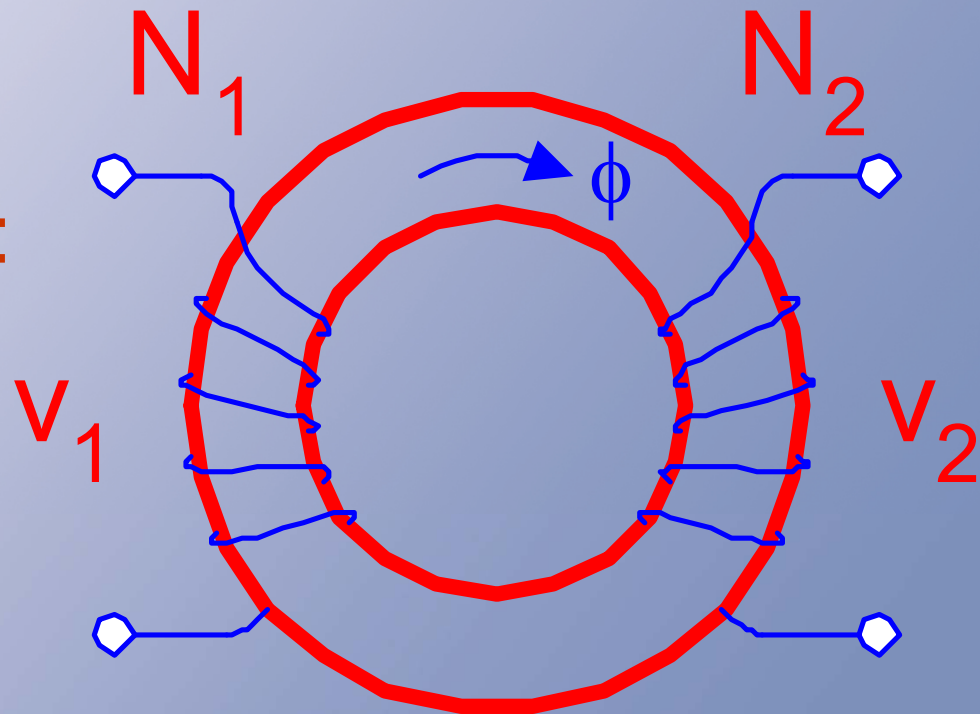



Faraday's Law: Implications

$$v_1 = N_1 \frac{d\phi}{dt} \quad \lambda_1 = N_1 \phi$$

÷

$$v_2 = N_2 \frac{d\phi}{dt}$$

$$\frac{v_1}{v_2} = \frac{N_1}{N_2} \quad \text{if} \quad \frac{d\phi}{dt} \neq 0$$

This is IDEAL CASE.


Real Transformer

$$v = d\lambda/dt,$$


$$\phi = Ni/\mathcal{R}$$

$$v = N^2/\mathcal{R} di/dt$$


$$= L di/dt$$

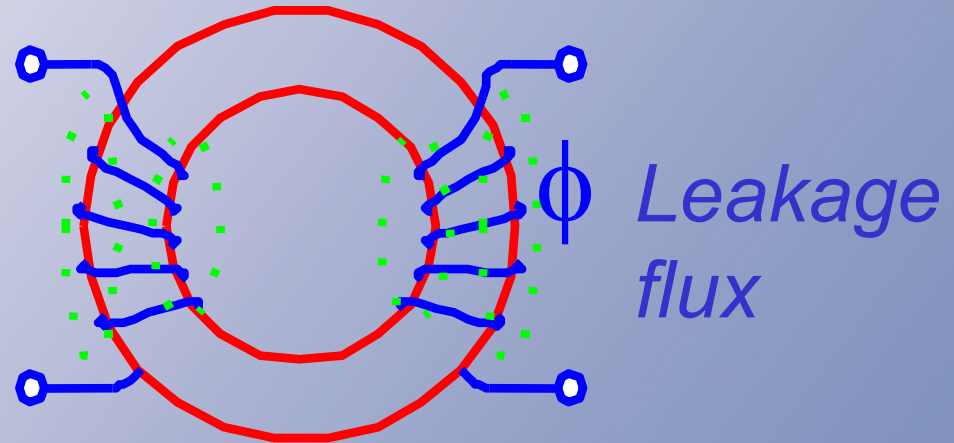

Circuit
Model:

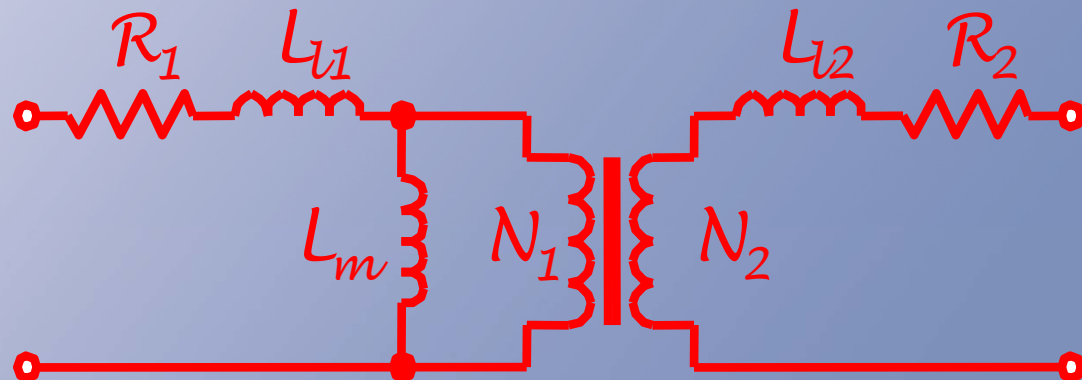


Real Transformer

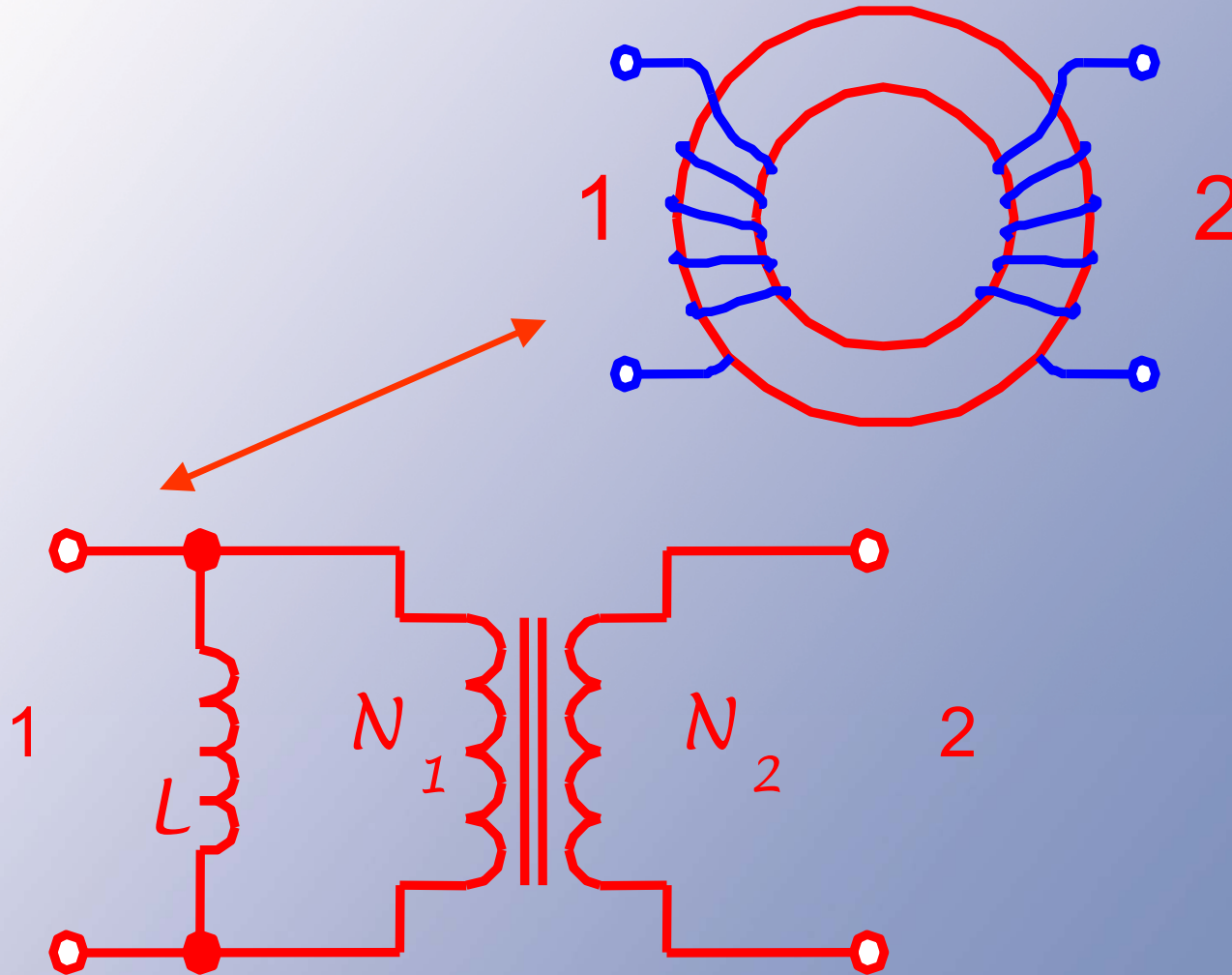

Real Transformer


small values

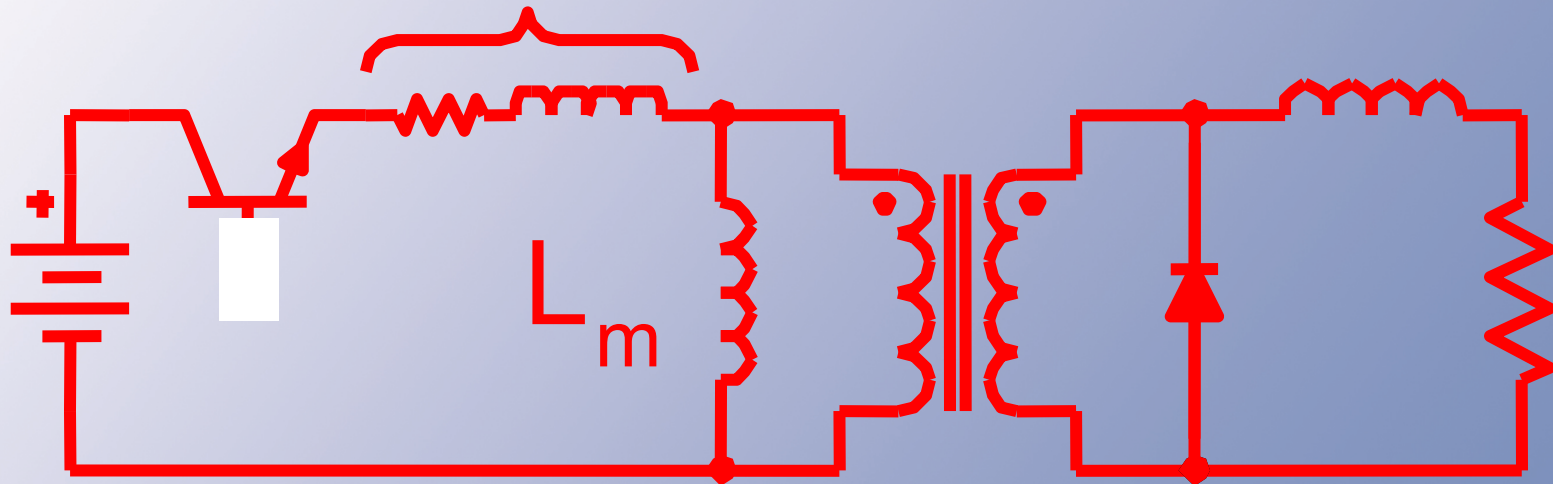

Does not work! Average voltage across L_m is not zero.



How to insert a transformer

Need an “ac” node



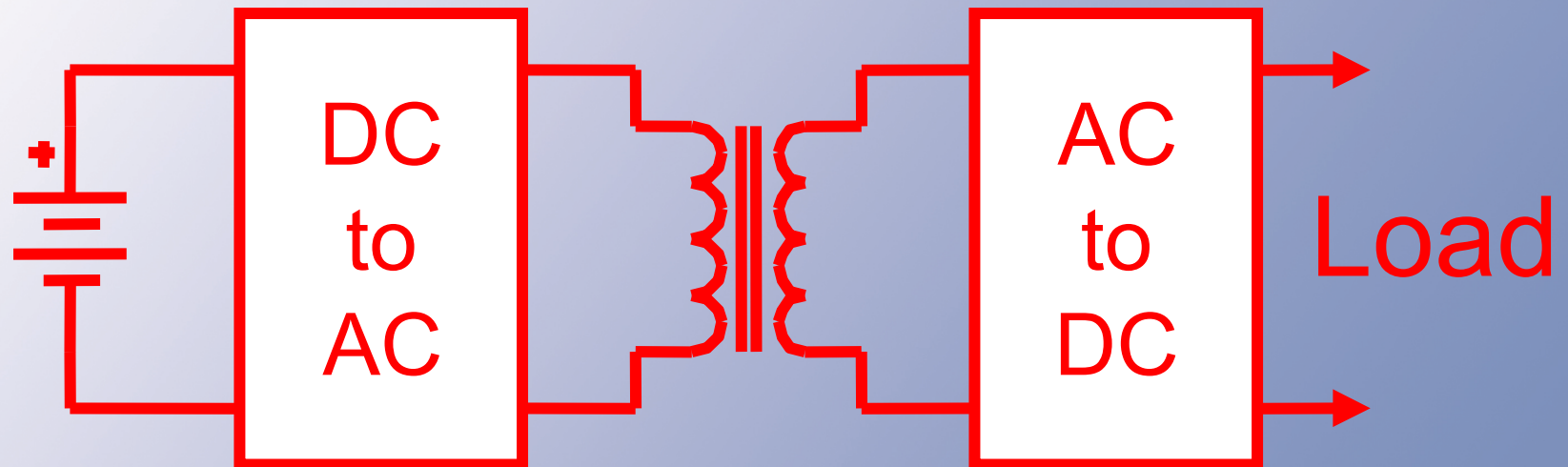


ac link converter




How to insert a transformer

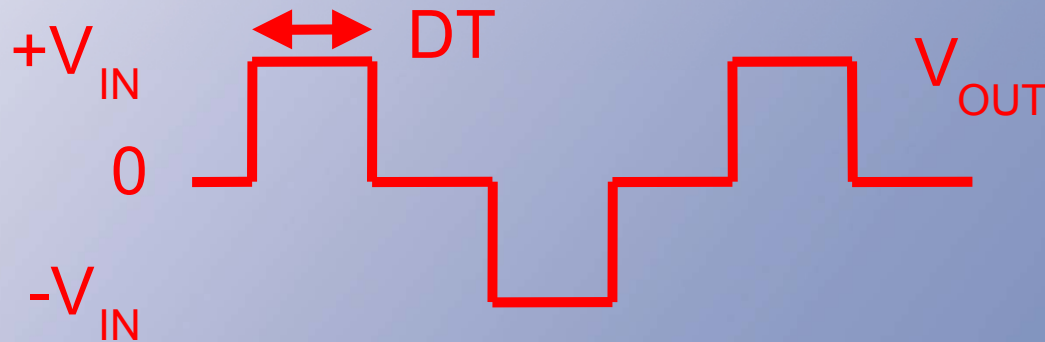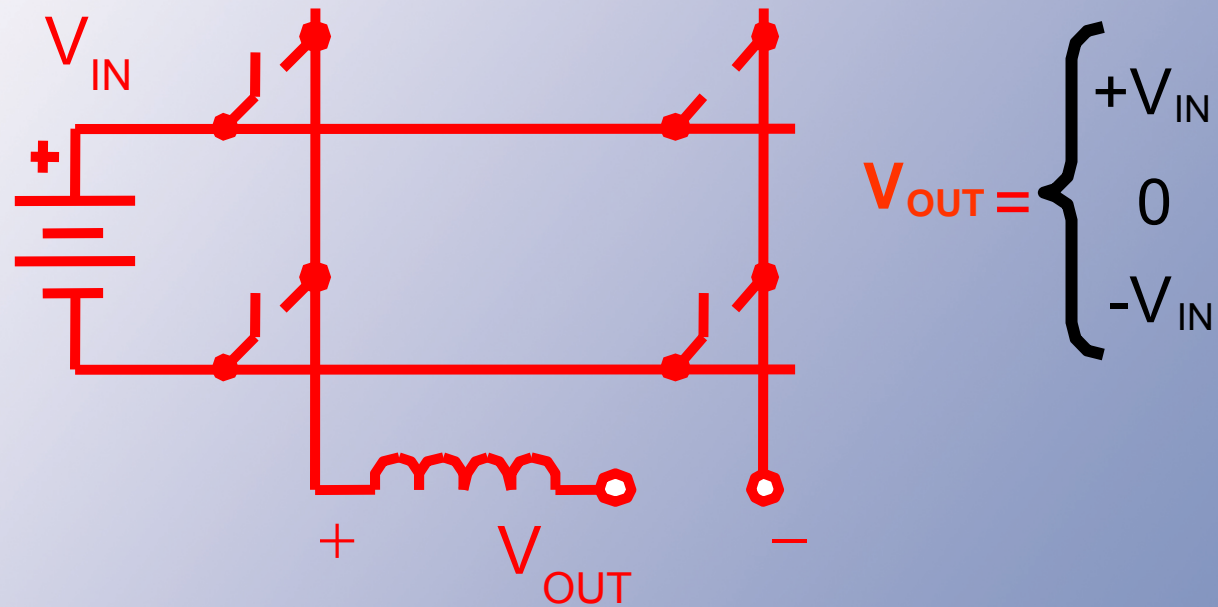


How to insert a transformer

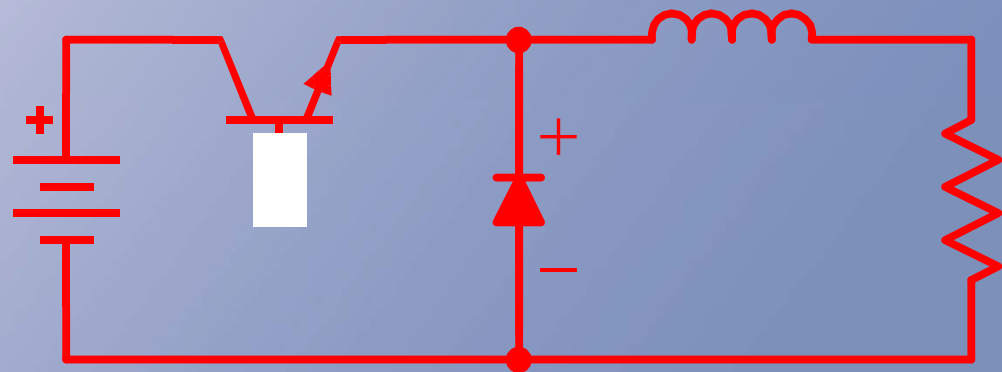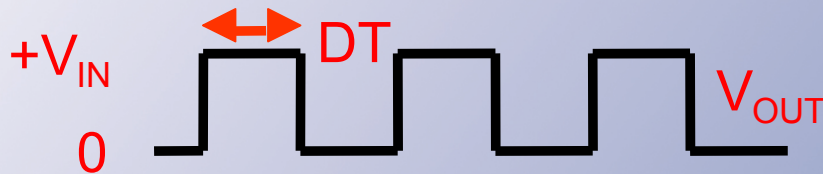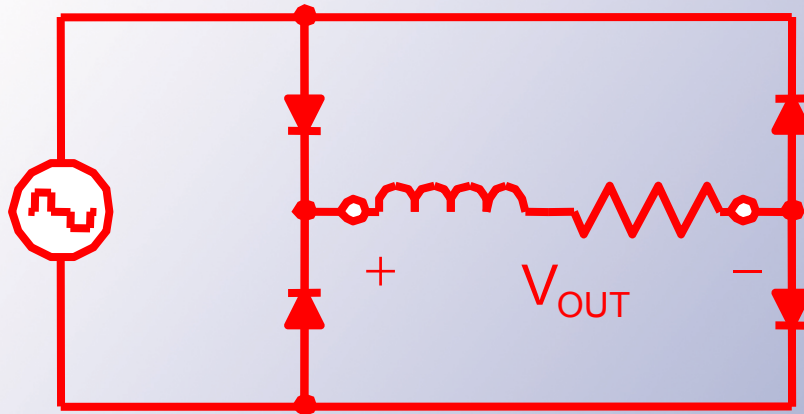

How to insert a transformer

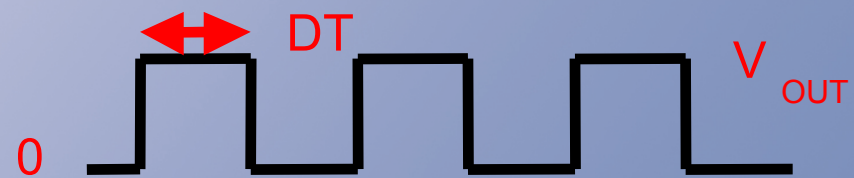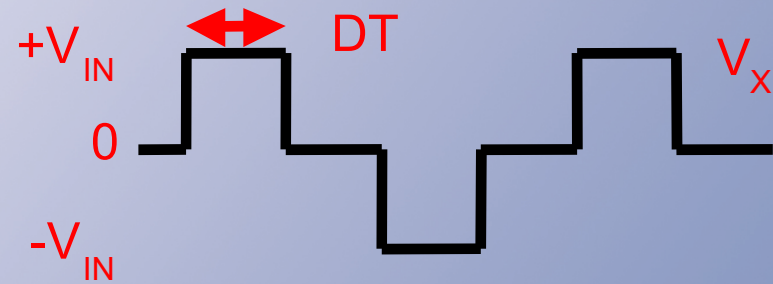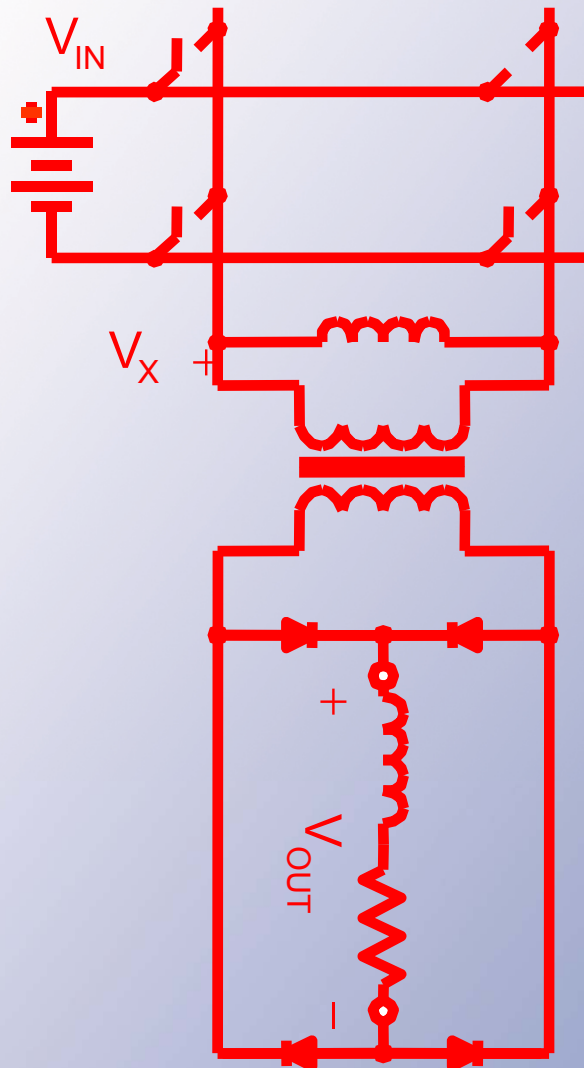

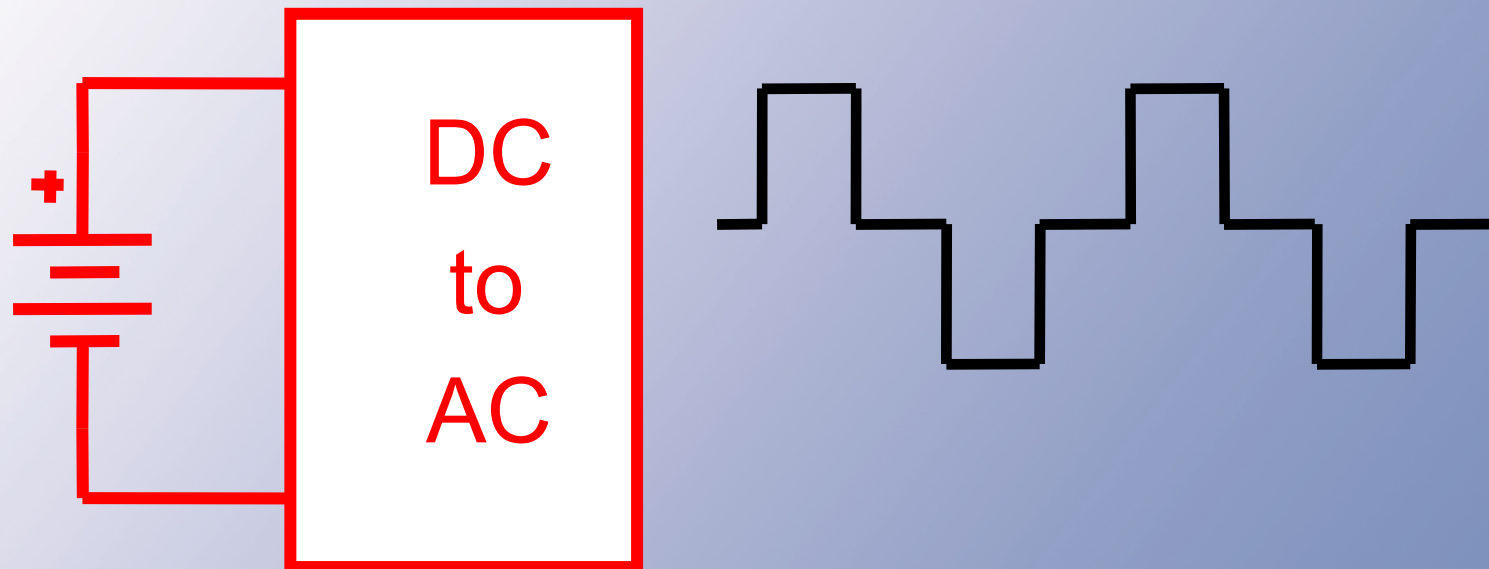Full-Bridge Forward Converters Buck “Matrix” Converter



500 W or more




Forward Converters

- When a magnetic transformer is inserted into a dc-dc converter, the resulting structure is called a *forward converter*.
- There are two general types:
 - Ac link converters
 - Flux reset converters.




Full-Bridge Forward Converters

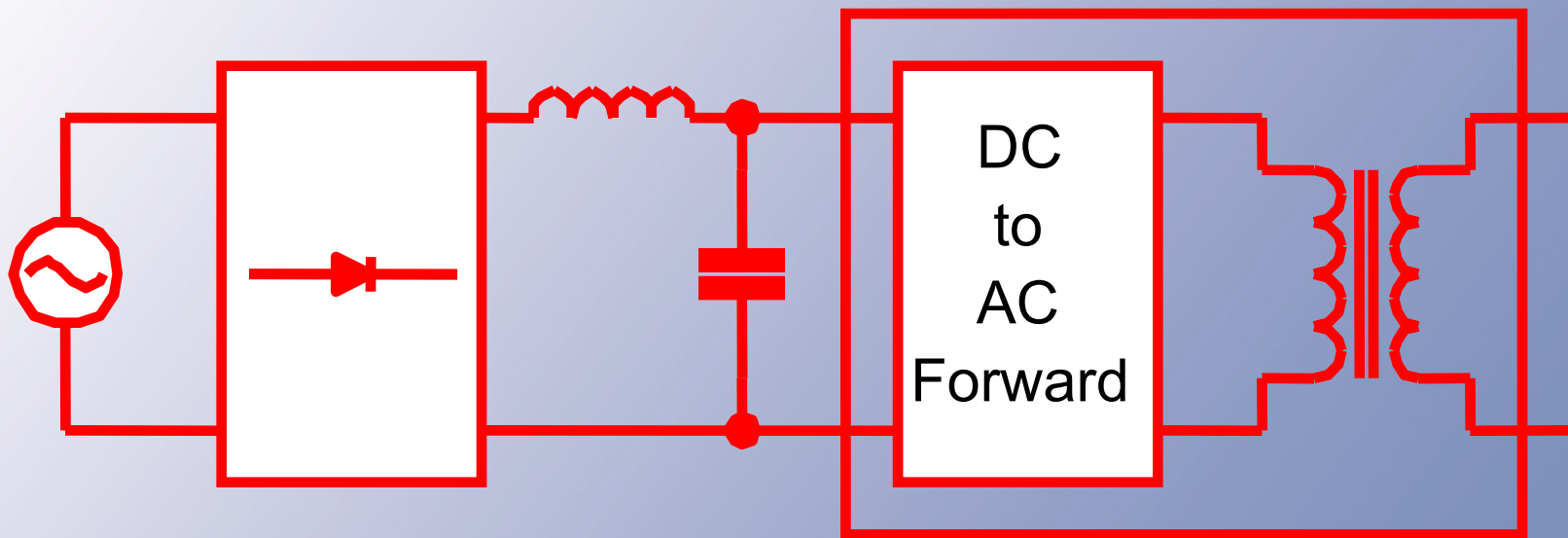


Matrix inverter

Full-Bridge & Single-Ended

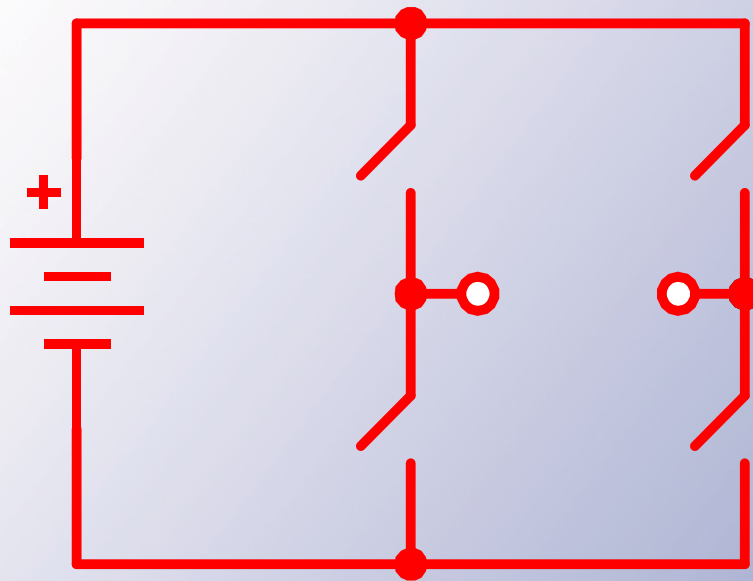


Full-bridge forward

“Single-ended” forward converter

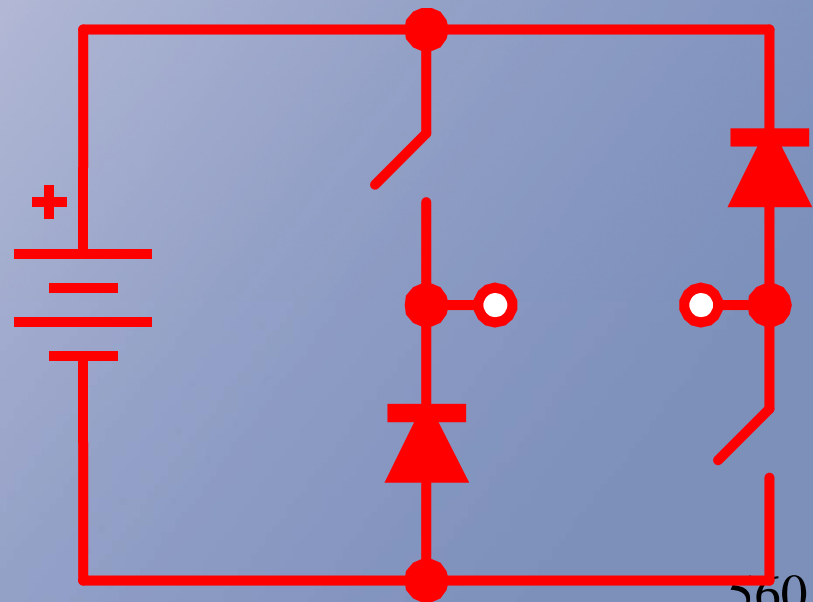

Push-Pull Forward Converter

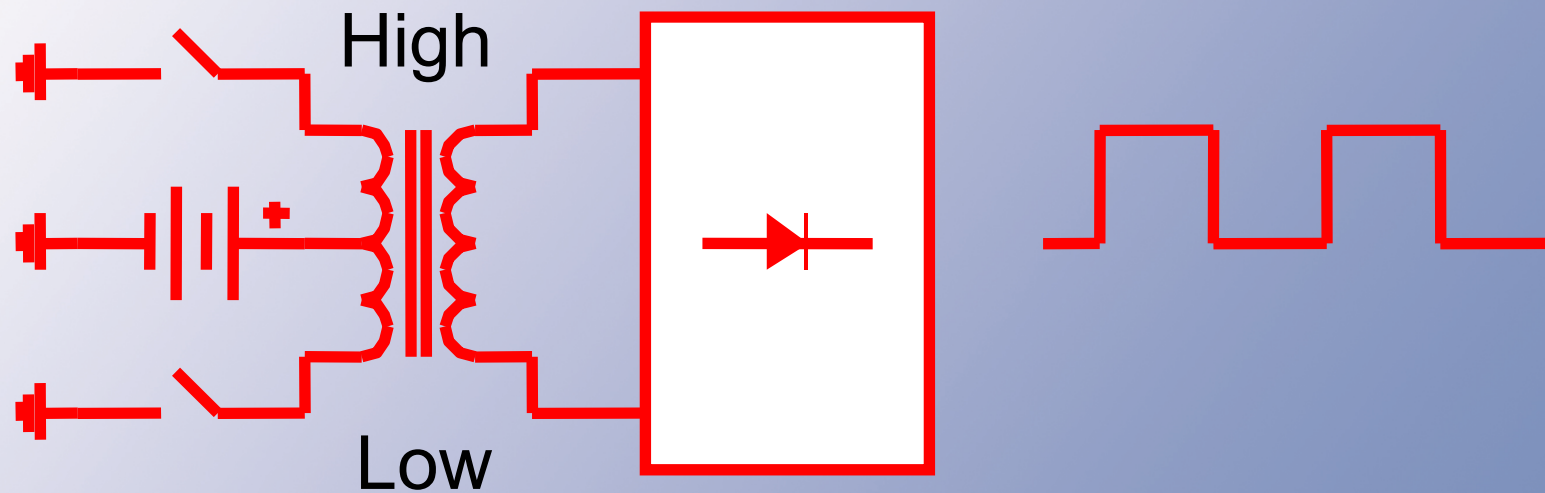



Forward Converters

- The converters so far are all ac link converters.
- They are based on the buck converter, and are called “buck-derived forward converters.”
- Boost-derived converters are just as feasible, and use an input current source.






Forward Converters

- Bridge-type forward converters are used at high power levels.
- Common at 1 kW and up.
- Flux reset converters tend to be simpler, and sometimes appear in place of flyback converters.
- The idea is to provide a current path with some other winding.



Catch-Winding Forward Converter

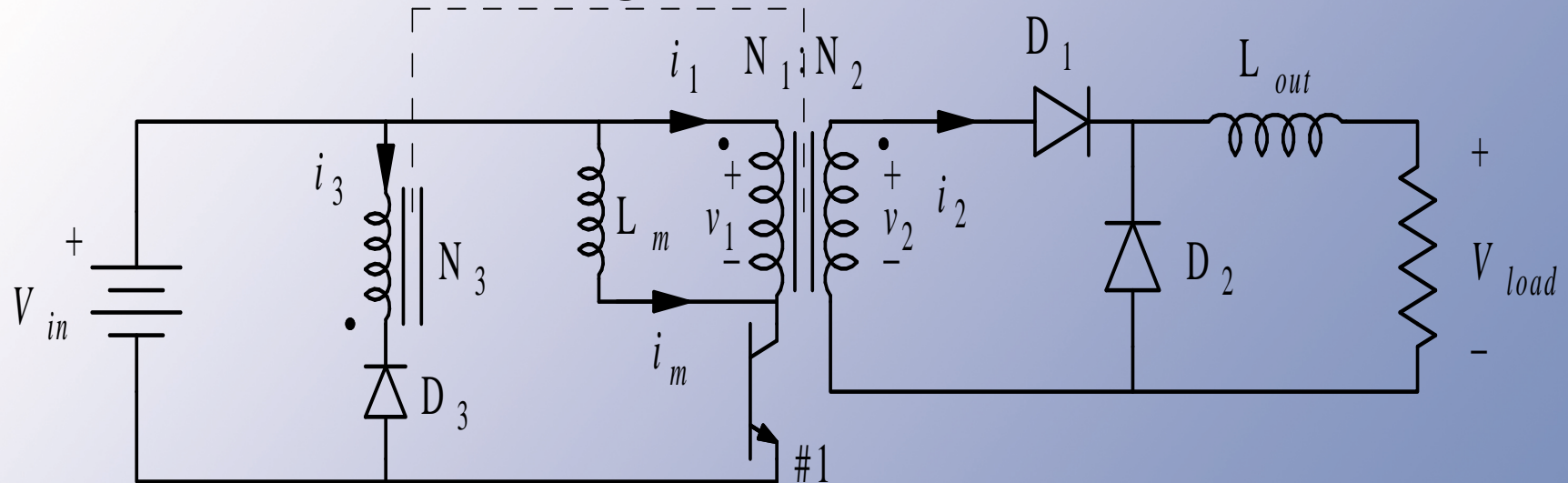


- In this circuit, a third winding acts like a flyback converter.
- The average voltage across L_m can be zero now, if duty ratio is limited.

Buck converter -- Filter

- A buck converter with 6 ohm load, 500 V input, 10 kHz switching, 1.5 mH output inductor.
- Duty is 10%.

Converter Analysis

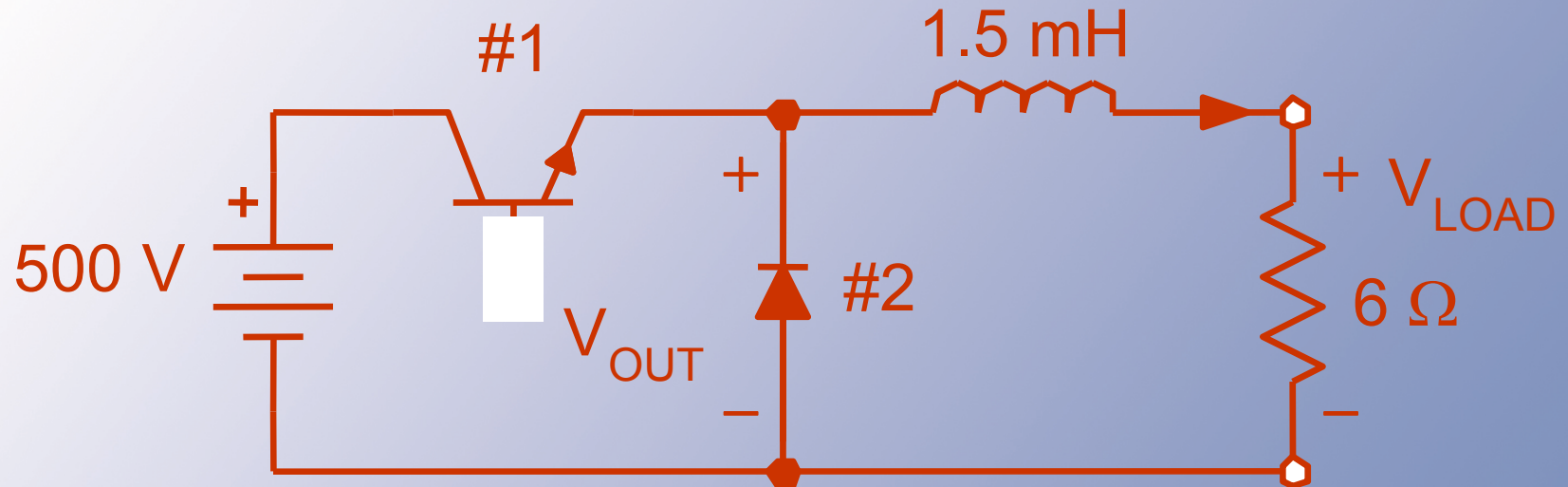

$$f_{\text{switch}} = 10 \text{ kHz}, D_1 = 10\%$$

$$V_{\text{out}} = q_1 V_{\text{in}} + q_2 (0)$$

$$\begin{aligned} \langle V_{\text{out}} \rangle &= D_1 V_{\text{in}} \\ &= \langle V_{\text{load}} \rangle \end{aligned}$$



Converter Analysis

- Average output: $D_1 V_{in} = 50 \text{ V}$
- Inductor current (average):
 $(50\text{V})/(6 \text{ ohms}) = 8.33 \text{ A}$
- Variation: with the diode on, the inductor ideally sees -50 V . This lasts 90% of a period, or 90 μs .



Filter Analysis

$$\langle V_{LOAD} \rangle = 50 \text{ V}$$

$$I_L = 50\text{V} / 6\Omega$$


$$= 8 \frac{1}{3} \text{ A}$$

#2 ON

$$v_L = -50 \text{ V}$$

$$= L \, di/dt$$

$$= L \, -\Delta i / \Delta t$$

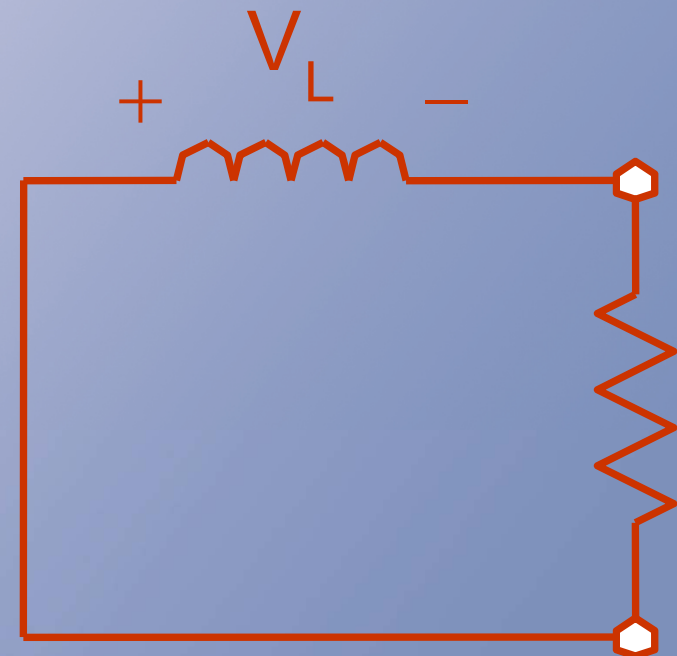



Filter Analysis

$$50 \text{ V} = L \, di/dt$$

$$\Delta t = 90\% \text{ of a period}$$

$$T = 100\mu\text{s}$$

$$\Delta t = 90\mu\text{s}$$

$$(50 \text{ V}) \, 90\mu\text{s} / 1.50 \text{ mH} = \Delta i$$

$$= 3 \text{ A}$$





Filter Analysis

- $50 \text{ V} = L \, di/dt$. Since $50 \text{ V}/L$ is intended to be constant, this is **nearly a slope**, $50\text{V} = L \, \Delta i/\Delta t$.
- $(50 \text{ V})(90 \text{ us})/(1.5 \text{ mH}) = 3 \text{ A}$.
- This translates to an output change of $\pm 18 \text{ V}$, hardly fixed.





Check Ideal Action



- Can the **ideal action assumption** still be used?
- For the actual exponential action, the average output is still 50 V.
- The actual Δi value is 2.996 A.
- **Ideal action overestimates by 0.12%.**



Filter Analysis

$$\Delta V_{LOAD} = 18 \text{ V}$$
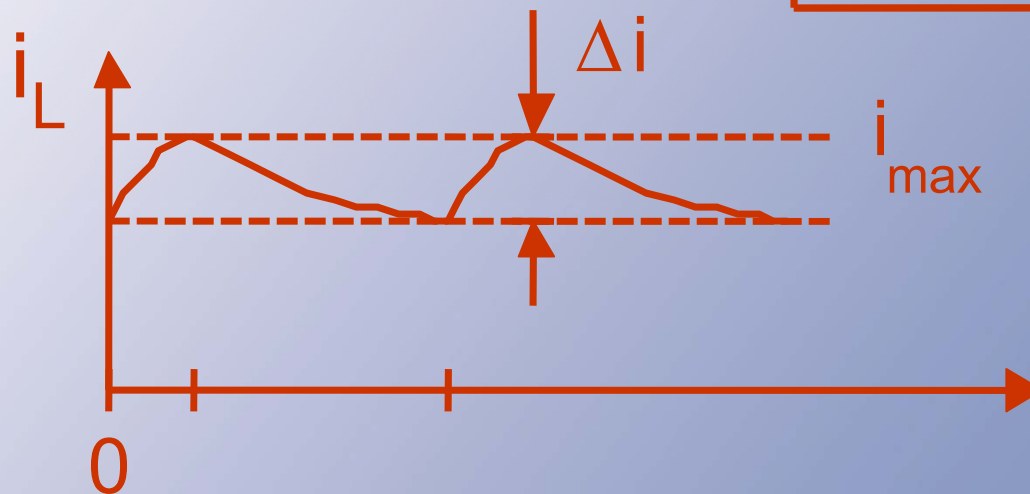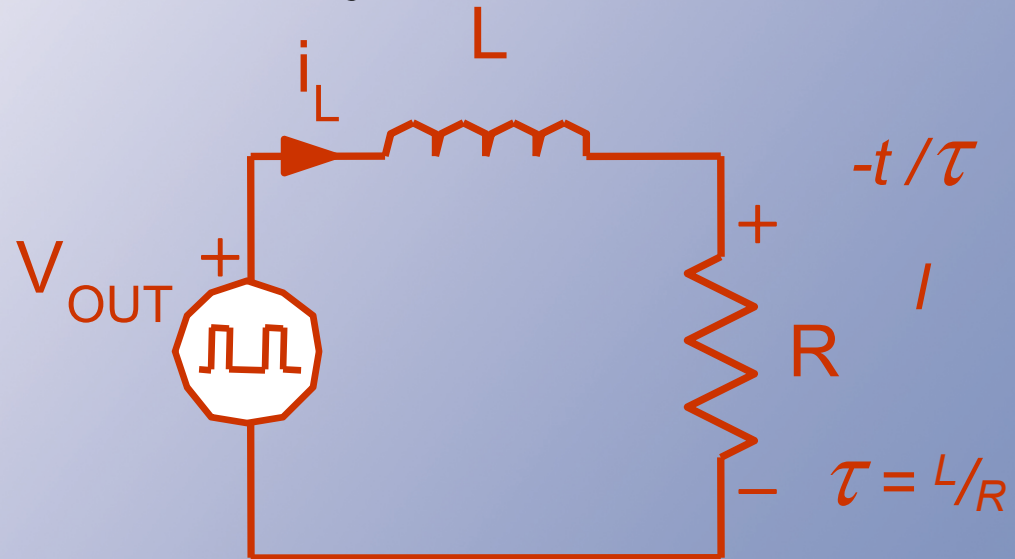
$$\langle V_{LOAD} \rangle = 50 \text{ V}$$



$$\Delta i_L = 2.996 \text{ A}$$

$$= 3.00 \text{ A}$$




Filter Analysis

- **Actual Δi is 0.12% lower** than the 3A from “Ideal Action,” **even though Δi is $\sim 35\%$ of $\langle I \rangle$.**
- This is a conservative estimate. (Ideal action overestimates the ripple.)




Capacitive Filter

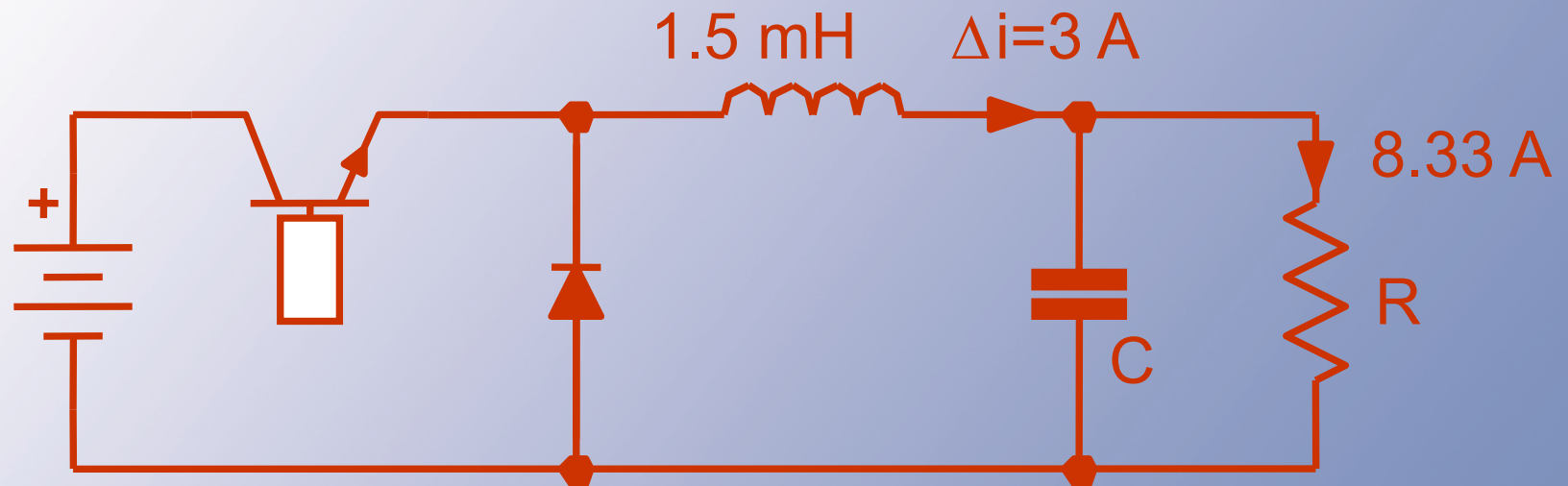


Add C to make $\Delta v_{\text{out}} < 1\%$ peak-to-peak.

Capacitive Filter

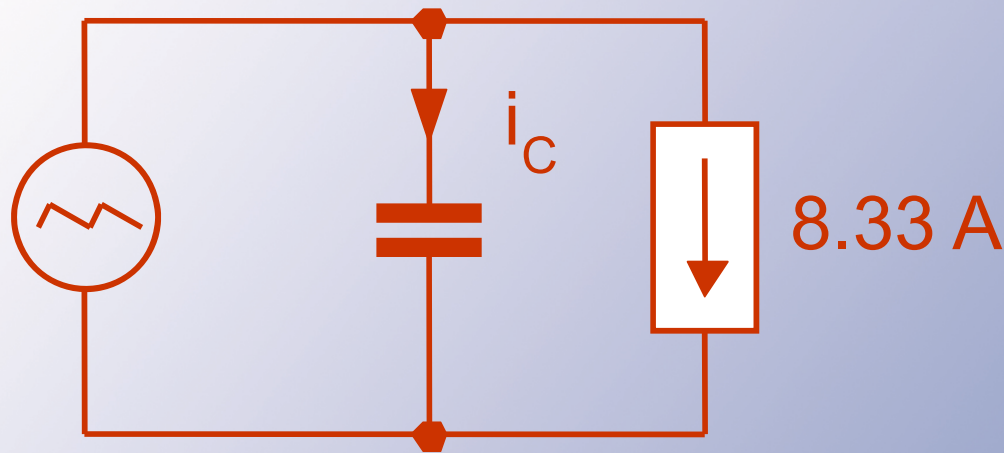

$$i_c = C \frac{dv}{dt}$$

$$\neq C \frac{\Delta v}{\Delta t}$$

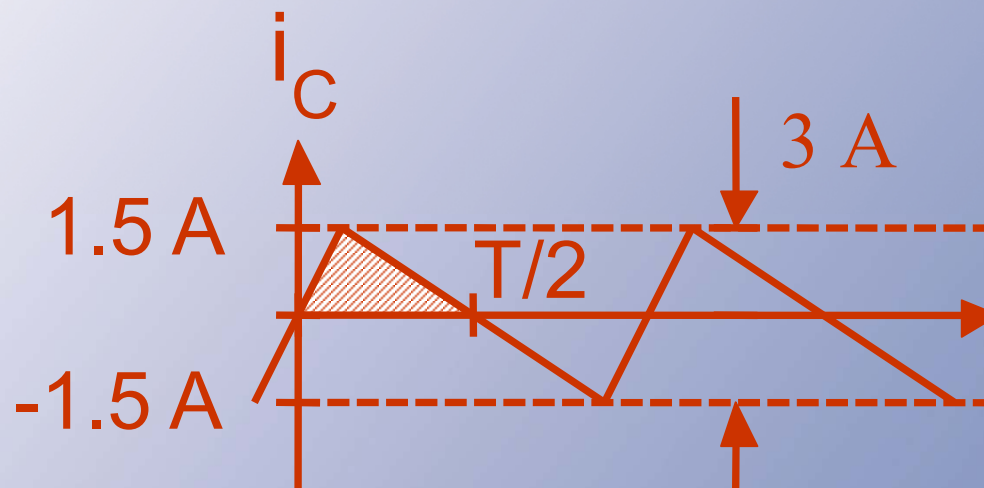

$$\frac{1}{c} \int i_c dt = v$$



Capacitive Filter

$$\frac{1}{C} \int_{t_0}^{t_1} i_c dt = v(t_1) - v(t_0)$$

- If we choose the right times, this gives Δv .
- The integral is the area under a triangle.





Capacitance Value

$$\frac{1}{C} \int_0^{T/2} i_C(t) dt = \Delta v_{peak-to-peak}$$

- The area integral: a triangle, $\frac{1}{2}$ x base x height, or $(1/2) \times (T/2) \times (\Delta i/2)$.
- Therefore:

$$\Delta v_{peak-to-peak} = \frac{1}{C} \frac{1}{2} \frac{T}{2} \frac{\Delta i}{2} = \frac{T}{8C} \Delta i$$



Capacitance Value

- We want $\Delta v < 0.5 \text{ V}$.
- $D_i/2 = 1.5 \text{ A}$.
- $(1/C) \times (25 \mu\text{s})(1.5 \text{ A}) = \Delta v < 0.5 \text{ V}$.
- This requires $C > 75 \mu\text{F}$.
- Might use $100 \mu\text{F}$.





Converter Example

- Input: +6 V to +15 V.
- Output: +12 V \pm 1%, 24 W.
- Common ground, input and output.
- This cannot be met with buck, boost, buck-boost, or boost-buck.
- Need flyback, SEPIC, or Zeta.
- Example: Flyback design.




Design:

Input: +6 V to +15 V

Output: +12 V \pm 1%, 24 W

Common ground

Flyback

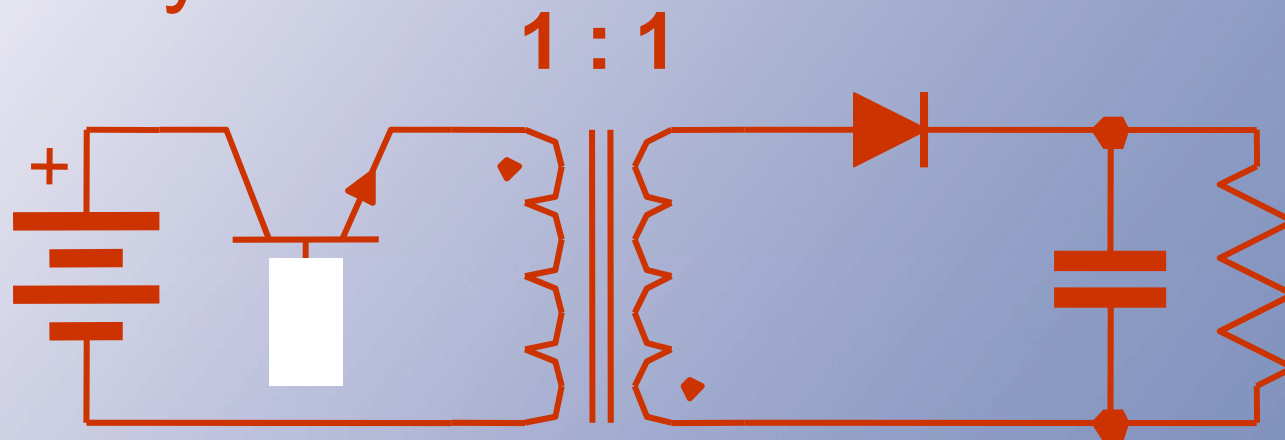


Equivalent Buck-Boost

Devices: MOSFET & Diode

$f_{\text{switch}} \sim 50 \text{ kHz to } 200 \text{ kHz}$

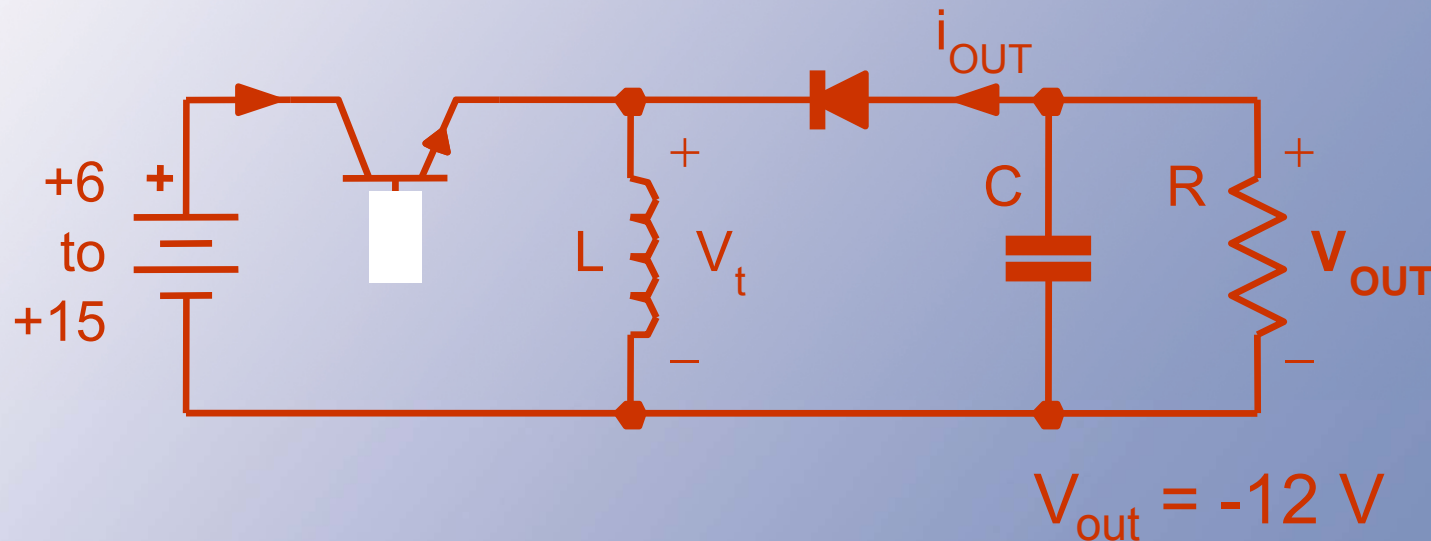24 W, 12 V output. Equivalent buck-boost:





Analysis

- Let $f_{\text{switch}} = 200 \text{ kHz}$. Then $T = 5 \text{ us}$.
- Transfer source: $v_t = q_1 V_{\text{in}} + q_2 V_{\text{out}}$.
- Since $\langle v_t \rangle = 0$, we have $D_1 V_{\text{in}} = D_2 |V_{\text{out}}|$
- Duty ratios: $(D_1/D_2) \times V_{\text{in}} = |V_{\text{out}}|$.





Duty Ratios

- For +6 V in, $D_1/D_2 = 2$, $D_1 = 2/3$, $D_2 = 1/3$.
- For +15 V in, $D_1/D_2 = 12/15$, $D_1 = 4/9$, $D_2 = 5/9$.
- Range: $4/9 < D_1 < 2/3$, $1/3 < D_2 < 5/9$.




Currents

- $I_{\text{out}} = (24 \text{ W})/(12 \text{ V}) = 2 \text{ A}.$
- $q_2 I_L = i_{\text{out}}$
- $D_2 I_L = \langle i_{\text{out}} \rangle = I_{\text{out}} = 2 \text{ A}.$
- $I_L = (2 \text{ A})/D_2$
- I_L range is 3.6 A to 6 A.
- For design, might let $\Delta i_L = \pm 10\%$, or 20% peak to peak.
- Requires $\Delta i_L < (0.2) \times (2 \text{ A})/D_2.$

Inductor Voltage

- $v_L = L di/dt$.
- When the diode is on, $v_L = -12 \text{ V}$, a constant. During that time, then, we have $v_L = L \Delta i/\Delta t$, with $\Delta t = D_2 T$.
- $(12 \text{ V}) (\Delta t)/L = \Delta i < (0.2)(2 \text{ A})/D_2$.
- Simplifies to $L > 30 D_2^2 T$.
- Need an L that works in all cases.

Equivalent Buck-Boost

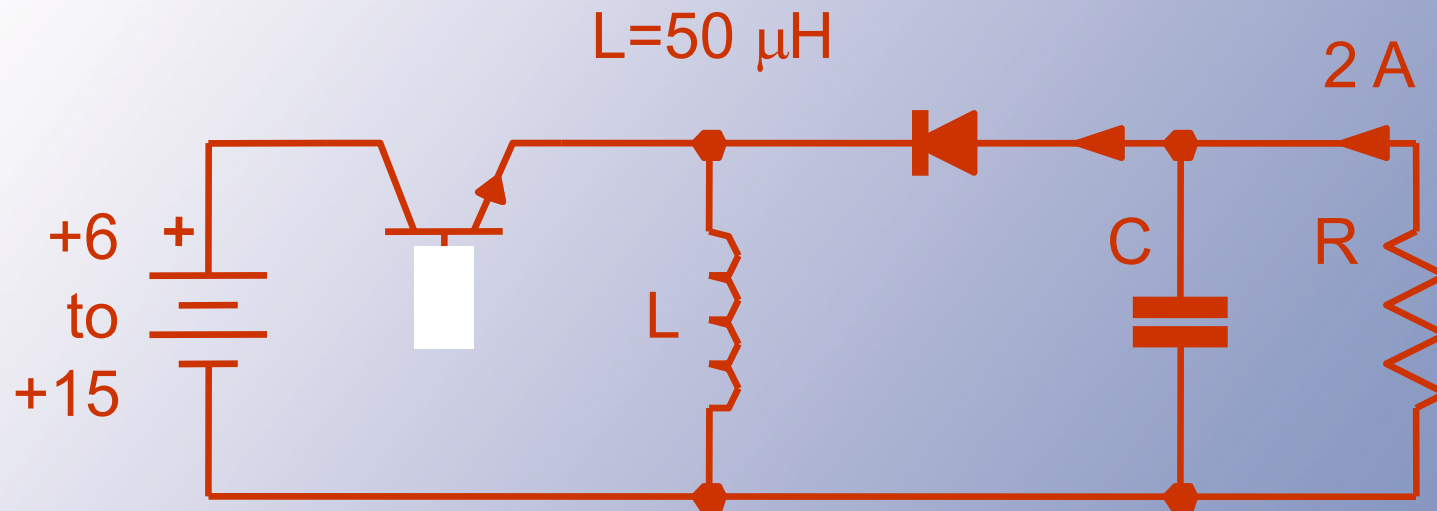

Now, output voltage ripple.

$$\text{Diode off: } i_c = 2A$$

$$\Delta t = D, T$$

$$= C \frac{dv}{dt} \quad \Delta v < (0.02)12$$

$$= C \frac{\Delta v}{\Delta t} < 0.24 \text{ V}$$




Output Voltage Ripple

- We know the capacitor current when the diode is off.
- Can find C .



Final Result

1 : 1

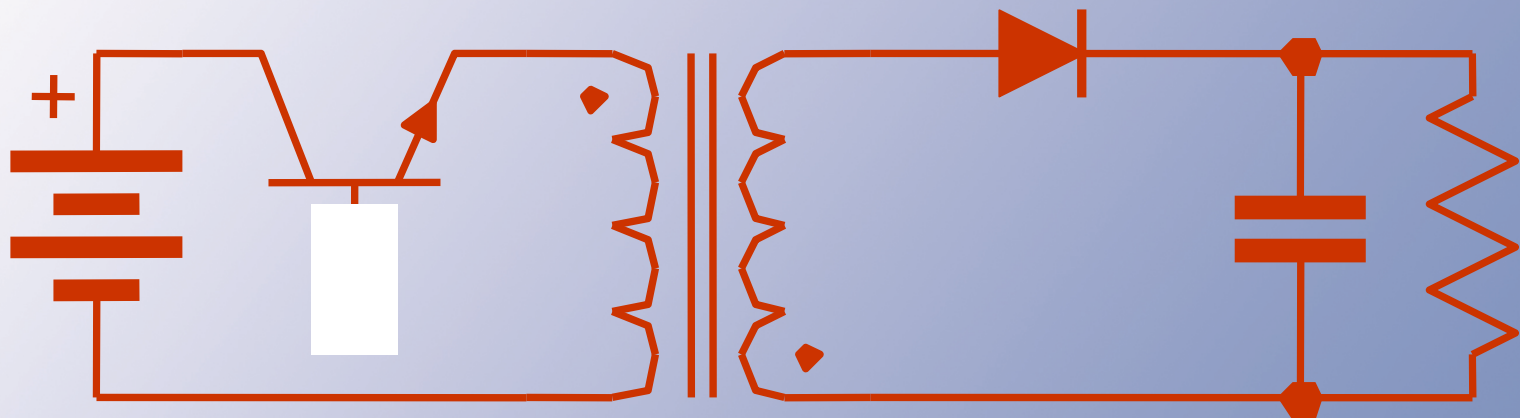

$R \rightarrow 6 \Omega$



$C = 30 \mu\text{F}$

Coupled L:


Either side: = $50 \mu\text{H}$










Same number of turns


Input filter?

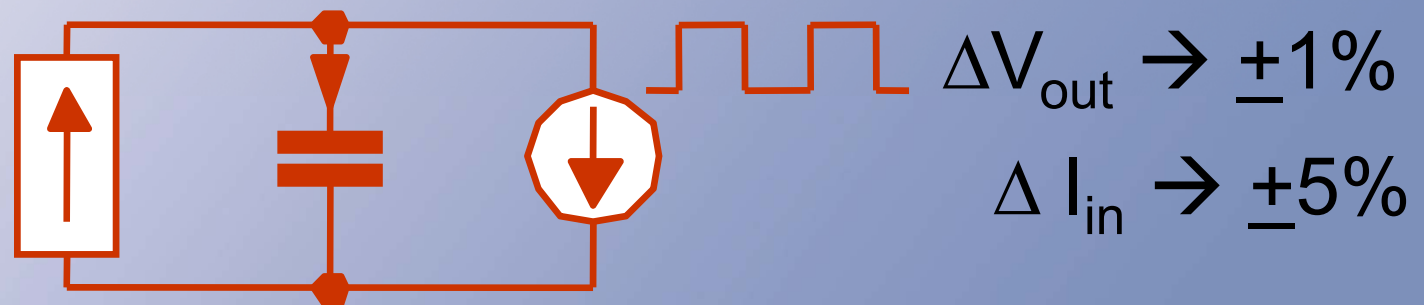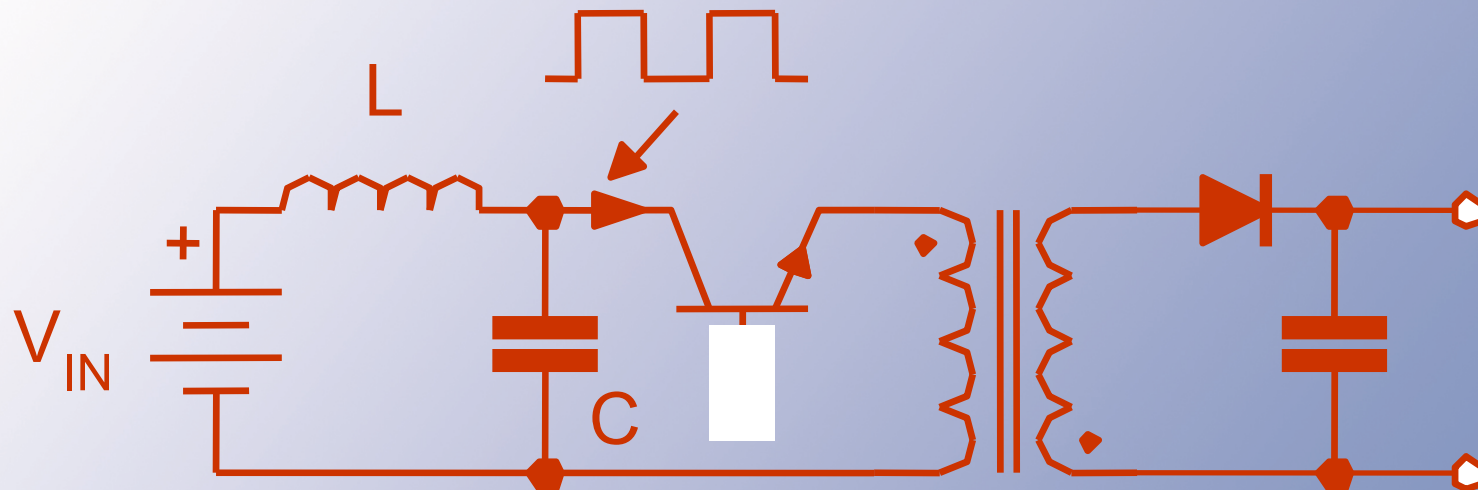

Ideal Action to Find Input

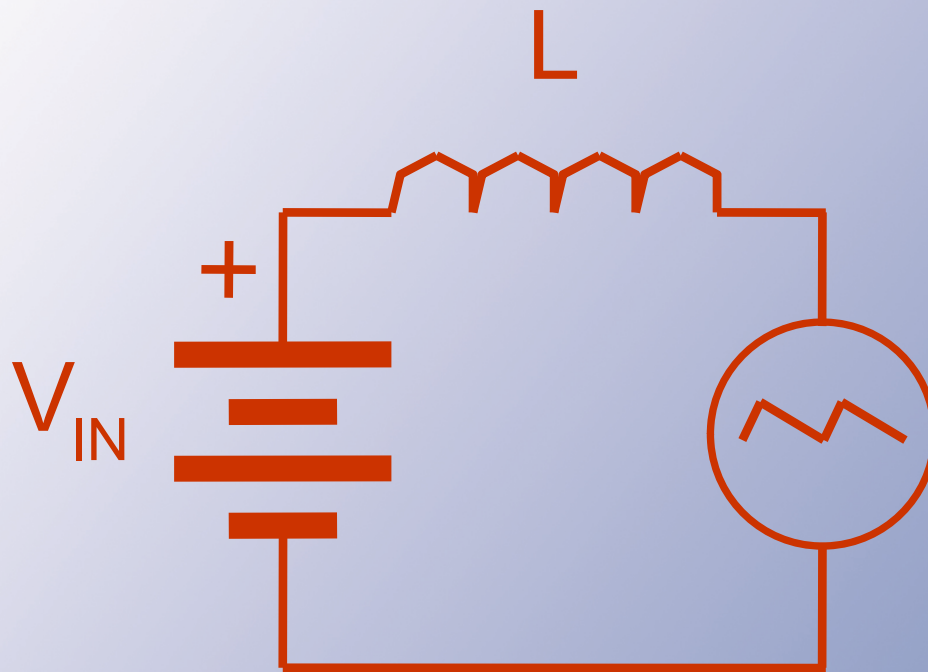

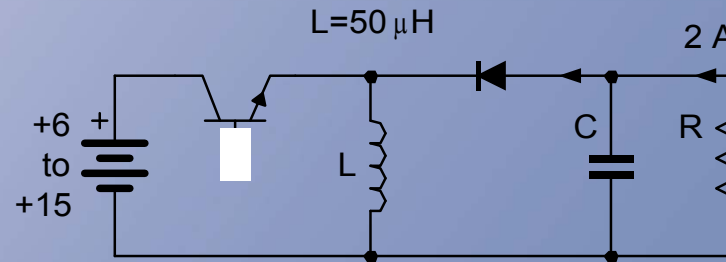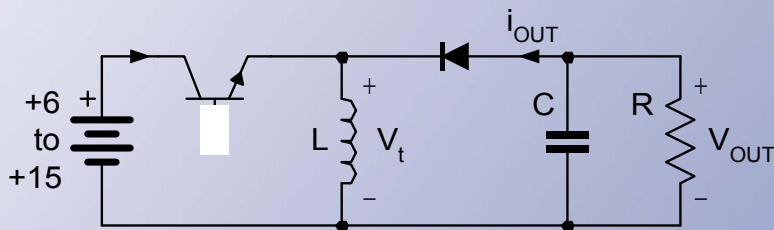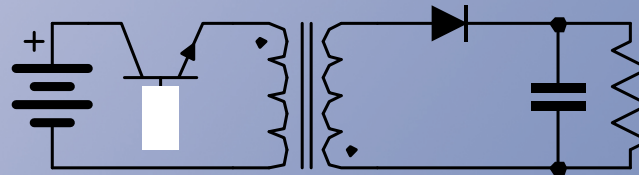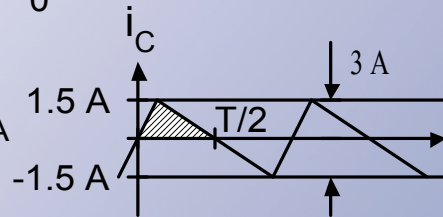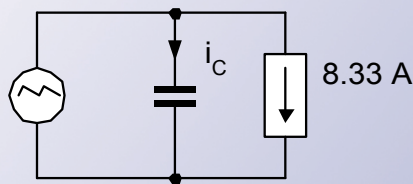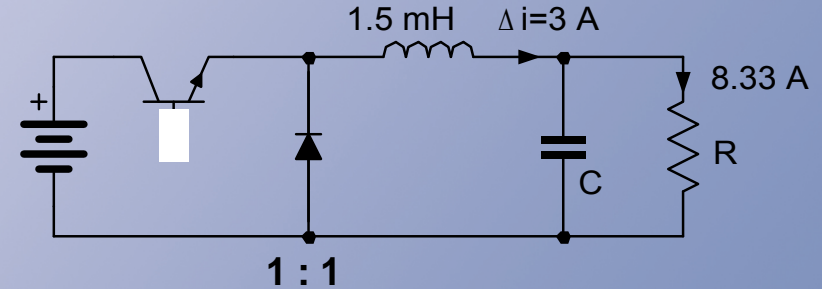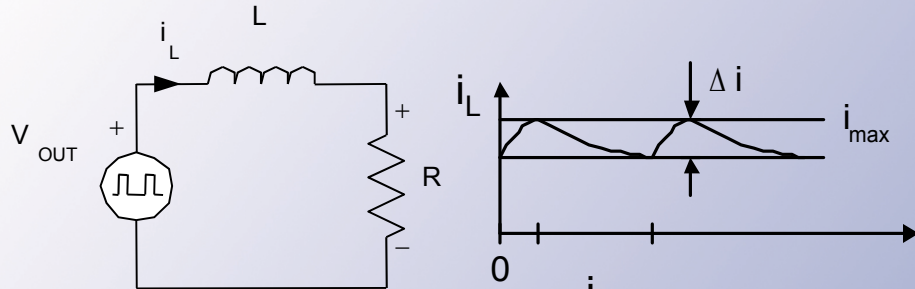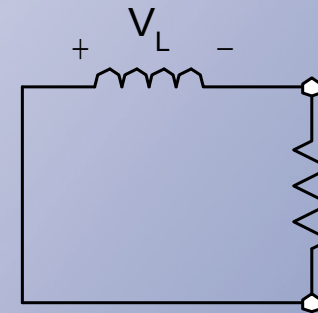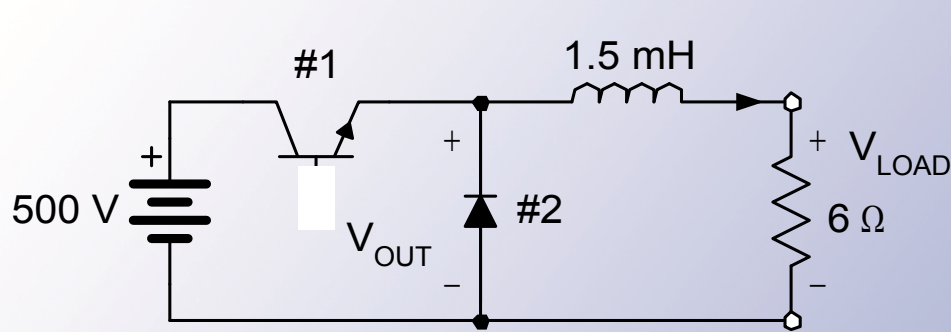

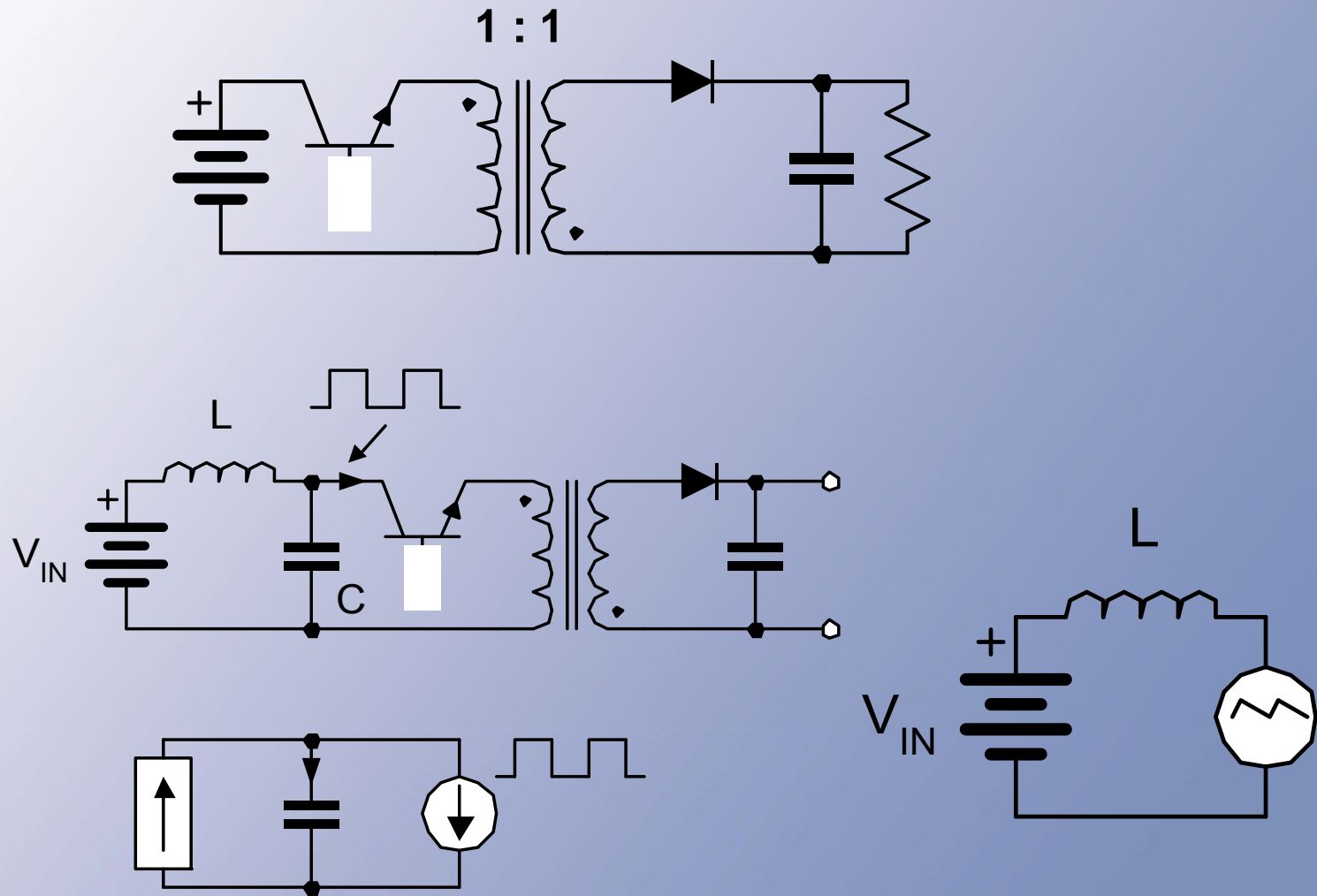



Introduction to Rectifiers

- **Rectifier** is a general term for ac-dc conversion.
- Usually the term implies converters with ac voltage source input.
- In principle, an ac current could also be used.





The Basics

- Consider direct ac voltage to dc current conversion -- a **2 x 2 matrix**.
- The switches should be FCBB (forward conducting, bidirectional blocking).
- SCRs and GTOs are appropriate.
- But we know that diodes can be used, too (but no control is possible!)





DAY 6 Start Frequency Matching

- The input frequency is the same as the ac source.
 - Low frequency mains (50 Hz, 60 Hz)
 - Higher frequencies if an ac link is involved
- The output frequency is 0 Hz.
- If $v_{out} = q v_{in}$, with $v_{in} = V_0 \cos(\omega t)$, the product trig identities for $q v_{in}$ give $\cos[(n\omega_{switch} \pm \omega)t]$.





Frequency Matching

- We want 0 Hz output.
- If switching is performed at the input frequency, the $n=1$ term gives rise to dc and to $2\omega_{in}$ at the output.
- Thus 50 Hz in \rightarrow 50 Hz switching
- This gives both 0 Hz output and 100 Hz ripple, plus harmonics.





Reality Issues

- To provide a current source, we need to keep current nearly constant under a large $2\omega_{in}$ ripple voltage.
- Consider 120 V_{RMS} input (170 V peak) at 60 Hz, with a 12 W load.
- The average current is ~ 0.1 A.





Filter Realities

- With 170 V peak input, if the inductor is large, the output could be $\langle |v_{in}| \rangle$, which is $2V_0/\pi$.
- The output is 108 V dc.
- What if the current ripple does not exceed $\pm 5\%$, or 0.01 A peak-to-peak?



Filter Realities

- To estimate the inductor size, we could formally integrate the voltage waveform.
- Instead, let us get a quick estimate.

What L is needed for a 60 V signal lasting $1/240$ s to give a change of less than 0.01 A?





Filter Realities

- $60V = L \, di/dt \sim L \, \Delta i/\Delta t$, $\Delta t = 1/240 \text{ s}$.
- $\Delta i < 0.01 \text{ A}$ requires $L > 25 \text{ H}$.
- These excessive inductor values are typical for low-power rectifiers.
- Can we dispense with the inductor entirely?






The Classical Rectifier

- The classical rectifier is a diode full-wave or half-wave circuit operating into a capacitive filter.
- This might be expected to have KVL problems, and it does!
- At low power levels, simplicity sometimes outweighs problems.
- Even so, circuit are disappearing in favor of switching converters.



Classical Rectifier

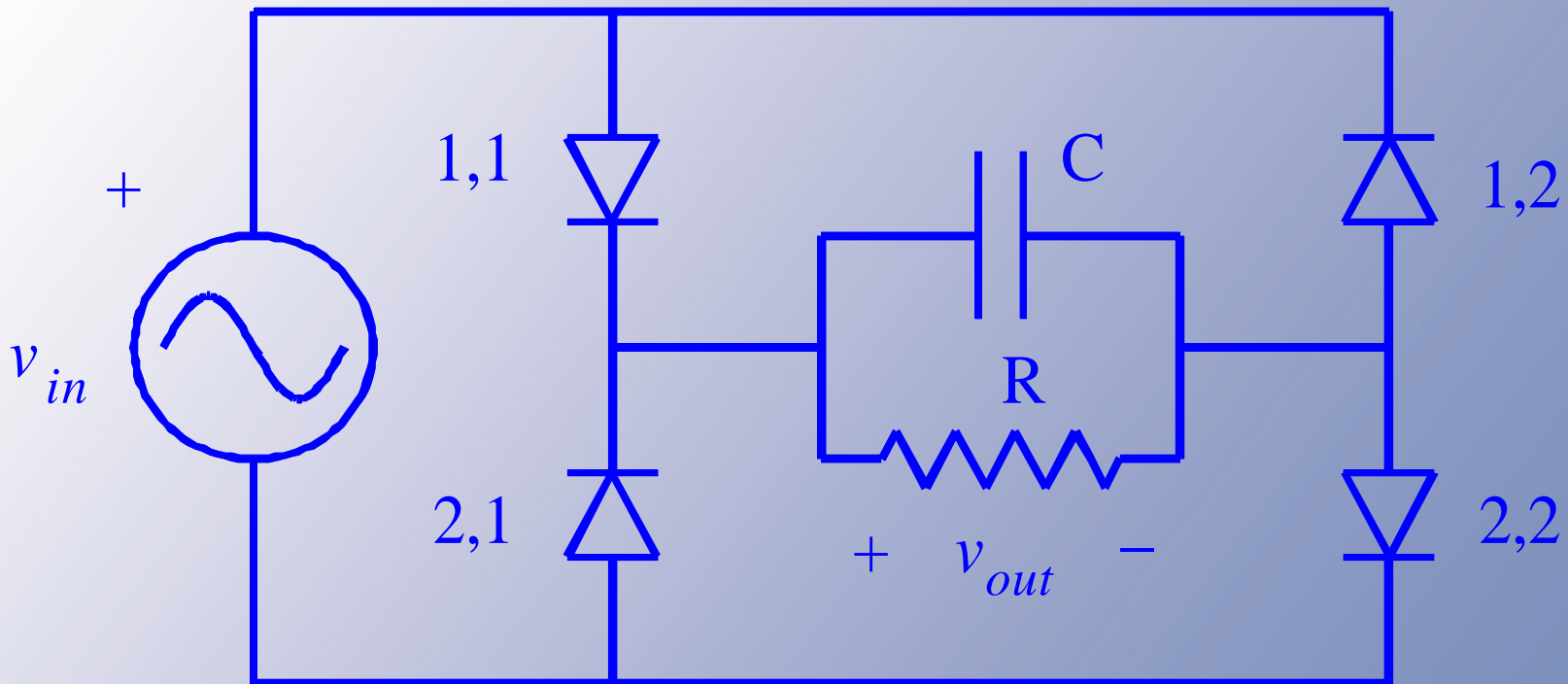

Notice the “voltage to voltage” arrangement.




Trial Method


- Three configurations are allowed :
 - 1,1 and 2,2 on is consistent when the **input current is positive.**
 - 1,2 and 2,1 on is consistent when the **input current is negative.**
 - **All off** is consistent when C keeps the **output about $|V_{in}|$.**




Trial Method

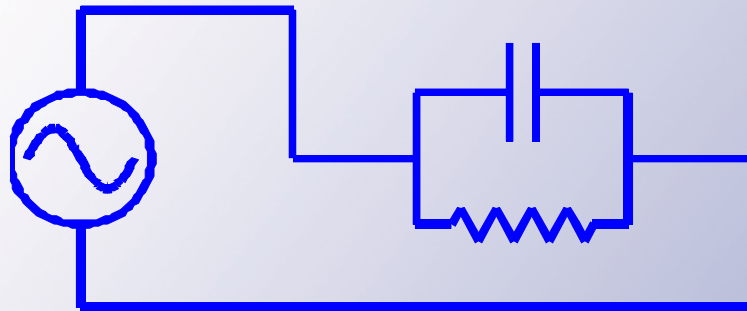

a) 1,1 and 2,2 on, $v_{out} = v_{in}$

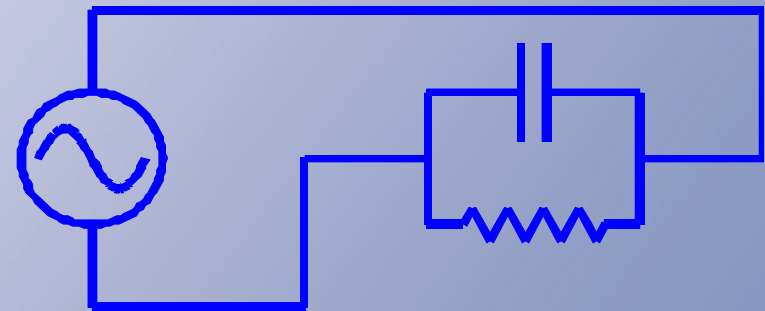

b) 1,2 and 2,1 on, $v_{out} = -v_{in}$

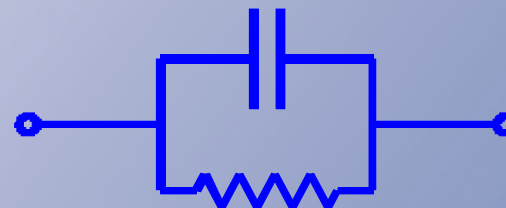

c) All off

In fact, “all off” is active almost all the time!



The Transitions

- Start at the input peak, time $t=0$.
- Let us set 1,1 and 2,2 on (trial method).
- The input current is $V_0/R + C dv/dt$, but $dv/dt = 0$ at $t = 0$.
- Input current > 0 -- consistent.
Off devices have $v < 0$ -- consistent.





The Transitions

- Slightly later, $i_{in} = v_{in}/R + C dv/dt$, and dv/dt is negative.
- After a time, the negative capacitor current plus the positive resistor current add to zero.
- At that moment, all diodes turn off.



The Transitions

- This happens when $-\omega CV_0 \sin(\omega t) + V_0 \cos(\omega t)/R = 0$, or
- $\tan(\omega t) = 1/(\omega RC)$.
- The resistor represents the load.
- Once the diodes are off, the output voltage decays exponentially.




The Exponential

- During the decay, $v_{\text{out}} = V_{\text{max}} e^{-t/\tau}$.
- We can keep the decay small (and the ripple small) with a long time-constant.
- How long? For any x , e^x is
$$e^x = 1 + x + x^2/2! + x^3/3! + \dots$$
- For small x , $e^x \approx 1 + x$. **Linear.**




Analysis

- The decay will continue until the exponential fall hits the rising voltage waveform, $V_{\max} e^{-t/\tau} = |V_0 \cos(\omega t)|$.
- We get a short sinusoidal piece attached to a nearly linear fall.

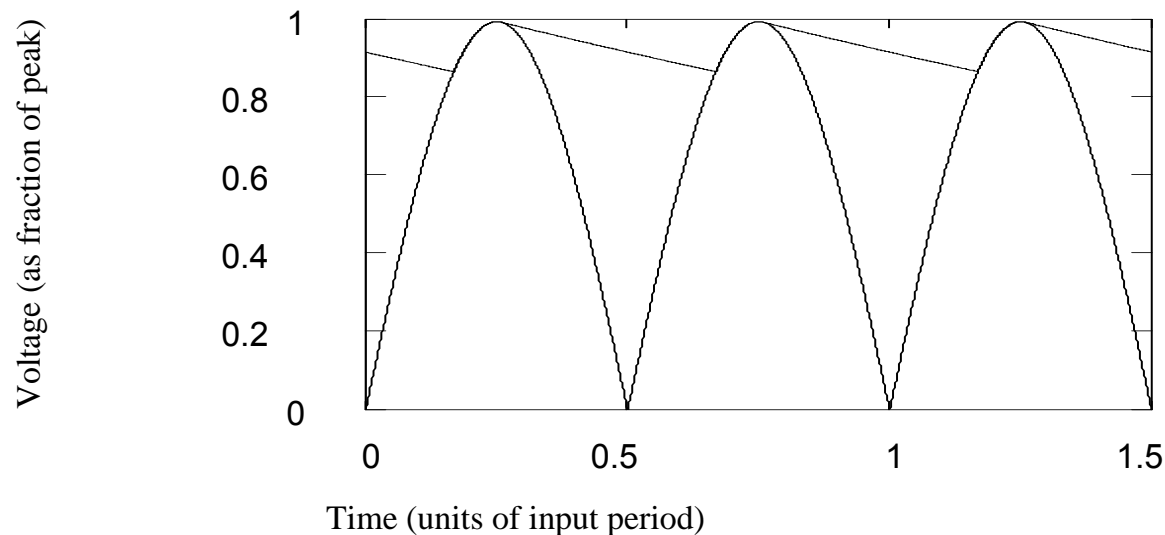

Worst-Case Ripple

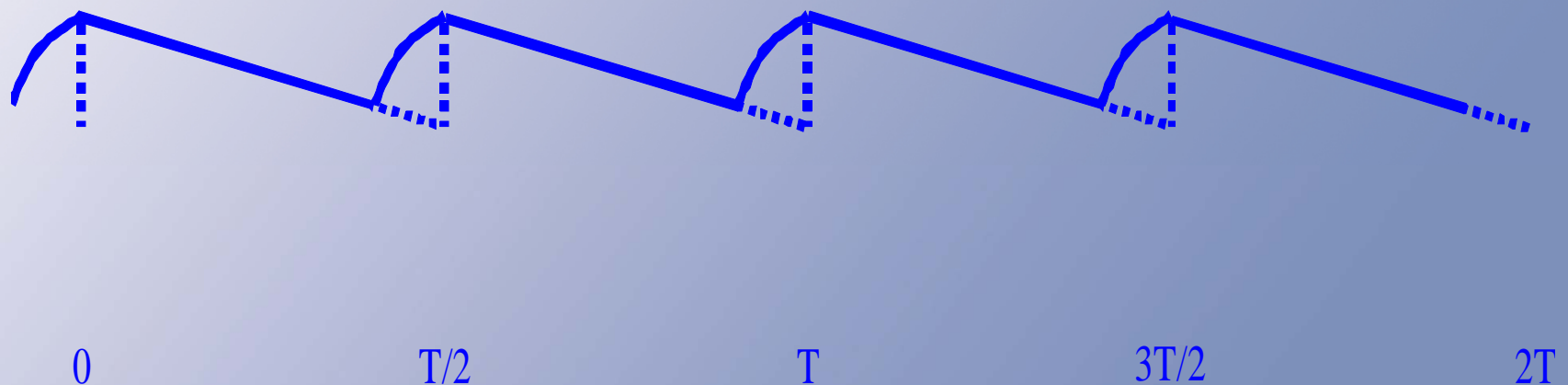- Worst-case ripple is easy to estimate.
- What if the fall is truly linear?
It cannot last longer than the time between voltage peaks.
- The time is $T/2$ in the full-wave case.





Worst-Case Ripple

- The fall is overestimated by the triangle,
 $V_0 e^{-(T/2)/\tau} \approx V_0 (1 - T/(2\tau))$.
- With the RC time constant, the actual fall is approximately $T/(2RC)$, with $T = 1/f_{in}$.
- Thus $\Delta v/V_0 \approx 1/(2f_{in}RC)$.
- Half-wave case has no 2.



Design

- The load current $I_{\text{load}} \approx V_0/R$.
- Therefore, $\Delta v = I_{\text{load}}/(2fC)$.
- Example: 12 V, 1 W supply with 1% ripple.
- $\Delta v = 0.12 \text{ V}$, $I_{\text{load}} = 0.083 \text{ A}$.
- We need $C = 5800 \text{ }\mu\text{F}$.



Design Example

- Example: 230 V rms input, 50 Hz.
- Want 5 V output at 10 W.
- Ripple should not exceed $\pm 0.5\%$.
- First, a peak value of 5 V is needed at the output. The input peak is 325 V, so a 65:1 transformer is needed.
- Second, $\Delta v = I/(2fC)$, and $\Delta v < 0.05$ V.
 - This gives $C > 400000$ μF .



Diode Timing

- If ripple is 1% peak to peak, the voltage falls just 1% before it hits the input ac waveform again.
- The inverse cosine of 0.99 suggests that the diodes are on for about 8° on the angular time scale.
- This is a duty ratio of $8/180 = 4.4\%$.
- Each diode is on less than 5% of a cycle!





Current

- If the diodes are on just 5% of the time, the input current waveform has a 5% duty ratio, too.
- To deliver energy, the input current must flow in brief, high spikes.
- Notice that as $C \rightarrow \infty$, the current must increase without bound.
- This is because we have a KVL problem!





Finding the Current

- The current includes a capacitance part $C dv/dt$ and a resistance part v/R .
- When a diode is on, $v = v_{in} = V_0 \cos(\omega t)$.
- Then $C dv/dt = -\omega C V_0 \sin(\omega t)$.
- This is highest at the moment of diode turn-on, perhaps 8° before the peak.
- Thus 1% ripple gives a peak current of more than $50 C V_0$ at 60 Hz.





Current Points

- The extreme current is almost all delivered to the capacitor.
- Current flows in short, high spikes.
- Ideally, the spikes are inversely proportional to the square root of the ripple spec.
- This means that the spike with 1% ripple is about 40% higher than that for 2% ripple.
- In reality, the current is limited mainly by line and stray transformer leakage inductance.





Current


- The power factor is especially poor.
- For 1% ripple we get ~ 0.26 power factor.
- Classical rectifiers are a major source of “power quality” problems.



Peak Input Current

- Low frequency \rightarrow large C, transformer
- “KVL violation”

Current flows in brief spikes

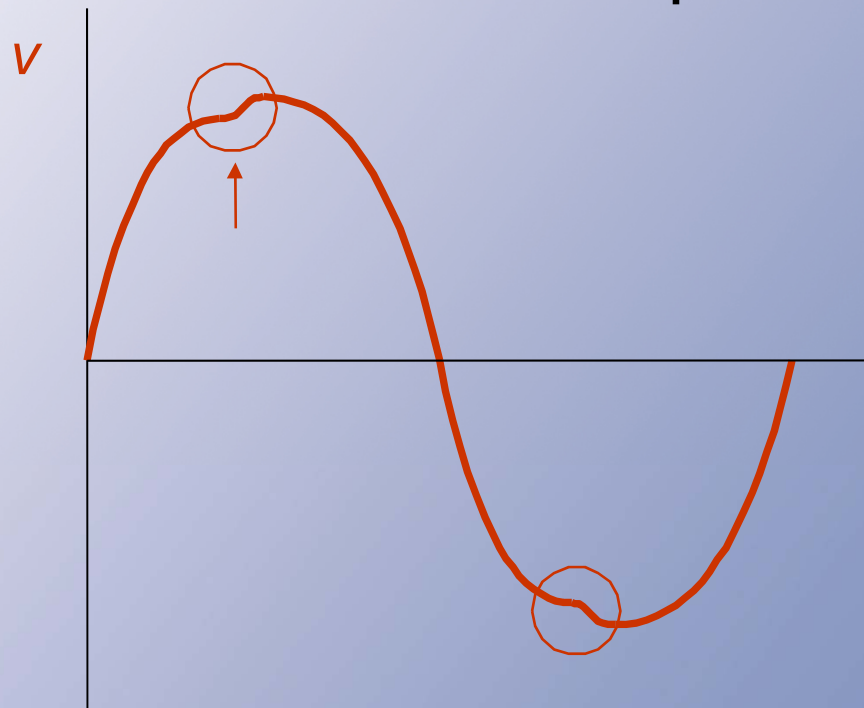



Regulation

- A classical rectifier has no line regulation: the output is proportional to the input voltage.
- The load regulation is half the ripple level (**think about why this is**).





Inductive Filtering

- We would rather use a series inductor to avoid the KVL problem.
- The inductor can be placed at either the input or the output, since the diodes will not turn off until the current $\rightarrow 0$.
- We can use an equivalent source method to estimate ripple when an inductor is present.






Design Example

- Example: 15 V, 0.2 A (3 W) for a computer network node.
- Set ripple of 1% peak-to-peak maximum.
- Compare approximate C with a precise result.



Design Example

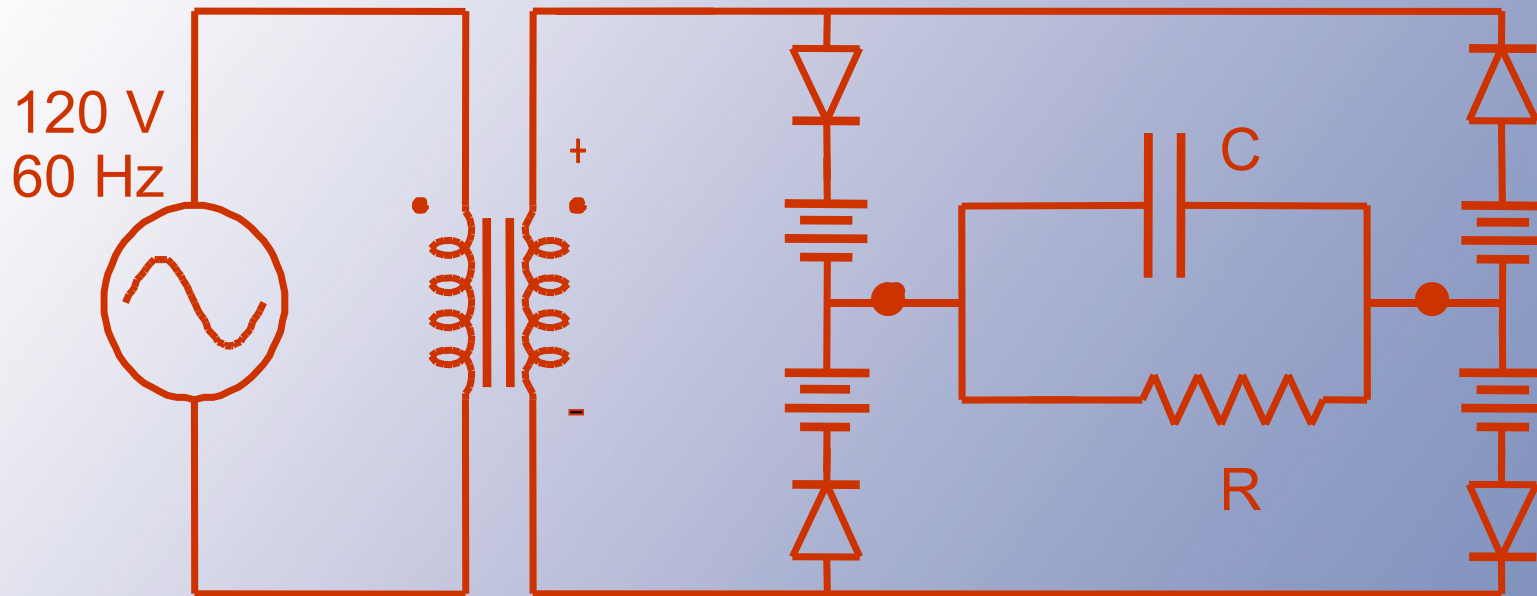

If diodes are on, there is a 2V drop.
 Want 15 V out \rightarrow 17 V peak



Design Example

- There are four diodes in the bridge, with two on at a time.
- We should account for the 1 V diode drops, since they are a large fraction of the output.
- To get 15 V out, we need 17 V peak.





Design Example

- 17 V peak corresponds to $(17 \text{ V})/\sqrt{2} = 12 \text{ V RMS}$.
- For 120 V, 60 Hz input, we should buy a 120 V/12 V transformer.





Design Example

- The capacitor value: We want the voltage change to be no more than 0.15 V with a 0.2 A load.
- $\Delta v_{\text{out}} = I_{\text{out}}/(2fC)$, $f = 60 \text{ Hz}$
- With the change less than 0.15 V, this gives $C > 11111 \text{ uF}$.
- Here $R = 75 \text{ }\Omega$, so $RC = 0.83 \text{ s}$.

Design Example

$$\Delta V_{OUT} = \frac{I_{OUT}}{2fC}$$

$$\Delta V_{OUT} < 0.15V$$

$$C > \frac{I_{OUT}}{2fC}$$

$$C > 11111 \mu F$$



Design Example

$$RC = 0.833 \text{ s}$$

$$\tau/T, T = 1/60 \text{ s}$$

$$\tau/T = 50$$

$$\tau/(T/2) = 100$$



Assumed $V_{\max} = V_{\text{peak}}$

Assumed turn-off \rightarrow peak

Assumed linear decay, lasting $1/20 \text{ s}$




Design Example

“Exact” 10.5 mF

vs. “Approximate” 11.1 mF $\leftarrow \pm 10\%$

12000 μF

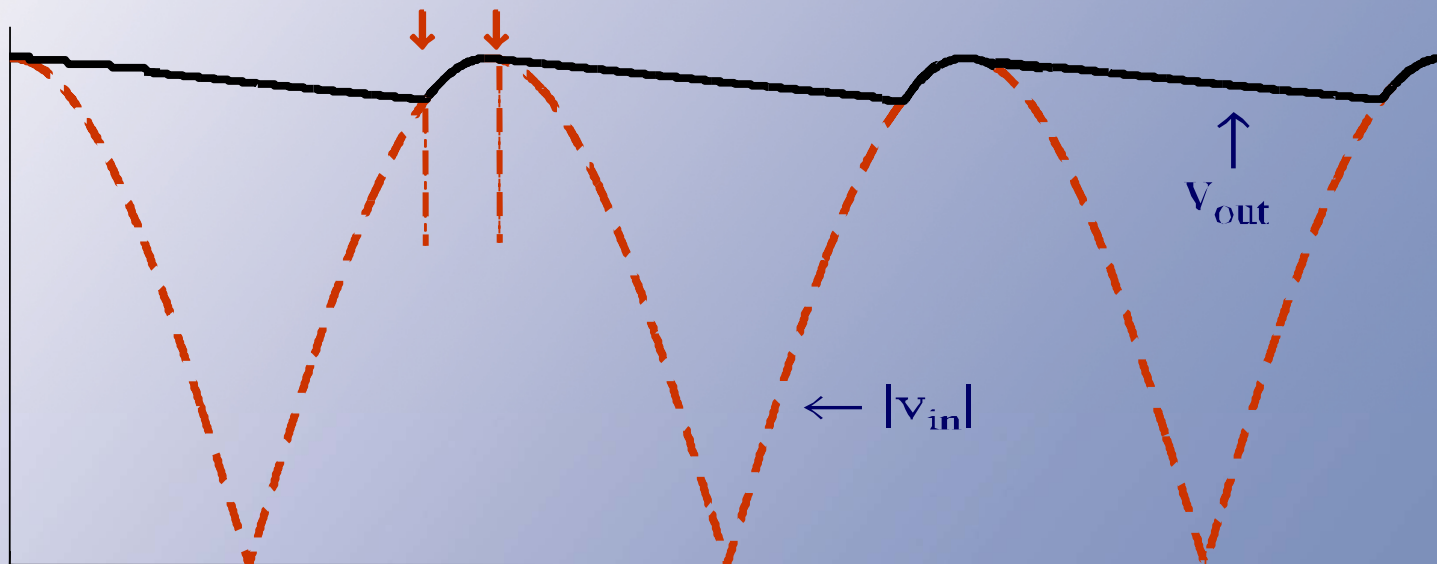



Peak Current

- For the current peak, we need the turn-on point.
- This is where a 15 V sine wave rises to 14.85 V.
- This occurs 8.11° before the peak.



Peak Current

Given:

$$v = 15 \cos (wt)$$

$$t_{on} = -8.11^\circ$$

$$0^\circ$$

$$i_c = -w C (15) \sin (wt)$$

$$i_{cmax} = w C V_o \sin (8.11^\circ)$$

$$i_c = C \, dv/dt$$

Peak Current

- The peak current is
 $\omega CV_0 \sin(8.11^\circ) = 8.9 \text{ A}$ by estimate.
- Actual value is 8.46 A.
- The RMS input is nearly 1 A.
- The transformer rating is 12 VA – for a 3 W load.



Peak Input Current

- Classical rectifiers → Common
- **Advantages:**
 - Simple
 - Easy design
 - Few parts
- **Disadvantages:**
 - No line regulation
 - Harmonics
 - Large, heavy
- Being phased out in favor of small switchers



Peak Input Current

- We are asking the utility to supply a distorted (spike) current.
- Useful work for only a portion of each cycle

$120V_{\text{RMS}} : 5V_{\text{RMS}}$ transformer

$5V_{\text{RMS}} : \rightarrow 200W$

170 A RMS

Input from utility : 170 A /24

Input ~ 7.1 A



Peak Input Current (cont.)

120 V, 15 A outlet

Two of these at most.

400 W → 1700 VA

- This poor power factor gives very poor system utilization.
- If $\text{pf} \rightarrow 1$, we could support nine units on a circuit instead of two.






Basic Target

- When a very large inductor is used, the output will look like a dc current source.
- If this is true, each diode will carry I_{out} when on.
- Each diode will have 50% duty.



Diode currents

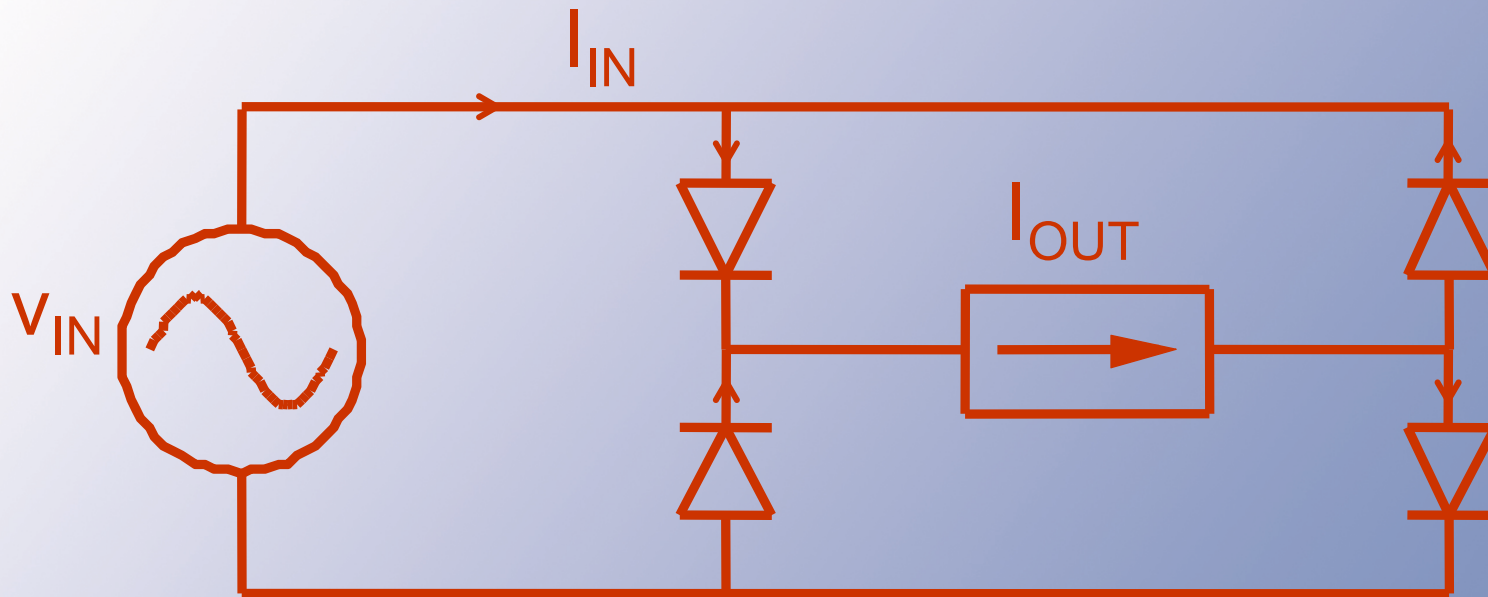

$$I_{IN} = \begin{cases} +I_{OUT} \\ -I_{OUT} \end{cases}$$

Diode currents: I_{OUT} , $D=50\%$




Output Voltage

- In the classical rectifier, the **output is close to V_{peak} -- IF the capacitor is large.**
- The voltage is more nearly the peak if the load is lighter.
- Good load regulation, up to a limit on the load.



Output Voltage

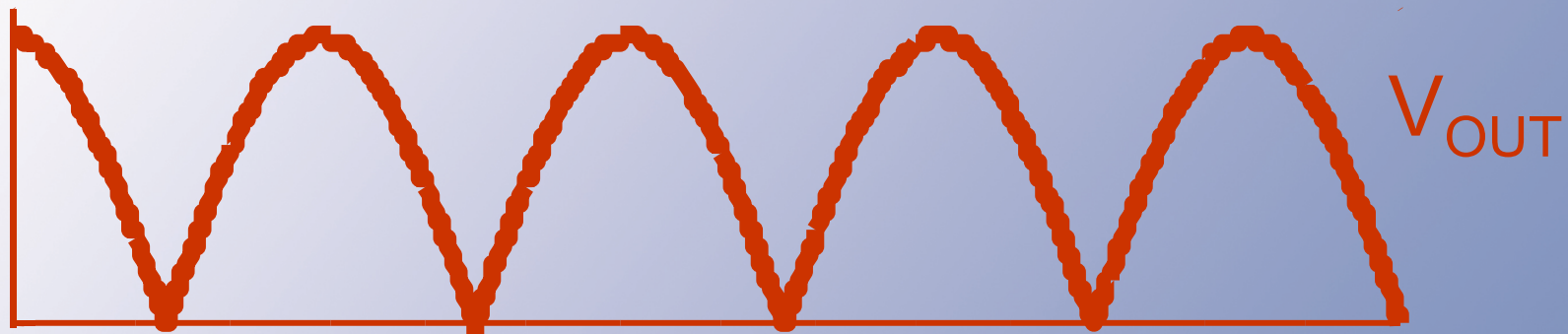

$$V_{OUT} = |V_{IN}|$$

Classical case: $V_{OUT} \approx V_{IN_{peak}}$

Output Voltage Classical case, large C



Up to a load limit, then


$\langle V_{OUT} \rangle \approx V_{peak}$; little change.

→ Good load regulation,
(not perfect) depends on C.

Output Voltage

- With large L , the output voltage from the diode bridge is a full-wave sinusoid.
- The load sees the average of this waveform, $\langle |V_0 \cos(\theta)| \rangle$.
- **Compute this. The result is $2V_0/\pi$, less any diode drops.**

Output Voltage Large L

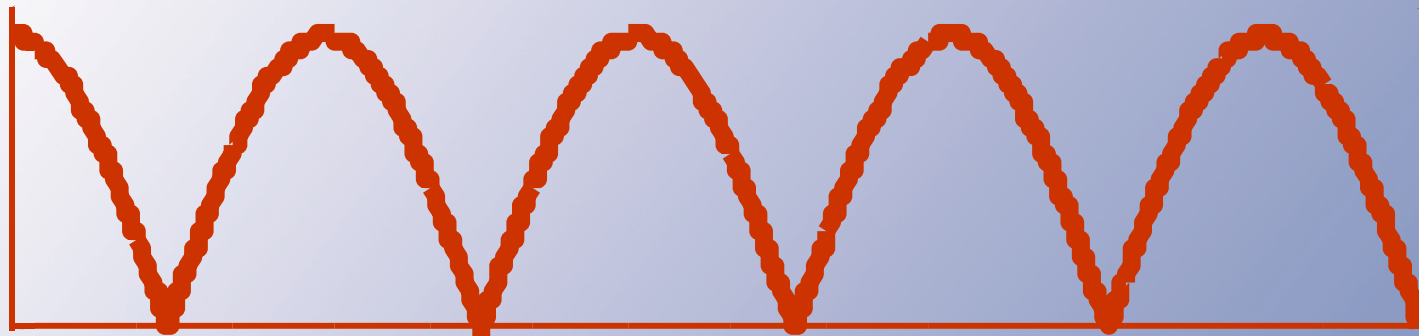

Waveform does not change,
provided L is big enough.

Load regulation – perfect.
No line regulation.




Output Voltage

- This output is independent of load as long as L is large enough.
- **We are still at the mercy of line variation.**




Output Voltage

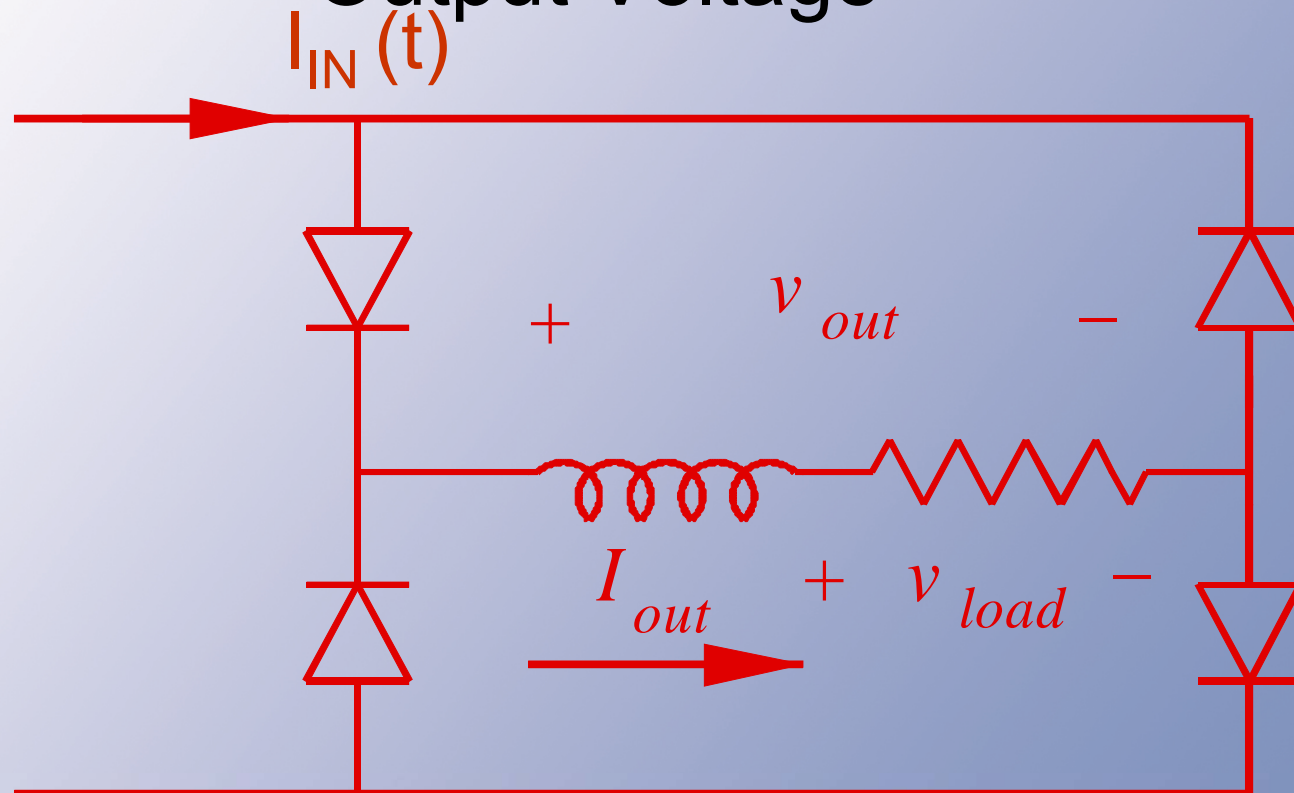


$$\begin{aligned} \langle V_{OUT} \rangle &= \langle |V_{IN}| \rangle \\ &= \langle |V_0 \cos(\omega t)| \rangle \end{aligned}$$

Output Voltage

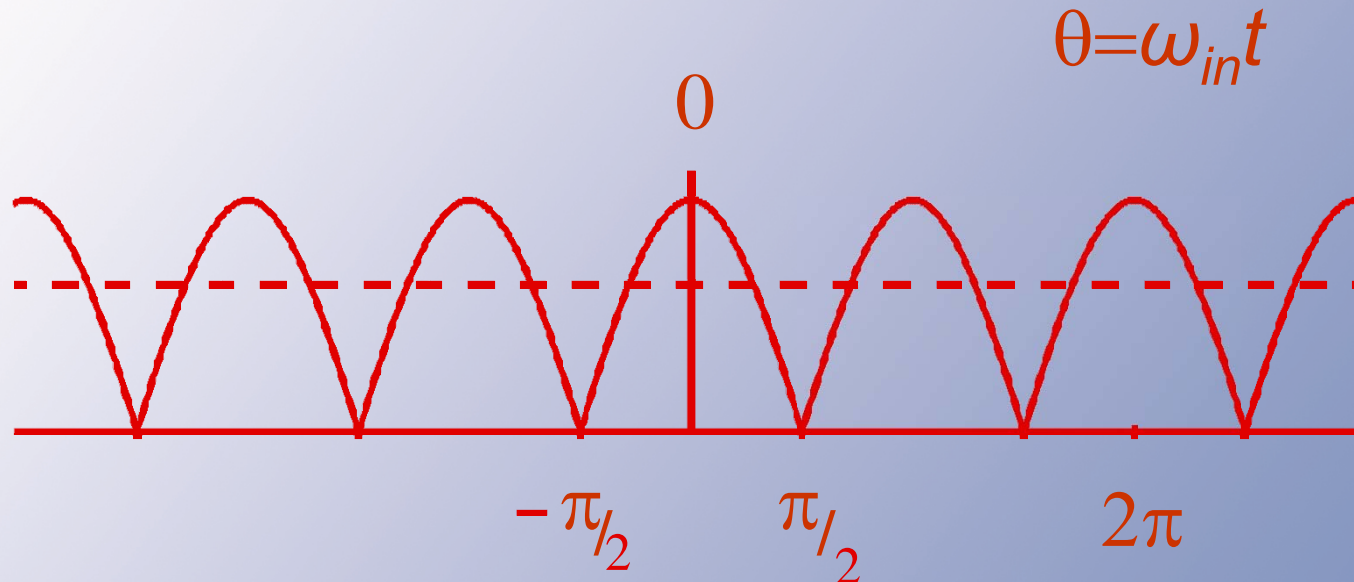

$$\begin{aligned}\langle |V_{IN}| \rangle &= \frac{1}{\pi} \int_{-\pi/2}^{\pi/2} V_0 \cos \theta d\theta \\ &= \frac{2V_0}{\pi} \text{ Lower than classical case}\end{aligned}$$

Output Voltage

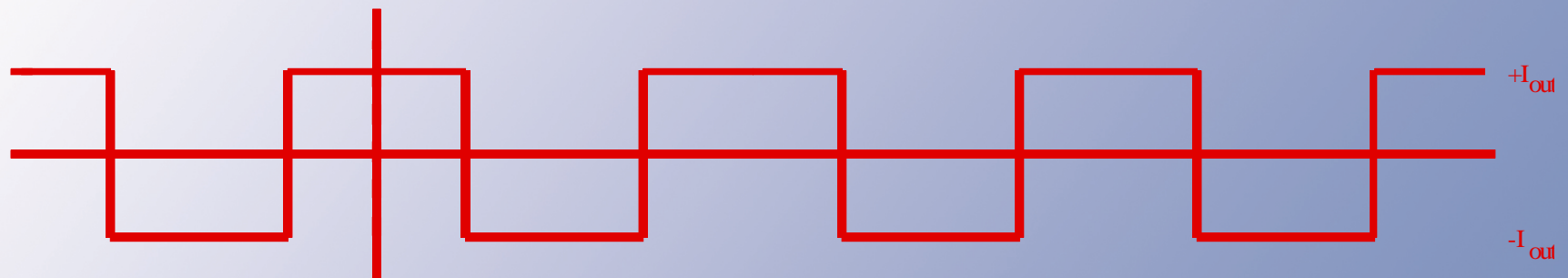

- With large L , input current is a square wave rather than short spikes.
- Much better power factor and lower current distortion.



Input Current

- The diodes ensure that the input current is either $+I_{\text{out}}$ or $-I_{\text{out}}$.
- The input current must be a square wave with peak value I_{out} and duty ratio of 50%.
- This is much less distorted than in the classical case.





Power Factor

- We can compute a power factor. The average power is $V_{\text{out}} I_{\text{out}} = (2V_0/\pi)(I_{\text{out}})$.
- The input RMS current is just I_{out} .
- The input apparent power $S = V_{\text{RMS}} I_{\text{RMS}}$ is $(V_0/\sqrt{2})(I_{\text{out}})$.
- $\text{pf} = P/S = (2/\pi)\sqrt{2} = 0.900$





Comments

- It is interesting that for large L the power factor does not depend on load, ripple, or anything else.
- A power factor of 90% is far better than for a classical case, but at low power levels L can be excessive.






Choosing L

- We can choose L by using the fundamental Fourier component for a ripple estimate.
- For a full-wave voltage, $c_1 = 4V_0/3\pi$ (see p. 175). The frequency is twice that of the input.



Inductor Value

Equivalent source approach with Fourier.

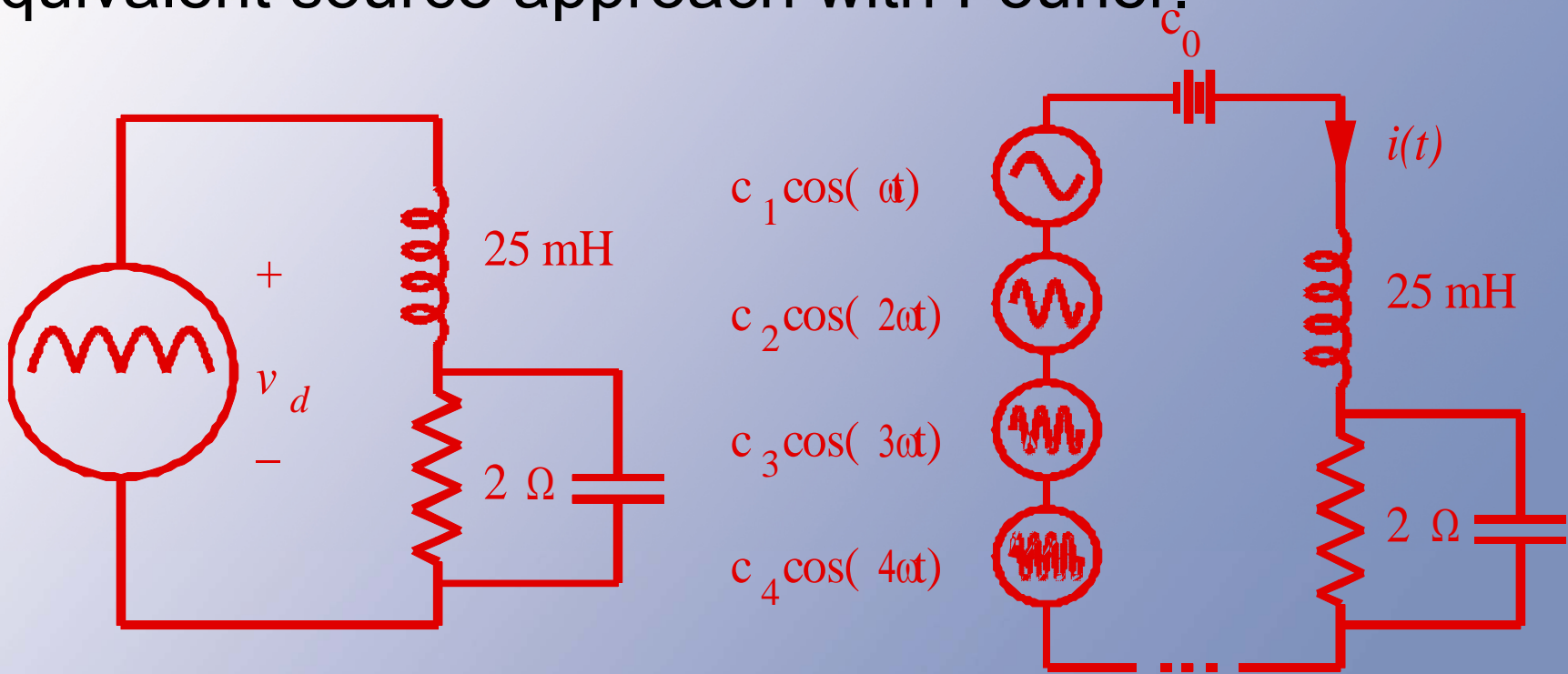



Inductor Value

- Focus on the first harmonic as a basis for estimation.
- We have a divider, $R \parallel C$ in series with L .
- The impedances are those at the main ripple frequency.
- Find the resistor current to estimate output ripple.
- Please see p. 176 for the details.



Choosing L

- This is a voltage and current divider.
- The ripple current in the resistor is given by

$$\frac{2\sqrt{2}V_0}{3\pi(R + j\omega L - \omega^2 RLC)}$$



Choosing L

- With this relation, a poor choice of L could actually increase the ripple.
- Good results require that the resonant frequency $1/\sqrt{LC}$ is much less than the ripple frequency.





Choosing L

- When both L and C are present, it is possible to get good results without excessive values of either.
- Even if L is not large, it will improve power factor and the input current waveform.

