



Power Electronics Day 8 -- Components

P. T. Krein

Department of Electrical and Computer Engineering
University of Illinois at Urbana-Champaign



Quasi-Steady Loads

- Examples are any load that does not change much during a switching period.
 - Motors
 - Loudspeakers
 - Batteries to be charged
 - Almost any load that includes a filtering effect





Quasi-Steady Loads

- We often make loads quasi-steady by adding series inductance or parallel capacitance so they will not change rapidly.
- From the converter, such loads act – on short time scales – like ideal sources.





Transient Loads

- Some loads change so fast that switch action does not do much.
- Good example: large microprocessor.
 - A processor with a 1000 MHz clock can change its current needs every 1 ns.
 - A lot of change can occur in between switching actions inside the power converter.





Transient Loads

- Transient loads must be addressed through energy storage, since switch action is not sufficient to provide the correct voltage or current.
- The energy storage needs become part of the power converter design.





Transient Loads

- Example: A certain microprocessor can be modelled as a capacitance (inside the CMOS chip) switching into the input voltage at 1000 MHz.
- Consider a 10000 pF capacitor switching into a 1 V source at this rate.
- Each time we switch, charge $CV = 10000$ pC must be delivered. At this rate, this is 10 A of current (or 10 W).





Transient Load Example

- With a 5 V to 1 V converter, the diode carries the load current most of the time.
- The concept: provide enough output capacitance that the load effect will make little difference.
- For example, a 10 μF capacitor should be able to charge 0.01 μF about 100 times before the voltage falls 10%.



Transient Loads

- This gives us 100 ns rather than 1 ns until the next switching is needed.
- This is still a power converter running at about 10 MHz.
- The reality is that even more capacitance is needed.





Source and Load Limitations

- For *any* real source or load, connection wiring is required.
- Connections always introduce resistance, but also inductance.
 - The inductance arises because any current generates a magnetic field.
 - The interaction between the field and the circuit is modelled as inductance.





Current Sources

- Fundamentally, this means **all sources and loads ultimately act like current sources**, at least at short enough time scales.
- We originally claimed that voltage and current sources are about equally common, but the reality is that everything is a current source (on a fast scale).





Current Sources

- At a fast enough time scale, the inductance will always be greater than the critical value.
- We will need to get an idea of wire inductance effects and evaluate their impact on switching.





Wire Inductance

- A wire has self-inductance, since the current in it generates a magnetic field that interacts with the return conductor.
- The field also interacts with part of the current inside the wire.





Wire Inductance

- There is internal inductance owing to the field inside the wire.
- External inductance is the interaction between field outside the wire and the current.
- Both are self-inductance, rather than mutual inductance.





Wire Inductance

- The self-inductance of a long wire is a classic electromagnetics problem.
- L (in henries) per unit length is $\mu_{\text{wire}}/(8\pi) + \mu/(2\pi) \ln D/R$.
- D is the center-to-center distance between the wire and the return conductor. R is wire radius.
- The value μ is the permeability.





Wire Inductance

- The first term, $\mu_{\text{wire}}/(8\pi)$, is the *internal self-inductance*.
- For aluminum, copper, silver, gold, $\mu_{\text{wire}} = \mu_0 = 4\pi \times 10^{-7} \text{ H/m}$.
- For steel or nickel, it is much higher.
- For μ_0 , the term is 50 nH/m.





External Inductance

- The external term $\mu/(2\pi) \ln D/R$ depends on μ of the insulating material. This is usually μ_0 .
- The spacing is not a very sensitive function.
- For $D/R = 10$, the value is about 460 nH/m.
- Add the internal effect, yields about 500 nH/m





Self-Inductance

- For copper wire and air, plastic, or varnish insulation, we have:

D/R	L	
100	950 nH/m	
10	500 nH/m	typical
3	250 nH/m	minimum

- For wire, 2 nH/cm is a lower bound.





Wire Inductance

- But, **we need two wires** (the second for return).
- Inductance is minimized when the wires are close together.
- Why? This tends to cancel external magnetic fields.



Wire Inductance

- For a wire pair, **10 nH/cm is a typical value.**
- 4 nH/cm is a dead minimum for a very tightly twisted pair.
- How to reduce these?
 - The ultimate twisted pair: Litz wire.
 - Bus bar.





Implications

- Think about a converter -- built with wires.
- Example: Buck converter with 10 cm of wire between source and switches.
- This gives about 100 nH total – 50 nH in each leg.



Switching Effects

- KCL problem! If we switch current instantly, the inductance generates infinite voltage.
- The saving factor is that switches take time to operate.
- What if 10 A is switched in 40 ns?





Switching Effects

- Then $v_L = L \, di/dt \approx 100 \text{ nH}(10\text{A})/(40 \text{ ns})$.
- The inductor voltage is 25 V.
- Now think about 100 cm of wire and 50 A of current -- 1250 V!





Effects

- Effects include
 - Time delay from source to input
 - The switches see a much higher than expected voltage.
 - Ground reference node – where should it be?
Ground bounce.
 - Voltage tolerance. The extra inductor voltage introduces ripple and error.
 - Extra losses and KCL problems.





Example

- Example: A boost converter delivers its square wave to a capacitive load through 2 cm of wire.
- The square wave is 20 A in amplitude, and the switching requires just 50 ns with a switching frequency of 250 kHz.
- If we estimate based on $v_L = L di/dt$, we get $v_L \approx (20 \text{ nH})(20 \text{ A})/(50 \text{ ns}) = 8 \text{ V}$.



Example

- Large impact of inductance on ripple waveforms.
- Real systems also show ringing and resonant behavior as well.





Critical L and C

- We know that $L > L_{\text{crit}}$ assures both $i_L > 0$ and $\Delta i < \pm 100\%$.
- Similarly for C.
- In general, the ratio L/L_{crit} serves as a measure of quality.
- If $L = L_{\text{crit}}$, we have a current source, but it is not ideal.
- $L \gg L_{\text{crit}}$ defines an ideal current source.



Critical L and C

- Since critical L and C are usually easy to compute, we can determine how much L or C to provide to make a source or load “ideal.”
- This is another approach to the “interface problem:” add passive storage elements to make a real source or load more nearly ideal.





Dc Source Interfaces

- To form a dc current source, simply add a series inductance (well) above the critical value.
- To form a dc voltage source, add parallel capacitance (well) above the critical value.



Example: Battery Source

- A battery has series L and R.
- Even ignoring the L, the resistance carries current part of the time: $P_{\text{loss}} = D I_L^2 R_s$.
- With an interface capacitor, the battery sees current ($D I_L$) instead.
- The loss is $(D I_L)^2 R_s$, which is lower by a factor of D.






Interface Example

- A battery with internal resistance of 0.1Ω supplies a buck-boost converter.
- The load is 200 W , and the nominal conversion is $+12 \text{ V}$ to -12 V .
- 50 kHz switching; $L \gg L_{\text{crit}}$.

Interface Example

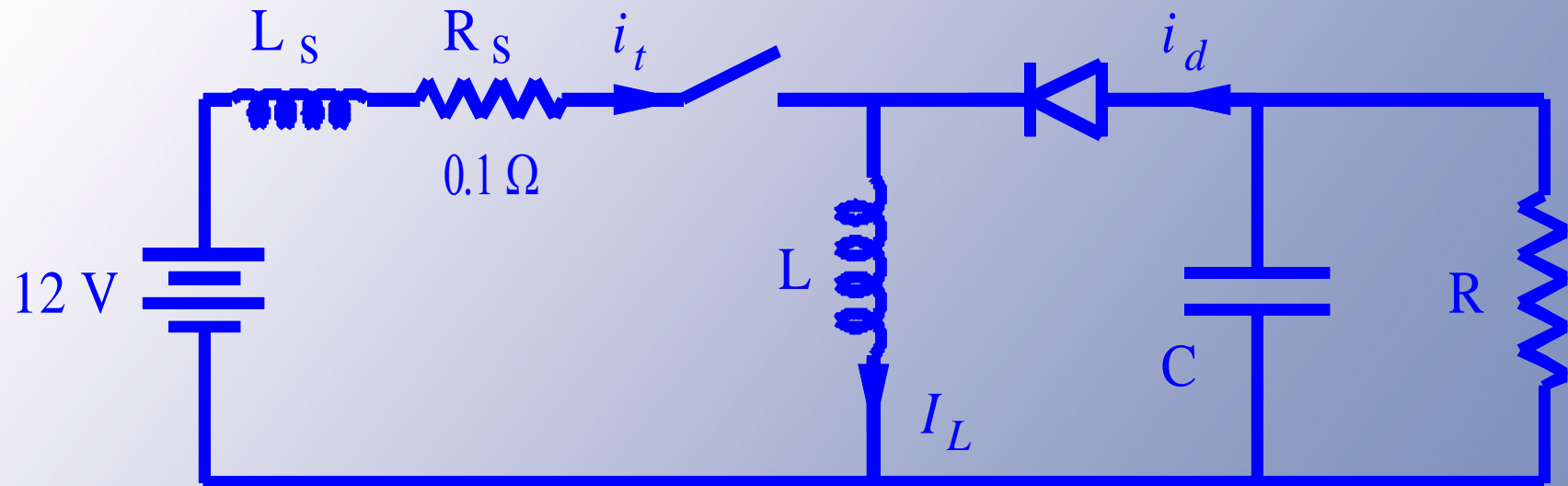

- Let $L \gg L_{\text{crit}}$, $C \gg C_{\text{crit}}$, $f_{\text{switch}} = 50 \text{ kHz}$.
- Ignore L_s for now.
- Voltage drop: $i_t R_s = q_1 I_L R_s$



Analysis

- The load current is $(200\text{W})/(12\text{V}) = 16.7 \text{ A}$.
- Notice that the transfer voltage is $v_t = q_1(V_{\text{bat}} - I_L \times 0.1 \Omega) + q_2(V_{\text{out}})$.
- The diode current is $i_d = q_2 I_L$.
- Averages: $I_{\text{load}} = D_2 I_L = 16.7 \text{ A}$;
 $\langle v_t \rangle = D_1(V_{\text{bat}} - 0.1 I_L) + D_2 V_{\text{out}} = 0$;
 $D_1 + D_2 = 1$.


Analysis

- This gives three equations in the unknowns D_1 , D_2 , and I_L .
- Combine to give:
$$12D_1 - 16.7(0.1)D_1/(1 - D_1) - 12(1-D_1) = 0.$$
- Two solutions: $D_1 = 0.607$ (the correct one),
 $D_1 = 0.823$ (a high-loss answer).

Loss Values

- With this result, $I_L = 42.4 \text{ A}$.
- The loss with no interface is $I_L^2(0.1 \ \Omega)$ while switch #1 is on.
- The average power loss is $D_1(42.4 \text{ A})^2(0.1 \ \Omega) = 109 \text{ W}$.
- Efficiency is 64.7%.

Loss Values

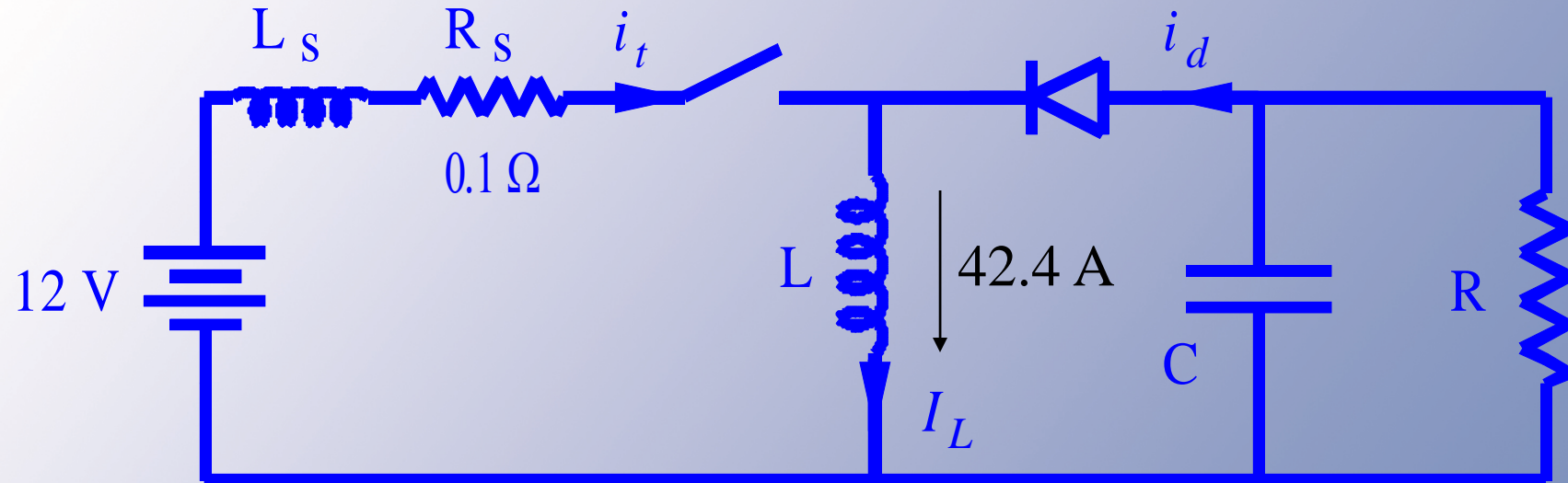


- $P_{\text{loss}} = D_1 (42.4^2 R_s) = 109 \text{ W}$
- $P_{\text{in}} = 309 \text{ W}, \eta = 64.7\%$.



Now, an Interface

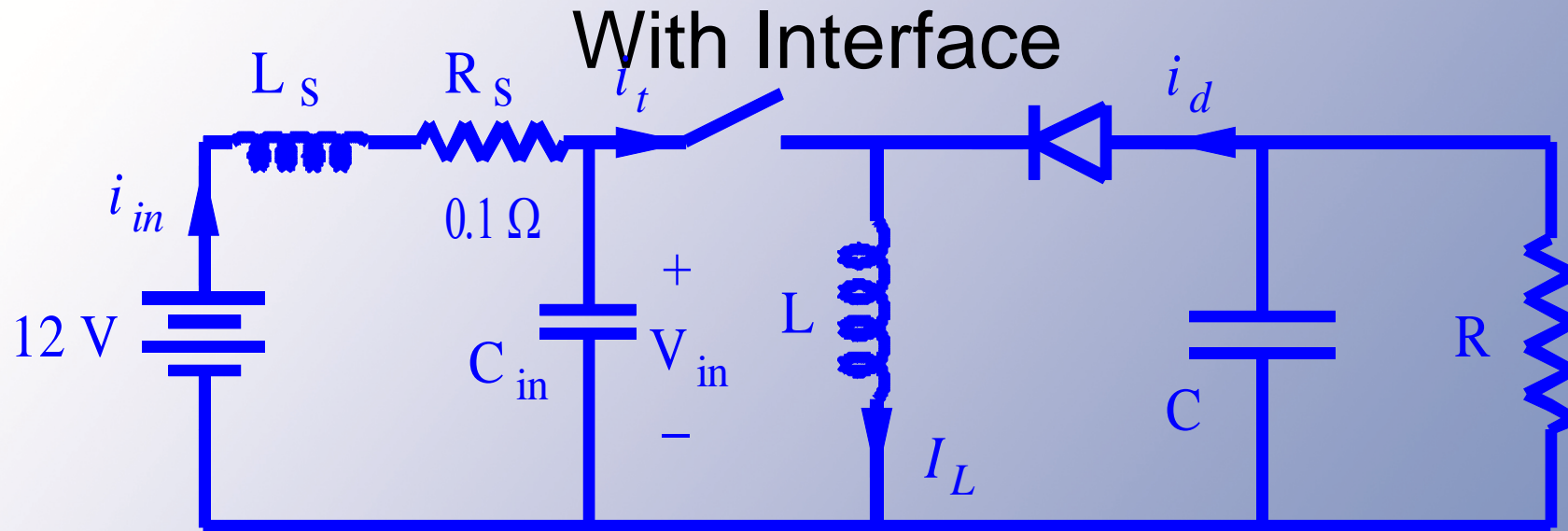- Instead, let us provide a large capacitor at the battery terminals.
- Now the battery is exposed to the average input current instead of the inductor current.
- The transfer voltage is
$$v_t = q_1(V_{\text{bat}} - I_{\text{in}} \times 0.1 \Omega) + q_2(V_{\text{out}}).$$



- C_{in} is the source interface.
- Now $i_t = q_1 I_L$, but $I_{in} = \langle i_{in} \rangle = \langle i_t \rangle = D_1 I_L$.
- $V_{in} = V_{bat} - I_{in} R_s = V_{bat} - D_1 I_L R_s$.



With Interface

- $v_t = q_1(V_{\text{bat}} - D_1 I_L R_s) + q_2(V_{\text{out}})$.
- $\langle v_t \rangle = 0 = D_1 (V_{\text{bat}} - D_1 I_L R_s) + D_2 V_{\text{out}}$
- Also, $i_d = q_2 I_L$, and $\langle i_d \rangle = I_{\text{load}} = 16.7 \text{ A}$.
- Then $0 = D_1 (V_{\text{bat}} - D_1/D_2 I_{\text{load}} R_s) + D_2 V_{\text{out}}$





With Interface

- Is this really any different? Now, $12D_1 - 16.7(0.1)D_1^2/(1 - D_1) - 12(1-D_1) = 0$.
- The solutions are $D_1 = 6/11$ (or 0.545) and $D_1 = 6/7$ (or 0.857). The first is correct, since the second involves high loss.
- $I_L = (16.7 \text{ A})/D_2 = 36.7 \text{ A}$, and $I_{in} = 20 \text{ A}$.





Current and Loss

- The loss is $I_{in}^2 R = 40 \text{ W}$.
 - The efficiency is 83.3%.
 - We cut out almost 70 W of loss just by adding an interface.
 - **The loss dropped by 64%**, just by adding one part!
- Source interfaces are essential for good design.





Source Impedance

- Ideal voltage (dc or ac):
 - Definite $v(t)$ function no matter what the current.
 - No loss (just output or input power).
 - No imposed current is associated with any voltage drop.
- This means $Z = 0$ (except that power flows at f_{source}).



Source Impedance

- The effect is well known: a dc voltage source acts like a short circuit to ac signals.
- It is also true that an ac voltage source acts like a short circuit (except at its own frequency).





Source Impedance

- Ideal current, ac or dc:
 - Definite current $i(t)$ no matter what the voltage.
 - No loss (just power flow).
 - Any imposed voltage does not generate an associated current.
- $Z \rightarrow \infty$ (except for f_{source})





Real Sources/Loads

- Series or parallel resistance causes loss.
- Series L causes impedance to rise with frequency.
- If ac sources must handle dc voltage or current, special problems arise.





Dealing with Z

- For dc voltage, a parallel capacitor will make Z fall with increasing frequency.
- A capacitor makes the source more ideal in several ways.
- For dc current, series L makes Z rise, and the source is more ideal.





Ac Sources

- Consider ac voltage: We want $Z = 0$, except that the interface should not cause trouble at f_{source} .
- Parallel L-C can do this: If we set $1/\sqrt{LC} = 2\pi f_{\text{source}}$, then this interface has no effect at f_{source} , but can have $Z \rightarrow 0$ elsewhere.



Ac Sources

- For ac current, series L-C is appropriate.
- Once again, we should choose the resonant frequency to match that of the source.



General Cases

- If we can avoid subharmonics, then these reduce to parallel C and series L.
- If not, true resonant pairs might be necessary.





Traps

- True resonant pairs end up with large parts when the frequencies are low.
- So far, we have focused on eliminating *all* frequencies other than the wanted one – any value $f \neq f_{in}$.
- Although the number of unwanted components is infinite, often the unwanted frequencies are known.





Tuned Traps

- We can focus instead on the unwanted frequencies, and block them specifically.
- This is the idea of a tuned trap: make $Z = 0$ or $Z \rightarrow \infty$ for specific unwanted frequencies rather than for a whole range.





Rectifier

- Example: Source interface for a six-pulse rectifier.
- We know the currents contain harmonics that are odd multiples of the ac line input.
- Resonant interfaces can be added at key unwanted frequencies to help reduce them.






Summary so far

- For dc sources, inductors and capacitors well above critical values serve as interfaces.
- For ac sources, series L and parallel C work in restricted frequency ranges.
- For ac sources, resonant LC filters and traps can be used to create more ideal characteristics.



Capacitor Types

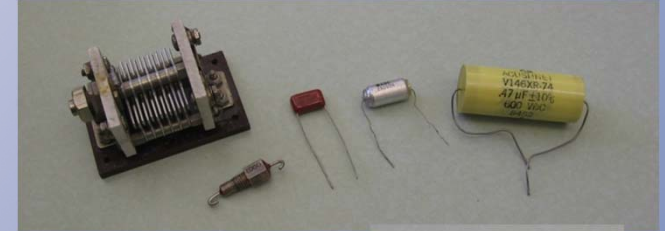- Simple dielectrics:
 - Two conductive plates with a planar dielectric in between.
 - A wide variety of dielectric materials.
- Electrolytics:
 - The dielectric is formed electrochemically on a metal.
- Double-layer





In General

- We define electrical permittivity, ϵ , and $C = \epsilon A/d$.
A is the plate area, d is the plate spacing.
- The permittivity of free space is $\epsilon_0 = 8.854 \text{ pF/m}$.
- Large plate areas and small spacings are needed.





Voltage Limits

- Any capacitor has a voltage rating, determined by the dielectric breakdown strength.
- The electric field is V/d . Typically, the limit is 10 MV/m or so. For a typical 25 μm dielectric, this gives 250 V or more.






Value Example

- It is difficult to build capacitors with large values.
- Example: Let $A = 1 \text{ m}^2$, $d = 5 \text{ }\mu\text{m}$.
- Since $\epsilon \approx 10 \text{ pF/m}$, the capacitance $C = \epsilon A/d$ is about $(10 \text{ pF/m})(1 \text{ m}^2)/(5 \text{ }\mu\text{m}) = 2 \text{ }\mu\text{F}$.
- This is a big object for such a modest value.




Simple Dielectrics

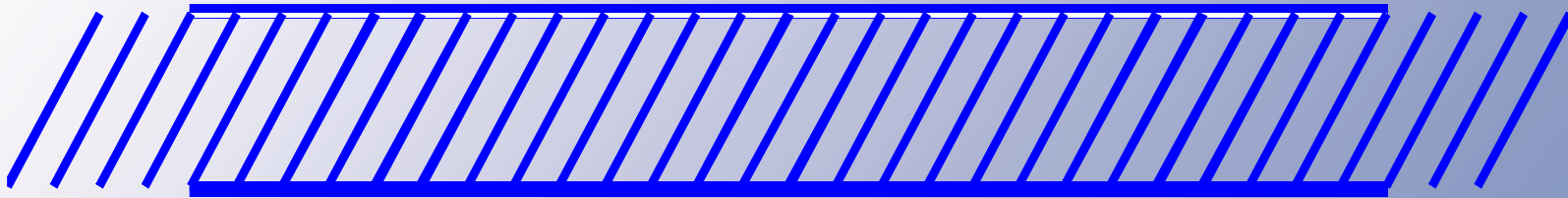

- Typical voltage ratings: 100 V and up.

Circuit Models

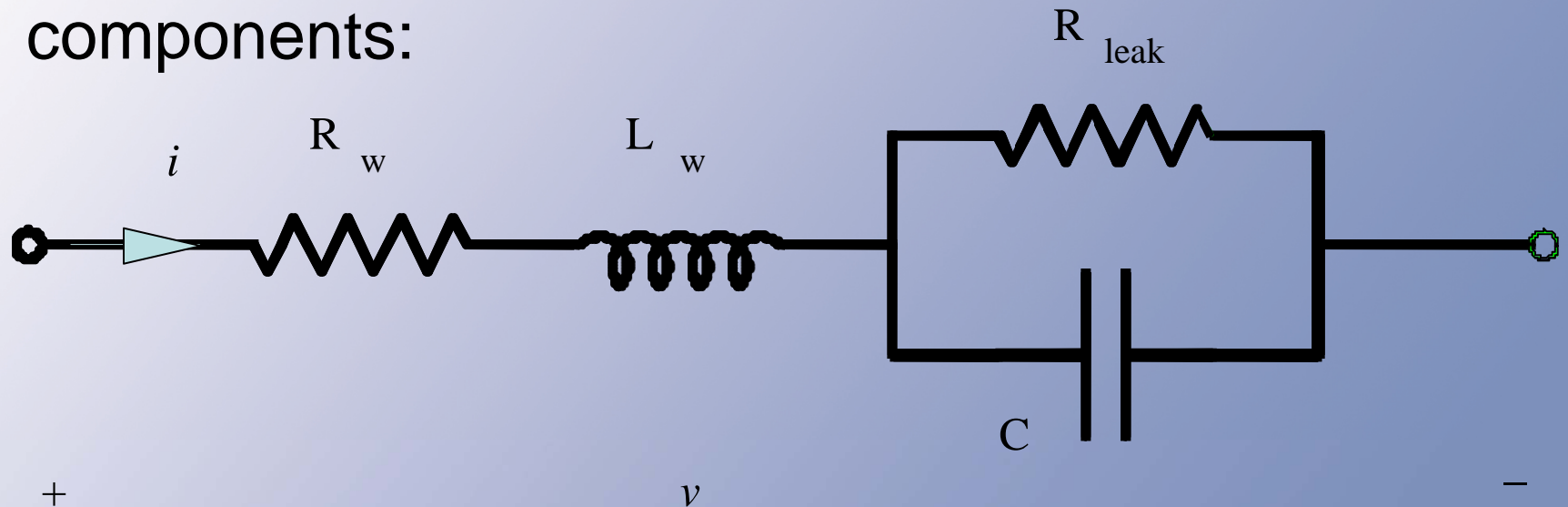- Because of wires, connections, and resistance, a capacitor really involves several extra components:





Circuit Model

- The wire must show resistance and inductance.
- The insulator should have some leakage resistance.
- In a converter, we should consider large unwanted components to understand capacitor action.






Circuit Model

- Focus on a single radian frequency ω .
- The parallel RC can be reduced to a series equivalent.
- We are left with R, L, and C as a series combination.




Circuit Model

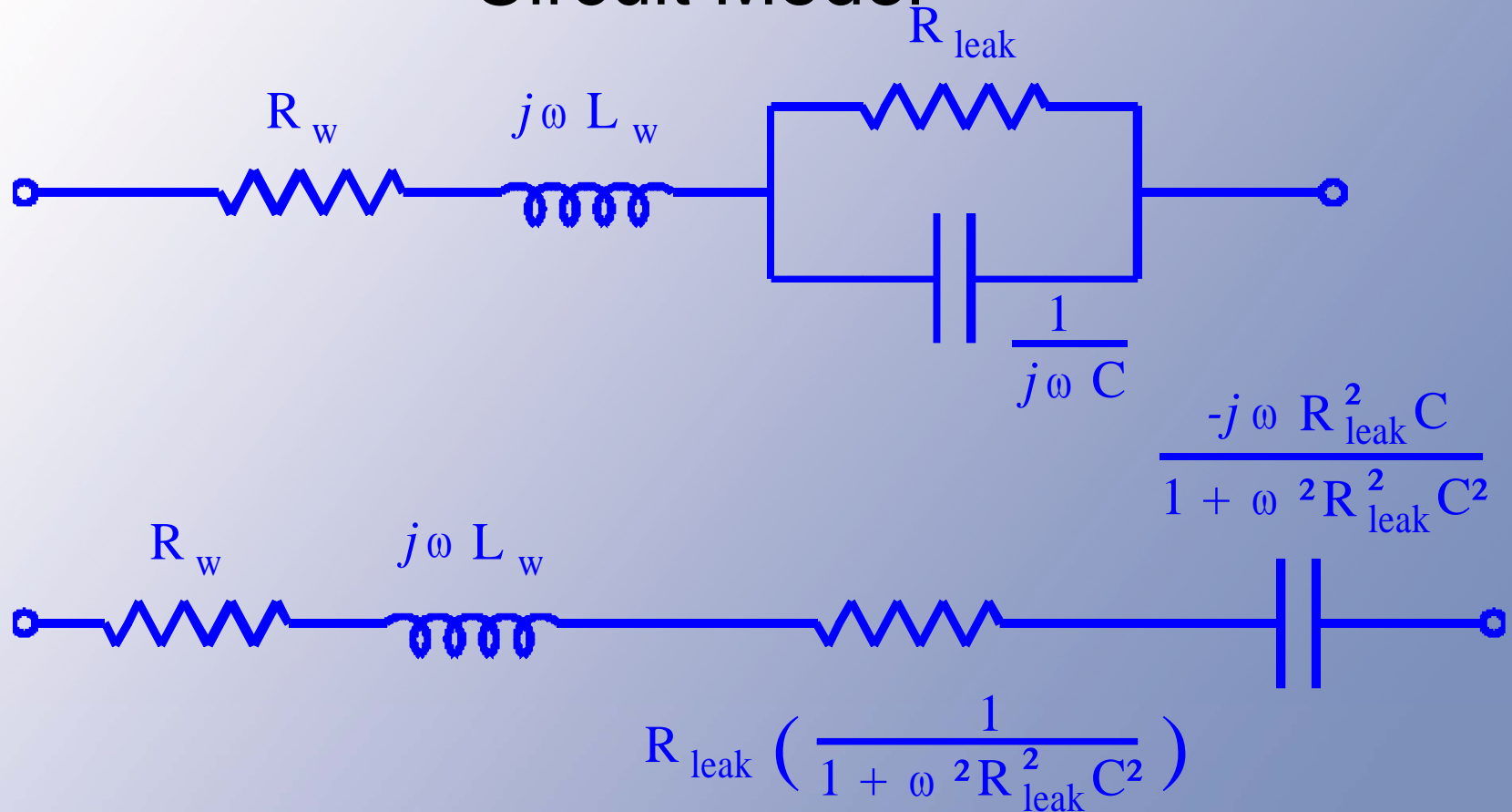

Circuit Model

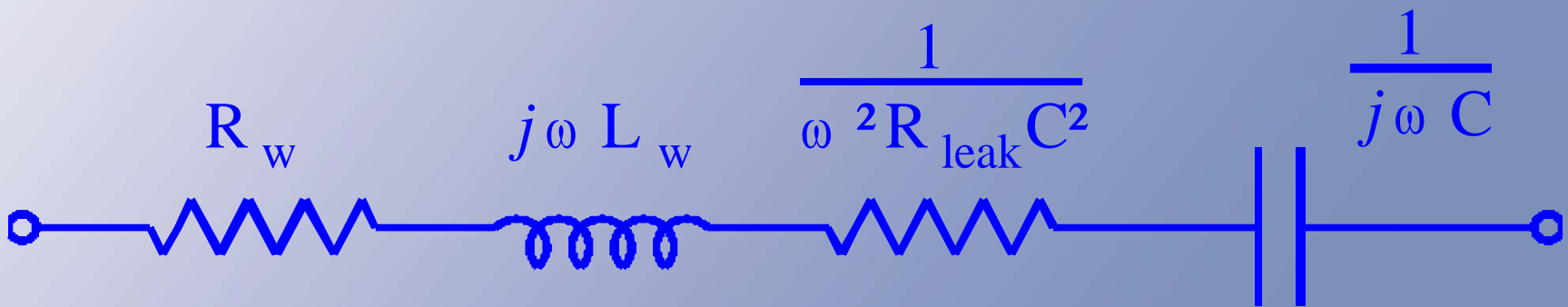- This looks complicated, but is easy to simplify because we expect a very long “leakage time constant” $R_{\text{leak}}C$.
- If $R_{\text{leak}}C$ is a long time, the ratio $R_{\text{leak}}C/T$ is large.
- In turn, the quantity $\omega^2 R_{\text{leak}}^2 C^2 \gg 1$.



Circuit Model

- Define equivalent series inductance, ESL, equal to L_w .
- Define *equivalent series resistance*, ESR, equal to $R_w + 1/(\omega^2 R_{\text{leak}}^2 C^2)$:





Implications

- This is a resonant circuit.
- Below resonance, the reactance is negative (we have C).
- Above resonance, the reactance is positive -- we have L!
- This is the *standard model of a capacitor*.



Some Concerns

- To get capacitive filtering, we need to operate below the *self-resonant frequency*,
 $f_r = 1/[2\pi\sqrt{(ESL)C}]$.
- This is nontrivial. For example, 20 nH and 500 uF yields 50 kHz as an upper limit.





Summary So Far

- ESL \rightarrow related to the geometry (wires, layout, internal construction)
- ESR \rightarrow wire effects plus transformed leakage resistance
- C \rightarrow the internal charge storage $\epsilon A/d$.





Behavior

- Consider $|Z|$ and $\angle Z$.
- Well below self-resonance, the impedance falls with frequency, and the angle is -90° .
- Well above self-resonance, the impedance *rises* with frequency, and the angle is $+90^\circ$.
- At self-resonance, $Z = ESR$, and the angle is zero.



Behavior

- The very best capacitors have low ESL and ESR values, and show a sharp self-resonance.
- Capacitors with higher ESR will show a shallower resonance effect, with a gradual change in the angle.





Some Concerns

- From a source impedance perspective, we have $|Z|$ that ultimately rises at high frequency.
- There is loss in the resistance.
- We want the resistive voltage drop to be negligible.






Finding ESR

- ESR comprises a leakage resistance effect plus series resistance of wires and materials.
- For simple dielectrics, we might estimate it with **low wire resistance**.
- Then $ESR \approx 1/(\omega^2 R_{\text{leak}} C^2)$.



Finding ESR

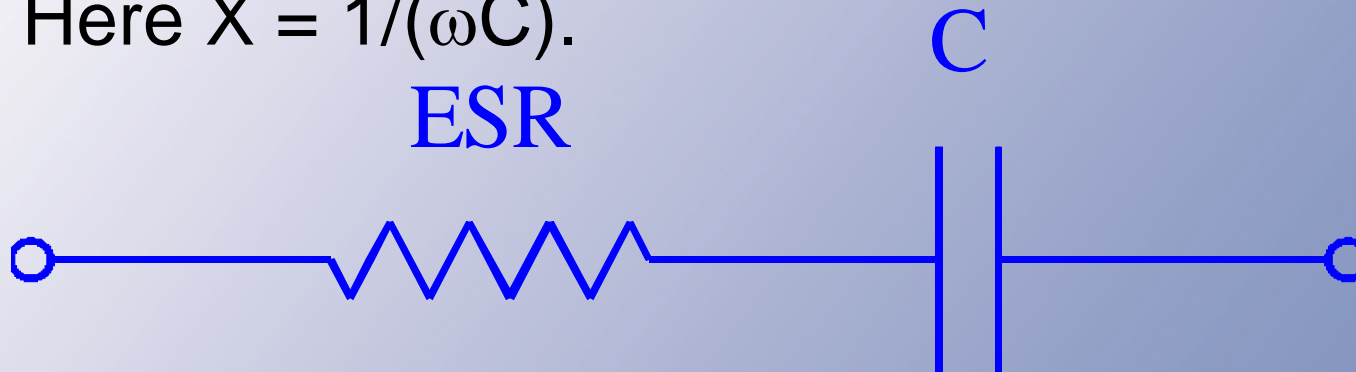- We define the *dissipation factor*, df , as the ratio R/X for the series model (at low frequency). Here $X = 1/(\omega C)$.



- This is $df = (ESR)\omega C \approx 1/(\omega R_{\text{leak}} C)$.
- The dissipation factor is also called the *loss tangent*, $\tan \delta$.



Finding ESR

- The loss tangent is a geometry-independent material property.
 - $C = \epsilon A/d$
 - $R_{\text{leak}} = \rho d/A$
 - $R_{\text{leak}} C = \rho \epsilon \leftarrow$ a material property
- For many good dielectric materials, the loss tangent is roughly constant with frequency.
- This allows us to say $\text{ESR} \approx (\tan \delta)/(\omega C)$.





Finding ESR

- More generally, $ESR = (\tan \delta)/(\omega C) + R_w$.
- For electrolytic capacitors, the connection resistance cannot be neglected, and ESR is more dominated by R_w .





Construction

- Most capacitors ultimately have two conducting surfaces and insulation in between.
- The *simple dielectric* construction is most direct, with clear plates and insulated spacers.





Simple Dielectric Materials

- Polymer films.
- Ceramics.
- Paper, mica, and other insulators.
- Ceramics for high ϵ . Others for low loss or low cost.
- Almost every planar insulation material has been tried (and sold).





Structure

- The planar structure might be flat (common with ceramics) or rolled (common with polymers or paper).
- Aluminum conductors are common.
- For polymer films the limits are on “thinness” of the films and conductors.
- *Multi-layer ceramic* capacitors place several layers in parallel.



Characteristics

- Simple dielectrics tend to follow the standard model very well.
- Voltage ratings are high.
- For polymers, ϵ is low (perhaps $2\epsilon_0$ to $3\epsilon_0$).
- For polymers, thin spacings but low capacitance per unit volume.





Characteristics

- Ceramic capacitors are built in simple dielectric form.
- For ceramics, ϵ up to $1000\epsilon_0$.
- The spacing must be thicker, although voltage ratings are still limited (by the material strength).
- Often sensitive to moisture.
- Expensive in “large” values.





Characteristics

- Many polymers provide $df < 0.01$, or $\tan \delta < 1\%$, and sometimes below 0.1% .
- Ceramics tend to have $\tan \delta$ in the range of 1% to 5% .
- Define *quality factor* $Q = Z_c/ESR$, where Z_c is the characteristic impedance $Z_c = \sqrt{ESL/C}$.
- Most simple dielectrics have high Q .



Electrolytics

- What does it take to get high C values in small packages?
 - Thin spacings
 - Large areas
 - High ϵ values
- How to accomplish all of this?





Electrolytics

- Certain metals have interesting insulating oxides.
- Classic example: alumina. This is a very high-quality oxide with good electrical properties.
- It forms a uniform protective layer on the surface of pure aluminum.



Electrolytics

- Most other oxides might shrink (to form exposed cracks) or grow (to lose contact with the metal).
- Aluminum and tantalum have the best oxide properties from an electrical standpoint.



Electrolytics

- Concept:
 - Etch material, or start with a fine powder, to get high surface area.
 - Electroplate the material with its own oxide.
 - Create electrical connections to the material and to the outer side of its oxide.
- The connections are the hard part.






Electrolytics

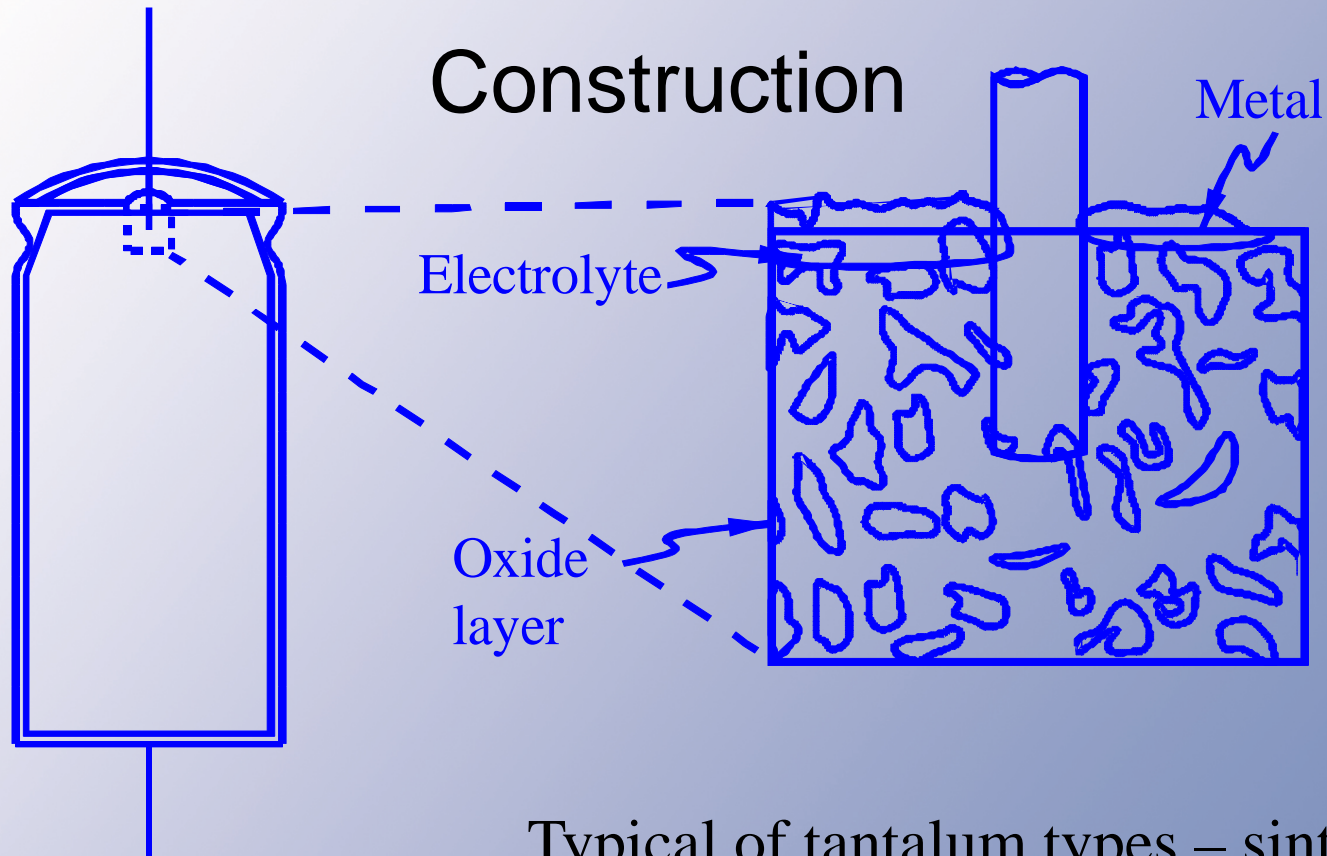- Problem: If we can plate the material, we can “unplate” it, too.
- Electrolytics have polarity.
- Reverse polarity will degrade the oxide layer and cause short circuit failure.





Typical of tantalum types – sintered.

Expanded view shows oxidized metal slug.
Voids must contain electrolyte.



Electrolytics

- Connections:
 - The metal is connected directly to a wire lead.
 - A sheet is etched for surface area, or
 - The powder is sintered to form connections among the particles.
- The other side could be connected with a liquid or solid conductor: the electrolyte.





Electrolytics

- The electrolyte that makes the second contact can be wet (often water-based) or dry (such as the manganese dioxide material used in dry cell batteries).
- The ESR values are higher for a given C than simple dielectrics because of the higher effective “wire” resistance.





Electrolytics

- Since the electrolyte introduces series resistance, the ESR is nearly constant with frequency.
- Electrolytics tend to have “short” failure modes: polarity reversal or heating will be concentrated at the thinnest part of the oxide, and it will degrade and short circuit.





Converter Effects

- We need to choose a capacitor with self-resonance well above the strong unwanted frequencies to be filtered.
- Below self-resonance, the circuit model is the ESR in series with C.






Sample Case

- Consider a boost converter.
- The output voltage ought to be fixed.
- Notice that the series ESR does not alter a key fact: $\langle i_C \rangle = 0$.
- In reality, leakage does allow small current flow (mA).



Boost Example

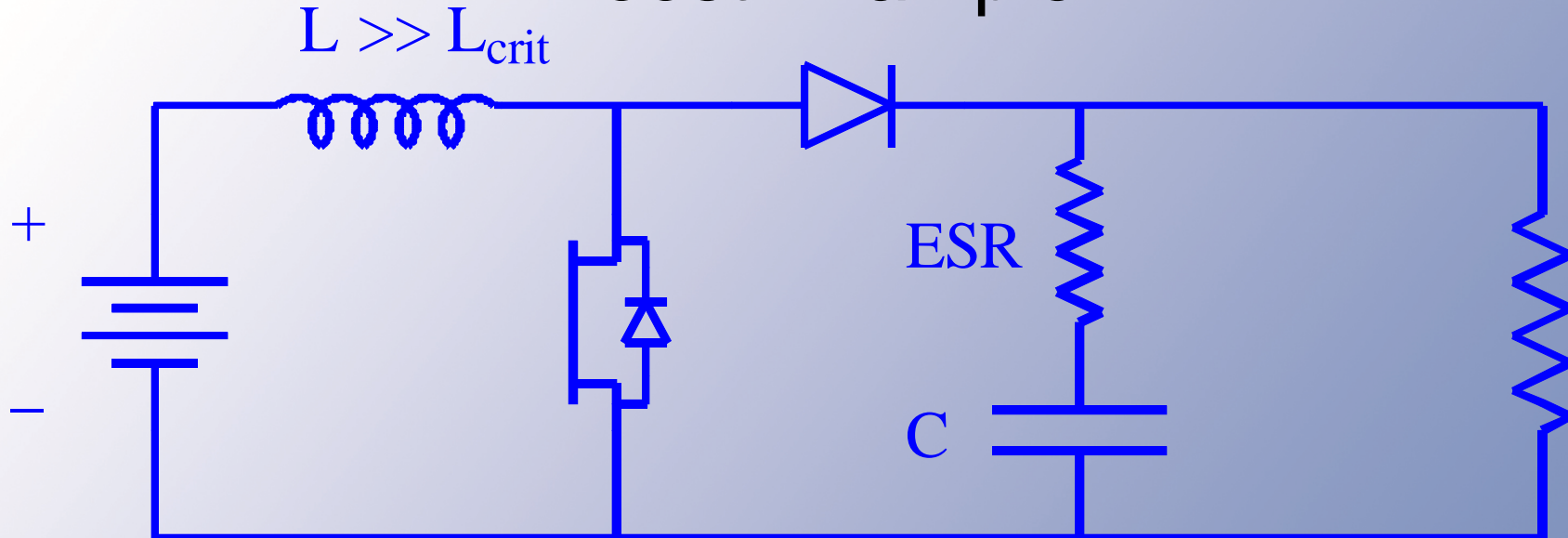

- Relationships are the same, but output ripple is different.

Converter Relationships

- Transistor voltage: $q_2 V_{out}$. The average is $D_2 V_{out} = V_{in}$.
- Diode current: $q_2 I_L$. The average is $D_2 I_L = I_{out}$.
- The ESR does not change the general behavior.

Ripple Effects

- For ripple, however, the output is now $v_C + V_{ESR} = V_{out}$.
- We expect v_C to be triangular as before, but what about v_{ESR} ?
- With the diode off, i_{out} flows out of the capacitor; v_C falls and v_{ESR} makes v_{out} lower.

Ripple Effects

- Diode off:

$$i_C = -I_{out}$$

$v_C \rightarrow$ falling

$$V_{out} = v_C - I_{out} ESR$$

- Diode on:

$$i_C = I_L - I_{out}$$

$v_C \rightarrow$ rising

$$V_{out} = v_C + (I_L - I_{out}) ESR$$

Ripple Effects

- With the diode on, current $I_L - i_{out}$ flows into the capacitor.
- The voltage v_C rises, and v_{out} is higher than v_C .
- What is the change?

$$\Delta v_{out} = \Delta v_C + \Delta v_{ESR}$$

Ripple Effects

- Δv_C :
 - Diode off, $i_C = -i_{out} = C dv_C/dt$, $\Delta v_C = i_{out} D_1 T/C$.
- Δv_{ESR} :
 - $\Delta v_{ESR} = (I_L - i_{out})ESR - (-i_{out})ESR$
 - $\Delta v_{ESR} = I_L ESR$



Ideal Case

- If R_w is small, $ESR = (\tan \delta)/(\omega C)$.
- The total change, when the ESR value can be found from $\tan \delta$, is
$$\Delta v_{out} = i_{out} D_1 T/C + I_L \tan \delta/(\omega C).$$
- This reduces to
$$\Delta v_{out} = i_{out} D_1 T/C + (2\pi/D_2)i_{out} (\tan \delta) T/C.$$
- The change is still proportional to $i_{out} T/C$, but is larger.



Nonideal case

- If R_w is not small, the ESR jump also includes a term $R_w I_L$ that is independent of frequency.
- However, in electrolytics, the electrolyte resistance depends on area, so higher C generally gives lower R_w .
- In any case, ripple is proportional to $1/C$.






Nonideal Case

- At the highest current levels (especially at low voltage), ESR jump dominates the ripple.
- The capacitor in a 5 V or lower converter is often selected based on ESR, not really on its value of C.



Numerical Example

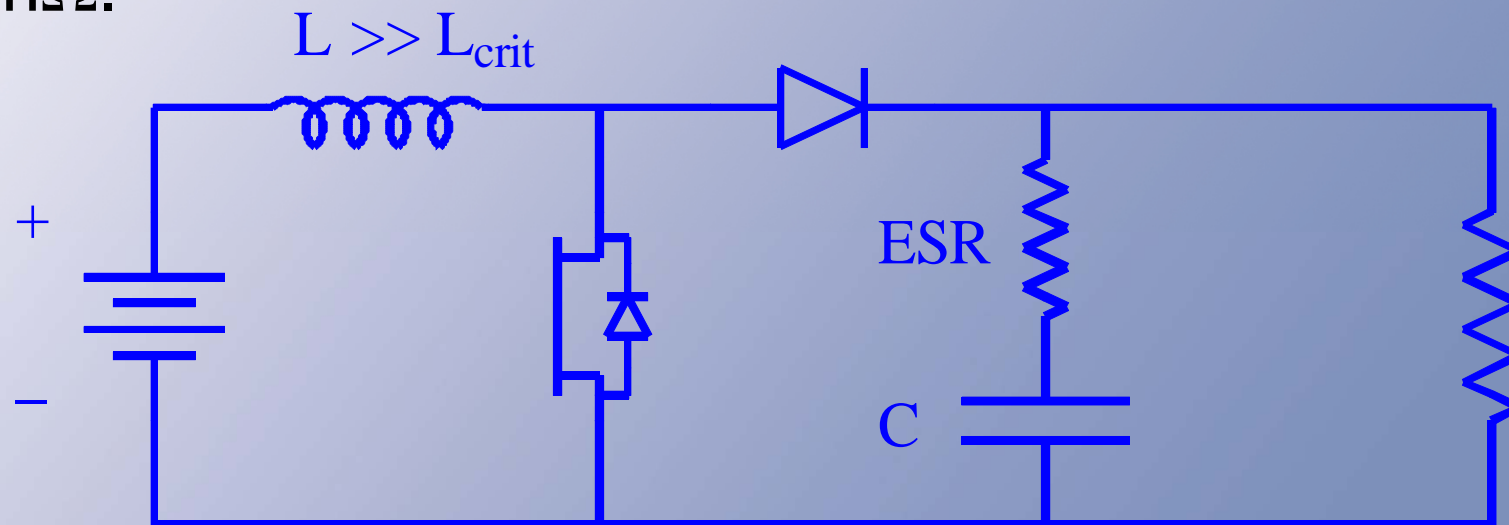- A 12 V to 48 V boost converter, 200 W, 50 kHz switching.
- Find C to provide $\pm 0.5\%$ ripple, given that $\tan \delta = 0.20$ and that R_w gives a minimum ESR of 10 m Ω .





Change

- The inductor current is $16 \frac{2}{3}$ A. The output current is $4 \frac{1}{6}$ A.
- D_1 is 0.75 and D_2 is 0.25.
- Ripple should not exceed 0.48 V.
- The change Δv_C is $i_{out} D_1 T/C = 62.5 \times 10^{-6}/C$.
- With no ESR, $C > 130 \text{ uF}$ works.





With ESR

- The ESR value: $0.01 + \tan \delta / (\omega C)$.
- The change is $16 \frac{2}{3} A$ times this, or $0.1667 V + 10.6 \times 10^{-6} / C$.
- The total required is now 233 μF , almost double.
- Notice that ripple below 0.35% cannot be achieved, because of R_w .





Summary So Far

- Real capacitors have a self-resonant frequency, and are useful below this frequency.
- In a power converter, the unwanted (ripple) frequencies determine this usefulness.
- We must include ESR to get accurate results.



Summary So Far

- ESR voltage drop adds a square wave ripple on top of the usual triangular ripple.
- This is called the ESR jump.
- At high currents and low voltages, ESR jump can dominate ripple.
- ESR is linked to both a loss tangent and series resistance effects.





Wire Resistance

- Wires have resistance, with $R = \rho l/A$ (ρ -- resistivity, l -- length).
- The power loss per unit volume of material is $i_{\text{RMS}}^2 R/(lA) = i_{\text{RMS}}^2 \rho/A^2$.
- Current per unit area is current density, J . The loss per unit volume is ρJ^2 .





Wire Resistance

- We would expect some limit on loss per unit volume.
- Perhaps a block of metal can dissipate 1 W/cm^3 without problems.
- This implies a limit on current density.
- For copper, $\rho = 1.724 \times 10^{-8} \Omega\text{-m}$.
- At 1 W/cm^3 , the limit is $7.62 \times 10^6 \text{ A}/\text{m}^2$.





Current Density Limits

- In power electronics practice, it is usual to limit current densities to the range of 10^6 to 10^7 A/m², or 100 to 1000 A/cm².
- The higher values apply when heat is less important.





Wire Size

- Consider a #18 AWG wire, which has a diameter very close to 1 mm.
- The cross section area is $\pi r^2 = 0.78 \text{ mm}^2$.
- At 1000 A/cm^2 , this implies a limit of 7.8 A.
- Sure enough, real products never push above 10 A in a #18 wire, and often closer to 5 A.



Wire Size

- In the U.S., we use “American Wire Gauge,” which is a complicated logarithmic scale.
- There is an easy way to remember it, though:
 - #18 wire is very close to 1 mm diameter.
 - Every 3 steps in gauge yields a factor of 2 in area.
 - #15 is twice as big as #18, #12 is 4x, etc.





Current Rating

- If #18 can carry 5 A easily, we expect #12 to carry 20 A.
- Sure enough, #12 AWG is used for 20 A house circuits.
- #24 wire can carry about 1.2 A without trouble.
- A table in the book gives sizes and current capacity examples.





Current Density Limits

- Since we seek efficiency, lower current densities are good.
- Example: #22 AWG wire carrying 3.26 A (1000 A/cm^2) has loss (per meter of length) of 0.57 W/m.
- This might seem low, but #18 loses only 0.23 W/m for this length.



Current Density Limits

- #22 with 10 A loses 5.4 W/m -- and gets hot.
- Voltage drop can also be an issue. Consider a 5 V, 200 W supply -- 5 V and 40 A.
- Even at 500 A/cm² (#8 wire), the drop is 84 mV/m.



Drop Issues

- Example: Use #8 wire to connect a 5 V supply to a 200 W load, 25 cm away.
- Total wire length: 0.5 m.
- Drop: 42 mV (0.84%).
- Loss: 1.7 W -- almost 1% of output.





Drop Issues

- Think about 2 V at 20 A (not an uncommon microcomputer supply).
- How big a wire, how much drop?





Drop Issues

- Perhaps we can use #12 AWG?
- The resistance is $5.3 \text{ m}\Omega/\text{m}$.
- At 20 A, the voltage drop is $0.11 \text{ V}/\text{m}$.
- 10 cm of wire yields 0.011 V drop, which is more than 0.5% of the intended 2 V.



Drop Issues

- It is also worth considering the inductance effect.
- A 10 cm wire has about 50 nH of inductance.
- A current change of 0 A to 20 A in 10ns will yield 100 V induced along the wire!
- Even 1 nH would yield 2 V drop.





Drop Issues

- Fast transient loads with low voltage supply levels cannot really be supplied through conventional wires.
- Small capacitors must be present right at the load.
- Even then, stray inductance is a problem.





Thermal Issues

- Loss leads to heat generation.
- Nearly all metals have a resistivity that rises with temperature. This is especially important for resistor design.





Temperature Coefficient

- Example case: Copper.
- The resistivity increases by $+0.39\%$ for each 1°C (1 K) increase.
- This seems small, but consider that a 20 K rise gives a 7.8% increase. Not good for resistors if precise values are desired.





Application Example

- An interesting effect occurs in heaters or lamps.
- For example, if we want an oven heating element at 350°C , made from copper, the “hot” resistance is 2.29 times that at 20°C .
- Sizing is a challenge.





Application Example

- Now, set it up for 4000 W at $230V_{\text{RMS}}$. This requires 13.2Ω at the high temperature.
- The current is 17.4 A.
- Copper at the low temperature would have resistance of only 5.78Ω , and $I = 39.8 \text{ A}$.
Inrush!





Frequency Issue

- Internal self-inductance forces the current toward the surface of a conductor as frequency increases.
- The “skin depth” is $d = \sqrt{2\rho/(\omega\mu)}$, or $(0.166) \sqrt{1/\omega}$ (in meters), for copper.





Frequency Issue

- At 50 kHz, this is 0.3 mm -- enough to matter for wire bigger than about #22.
- The net effect is an increase of resistance with $\omega^{-1/2}$.
- Litz wire and thin bus bar can avoid this. (Why?)





Resistance

- To avoid large changes, resistors should be made of materials with low thermal coefficients of resistivity.
- Classic example: nichrome (80% nickel, 20% chromium) with 0.01% change per degree.





Resistance

- Nichrome is very widely used in heating applications.
- For our oven, the change is only 3.3% over the full range, and the inrush problem is avoided.





Resistors -- Points

- We want to make resistors from thermally constant materials.
- Resistors (especially those wound with wire) have inductance and capacitive effects.
- For “film” resistors, the frequency effects are small.





Resistors -- Points

- For wirewound resistors, inductive effects can be very large -- perhaps 10 nH for each cm of total wire length.
- We could wind them with dual opposite wires. This cancels much of the inductance.

