


Phys 102 – Lecture 6

Circuit elements: resistors, capacitors, and batteries


Today we will learn about...

Circuit elements that:

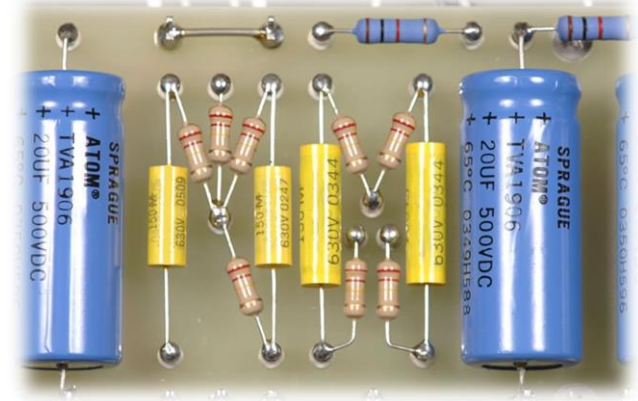
- 1) Serve as conduits for charge – wires
- 2) Pump charges around – batteries
- 3) Regulate flow of charge – resistors
- 4) Store and release charge – capacitors



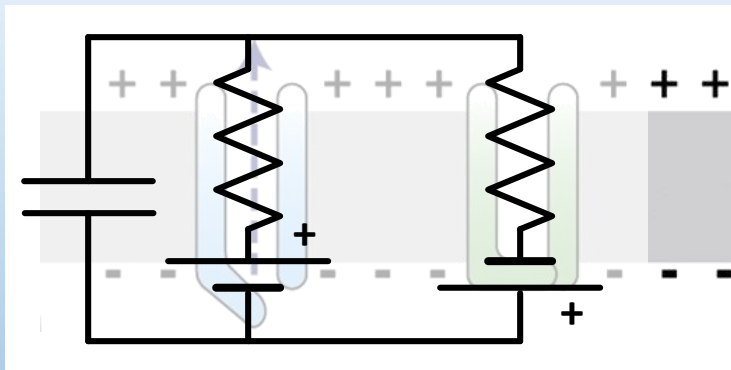These elements are idealizations of components in electronic circuits & in nature



Ex: neurons, circulatory system

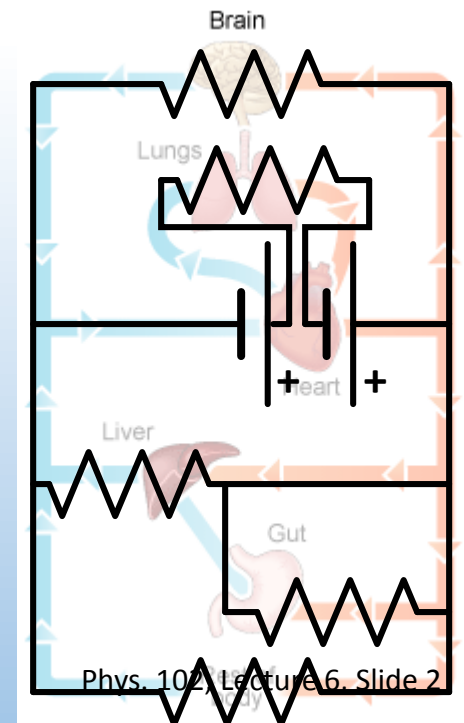


Electric current

Current – measure of flow of charge (+ charge, by convention)
Counts total charge ΔQ passing through area in a time interval Δt

$$I \equiv \frac{\Delta Q}{\Delta t}$$

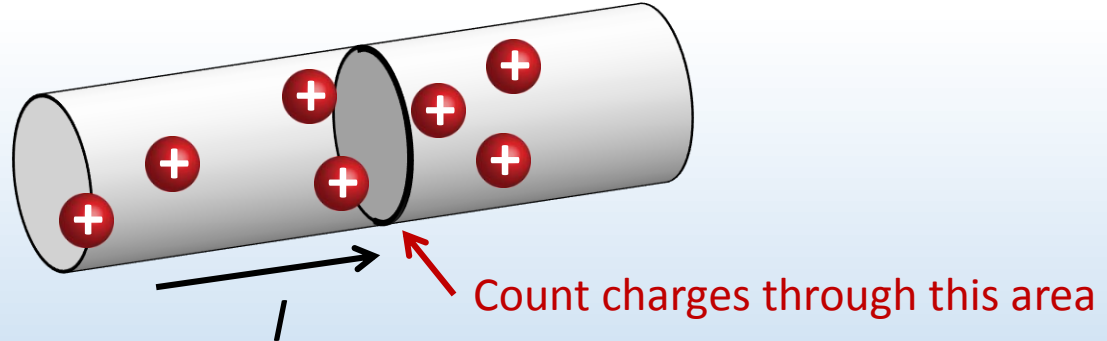Unit: A (“Amp” or “Ampere”)
 $1\text{A} = 1\text{C/s}$




In electronic circuits, electrons ($-e$) carry current, flow opposite to current

In liquid or gas, both cations and anions can carry current



ACT: two light bulbs

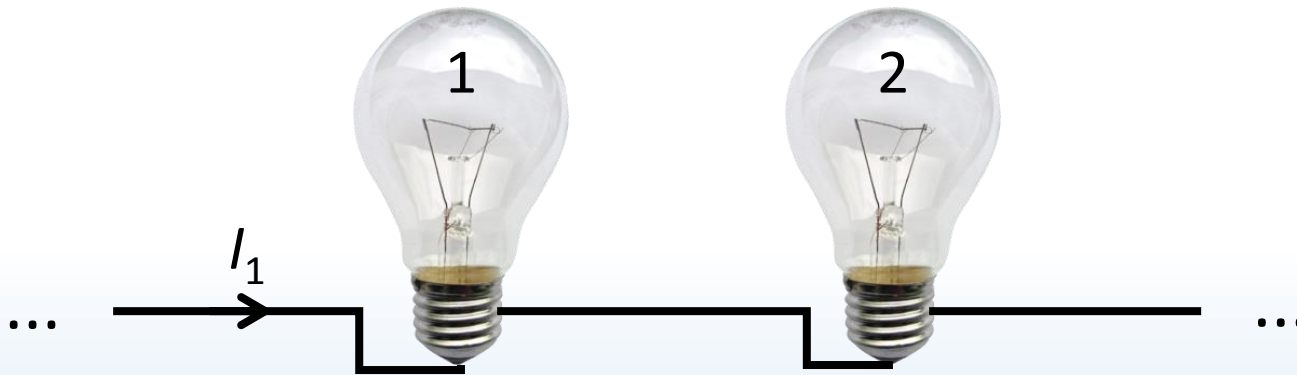Two light bulbs 1 and 2 are connected end-to-end by conducting wire. If a current I_1 flows through bulb 1, what is the current I_2 in bulb 2?




- A. $I_2 < I_1$
- B. $I_2 = I_1$
- C. $I_2 > I_1$

Batteries & electromotive force

Battery – maintains a constant electric potential difference (“Electromotive force” – emf ϵ)



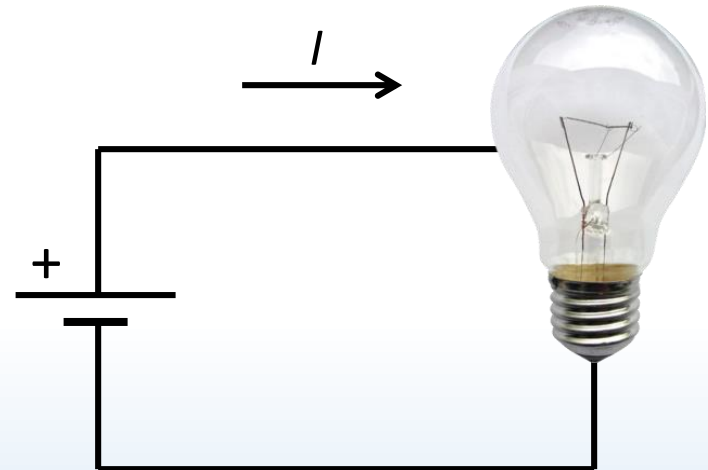Electric potential is 9 V higher at + end relative to – end. Potential difference across a circuit element is its “voltage”




Electric potential difference drives current around circuit
Battery does NOT determine how much current flows
Battery does NOT generate new charges, it “pushes” charges, like a pump



ACT: Two batteries

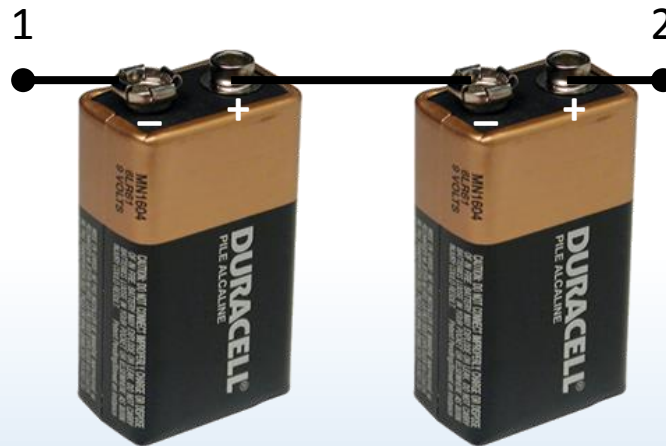
Two 9 V batteries are connected end-to-end by conducting wire. What is the electric potential at point 2 relative to point 1?



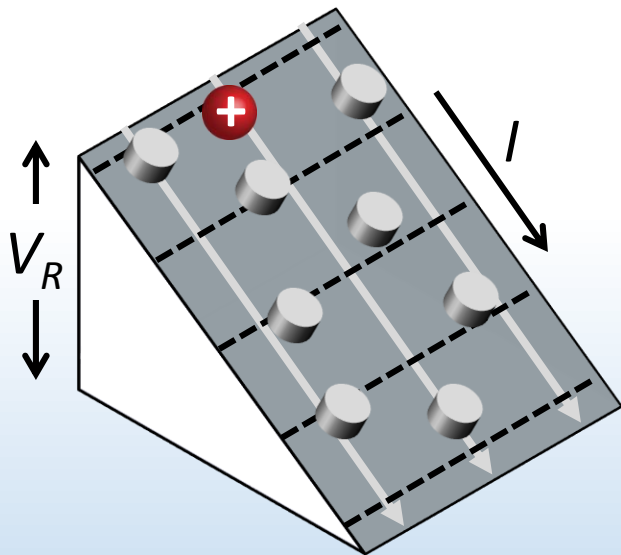- A. +18 V
- B. +9 V
- C. -18 V
- D. -9 V

Resistance and Ohm's law

Moving charges collide with each other, ions, defects inside material
Flow rate depends on electric potential difference



$$I \propto V_R \quad \leftarrow \text{Double potential difference, double current}$$

DEMO

Resistance – proportionality constant between current and voltage

Ohm's law: $R \equiv \frac{V_R}{I}$ Units: Ω ("Ohms")

Potential difference causes current to flow ("downhill", by convention)

Resistance regulates the amount of flow

Physical resistance

Resistor – circuit element designed to have resistance



Resistance depends on material parameters and geometry

Resistivity – density of scatterers

DEMO

$$R = \rho \frac{L}{A}$$

Length – the longer the resistor, the more scattering

Cross sectional area – the wider the resistor, the more charges flow


Material	ρ ($\Omega \cdot \text{m}$)
Copper	1.7×10^{-8}
Iron	9.7×10^{-8}
Sea water	0.22
Muscle	13
Fat	25
Pure water	2.4×10^5




ACT: CheckPoint 1.1

Which of the following three copper resistors has the *lowest* resistance?


A.

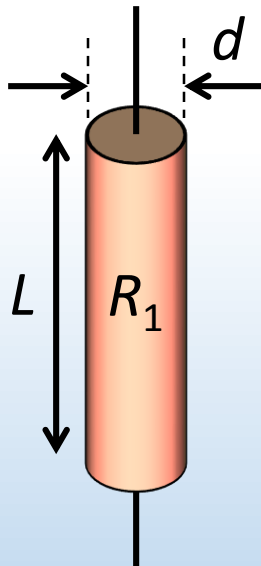

B.

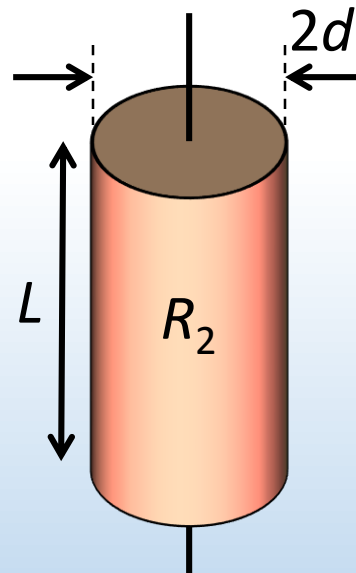

C.

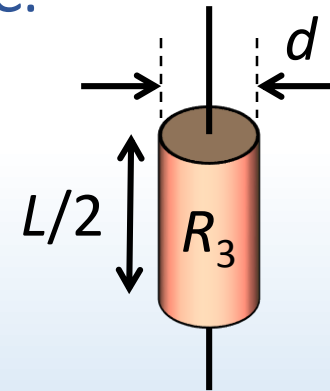

Power generated and dissipated

Battery does work pumping charges through circuit

Ex: a 9 V battery does 9 J of work per 1 C of charge pumped

Power – rate of energy conversion

$$P_{batt} = \frac{\Delta U}{\Delta t} = \frac{\Delta Q}{\Delta t} \varepsilon = I\varepsilon$$


Units: W (“Watts”)
1 W = 1 J/s = 1 V A

Resistor dissipates electric potential energy

Charges lose electric potential energy in collisions inside resistor

$$P_{diss} = IV_R = I^2 R = \frac{V_R^2}{R}$$

Calculation: light bulb filament

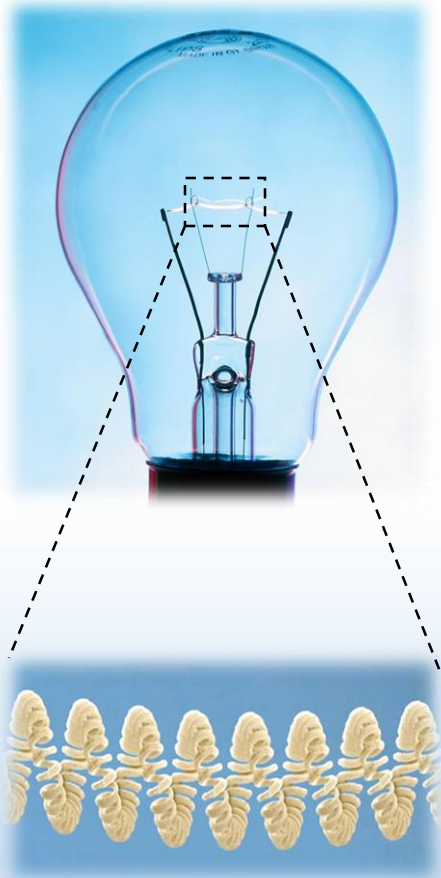


An incandescent light bulb is essentially a resistor that dissipates energy as heat and light. A typical light bulb dissipates 60 W with 120 V from an outlet.

The resistive element is a thin (40- μm diameter) *filament* of tungsten. How long must the filament be?

Capacitance

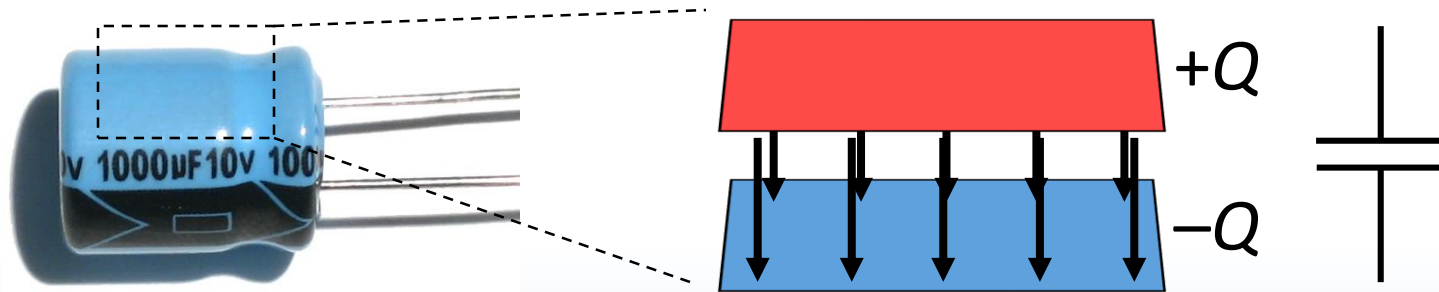Capacitor – circuit element that stores separated charge
Consists of two conductors separated by a small gap



Capacitance – measures the ability to store charge Q given a voltage V_C applied between the conductors

$$C \equiv \frac{Q}{V_C}$$


Units: F (“Farad”)

1 F = 1 C/V

Physical capacitance

Parallel plate capacitor made up of two large conducting plates of area A separated by a small gap d

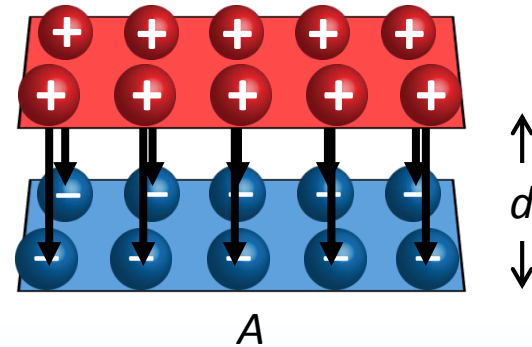Electric field is uniform between plates (Recall Lect. 3)



$$E = \frac{Q}{\epsilon_0 A}$$

Field strength \propto density of field lines \propto density of charges

Work to move $+q$ from $+$ to $-$ plate in uniform E field (Recall Lect. 4)

$$W_E = +qEd = -\Delta U$$

$$\Delta V = \frac{\Delta U}{q} = +Ed = V_C$$

Capacitor voltage


For a parallel plate capacitor: $C = \frac{\epsilon_0 A}{d}$

Capacitance depends on geometry



ACT: Parallel plates

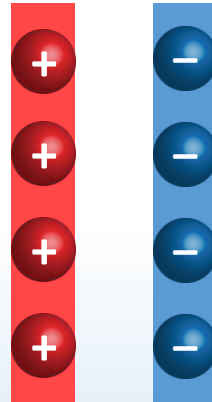A parallel plate capacitor carries a charge Q . The plates are then pulled a small distance further apart.




What happens to the charge Q on each plate?

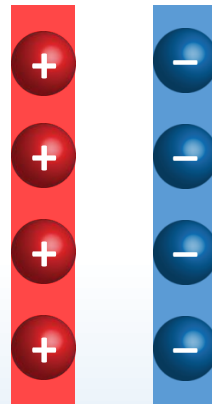- A. Q increases
- B. Q stays constant
- C. Q decreases



ACT: Parallel plates 2

A parallel plate capacitor carries a charge Q . The plates are then pulled a small distance further apart.



DEMO

The voltage V_C between the plates

- A. Increases B. Stays the same C. Decreases

Dielectrics


Imagine placing insulating material (dielectric) between plates

External field polarizes dielectric
Excess $+q$ and $-q$ charges build up on opposite planes

Parallel planes of $+q$ and $-q$
create own E field, cancel out part of external E field

$$\vec{E}_{diel} = \frac{\vec{E}_{ext}}{\kappa}$$

Dielectric constant $\kappa > 1$

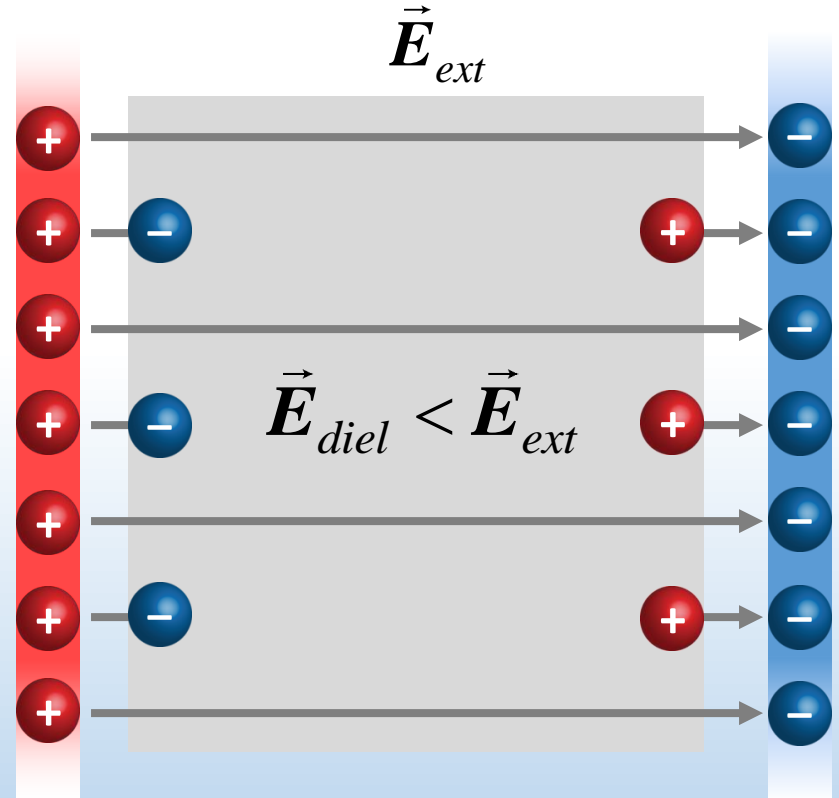

(Recall Lect. 3 – conductors)

Dielectric constant κ

Dielectric constant κ measures how much a material is polarized by electric field

Since $\vec{E} = \vec{E}_0/\kappa$, need less E (or V) to store same Q , so $C = Q/V$ increases:


Capacitance with dielectric

Dielectric constant

$$C = \kappa C_0$$

Capacitance without dielectric

Material	$\kappa (> 1)$
Vacuum	1 (exactly)
Air	1.00054
Rubber	3-4
Glass	5
Cell membrane	7-9
Pure water	80

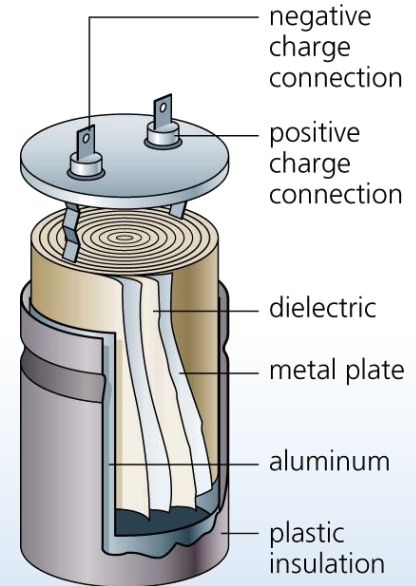


Capacitance depends on material parameters (dielectric) and geometry

Calculation: capacitance of a cell

Channels in a cell's membrane create a charge imbalance (recall Lect. 5), with + charge outside, – inside. The separated charge gives the cell *capacitance*, with the membrane acting as a dielectric ($\kappa = 7$).

Based on EXAM 1, FA09

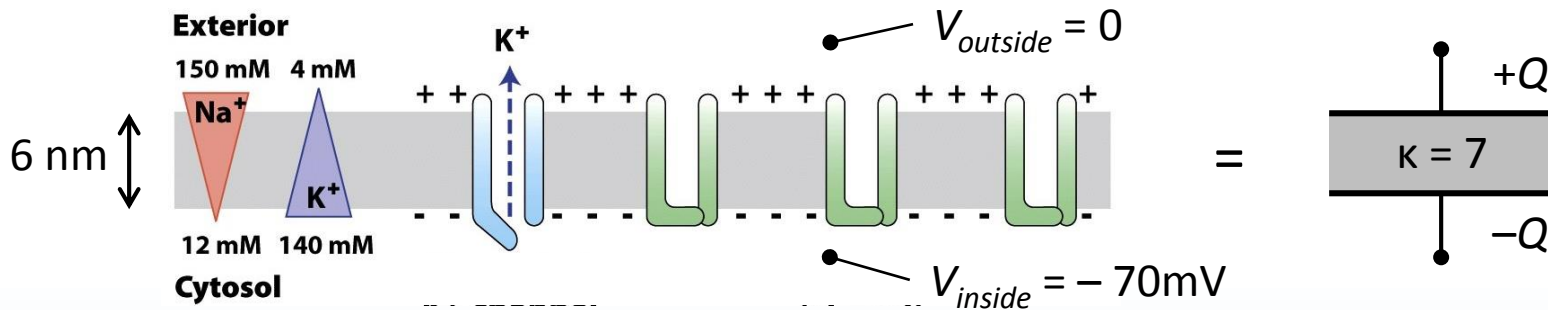

What is the capacitance of a $1\text{-}\mu\text{m}^2$ flat patch of cell?

At rest, a cell has a -70 mV voltage across it. How much charge is necessary to generate this voltage?

Capacitor energy

Separated charges have potential energy (Recall Lect. 4)

$$U_C = \frac{1}{2} QV_C = \frac{1}{2} CV_C^2 = \frac{1}{2} \frac{Q^2}{C}$$

Important factor of $\frac{1}{2}$! Don't confuse this equation with $U = qV$ for individual charge q


Why separate charge?



Camera flash



Defibrillator

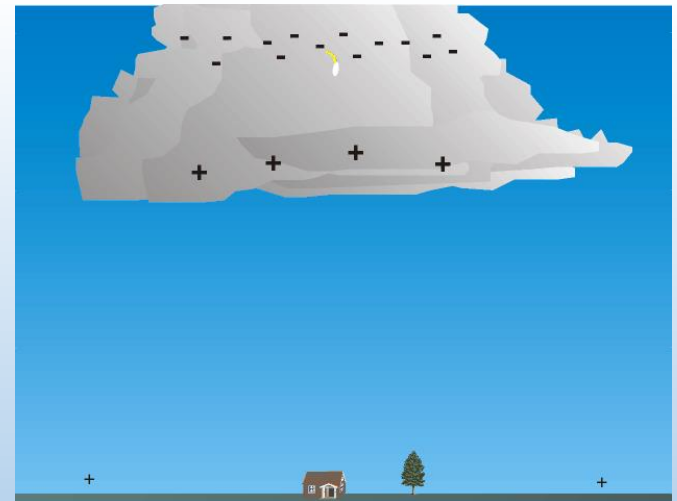


Lightning strike

A way to store *and* release energy



ACT: Capacitor dielectric

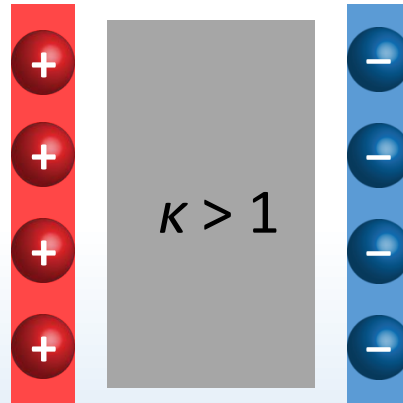A parallel plate capacitor carries a charge Q . A dielectric with $\kappa > 1$ is inserted between the plates.



What happens to energy U_C stored in the capacitor?

- A. U_C increases
- B. U_C stays constant
- C. U_C decreases

Summary of today's lecture

- Batteries generate emf ϵ , pump charges
- Resistors *dissipate* energy as power: $P = IV$
Resistance: how difficult it is for charges to get through: $R = \rho L/A$
Voltage determines *current*: $V = IR$
Ideal wires have $R = 0$, $V = 0$
- Capacitors *store* energy as separated charge: $U = \frac{1}{2}QV$
Capacitance: ability to store separated charge: $C = \kappa\epsilon_0 A/d$
Voltage determines *charge*: $V = Q/C$
- Don't mix capacitor and resistor equations!