



# SUCCESSIVE APPROXIMATION ADCS

BY MIKE HABISOHN, MICHAEL BENGSTON, JUSTIN LANGUIDO, AND CHRISTIAN  
WILLIAMS

# WHAT IS A SUCCESSIVE APPROXIMATION ADC?

- Analog-to-digital signal converter
  - Requires a sampling rate under  $10 \times 10^6$  samples per second or 10MSPS
- Great for 8-16 bits: higher possible but limited by resolution of DAC


# HOW DOES IT WORK?

- Uses a counter circuit, called a SAR (Successive Approximation Register).
- Instead of counting in a binary manner, tries all values of bits
  - Starts from most-significant bit and goes to least-significant bit.
- SAR looks at the comparator's output to check if the binary count is less-than or greater-than the analog signal input.
  - “trial by fit”


# WHY USE A SUCCESSIVE APPROXIMATION ADC?

- offers one distinct advantage
  - Converges much faster to an analog signal than a 0 to full counter.
    - Stepping every clock cycle

# DIAGRAM OF ADC

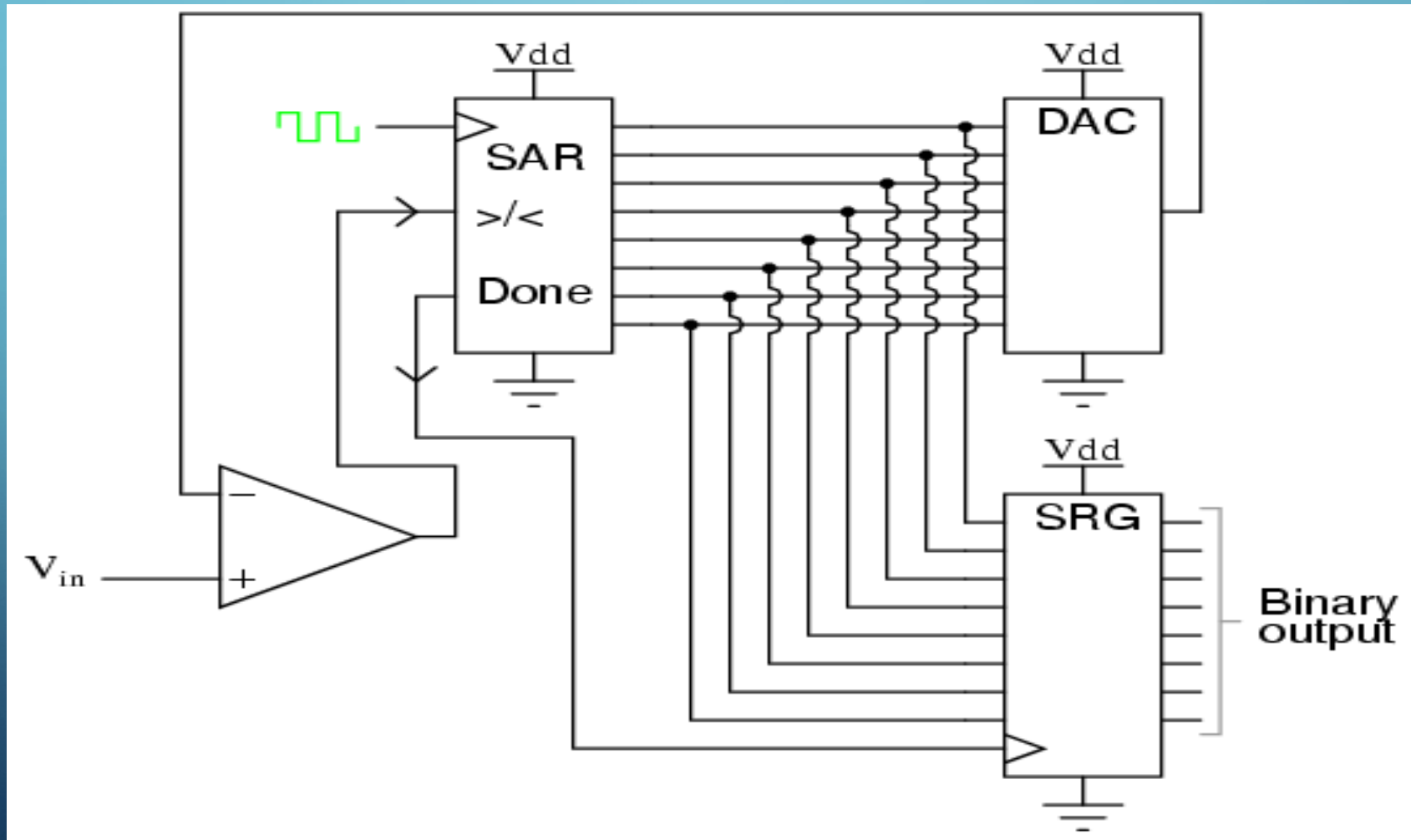

# OUTPUT

 

# REFERENCES

- <https://www.allaboutcircuits.com/textbook/digital/chpt-13/successive-approximation-adc/> (used for all figures as well as information).