

PHASED SPEAKER ARRAY : PHASE OF OUR LIVES

ECE 445 - SENIOR DESIGN

---

# DESIGN DOCUMENT

---

**February 19, 2019**

DAVE SIMLEY (simley2) and ROSEMARY MONTGOMERY (rjmontg2)

TEAM 68

TA: Kyle Michal

University of Illinois at Urbana Champaign

Department of Electrical and Computer Engineering

# Contents

0.1	Introduction . . . . .	1
0.2	Design . . . . .	3
0.3	Ethics and Safety . . . . .	10

## 0.1 Introduction

### Objective

Music can really brighten the mood and complement the atmosphere. What one may not realize, however, is that interference patterns greatly affect the quality of the sound. Say someone has a stereo in their living room, but likes to listen to music while preparing food in the kitchen. Destructive phase relationships can cause the listener to hear music that's tinnier and lacking warmth.

Our solution is to design a four speaker array which can “steer” the sound into a single direction. Our design will use one or more IR sensing cameras to detect where the listener is in the room and apply a linear time delay across the speakers to direct the sound towards the listener.

### Background

A collinear array of speakers create overlapping signals with the peak intensity of sound across all frequencies extending out directly from the center of the array. By applying a linear time delay across the array, the line of peak intensity steers away from the center at an angle. With the help of IR sensors, we can track where a person is in the room and use this information to adjust how much we need to angle our line of peak intensity so that it runs through our listener.

Our project would allow a user listening to music to walk around a room and experience little to no phase cancellation. Therefore, our project would be useful for audio enthusiasts who admire superior sound quality. In addition, our project holds great educational merit, as it provides a platform where one can model and physically experience the effects of wave interference.

### High-Level Requirements


1. A numerical parameter we plan to use to quantify the quality of phase accordance will take the root-mean-square error (RMS error) of the time delays between signals (comparing them to an average, ideal time delay). When steering is implemented at  $30^\circ$  from center, phase accordance between signals will significantly improve, resulting in a lower RMS error. A specific range of values cannot be presented at the moment, but we hope to reduce the RMSE of the signals by 75%.

2. The sound quality improvement must be apparent to the user qualitatively.
3. The direction of the improved sound quality should be updated at least every two minutes so that the user could reasonably move about the room with the improved sound quality following the user.

## 0.2 Design

### Block Diagram


Our design has several modules including: the signal input module, the control module, which contains the microcontroller and the DACs, the speaker array module, the power module, and the IR cameras. The control module takes an audio signal in and delays it accordingly. These delayed signals are then put through the speaker array, and they are played through four collinear speakers.

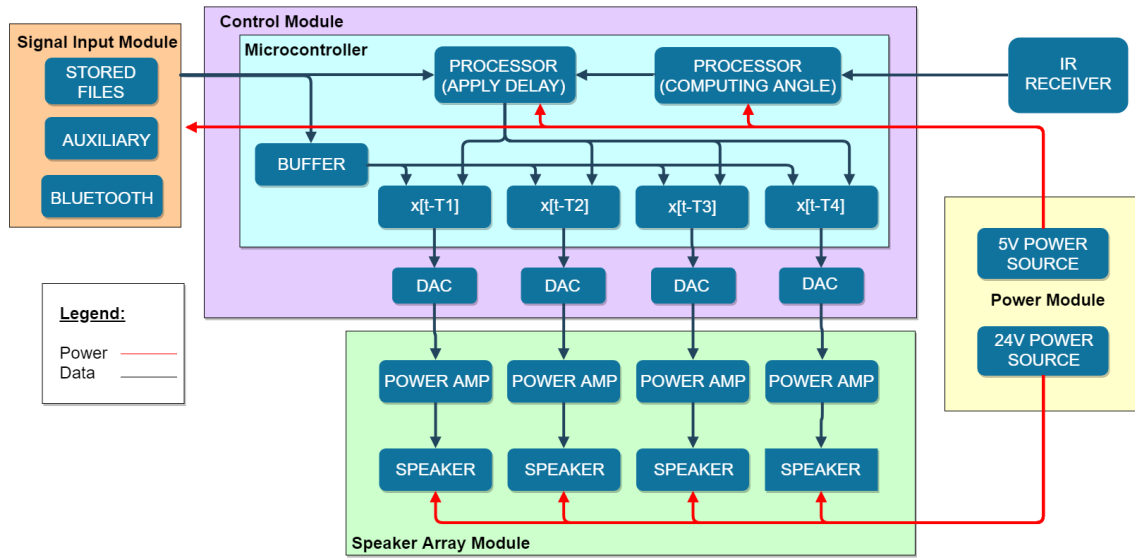

**Figure 1:** Block Diagram

### Physical Design

The physical design will consist of an array of four speakers separated in the middle by two IR sensing cameras. The speakers and cameras will be contained in an enclosure with the approximate dimensions shown in the diagram. There will also be a separate module including the control module and input module.

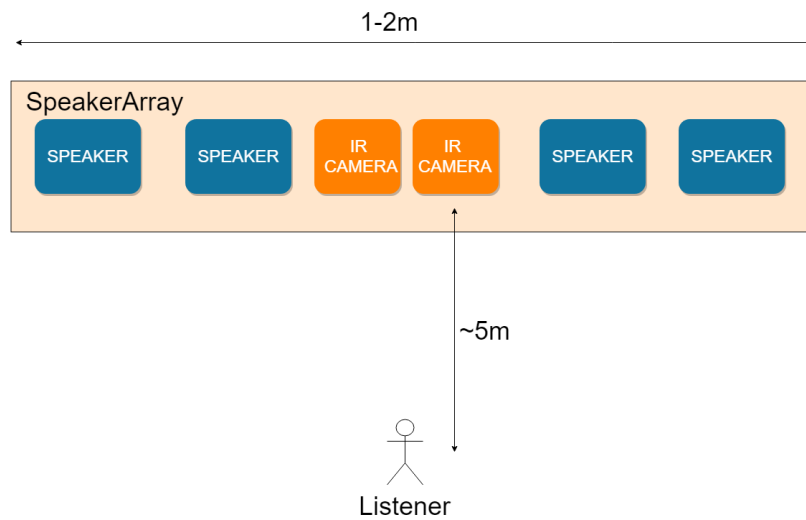

**Figure 2:** Physical Design

## Functional Overview and Block Requirements

- Speaker Array Module

- **Power amplifiers:** The power amplifiers are needed to amplify the sound so that the speakers can use it. It will be at the output of the DACs and at the input of the speakers.

**Figure 3:** Power Amplifier Schematic

Requirements	Verification
Must be able to output at least 1W of power to speakers.	Apply a load at the output of the power amplifier circuit. Set the power supply to 24V. Use a multimeter to measure the voltage and current across the load. Use $P=IV$ to calculate the power.
Power supply must be less than or equal to 24V.	Apply a load at the output of the power amplifier circuit. Set the power supply to 24V. Use a multimeter to measure the voltage and current across the load. Use $P=IV$ to calculate the power.
Power output must be within 20% (1dB) of other speakers.	Use $NdB = 20 \cdot \log(P_o/P_i)$ where $P_i$ is the power calculated in part 1,2 and $P_o$ is the power used by the speakers, found in the verification below.

- **Speakers:** The speakers convert the electronic audio signal of the song being played to the correct sounds. It will be at the output of the power amplifiers.

Requirements	Verification
Volume output must be within 20% (1dB) of other speakers.	Set a microphone 3m away from a speaker. Apply a constant signal to the input of the speaker. Use the microphone to record the output of the speaker. Use Matlab to determine the volume output. Repeat for the other speakers and compare the results.

- **IR sensing camera(s):** IR sensing cameras will be used to detect where the listener is in the room. This tracking information (the x-y location) will be sent to the microcontroller to be processed. We would need two of these cameras because each one detects a range of about 33 degrees, so two cameras would give us a more reasonable range for a room.

Requirements	Verification
Must be able to detect angle towards infrared source within 5% accuracy.	Set up camera so that it is horizontal to the ground and apply a 3.3V/5V voltage supply to power it. Measure out three positions a 0-3m radius from the camera and supply a heat source at each spot. Record the location using the IR camera at each point.
Must be capable of updating the position at least every 2 minutes.	Set up the camera as described above. Record measurements every 2 minutes.

## • Power Module

- **Power Supply (5V):** A 5V power supply will be used to supply power to the control and signal input module. The supply will need to be steady, well-



filtered, and able to provide enough current to adequately power the digital circuitry involved in processing the audio signal.

Requirements	Verification
Must provide 5V $\pm 5\%$ at peak output current draw of 300mA.	Apply a load at the output of the power supply. Set the power supply to 5V. Use a multimeter to measure the voltage and current across the load.

- **Power Supply (24V):** A 24V power supply is necessary to provide power to the power amplifiers. The power amplifiers require a stronger power supply because the electrical output of the amplifiers are physically moving the diaphragms of the speakers. Therefore, a higher current draw should be expected.

Requirements	Verification
Must supply 24V $\pm 5\%$ at peak output current draw of 1A.	Apply a load at the output of the power supply. Set the power supply to 24V. Use a multimeter to measure the voltage and current across the load.


## Schematics and Calculations

Above we can see the schematic design of the power amp, along with it's frequency response. Given that our power amp needs to deliver 1W of power to the speaker, we find that to deliver 1W of power, we need to apply a voltage of approximately 3V and deliver approximately 0.5 Amps. Therefore, we need to use a Darlington pair of BJTs to deliver the current, and the preamp has a low gain.


$$P_{tot} = V_{tot}I_{tot} = \frac{V_{tot}^2}{R} = \frac{V_{tot}^2}{8\Omega} = 1W$$

$$V_{tot} = 2.82V$$

$$I_{tot} = 353mA$$

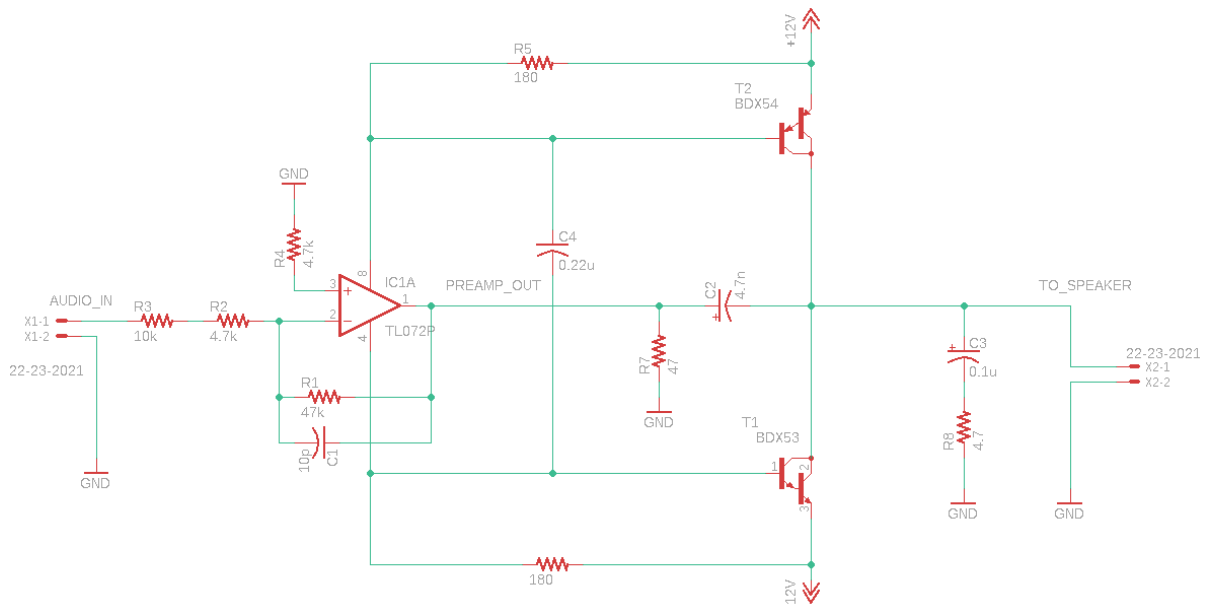

**Figure 4:** Power Amplifier Schematic

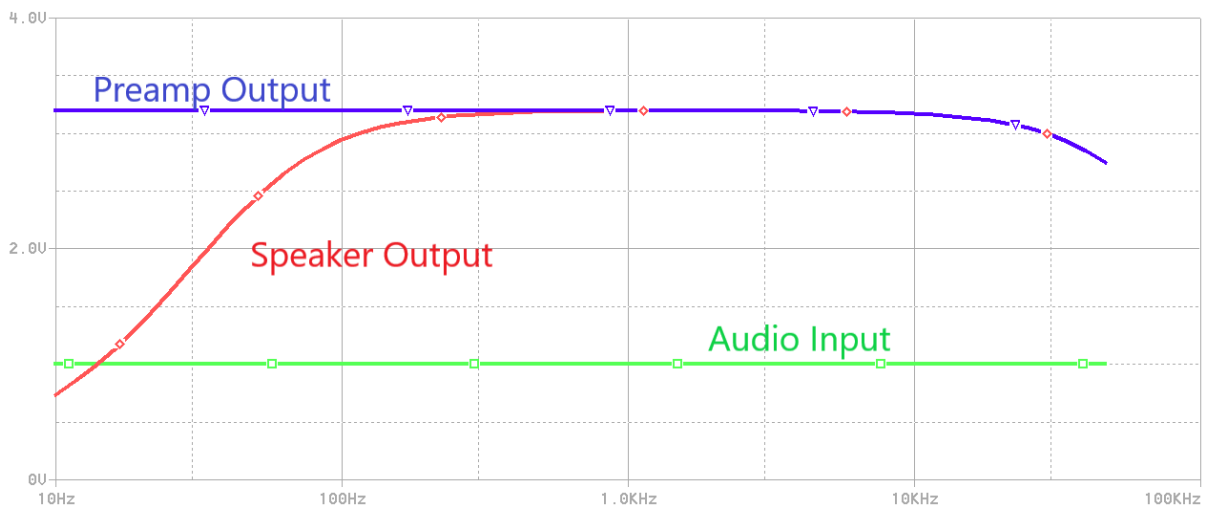

**Figure 5:** Frequency Response of Power Amp

## Risk Analysis

The part of our project that imposes the greatest risk of failure would be the control module. It demonstrates the most complex interfacing between modules and the success of the project relies nearly entirely on the ability of the microcontroller to delay an analog signal to four different degrees and send them to four different speakers. Furthermore, device calibration cannot be done by ear or human inspection; a professional-grade digital audio workspace, microphones with good audio clarity, and a reliable computer are needed

to make sure the device is operating properly.

While calibration may be tedious, the end result will be impressive. In addition, our team has access to not only every item needed to calibrate the system, but also access to a wealth of university resources and insightful advice from our professors and TA's. In conclusion, our project will be challenging, but our determination and the supportive course staff will keep us focused and assure our project's success.

### 0.3 Ethics and Safety

On the surface, our project poses no immediate ethical or safety concern. Our project cannot endanger others, won't have a minuscule effect on global health, nor does it deal with any personal information. However, our project does pose a few health risks to those who operate it and to those who are in the direct path of sound.

The greatest risk our project poses to public health is that exposure to loud sounds for long periods of time can lead to hearing loss. To address this, we put proper constraints in place at multiple levels of the project to assure auditory safety. Our power amps will deliver at most 1W of power through each speaker, which will provide approximately 80dB of sound to a listener standing one meter away from the speaker array. We predict that we will likely restrict our speakers to only put out a quarter watt of power, but may require extra headroom in case outside noises become a concern while calibrating our system.

In addition, our project involves designing and constructing power amplifiers for the speaker array. The power amp will run off of a 24V power supply, so we must be conscientious of those who construct and operate this device. Our power amps will be enclosed and wires coming to and from the amplifier module will be fastened securely. In addition, multiple circuit breakers will exist at every level of power consumption to assure that any shorts won't harm the circuitry or, more importantly, the user. We will adhere to #1 in the IEEE Code of Ethics and make design decisions "consistent with the safety, health, and welfare of the public" [2].

Finally, we will act in accordance of #5, #6, and #7 of the IEEE Code of Ethics [2] in order to contribute to the development of audio technology. We will do this by seeking out criticism of professors and teaching assistants that have expertise on the details of our design, and properly credit them for their involvement.

# References

- [1] Electronic Circuits and Diagrams-Electronic Projects and Design. (2019). *Electronic Circuits and Diagrams-Electronic Projects and Design - An Authentic Resource on Electronics*. [online] Available at: <http://www.circuitstoday.com/> [Accessed 19 Feb. 2019].
- [2] Ewh.ieee.org. (2019). [online] Available at:  
[http://ewh.ieee.org/cmte/substations/posted\\_documents/ieee\\_codeofethics.pdf](http://ewh.ieee.org/cmte/substations/posted_documents/ieee_codeofethics.pdf)  
[Accessed 19 Feb. 2019].
- [3] Kinsler, L. (2000). *Fundamentals of acoustics*. 4th ed. New York: John Wiley & Sons.